

# EDN<sup>®</sup>

Designer's guide to  
flash-ADC testing—Pt 3

Timing-analysis tools  
examine delay paths


Designing switch-mode  
power supplies

Thermal-analysis software

ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS


Add-on buses expand the  
computer board's  
horizons

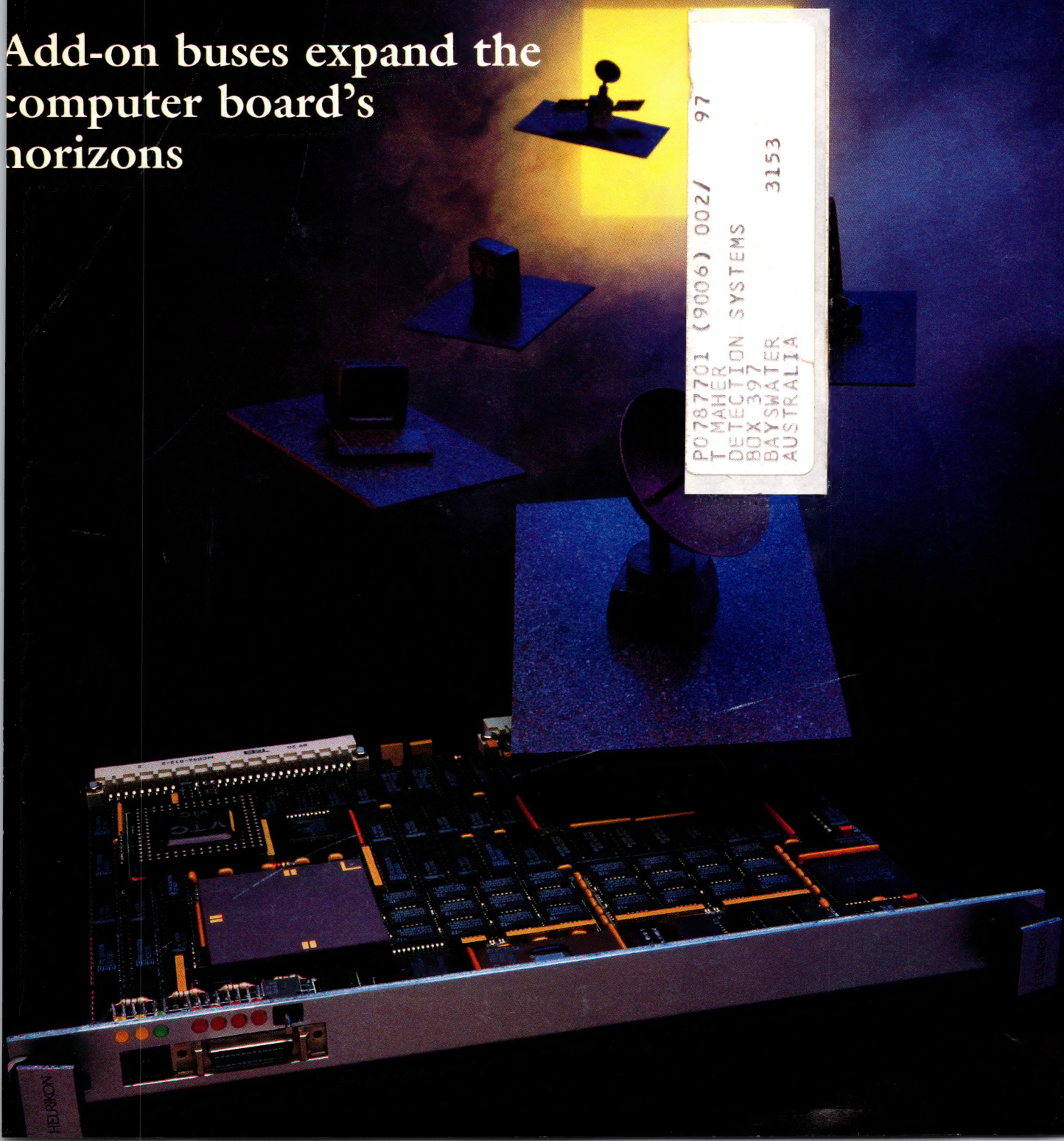P0787701 (9006) 002/ 97  
T. MAHER  
DETECTION SYSTEMS  
BOX 397  
BAYSWATER  
AUSTRALIA 3153





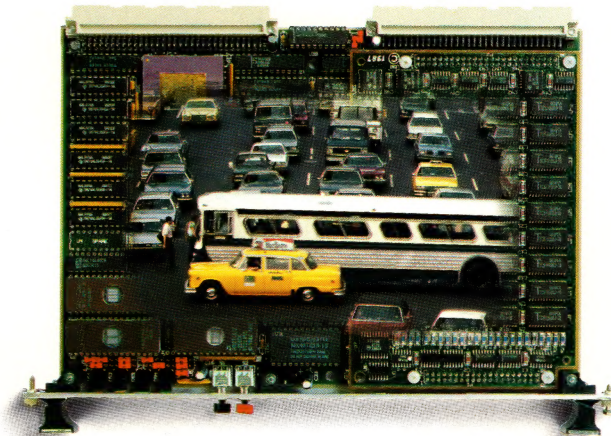
# THEMIS SINGLE BOARD COMPUTER ELIMINATES DATA-FLOW BOTTLENECKS



*Arbitration Delays*

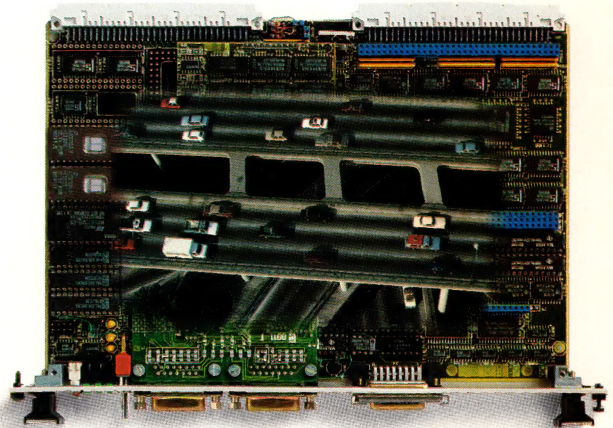

*Concurrent Transfers*

Until now shared memory architectures have resulted in data-flow bottlenecks. The resulting arbitration delays cause unpredictable data transfer latencies, unwelcome in real-time systems.

The Themis TSVME 133 relieves this shared resource bottleneck by providing dedicated paths and memories for high speed transactions. Thus, three levels of concurrent operation are possible:

- 68030 Transfers with Local Memory
- Global VMEbus Transfers with Shared Memory
- Ethernet Transfers with Buffer Memory

If you have to manage VMEbus, VSB, Ethernet, SCSI, FDC and Serial-line ports, the TSVME 133 will keep your data moving!

*Themis Computer offers VMEbus board, system and software solutions for applications in real-time Processing, Industrial I/O, Communications, Video/Graphics, DSP and Robotics.*



For information, call Themis Computer  
*Americas and Pacific Rim:*

(415) 734-0870, FAX (415) 734-0873

*Europe:*


(331) 69.86.15.25, FAX 64.46.45.50

Americas: 6681 Owens Drive, Pleasanton, CA 94566

Europe: 29, Av. de la Baltique, 91953 Les Ulis Cedex-France

CIRCLE NO. 3





# A core, two caps and Nichrome film can't get you to market sooner.


Metal film resistance. Lots of people supply it, but at Dale® we have more ways to make it work to your advantage.

From the start, we'll give you more alternatives for fine-tuning resistance to your application — right out of the catalog. Low cost commercial to ultra precision.



Dale Makes Your Basics Better

## Dale® Can.

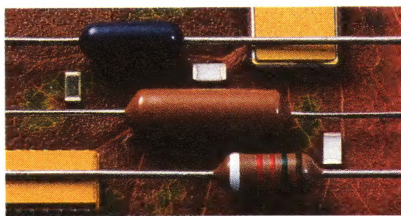

High power. Ultra high or low value. Tight tolerance. Matched sets. Thick film chips plus thin film chips and networks for surface mounting. MIL qualifications from MIL-R-22684 through MIL-R-122. All guided

by Statistical Process Control and Just-In-Time delivery systems.

Whether your need is for high performance, high volume or both, Dale has the products and the commitment to meet your exact needs for quality and delivery. Start saving time right now.

Contact your Dale representative or phone 402-371-0080. Dale Electronics, Inc., 2300 Riverside Blvd., Norfolk, NE 68701-2242.

**DALE ELECTRONICS, INC.**  
... a VISHAY Company




# A DUO OF DUALS

## POWER DUAL OPERATIONAL AMPLIFIERS

- ▶ Low Cost - 21.<sup>50</sup> in 100's
- ▶ High Output Current - 3 Amps
- ▶ Saturation Voltage <3.5 Volts
- ▶ Thermal Shutdown
- ▶ Ideal for Single Supply Operation


### PA21

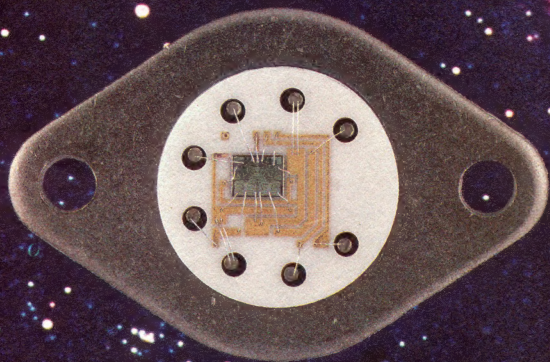

POWER AND  
PERFORMANCE  
GIVE YOU THE EDGE

To Place An Order Call  
**602•742•8601**

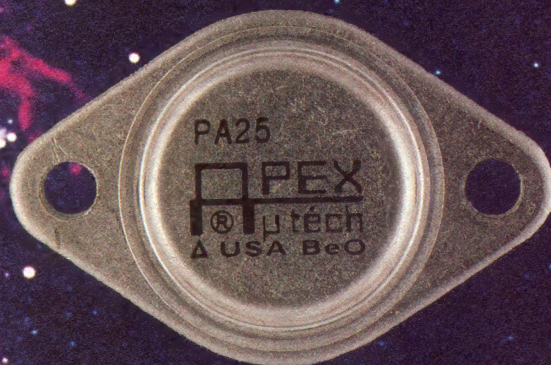For Applications Assistance Call  
**1•800•421•1865**



### PA25A

- ▶ Pin compatible with OPA2541
- ▶ Provides a high-performance second source when supply voltages are less than 40 volts

**APEX**<sup>®</sup>  
**µtech**  
DEDICATED TO EXCELLENCE



To receive your  
copy of our High  
Performance Amplifier  
Handbook please call  
**1•800•448•1025**

APEX MICRATECHNOLOGY CORPORATION

5980 North Shannon Road, Tucson, AZ 85741

CIRCLE NO. 2



# TINY SPDT SWITCHES

## ABSORPTIVE... REFLECTIVE

*dc to 4.6 GHz from \$32<sup>95</sup>* (10-24)

Tough enough to pass stringent MIL-STD-883 vibration, shock, thermal shock, fine and gross leak tests... useable to 6GHz... smaller than most RF switches... Mini-Circuits' hermetically-sealed (reflective) KSW-2-46 and (absorptive) KSWA-2-46 offer a new, unexplored horizon of applications. Unlike pin diode switches that become ineffective below 1MHz, these GaAs switches can operate down to dc with control voltage as low as -5V, at a blinding 2ns switching speed.

Despite its extremely tiny size, only 0.185 by 0.185 by 0.06 in., these switches provide 50dB isolation (considerably higher than many larger units) and insertion loss of only 1dB. The absorptive model KSWA-2-46 exhibits a typical VSWR of 1.5 in its "OFF" state over the entire frequency range. These surface-mount units can be soldered to pc boards using conventional assembly techniques. The KSW-2-46, priced at only \$32.95, and the KSWA-2-46, at \$48.95, are the latest examples of components from Mini-Circuits with unbeatable price/performance.

Connector versions, packaged in a 1.25 x 1.25 x 0.75 in. metal case, contain five SMA connectors, including one at each control port to maintain 3ns switching speed.

**Switch fast... to Mini-Circuits' GaAs switches.**

### SPECIFICATIONS

Pin Model	KSW-2-46		KSWA-2-46	
Connector Version	ZFSW-2-46		ZFSWA-2-46	
FREQ. RANGE	dc-4.6 GHz		dc-4.6 GHz	
INSERT. LOSS (db)	typ	max	typ	max
dc-200MHz	0.9	1.1	0.8	1.1
200-1000MHz	1.0	1.3	0.9	1.3
1-4.6GHz	1.3	1.7	1.5	2.6
ISOLATION (dB)	typ	min	typ	min
dc-200MHz	60	50	60	50
200-1000MHz	45	40	50	40
1-4.6GHz	30	23	30	25
VSWR (typ)	ON	1.3:1	1.3	
	OFF	—	1.4	
SW. SPEED (nsec)				
rise or fall time	2(typ)		3(typ)	
MAX RF INPUT (bWm)				
up to 500MHz	+17		+17	
above 500MHz	+27		+27	
CONTROL VOLT.	-8V on, OV off		-8V on, OV off	
OPER/STOR TEMP.	-55° to +125°C		-55° to +125°C	
PRICE (10-24)	\$32.95		\$48.95	
	\$69.95		\$79.95	

finding new ways ...  
setting higher standards

**Mini-Circuits**

A Division of Scientific Components Corporation

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500  
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

WE ACCEPT AMERICAN EXPRESS

CIRCLE NO. 4

C 117 REV. G



# SPDT & SP4T SWITCHES

## WITH BUILT-IN DRIVERS



### 10 to 3000MHz from \$39<sup>95</sup>

Now, high-speed, high-isolation switches with built-in drivers, tough enough to pass stringent MIL-STD-202 tests. There's no longer any need to hassle with the complexities of designing a TTL driver interface and then adding yet another component to your subsystem...it's already included in a rugged, low-cost, compact assembly.

Available in the popular hermetically-sealed TO-8 package or a small EMI-shielded metal connectorized case, these tiny PIN-diode reflective switches, complete with driver, can operate over a 10 to 3000MHz span with a fast 2μsec switching speed.

Despite their small size, these units offer isolation as high as 40dB(typ), insertion loss of only 1.1dB(typ), and a 1dB compression point of +27dBm over most of the frequency range. All models are TTL-compatible and operate from a dc supply voltage of 4.5 to 5.5 V with 1.8mA quiescent current.

Switch to Mini-Circuits for highest quality innovative products...and leave the driving to us.

finding new ways...  
setting higher standards

### Mini-Circuits


A Division of Scientific Components Corporation  
P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500  
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

WE ACCEPT AMERICAN EXPRESS

#### SPECIFICATIONS

	TOSW-230 ZSDR-230		TOSW-425 ZSDR-425	
Freq. Range(MHz)	10-3000		10-2500	
Insert. Loss (dB)	typ.	max.	typ.	max.
10-100MHz	1.3	1.9	1.3	1.7
100-1500MHz	1.1	1.9	1.1	1.7
1500-3000MHz	1.8	2.7	1.8	2.5
Isolation(dB)	typ.	min.	typ.	min.
10-100MHz	60	40	60	40
100-1500MHz	40	28	40	30
1500-3000MHz	35	22	35	22
1dB Compression(dBm)	typ.	min.	typ.	min.
10-100MHz	17	6	17	6
100-1500MHz	27	19	27	19
1500-3000MHz	30	28	30	28
VSWR(ON)	typ.	max.	typ.	max.
	1.3	1.6	1.3	1.6
Switching Time (μsec)	typ.	max.	typ.	max.
(from 50% TTL to 90% RF)	2.0	4.0	2.0	4.0
Oper. Temp.(°C)	-55 to +100		-55 to +100	
Stor. Temp.(°C)	-55 to +100		-55 to +100	
Price (10-24)	\$39.95		\$59.95	
(1-9)	\$89.95		\$109.95	



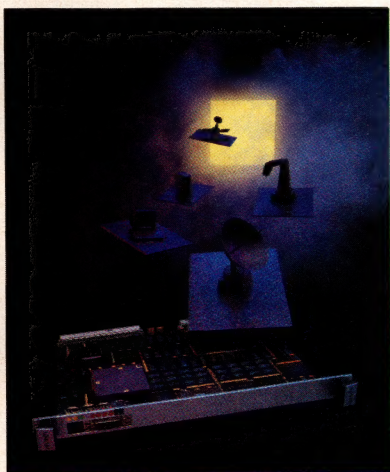

**On the cover:** Many add-on buses exist to help you expand your computer's capabilities at low cost. However, you should consider the ramifications of choosing a bus that only a few manufacturers support. See the Special Report on pg 82. (Photo concept and production by Heurikon Corp; photography by Ray Perkins Photography)

## SPECIAL REPORT

### Add-on buses

82

Add-on buses let you attach small I/O boards to your computer at low cost. However, these devices aren't without controversies, which revolve around technical issues, standards, and just how open the architectures of many add-on buses really are.

—Jon Titus, Editor

## DESIGN FEATURES

### Designer's guide to flash-ADC testing—Part 3 103

The first two parts of this series described the subtleties of flash A/D converters and the test methods used to evaluate these devices. Part 3 concludes the series with a discussion of the actual measurements you'll need to fully characterize flash A/D converters.—Walt Kester, Analog Devices

### Path-distribution analysis simplifies logic-circuit timing

125

Whereas logic simulators let you prove your circuit does what you want it to, timing-analysis CAD tools provide a more detailed examination of delay paths. Building a design from the results of a simulator without using a timing analyzer is like reading only the beginning of a story—you can't be quite sure how it will turn out.—Chi-Lai Huang and Marek Ryniewski, Cadence Design Systems Inc

## TECHNOLOGY UPDATES

### Switch-mode power-supply ICs: Smart parts let nearly any EE design switchers 29

Although available parts and literature recently made it possible for you to design your own switch-mode power supplies, making a supply that's cost-effective and reliable still requires expertise. You will benefit, however, from learning about this rapidly changing discipline so you can troubleshoot and understand how a supply helps or hinders your system's capabilities.


—Dan Strassberg, Associate Editor

Continued on page 7

EDN<sup>®</sup> (ISSN 0012-7515) is published 49 times a year (biweekly with 2 additional issues a month, except for February, which has 3 additional issues and July and December which have 1 additional issue) by Cahners Publishing Company, A Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158-1630. Terrence M McDermott, President; Frank Sibley, Senior Vice President/General Manager, Boston Division; Jerry D Neth, Senior Vice President/Publishing Operations; J J Walsh, Senior Vice President/Finance; Thomas J Dellamaria, Senior Vice President/Production and Manufacturing; Ralph Knupp, Vice President/Human Resources. Circulation records are maintained at Cahners Publishing Company, 44 Cook Street, Denver, CO 80206-5800. Telephone: (303) 388-4511. Second-class postage paid at Denver, CO 80206-5800 and additional mailing offices. POSTMASTER: Send address corrections to EDN<sup>®</sup> at the Denver address. EDN<sup>®</sup> copyright 1990 by Reed Publishing USA; Ronald G Segel, Chairman and Chief Executive Officer; Robert L Krakoff, President and Chief Operating Officer; William M Platt, Senior Vice President. Annual subscription rates for nonqualified people: USA, \$105/year; Canada/Mexico, \$125/year; Europe air mail, \$150/year; all other nations, \$150/year for surface mail and \$230/year for air mail. Single copies are available for \$10. Please address all subscription mail to Eric Schmieder, 44 Cook Street, Denver, CO 80206-5800.



# Twice the Power:

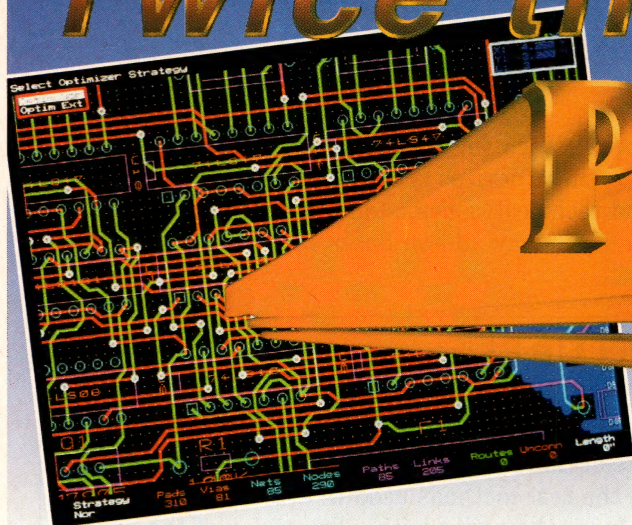

## PCB II

PC Board Layout  
on your PC

OrCAD Systems Corporation, the world's largest marketer of PC-based CAE software, has completely upgraded its popular printed circuit board layout software. Now you can have all the power features you need for your board designs on the PC you already own.

### Twice the capacity

OrCAD/PCB II has over double the capacity using a flexible, user-definable memory allocation system. The product now supports over 270 14-pin IC equivalent designs, 6000+ pads, 16,000+ equivalent track segments.

### Twice the options

OrCAD/PCB II comes with over 50 different printer drivers including most popular dot matrix and laser printers, over a dozen plotter drivers and over 50 display drivers. We conform to your system better than anyone.

### Twice the features

- Improved autorouting strategies means a faster route with more completions.
- Design Rule Check available as OrCAD/PCB II runs. Parameters are user configurable.
- Via and Track Optimization. Minimize vias and improve routing automatically.

OR8944-Intl.

- On-Line module browsing and reading. Call up modules and browse through their graphic descriptions.
- Gerber Viewer generates screen version of Gerber file to check output.

### Twice the value

OrCAD's commitment to you is that all of our powerful software will give you workstation performance without extra hardware, all handled within 640k RAM.

And the price? The package comes complete with autorouter, printer and plotter support, excellent documentation and more for a very reasonable price.

The price also includes one year of technical support, free product updates and access to our 24 hour BBS.

### Curious? Try it yourself with our demo disk.

Call for our demonstration disk and information packet. You'll see why more designers look to OrCAD for their design solutions.

**OrCAD**   
**Systems Corporation**

3175 NW Aloclek Drive  
Hillsboro, Oregon 97124  
(503) 690-9881

**If you would like more information about this or any other OrCAD product, contact your local OrCAD representative.**

<b>AUSTRIA</b> <b>Dahms</b> <b>Elektronik</b> 0316/64030-0 Fax: 64030-29	<b>ITALY</b> <b>BRM Italiana</b> TEL: 011/771.00.10 FAX: 011/771.01.98
<b>BELGIUM</b> <b>INEX</b> (02) 649.99.91 Fax: (02)649.27.92	<b>ITALY</b> <b>MicroData Systems</b> 0187/966123 Fax: 0187/988322
<b>DENMARK/</b> <b>NORWAY</b> <b>NordCAD</b> 98 17 32 99 Fax: 98 17 37 41	<b>SPAIN</b> <b>Next-For S.A.</b> 504 02 01 Fax: 504 00 69
<b>UK</b> <b>ARS Micro-</b> <b>systems</b> (0276) 685005 Fax: (0276) 61524	<b>SWEDEN</b> <b>Technology Partners</b> (468)790 97 75 Fax: (468)16 77 86
<b>FINLAND</b> <b>Elektrotel OY</b> (358 0)754-3122 Fax: 754-2593	<b>SWITZERLAND</b> <b>Logmatic AG</b> 056/83 38 38 Fax: 056/83 38 40
<b>FRANCE</b> <b>ALS Design</b> (331) 46 04.30.47 Fax: 48 25.93.60	<b>W. GERMANY</b> <b>Compware, GmbH</b> 4940/81 80 74 Fax: 4940/81 10 37

**Call today for your demo disk**



**VP/Publisher**  
Peter D Coley  
**VP/Editor/Editorial Director**  
Jonathan Titus  
**Managing Editor**  
Joan Morrow

**Assistant Managing Editor**  
Susan L Rastellini  
**Special Projects**  
Gary Legg

**Home Office Editorial Staff**  
275 Washington St, Newton, MA 02158  
(617) 964-3030

Tom Ormond, *Senior Editor*  
Charles Small, *Senior Editor*  
Jay Fraser, *Associate Editor*  
John A Gallant, *Associate Editor*  
Michael C Markowitz, *Associate Editor*  
Dave Pryce, *Associate Editor*  
James P Scanlan, *Associate Editor*  
Julie Anne Schofield, *Associate Editor*  
Dan Strassberg, *Associate Editor*  
Anne Watson Swager, *Associate Editor*  
Chris Terry, *Associate Editor*  
Kathleen M Vejvoda, *Associate Editor*  
Helen McElwee, *Senior Copy Editor*  
Susan Bureau, *Copy Editor*  
Christine McElvenny, *Senior Production Editor*  
Gabriella A Fodor, *Production Editor*  
Brian J Tobey, *Production Editor*

**Editorial Field Offices**  
Steven H Leibson, *Senior Regional Editor*  
Boulder, CO: (303) 494-2233  
Doug Conner, *Regional Editor*  
Atascadero, CA: (805) 461-9669  
J D Mosley, *Regional Editor*  
Arlington, TX: (817) 465-4961  
Richard A Quinnett, *Regional Editor*  
Aptos, CA: (408) 685-8028  
Maury Wright, *Regional Editor*  
San Diego, CA: (619) 748-6785  
Brian Kerridge, *European Editor*  
011-44-603-630782  
(St Francis House, Queens Rd,  
Norwich, NR1 3PN, UK)

**Contributing Editors**  
Robert Pease, Don Powers,  
Bill Travis

**Editorial Coordinator**  
Kathy Leonard

**Editorial Services**  
Helen Benedict, Nicky Woodlock

**Art Staff**  
Ken Racicot, *Senior Art Director*  
Chinsoo Chung, *Associate Art Director*  
Cathy Madigan, *Staff Artist*  
Martha Crowell, *Staff Artist*

**Production/Manufacturing Staff**  
Andrew A Jantz, *Production Supervisor*  
Michele R Weinberg, *Production Assistant*  
Deborah Hodin, *Production Assistant*  
Lisa K Mariano, *Production Assistant*  
Diane Malone, *Composition*

**Director of Art Department**  
Joan Kelly  
Norman Graf, *Associate*

**VP/Production/Manufacturing**  
Wayne Hulitzky

**Director of Production/Manufacturing**  
John R Sanders

**Business Director**  
Deborah Virtue

**Marketing Communications**  
Anne Foley, *Promotion Manager*  
Sara Morris, *Marketing Services Administrator*  
Gordon Keegan, *Promotion Specialist*

## Thermal-analysis software: 47 Thermal images provide reliability clues

Reliability is critical for products that aren't easily serviced, require extreme safety and precision, and are dangerous to operate. Unfortunately, the delicate relationship between temperature and performance makes predicting reliability tricky. Thanks to new thermal-analysis software for EEs, though, you can identify thermal problems and alter your design before you build it.—Anne Watson Swager, *Associate Editor*

## PRODUCT UPDATES

High-performance 32-bit $\mu$ P	65
Network interface controller	68
CISC workstations	70

## DESIGN IDEAS

Averaging increases $\mu$ P's ADC resolution	139
Precision amplifier turbocharges buffer	140
Feedback enhances thermometer accuracy	142

## EDITORIAL 25

The facsimile machine gives engineers a new way to get information. Soon you can help test an EDN FAX service that will send you product information in seconds.

## NEW PRODUCTS

Components & Power Supplies . . . . .	149
Computers & Peripherals . . . . .	152
CAE & Software Development Tools . . . . .	156
Integrated Circuits . . . . .	162
Test & Measurement Instruments . . . . .	166

## DEPARTMENTS

News Breaks . . . . .	15
Career Opportunities . . . . .	177
EDN's International Advertisers Index . . . . .	183

Cahners Publishing Company, A Division of Reed Publishing USA ☐ Specialized Business Magazines for Building & Construction ☐ Manufacturing ☐ Foodservice & Lodging ☐ Electronics & Computers ☐ Interior Design ☐ Printing ☐ Publishing ☐ Industrial Research & Technology ☐ Health Care ☐ and Entertainment. Specialized Consumer Magazines: ☐ American Baby ☐ and Modern Bride.







# Fiber Op

With FDDI, it'll seem like your data gets there before it's sent. Because FDDI is ten times faster than Ethernet.

And if you thought FDDI was just a dream, you can open your eyes. Now there's an FDDI chip set—just ask any of the companies bringing systems to market.

The chip set is called SUPERNET™ and it's a lot more than just a few sleek chips. Because AMD brings more knowledge and expertise to FDDI systems than any other component manufacturer.

In fact, AMD founded the Advanced Networking Group—a meeting of the minds of the most important mainframe, workstation, board,

network, semiconductor and software companies. They're getting together to insure compliance and interoperability so FDDI will be a wise choice for your customers.

AMD was part of setting the standards long before the Advanced Networking Group. (We've been on the ANSI standard committee since its inception.)

More good news. Because SUPERNET based systems meet standards, they're interoperable with FDDI systems from other vendors.

If you've been waiting to design an FDDI system, don't let another second slip away. Contact us to find out more about FDDI and the World Network.™

## Advanced Micro Devices

For more information write "FDDI" on your letterhead and mail to: (In Europe) AMD Mail Operations, P.O. Box 4, Westbury-on-Trym, Bristol BS9 3DS United Kingdom  
(In Asia) Advanced Micro Devices Far East Ltd., Rm. 1201-2 Harcourt House, 39 Gloucester Road, Hong Kong, Attn: Andrew Ng. (In Japan) Advanced Micro Devices Japan Ltd., Shinjuku Kokusai Bldg., 6-6-2 Nishi-Shinjuku, Shinjuku-ku, Tokyo 160, Japan.




**SIEMENS**



**More than a microcontroller look-alike**

# **The New Reference Class**



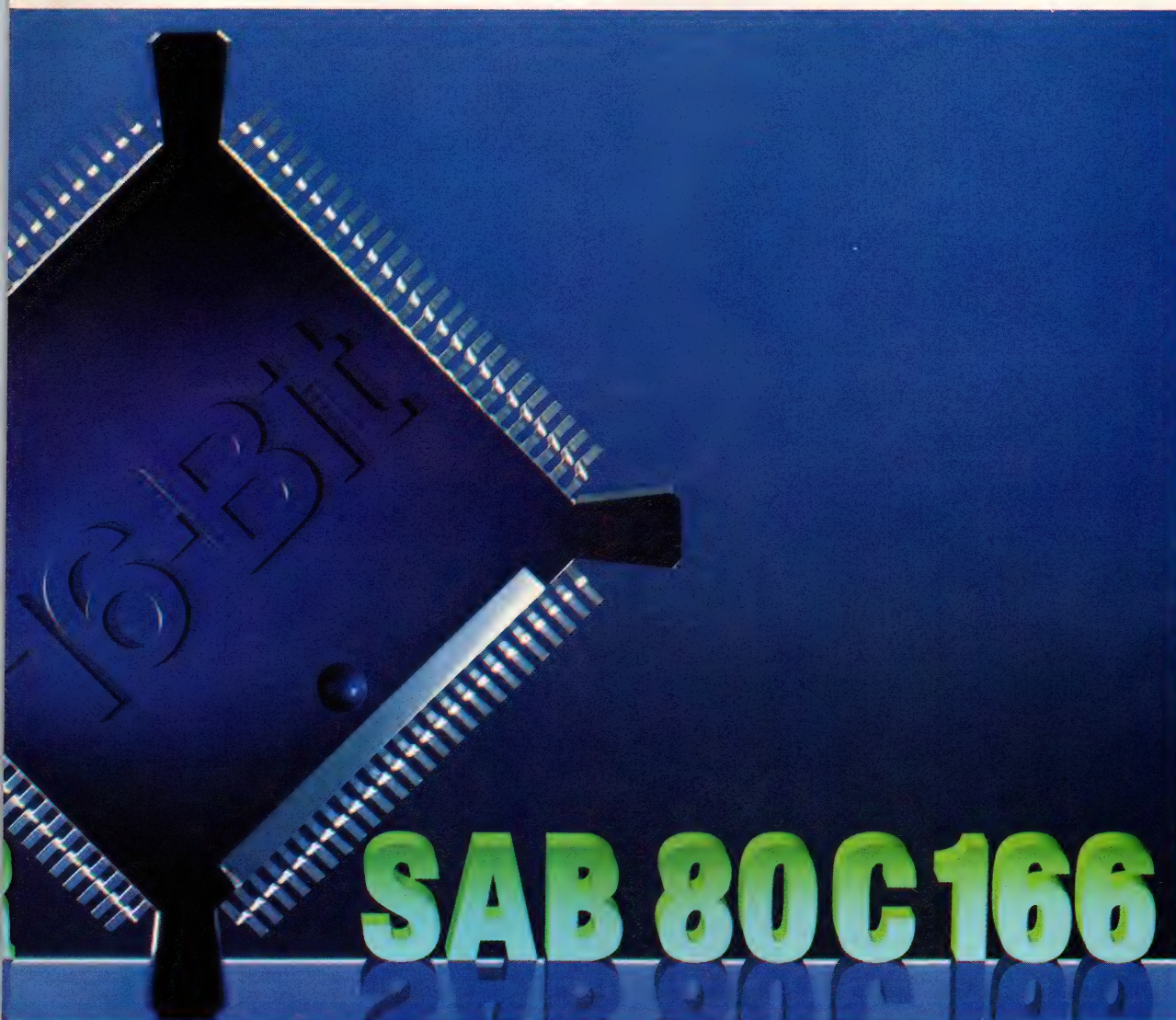

MC&D

A19100-HL5818-X-7600

The SAB 80C166 integrates the best from today's new processors & advanced microcontrollers: the processing speed and data throughput of the micro processors plus the fast response and peripheral integration of the micro controllers.

The 16-bit SAB 80C166 microcontroller is tailored to high-speed real-time processing, satisfying all the demands of modern embedded-control systems. In other words it is just as much at home in the complex control

world of automobiles as it is in fast data terminals or time-critical industrial control systems.

Here's a taste of how this new 16-bit controller performs: instruction cycle time 100 ns, processes 90% of all instructions in one cycle (that's typical RISC performance), interrupt response 400 ns (worstcase!), complete task switch 100 ns.

If that goes down well and you want to find out more, contact your local Siemens office or just write to:


Europe:

Siemens AG, Infoservice HL 5818, Postfach 2348, D-8510 Fürth

USA:

Siemens Semiconductor Group, 2191 Laurelwood Road, Santa Clara, CA 95054

Quoting: „SAB 80C166“.

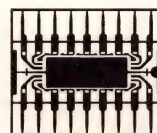


**TopTech  
Semiconductors  
Siemens**





Even though our products have  
been to Jupiter and beyond, you can  
still find them out in your garage.





Whether it's one of the switches in your automobile, or connectors used in space exploration, you'll find the products of ITT ElectroMechanical Components Worldwide everywhere.

With seventy-five years of leadership in the electronics industry, ITT EMC Worldwide is one of the world's leading suppliers of electronic components. You know us as ITT Cannon, Schadow, Jeanrenaud, Pomona Electronics, MTI and Seaelectro. With manufacturing facilities, engineering centers and customer service represen-

tatives in virtually every part of the world.

Our history is one of innovation, and ever-increasing capabilities. That's precisely why many of our products go on to become industry standards.

At ITT EMC Worldwide, we build reliability into every product we sell. That's why you'll find us in everything from appliances to satellites.

Our philosophy of "building in" quality control and testing means that you get the best possible product, every time. What's more, ITT EMC


Worldwide manufactures and sells quality test accessories, to assist you in building a quality product as well.

No matter where in the world you are, chances are we have an office nearby. So drop us a line today. Even though we're an international company, we may be closer than you think.

*1851 East Deere Avenue  
Post Office Box 35000  
Santa Ana, CA 92705-6500  
Or call (714) 261-5300*

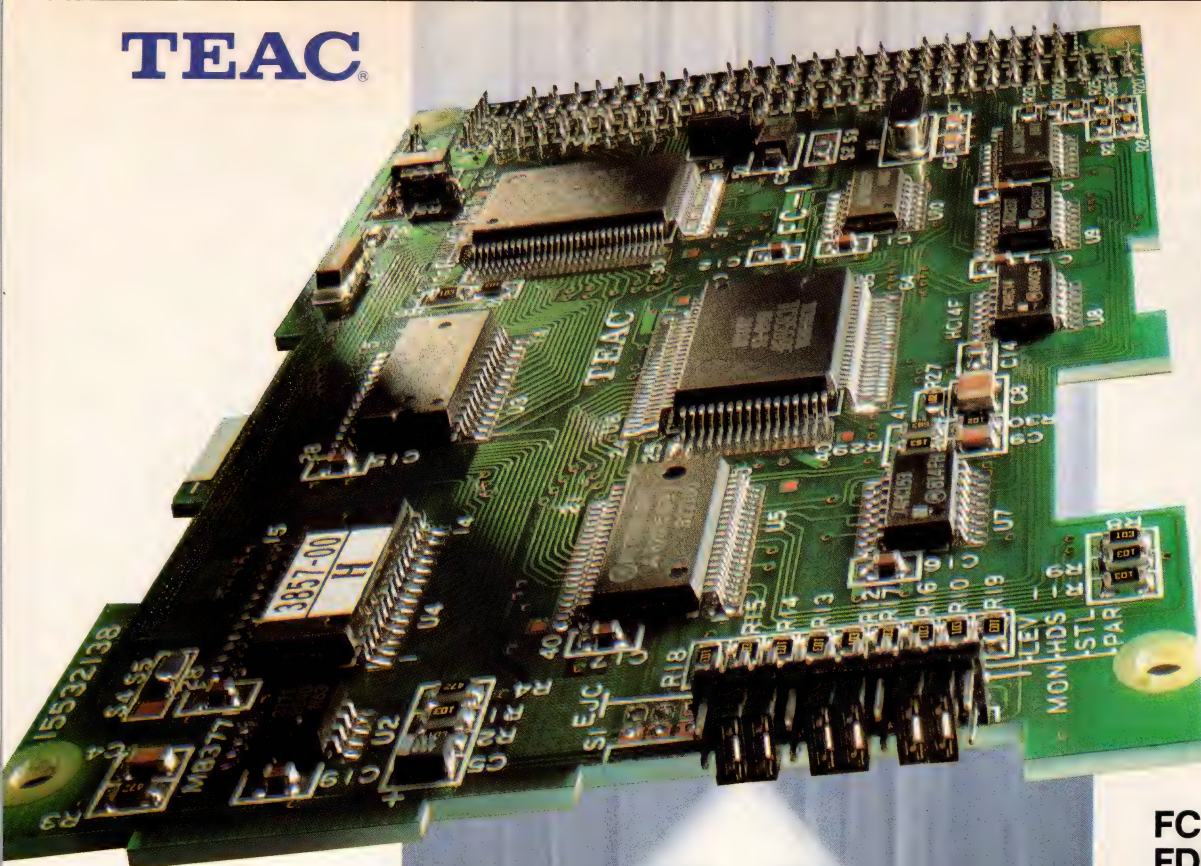**ITT** ElectroMechanical  
Components Worldwide  
*Discover our strengths.*



**TEAC**

**FC-1**  
FDD SCSI Interface  
Controller

# The FC-1: A Fast and Flexible SCSI FDD Controller

## The Easy Way to Make Your Floppy Disk Drives Intelligent

An FC-1, small enough to fit inside a 3.5" FDD, has the intelligence to handle device-independent control of 3.5 and 5¼" FDDs for the host computer. At its best with 4MB perpendicular recording method drives like the TEAC FD-235J, and equally happy with formats down to 0.5MB, it is compact, lightweight, and competitively priced. Also offering expansibility and reduced host loads, the FC-1 is ideal for the widest possible range of applications.

TEAC FDDs with built-in FC-1 SCSI controllers, including the FD-235HS and FD-235JS, are also available.

CIRCLE NO. 11



**FD-235J**  
3.5" Micro Floppy Disk Drive

**TEAC CORPORATION** 3-7-3 NAKA-CHO, MUSASHINO, TOKYO, JAPAN TEL: (0422)52-5041 TLX: 2822451 FAX: (0422)55-2554

■Hong Kong, Nissei Sangyo Co., Ltd. Hong Kong Branch Tel: 3-343441-6; KARIN ELECTRONIC SUPPLIES CO., LTD. Tel: 3-898252 ■Singapore, NISSEI ELECTRONICS, LTD. SINGAPORE BRANCH OFFICE Tel: 2357900; UAC SINGAPORE REP. OFFICE Tel: 2922608 ■New Zealand, DATAMATIC NETWORKS LIMITED Tel: 09-444-0760 ■Australia, AWA DISTRIBUTION Tel: 02-888-9000 ■Indonesia, CHUGAI BOYEKI CO., LTD. Tel: 370824 ■Philippines, COMPEX INTERNATIONAL INC. Tel: 213020 ■India, Priya Electronics & Chemicals Limited Tel: 2863611 ■Kuwait, Bader Al Mulla & Brothers Co. W.L.L. Tel: 2423250 ■United Kingdom, TEKDATA LIMITED Tel: 0782 577677; Data Peripherals (UK) Limited Tel: 0785 57050 ■F.R. Germany, nbn Elektronik GmbH Tel: 08152/390 ■Austria, nbn Elektronik GmbH Tel: 0316/40 28 05 ■Netherlands, SIMAC DATA B.V. Tel: 040-582933 ■Belgium & Luxemburg, SIMAC ELECTRONICS SPRL/BVBA Tel: 02/252.36.90 ■France, TEKELEC AIRTRONIC S.A. Tel: (1)4534-75-35 ■Italy, A.E.S.S.E. S.p.A. Tel: 02/54.64.741 ■Spain, ATAIO INSTRUMENTOS S.A. Tel: 733 05 62 ■Portugal, BASF PORTUGUESA LDA. Tel: (351) 1-562511 ■Switzerland, WENGER PERIPHERALS AG Tel: 01/830 75 55 ■Denmark, Dansk Binær Teknik A/S Tel: 03/66 20 20 ■Sweden, MACROTEC AB Tel: 08-733 02 20 ■Norway, SCANTELE A/S Tel: (02)65 69 20 ■Finland, INSTRUMENTARIUM CORPORATION Tel: 90-528 4338

\*If no distributor listed above is in your area, please contact us directly for further details about our products.



# NEWS BREAKS

---

EDITED BY JULIE ANNE SCHOFIELD

## **FIBER-OPTIC DATA LINKS REPLACE CABLES**

Concise Technology's (Pontypridd, UK, FAX 603-401158) fiber-optic interfaces can replace RS-232C, RS-422, and RS-423 cards without requiring that you change your communications software. Model CPCFS of the FOSIL (Fiber-Optic Standard Interface Link) 2-cable interface is a short card that fits IBM PC/XT and PC/AT expansion slots; model CVMEFS is a 3U or 6U VMEbus module. The company claims that the interfaces work over a distance of 1.4 miles using 100/140- $\mu$ m optical fiber at standard baud rates. These cards process all RS-232C signals, control as well as data. The company also offers external repeaters, which let you extend the length of a link. The interfaces cost £175 per channel. The company is developing cards for STE Bus and STD Bus systems. The company hopes that the industry will adopt FOSIL as a standard and will answer any serious inquiries.—Brian Kerridge

## **VMEbus CPU CARD INCLUDES 50-MHz LOCAL BUS**

Heurikon Corp's (Madison, WI, (608) 271-8700) 68040-based Model HK68/V4F VMEbus CPU card includes a 50-MHz 200M-byte/sec synchronous local bus. Called Corebus, this local bus connects the onboard CPU, memory, and I/O subsystems, and provides expansion capability via daughter cards. The card also includes an industry-standard VSB interface with master/slave support. Standard features of the card include 2M to 8M bytes of 70-nsec 2-way-interleaved static-column dynamic RAM and as much as 2M bytes of EPROM. The card also includes 512 bytes of nonvolatile RAM that can store configuration information; the card can address an additional 960M bytes of memory via the VSB interface. I/O capabilities include two RS-232C ports and an optional RS-422 port. You can add support for Ethernet or SCSI via Corebus cards. Software support for the HK68/V4F includes the Unix, OS-9, VRTX, and VxWorks operating systems. A version of the board with a 25-MHz 68040 and 2M bytes of memory will be available the second quarter of this year for \$3495.—Maury Wright

## **PARALLEL COMPUTER OPERATES WITH UNIX SUBSYSTEM**

The MP-1 family of data-parallel computers from Maspar Computer Corp (Sunnyvale, CA, (408) 736-3300) consists of eight models. The models have 1024 to 16,384 processing elements (PEs) arranged in a single-instruction, multiple-data (SIMD) array. A distributed-memory architecture provides each PE with its own local memory ranging from 16M to 256M bytes. The computer uses a 500,000-transistor custom ASIC, which includes 32 PEs, the local memory, and the interprocessor interfaces.

The computer communicates with a DEC VAXstation 3520 subsystem, which uses the Ultrix operating system. This combination lets the user create parallel programs using X-Windows for the Unix operating system. The 16,384-PE model delivers as many as 30,000 MIPS and 1250M flops. Prices start at \$160,000 for the 1024-PE model; the 16,384-PE model costs \$800,000.—John Gallant



# NEWS BREAKS

---

## **BUY CAE SOFTWARE, GET A WORKSTATION**

In a pitch reminiscent of the consumer electronics wars, Racal-Redac (Westford, MA, (508) 692-4900) will give you a Sun Microsystems' (Mountain View, CA, (415) 960-1300) Sparcstation 1 when you purchase its \$49,950 Visula Plus CAE software. As an added inducement, the company will also include a 6-month subscription to Logic Automation's (Beaverton, OR, (503) 690-6900) Smartmodels hardware-modeling library. Visula Plus contains a schematic-capture package and the Cadat simulator. It's based on a nonproprietary relational database with structured-query-language (SQL) access.—Michael C Markowitz

## **RISC $\mu$ P CHIP SET GETS AN ALTERNATE SOURCE**

Since its initial availability in 1986, the Clipper RISC processor has gone through some tough times. National Semiconductor Corp acquired the  $\mu$ P chip set through its purchase of Fairchild Semiconductor Corp and then sold the set to its current owner, Intergraph Corp, forming the core product of Intergraph's Advanced Processor Div (Palo Alto, CA, (415) 852-2365). Now the rough waters seem to be quieting for the  $\mu$ P as a second source, Samsung Electronics Co Ltd (Seoul, Korea, (02) 751-3921), comes on board. Initially, Samsung will fabricate the second-generation C300 chip set and has a worldwide, nonexclusive right to market this product. It expects to begin production in July and will have production volumes in December. The company will also manufacture the first-generation C200 chip set for Intergraph APD and has the option of acquiring marketing rights for this product as well.—Steven H Leibson

## **VMEbus BACKPLANE TIGHTENS SPECIFICATION**

If your VMEbus card cage is running close to its limit, consider the V346/HS VMEbus backplane from Dage (GB) Ltd (Aylesbury, UK, FAX 296-435408). The backplane can withstand harsh environments and lifts card-cage constraints from your VMEbus system's performance. Off-board active-line terminators and a stripline tracking technique guarantee you a characteristic signal-line impedance of  $52 \pm 2\Omega$  on all data lines. Insulated 120A busbars are connected to the 0 and 5V rails by studs uniformly distributed across the assembly for uniform, minimized dc resistance. The full-width 21-slot double-height model is available now for £525; 5- and 9-slot versions will follow.—Brian Kerridge

## **MENTOR TAKES ON A NEW STUDENT AND WORKSTATION**

Mentor Graphics (Beaverton, OR, (503) 626-7000) is killing two birds with one stone. Under pressure from Apollo Computer's (since acquired by Hewlett-Packard (Palo Alto, CA, (800) 752-0900)) fall from its perch as the workstation market leader and the consolidation of Cadence Design Systems (San Jose, CA, (408) 943-1234) and Gateway Design Automation, Mentor has responded by announcing the acquisition of Silicon Compiler Systems (San Jose, CA (408) 371-2900) in a deal valued at approximately \$110 million. With research facilities in Belgium, England, Japan, Singapore, Oregon, California, Michigan, Utah, and New Jersey, the expanded company will have worldwide development facilities. The move both strengthens Mentor's IC-design and -simulation capability and provides the resources and expertise to port Mentor's tools to Sun Microsystems' (Mountain View, CA, (415) 960-1300) workstations. Mentor Graphics expects to release its products on Sun workstations by late 1990.—Michael C Markowitz



20ns  
CY7C291A  
2K x 8  
PROM

15ns  
CY7C245A  
2K x 8  
Registered  
PROM

**On one hand,  
we're the fastest.**

**On the other  
hand, we're the  
densest.**

30ns  
CY7C277  
32K x 8  
Registered PROM

35ns  
CY7C271  
32K x 8  
Power Down  
PROM

35ns  
CY7C279  
32K x 8  
Latched PROM

35ns  
CY7C274  
32K x 8  
EPROM Pinout

### **If you need speed in a PROM, call us.**

We have the world's fastest CMOS reprogrammable PROMs, from 4K to 256K.

Our new 20ns 16Ks, 7C291A and 7C293A, can improve system performance by running high speed programs straight from PROM without downloading to RAM. Yet using the 7C293A you can power down to 30mA.

Save board space, cost, power.

For high-speed pipelined applications, our 16K 7C245A registered PROM accesses data in just 10ns, and requires only 15ns setup.

### **If you need the densest PROM, call us.**

We have four 256Ks that can pack the maximum available high speed storage into a space-saving 300 mil DIP, or PLCC that requires just .3 square inches, all at a record setting 35ns.

**512 x 8. 1K x 8. 2K x 8.  
8K x 8. 16K x 8. 32K x 8.**

We have registered versions. Registered

diagnostic versions.

EPROM pinouts.

Power switched versions.

We have the PROM you

need with the speed and features you want.

**PROM.**

### **Reprogrammable PROM.**

Our CMOS floating-gate memory means you can order windowed versions of almost every part. You get the high speed of a PROM, with the benefits of reprogrammability.

### **Cool, low power CMOS.**

So you don't use a lot of power, even when you need a lot of memory. Many parts power down even further when deselected.

**Call. Get your hands on our data book.**

**Data Book  
Hotline**

**1-800-952-6300\***

**Ask for dept.  
C4E**



**CYPRESS  
SEMICONDUCTOR**




\*1-800-387-7599 In Canada. (32)2-672-2220 In Europe.  
©1989 Cypress Semiconductor, 3901 North First Street, San Jose, CA 95134  
Phone: (408)943-2666, Telex 821032 CYPRESS SNJUD, TWX 910-997-0753.



# RF TRANS

*Over 50 off-the-shelf models...*

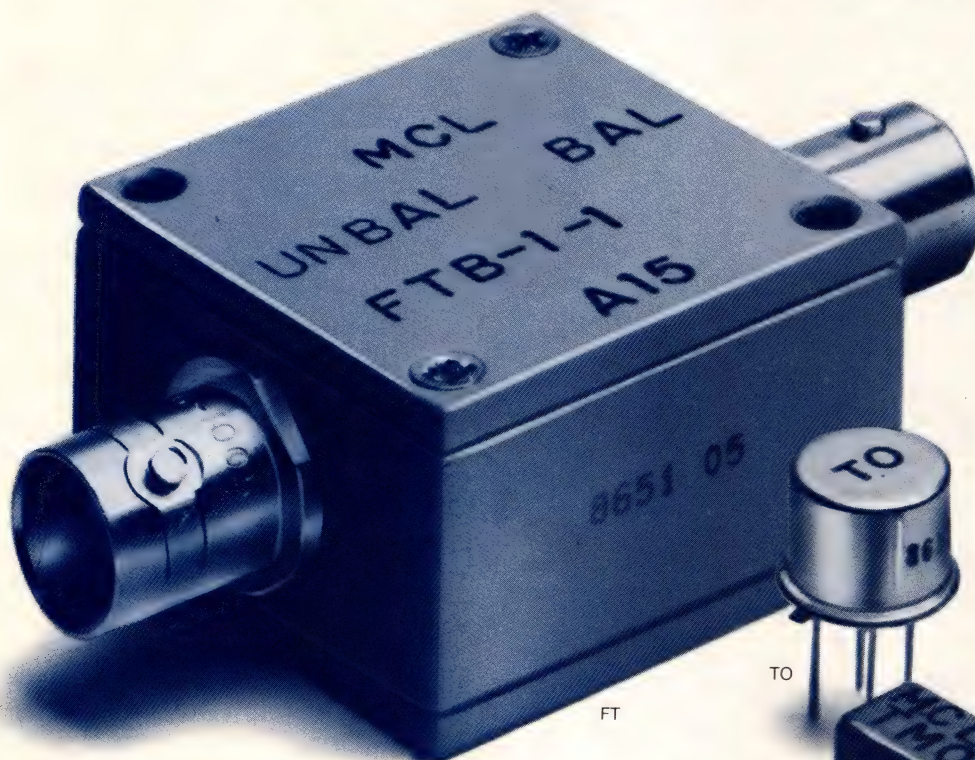


Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specific frequency range? ...Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, connector or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements\*). Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100 mA DC primary current, use the T-H series. Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard; request other types.

Available for immediate delivery with one-year guarantee.

Call or write for 68-page catalog or see our catalog in EEM, or Microwaves Product Data Directory.

\*units are not QPL listed

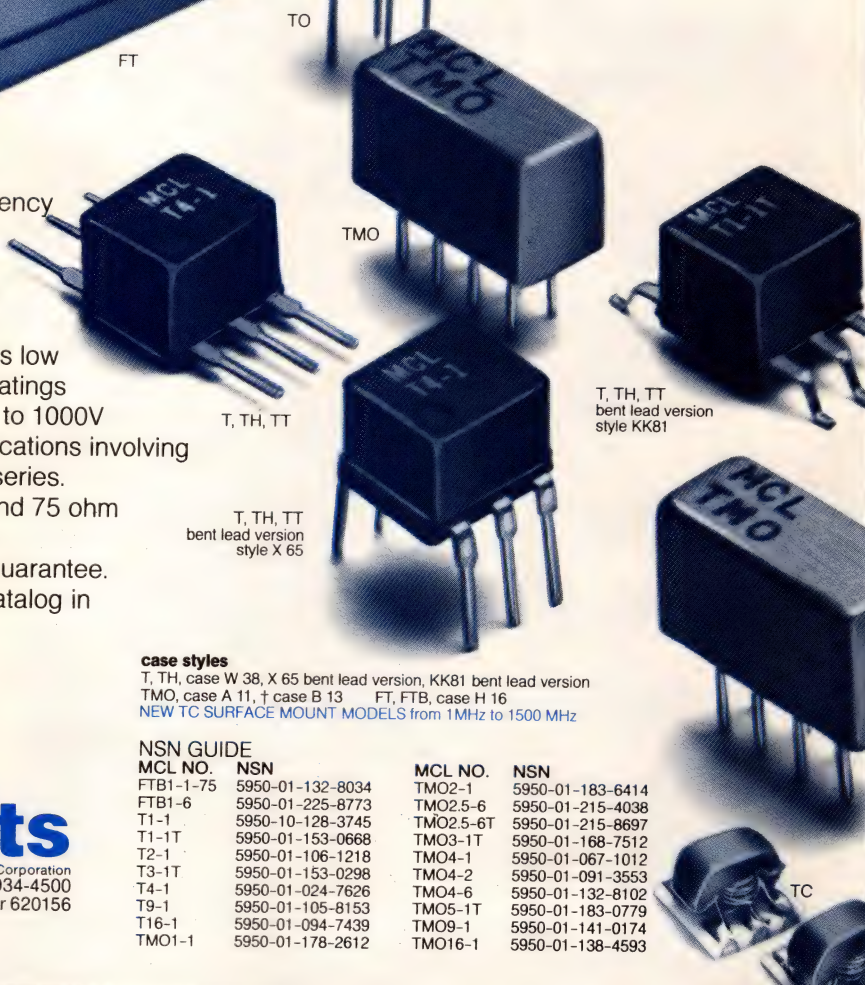

#### case styles

T, TH, case W 38, X 65 bent lead version, KK81 bent lead version  
TMO, case A 11, † case B 13 FT, FTB, case H 16  
NEW TC SURFACE MOUNT MODELS from 1MHz to 1500 MHz

#### NSN GUIDE

MCL NO.	NSN
FTB1-1-75	5950-01-132-8034
FTB1-6	5950-01-225-8773
T1-1	5950-10-128-3745
T1-1T	5950-01-153-0668
T2-1	5950-01-106-1218
T3-1T	5950-01-153-0298
T4-1	5950-01-024-7626
T9-1	5950-01-105-8153
T16-1	5950-01-094-7439
TMO1-1	5950-01-178-2612

MCL NO.	NSN
TMO2-1	5950-01-183-6414
TMO2.5-6	5950-01-215-4038
TMO2.5-6T	5950-01-215-8697
TMO3-1T	5950-01-168-7512
TMO4-1	5950-01-067-1012
TMO4-2	5950-01-091-3553
TMO4-6	5950-01-132-8102
TMO5-1T	5950-01-183-0779
TMO9-1	5950-01-141-0174
TMO16-1	5950-01-138-4593

finding new ways ...  
setting higher standards

## Mini-Circuits

A Division of Scientific Components Corporation  
P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500  
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

CIRCLE NO. 12



# FORMERS

3KHz-800MHz from \$3<sup>25</sup>

case style number see opposite page			MODEL NO.	$\Omega$ RATIO	FREQUENCY MHz	INSERTION LOSS			PRICE \$	
						3dB MHz	2dB MHz	1dB MHz	Qty. (1-9)	
A*		T	T1-1T	1	.05-200	.05-200	.08-150	2-80	4.45	
			T1-6T	1	.003-300	.003-300	.01-150	.02-50	6.95	
			T2-1T	2	.07-200	.07-200	.1-100	.5-50	4.95	
			T2.5-6T	2.5	.01-100	.01-100	.02-50	.50-20	4.95	
			T3-1T	3	.05-250	.05-200	.1-200	.5-70	4.95	
			T4-1	4	2-350	2-350	.35-300	2-100	3.25	
			T4-6T	4	.02-250	.02-250	.05-150	.01-100	4.45	
			T5-1T	5	3-300	3-300	.6-200	.5-100	4.95	
			T8-1T	8	.03-140	.03-140	.10-90	1-60	7.95	
			T13-1T	13	3-120	3-120	.7-80	.5-20	4.95	
			T16-6T	16	.03-75	.03-75	.06-30	.1-20	5.65	
			TH	T4-1H	4	10-350	10-350	15-300	25-200	5.95
			TMO	TMO1-1T	1	.05-200	.05-200	.08-150	2-80	7.95
				TMO2-1T	2	.07-200	.07-200	.1-100	.5-50	8.45
				†TMO2.5-6T	2.5	.01-100	.01-100	.02-50	.05-20	8.45
				†TMO3-1T	3	.05-250	.05-250	.1-200	.5-70	7.95
				TMO4-1	4	2-350	2-350	.35-300	2-100	6.25
				TMO5-1T	5	3-300	3-300	.6-200	.5-100	8.45
				TMO13-1T	13	3-120	3-120	.7-80	.5-20	8.45
B*		TT		TT1-6	1	.004-500	.004-500	.02-200	.1-50	6.95
			TT1.5-1	1.5	.075-500	.075-500	2-100	1-50	5.95	
			TT2.5-6	2.5	.01-50	.01-50	.025-25	.05-10	6.45	
			TT4-1	3	.05-200	2-50	2-50	1-30	5.95	
			TT4-1A	4	.01-300	.01-300	.02-250	.03-180	6.95	
			TT25-1	25	.02-30	.02-30	.05-20	.1-10	9.95	
			TTMO	TTMO25-1	25	.02-30	.02-30	.05-20	.1-10	11.95
			TTMO1-1	1	.005-100	.005-100	.01-75	.05-40	11.45	
			TTMO4-1A	4	.01-300	.01-300	.02-250	.03-180	13.95	
			C		T	T1-1	1	.15-400	.15-400	.35-200
T1.18-3	1.18	.001-250				.001-250	.002-200	.003-50	5.65	
T1-6	1	.01-150				.01-150	.02-100	.05-50	5.65	
T1.5-1	1.5	.1-300				.1-300	2-150	.5-80	4.45	
T1.5-6	1.5	.02-100				.02-100	.05-50	.01-25	5.65	
T2.5-6	2.5	.01-100				.01-100	.02-50	.05-20	4.45	
T4-6	4	.02-200				.02-200	.05-150	.1-100	4.45	
T9-1	9	.15-200				.15-200	.3-150	2-40	3.95	
T16-1	16	3-120				3-120	.7-80	.5-20	4.45	
T36-1	36	.03-20				.03-20	.05-10	.1-5	6.95	
TO	TO-75	1				10-500	—	10-500	40-250	6.95
TH	T1-1H	1				8-300	8-300	10-200	25-100	5.95
	T9-1H	9				2-90	2-90	3-75	6-50	6.45
	T16-H	16				7-85	7-85	10-65	15-40	6.45
	TMO	TMO1-02				1	1-800	1-800	2-500	—
TMO	TMO1-1	1				.15-400	.15-400	.35-200	2-50	6.25
	TMO1.5-1	1.5				.1-300	.1-300	2-150	.5-8	8.45
	†TMO2.5-6	2.5				.01-100	.01-100	.02-50	.05-20	7.95
	†TMO4-6	4				.02-200	.02-200	.05-150	.1-100	7.95
	TMO6-1	6				3-200	3-200	.5-150	.5-50	7.95
	TMO9-1	9	.15-200	.15-200	.3-150	2-40	7.95			
	TMO16-1	16	.3-120	3-120	.7-80	.5-20	7.95			
	D		T	T2-1	2	.050-600	.050-600	.1-400	5-200	3.95
T3-1				3	5-800	5-800	2-400	—	4.45	
T4-2				4	2-600	2-600	5-500	2-250	3.95	
T8-1				8	.15-250	.15-250	.25-200	2-100	3.95	
T14-1				14	2-150	2-150	.5-100	2-50	4.95	
TMO				TMO2-1	2	.050-600	.050-600	.1-400	5-200	7.95
TMO3-1				3	5-800	5-800	2-400	—	8.45	
TMO4-2				4	2-600	2-600	5-500	2-250	7.95	
TMO8-1				8	.15-250	.15-250	.25-200	2-100	7.95	
TMO14-1				14	2-150	2-150	.5-100	2-50	8.45	
FT	FT1.22-1	1.22	.005-100	.005-100	.01-50	.05-25	35.95			
	FT1.5-1	1.5	.1-400	.1-400	5-200	1-100	35.95			
	E		FTB	FTB-1	1	2-500	2-500	.5-300	1-100	36.95
FTB1-6				1	.01-125	.01-125	.05-50	.1-25	36.95	
■FTB-1-75				1	.5-500	.5-500	.5-300	10-100	36.95	
F					T	T-622	1	0.1-200	0.1-200	0.5-100
	T626	1	0.01-10			0.01-10	0.2-5	.04-2	3.95	

■ Denotes 75 ohm models

\* FOR A AND B CONFIGURATIONS

Maximum Amplitude Unbalance  
0.1 dB over 1 dB frequency range  
0.5 dB over entire frequency range

Maximum Phase Unbalance  
1.0° over 1 dB frequency range  
5.0° over entire frequency range



# At the 4front of 4

## Introducing Oki's 4-Meg DRAMs and Modules

End-user demand for more memory-intensive, high-performance systems continues to complicate your design tasks. You're pressured to increase memory capacity, yet decrease board space. Increase reliability, yet cut costs. And beat the competition to market by reducing design time.

OKI 4-MEG PRODUCT LINE-UP			
Device	Organization	Access Mode	Access Time MAX. (ns)
MSM514100-8XX	4M x 1	Fast Page	80
MSM514100-10XX			100
MSM514102-8XX	4M x 1	Static Column	80
MSM514102-10XX			100
MSM514400-8XX	1M x 4	Fast Page	80
MSM514400-10XX			100
MSM514402-8XX	1M x 4	Static Column	80
MSM514402-10XX			100
Packaging Options Include:			
XX = 'JS'...350 mil SOJ			
'RS'...400 mil DIP			
'ZS'...400 mil ZIP			
MSC2340-XY59	4M x 9	Fast Page	80, 100
Speed Options Include:			
X = '8'...80 ns.			
'10'...100 ns.			

Oki's advanced 4-Meg DRAM technology can ease the pressure. Our space-saving 4-Megx9 single inline memory module, 4-Megx1 and 1-Megx4 DRAMs offer the problem-solving advantages you need to simplify high-density design tasks. Like quadrupling memory with our 4-Megx9. Manufactured to JEDEC standard dimensions and pin-outs like our 1-Megx9, Oki's 4-Megx9 easily replaces the 1-Meg—saving valuable redesign time, increasing reliability, and cutting costs.

And when it comes to superior performance and wide-ranging capabilities, no other 4-Meg supplier can match Oki's offering: The lowest operating and standby currents. 1,024 cycles/16ms refresh. Multi-bit test mode capability. Proven stacked capacitor technology. A variety of packaging options. And both custom IC and board-level solutions for unique high-density design requirements.

Call Oki today and let us take you to the 4front, speeding your product to market with our high-performance 4-Meg technology.



**So. Calif.**  
(Irvine)  
714/752-1843  
(Sherman Oaks)  
818/990-3394  
**No. Calif.**  
(San Jose)  
408/244-9666

**Boca Raton, FL**  
407/394-6099  
**Atlanta, GA**  
(Norcross)  
404/448-7111  
**Chicago, IL**  
(Rolling Meadows)  
312/870-1400

**Boston, MA**  
(Stoneham)  
617/279-0293  
**Detroit, MI**  
(Livonia)  
313/464-7200  
**New York, NY**  
(Poughkeepsie)  
914/473-8044

**Philadelphia, PA**  
(Horsham)  
215/674-9511  
**Dallas, TX**  
(Richardson)  
214/690-6868




# Meg Technology




CIRCLE NO. 13




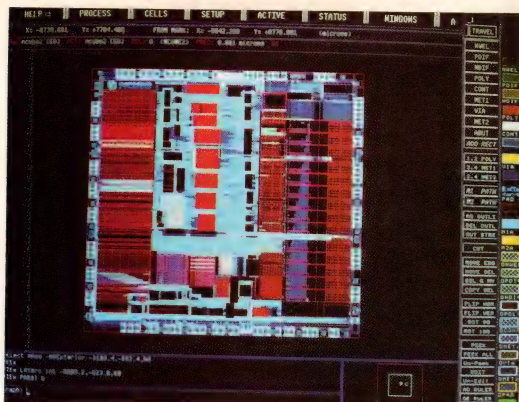

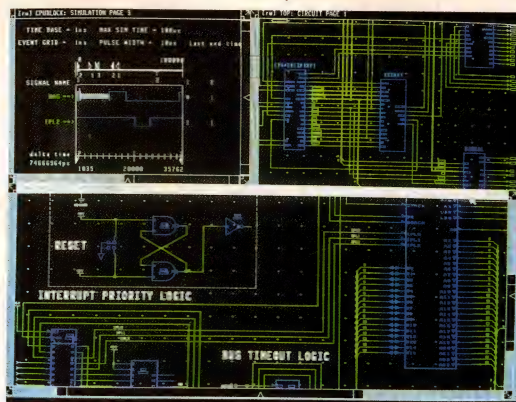
*Mentor Graphics delivers a broad line of integrated EDA software, including advanced custom and semicustom IC tools.*



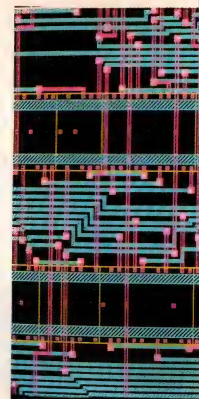*HP DesignCenter provides integrated tools for digital, analog, and microwave circuits, as well as ME CAD and CASE.*




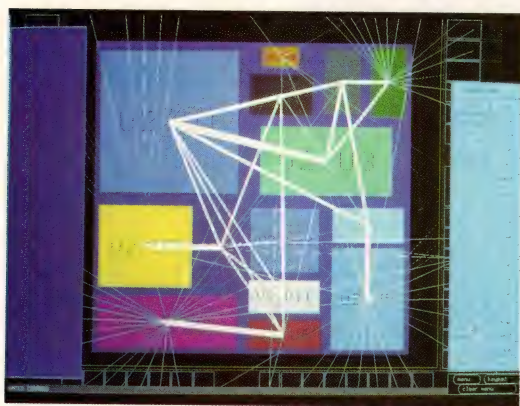*Cadence Design high-performance integrated design*




*LSI Logic's FloorPlanner™ tool is used for designing a broad range of complex ASICs.*


# Come to us We've tried

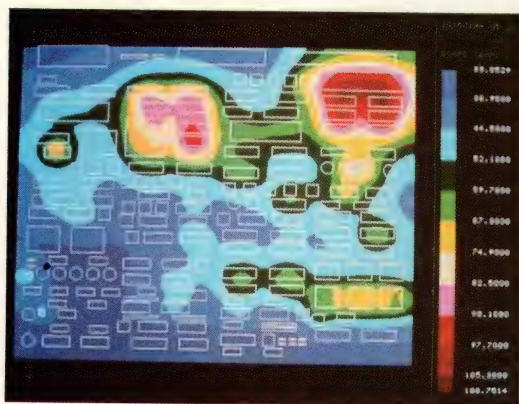

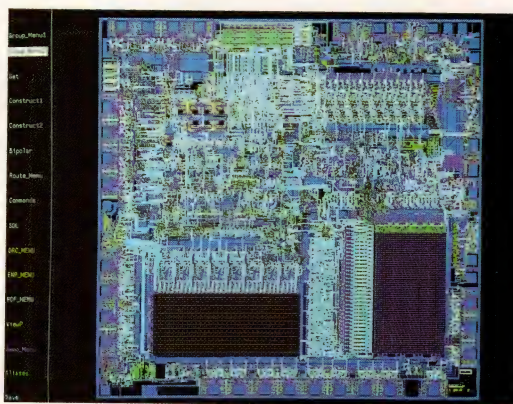*Pacific Numerix concurrent engineering solutions simulate the performance and manufacturability of PCB designs.*




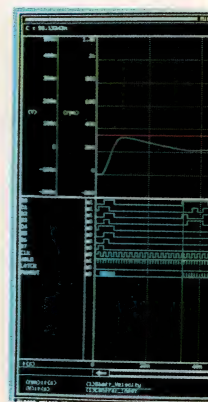*Silicon Compiler Systems' ASIC and IC design tools support all phases of design in an open framework.*



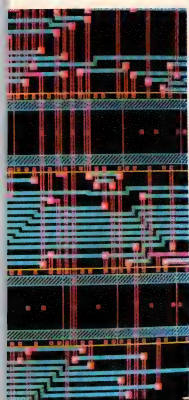*Analogy's® Saber™ both analog and as well as non-*





systems provides  
design tools in an  
environment.



Valid's Analog Workbench™ features  
an integrated environment for the design and  
simulation of analog circuits.




Racal-Redac's Visula™ EDA system provides  
tools for quality design through manufacturing.

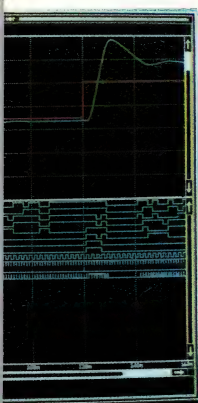
# for advice. everything.




Synopsys Design Compiler™ extracts  
state tables from netlists and optimizes state  
assignments to reduce gate count.



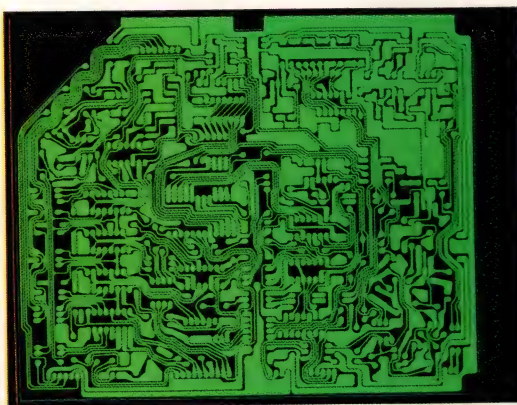simulator handles  
digital circuits,  
electrical devices.



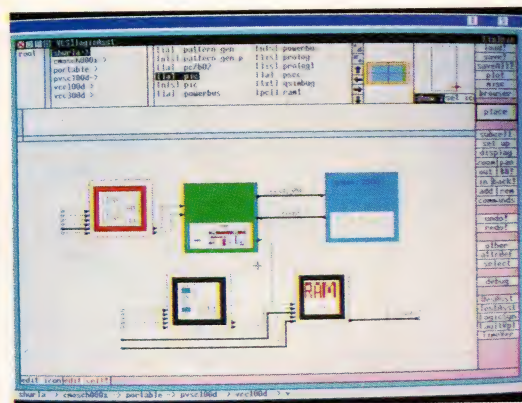Zuken America's CR-3000 system  
for analog PCBs offers true curves and arcs on  
the screen and in the database.



VLSI Technology's V8 ASIC Design  
Platform™ significantly speeds time-to-market  
and optimizes device performance.

At Hewlett-Packard, we've been  
automating our electronic design  
process for years. And we've  
faced the same problems you've  
faced. Time to market. Productivity.  
Profitability. All of them.

That's why we now have a  
better way.

Together with our software suppliers,  
we offer the broadest EE application  
selection in the industry.

try. And the strongest commitment  
to helping your team find,  
evaluate, and implement the right  
EDA tools for the task at hand.

Our goal is to give you solutions  
that support your entire product  
development cycle. Solutions  
that get your products to market  
faster and lead to increased  
profitability.

To arrive at the right solutions

for your next design project,  
start with the workstation  
vendor that has them and knows  
how to use them. Call HP today  
at 1-800-752-0900, Ext. 219W


**There is a better way.**



**HEWLETT  
PACKARD**



THE FINE ART OF DISC DRIVES

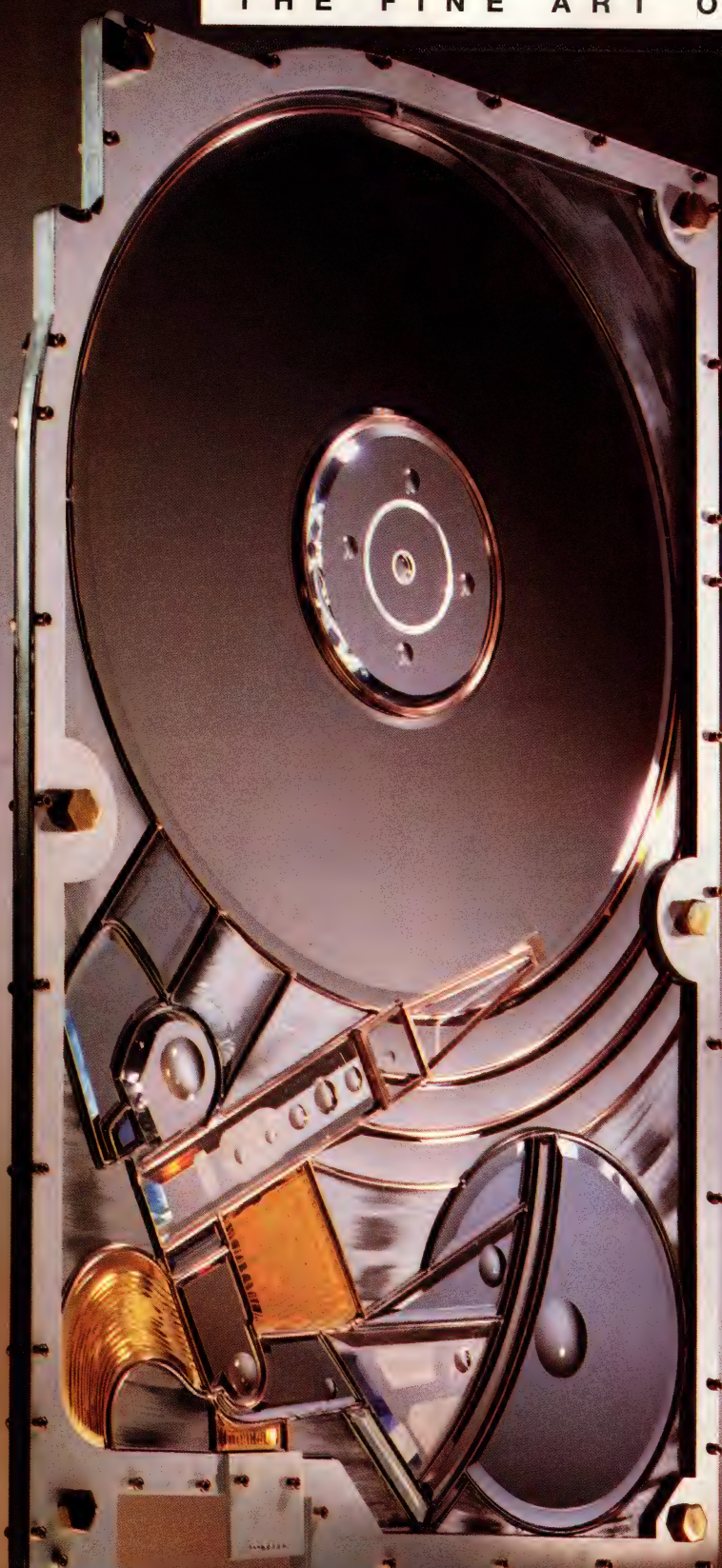


*Beveled Glass Window by  
Thomas Tisch & Andreas Lehmann  
Oakland, California*

Even to the experienced observer, a disc drive is a technological marvel. With discs spinning at 60 revolutions per second, the mechanics involved are astounding. It takes a company with a unique level of skill and experience to produce drives in volume that perform reliably year after year. A company like Seagate.

Our 3.5" ST1096 family is a great example of Seagate craftsmanship. Featuring a choice of 42, 60 or 83 formatted megabytes, these high performance (24 msec average access time) drives are ready for demanding PC and Apple® applications. The family offers ST412/MFM and SCSI interfaces for application flexibility. And they all feature a 50,000 hour mean-time-between-failure rate.

Like the artist who spends years perfecting his craft, Seagate has spent the past decade mastering the fine art of disc drives. For more information on our multi-faceted product line, contact your authorized Seagate distributor, or call Seagate directly at 800-468-DISC, or 408-438-6550.

 **Seagate**

Apple is a registered trademark of Apple Computer, Inc.  
Seagate and the Seagate logo are registered trademarks of Seagate Technology, Inc.  
© 1989 Seagate Technology, Inc.



# EDITORIAL

## Get ready for a FAX test



Although FAX machines have been available for years, only during the last year have they become widespread in business and industry. Many mail-order firms now let you place orders by FAX, and you can send binding signed documents by FAX. The popularity of FAX communications is apparent in advertisements and product announcements, too. A year ago, few advertisers put FAX numbers in their ads. Today, there are few ads that don't furnish a FAX number. FAX numbers also show up in new-product announcements, on business cards, and on letterhead.

FAX transmissions are changing the way engineers communicate, too. We can transmit schematics, sketches of prototypes, and product information by FAX. Also, several companies already offer a fast-inquiry service that transmits product literature to you via FAX. And, several magazines offer reader-service cards that you can return via FAX. However, those services don't fulfill the promise of a FAX unit. You should be able to get information quickly on many products from a single data service.

In our next issue, you'll find a special reader-service card that you can return by FAX. That card does more than bypass the postal service's link between us. When you return the "card" by FAX, our computer scans it, selects stored FAX images of the literature you need, and returns it to your FAX within a minute or two. Thus, if you need information about an advertised computer board and a switching power supply, you can get both—from different suppliers—within minutes. Keep in mind that this is a test, so we've limited the first FAX-inquiry card to a handful of advertisers. If you like and use the service, we'll expand the system.

Obviously our FAX system isn't going to dump a complete 300-pg CMOS databook to your machine. But you will get four to five pages of pertinent information about advertisers' products. I remember waiting six to seven weeks to get information via a reader-service postcard. Even when I called a sales office it could take weeks to get spec sheets. Using a central FAX service puts you in immediate contact with companies and their products.

As part of the FAX test, I want to know more about your access to and use of FAX machines. Please read the statements below and circle the corresponding numbers on one of our reader-service cards. Sorry, no FAX responses; instead, I'll let our card-processing people tabulate the results.

I have no access to a FAX machine.

Circle No. 688

We'll have a FAX machine within six months.

Circle No. 689

My group/department has a FAX machine.

Circle No. 690

I have direct access to a FAX machine.

Circle No. 691

A secretary or clerk controls our FAX machine.

Circle No. 692

FAX machine is within a 1-minute walk of my office.

Circle No. 693

I send/receive information via FAX.

Circle No. 694

Thanks for your help.



Jesse H Neal  
Editorial Achievement Awards  
1987, 1981 (2), 1978 (2),  
1977, 1976, 1975  
American Society of  
Business Press Editors Award  
1988, 1983, 1981

A stylized, handwritten signature in black ink.

Jon Titus  
Editor




# A Set Is A Set



Western Digital is a registered trademark of Western Digital Corporation. All other marks mentioned herein belong to other companies.



# Right?

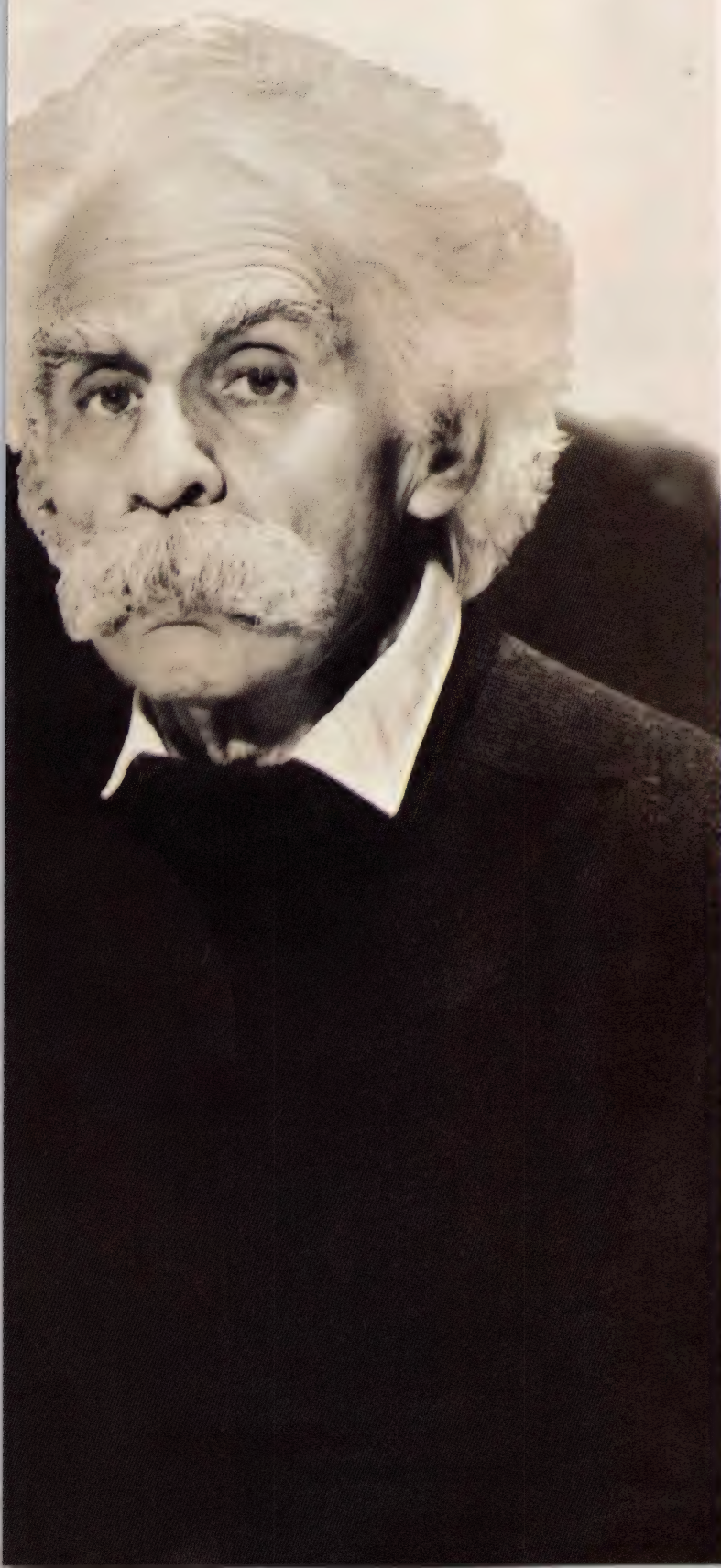

*It doesn't take a poke in the eye to figure out that great components don't necessarily lead to a great set.*

*What does, is what separates Western Digital XT, AT and Micro Channel-compatible chipsets from the rest. And what gives us the performance, compatibility and value we're more or less legendary for.*

*Consider, if you have a spare moment or two, these facts:*

*We design our chips with all the right hooks, so you get the kind of design flexibility you've always dreamed of.*

*We spent years developing our sets and software drivers, so you don't have to spend time doing it yourself.*

*We give you the ability to buy virtually all your chips from one vendor, so you eliminate incompatibility between chips. Not to mention incompatibility between chip vendors.*

*We offer unmatched EMI system expertise, so your designs can be close to noise-free. And so can your quality control people.*

*We manufacture chips by the millions and sell them to just about every big name PC manufacturer in the world, so compatibility is one less thing you have to worry about.*

*The point is, what you need is what we have. Storage, Imaging, Communications, and Core logic.*

*Systems expertise, high volume/cost-effective LSI production, turnkey manufacturing packages, and design support.*

*It's all designed to work together. It's all from one source. From the IC company that understands systems.*

*That's right, Einstein. From Western Digital.*

*For more information or a free poster version of this ad, call 1-800-847-6181. In Canada, call 1-800-448-8470.*

**Matched sets to match your needs.**

**WESTERN DIGITAL**  
Semiconductors-Storage-Imaging-Communications

CIRCLE NO. 26



# Solving the Puzzle

## IDT's Cache Memory Subsystems



SEND IN THIS AD AND  
GET A FREE PUZZLE!

### The First High-Performance Cache Solution

The technology of the future is RISC—and RISC microprocessors need cache memory for maximum performance. IDT now offers the first family of cache memory modules, part of IDT's "Building Blocks for the '90s", to optimize RISC performance.

### Cache-ing In On Technology

We offer an entire family of cache modules, like the IDT7MB6049, to suit a variety of cost/performance needs. The IDT7MB6049 is a dual 16Kx60 multiprocessor cache module which operates as a complete instruction and data cache solution for the R3000. It also features on-board address latches to reduce capacitive loading and instruction address invalidation to support multiprocessor systems. The 120-pin QIP (quad in-line) package provides a space savings of 60% over conventional DIP solutions by using surface mounted components on both sides of the circuit board.

### We'll Help You Solve the Puzzle

All of our Building Blocks for the '90s offer solutions unavailable using conventional design technology—solutions that maximize performance and minimize board space. And if our standard family of subsystems don't address your specific problem, we will design custom modules for your application. We design, manufacture, test, and burn-in all our modules before they go out the door for guaranteed reliability—all you have to do is plug them in! Standard modules are available immediately, and custom modules can be plugged in as fast as 6 weeks after your order is placed.

### You Can Count On Us

Call our Marketing Hotline at **(408) 492-8551, Dept. CM90** today for technical information. Or call (408) 492-8225 for a copy of our Subsystems Short-Form Catalog, Custom Modules Information Packet, and 1989 Data Book Supplement with details about our RISC modules and subsystems.

IDT, Corporate Marketing,  
2975 Stender Way, Santa Clara, CA  
95052-8015, FAX 408-492-8674.

*When cost-effective performance counts*



**Integrated  
Device Technology**



# TECHNOLOGY UPDATE

## SWITCH-MODE POWER-SUPPLY ICs

# Smart parts let nearly any EE design switchers



Though you can design switchers yourself, you'll probably want to call on experts for cost-effective, reliable supplies that emit low EMI and meet international safety standards.

**Dan Strassberg,**  
Associate Editor


**D**esigning switch-mode power supplies isn't what it used to be. Once the private preserve of only a few thousand specialists throughout the world, it has turned into an arena in which any number can play. Thanks to the increasingly intelligent ICs and a torrent of applications literature spewing forth from a score of vendors, nearly any electronic engineer with hardware-design experience can create an ac-line-to-dc switcher or a dc-dc converter that works. But, except for the lowest performance applications, making a supply that not only works, but also is cost-effective and reliable, reproducible in volume, and meets worldwide EMI and safety standards usually still requires specialized expertise.

Furthermore, if, for example, your job is designing  $\mu$ P-based systems, your

employer has every right to ask whether power-supply design represents an appropriate use of your time. What's more, building power supplies isn't necessarily an effective use of your company's manufacturing resources; purchasing the supplies you put in your products might make a lot more sense. (A possible exception—a type of supply you should consider designing and building—is a nonisolated, low-power, dc-dc converter mounted on a primarily digital pc board to power functions that require supply voltages different from those available in your system.)

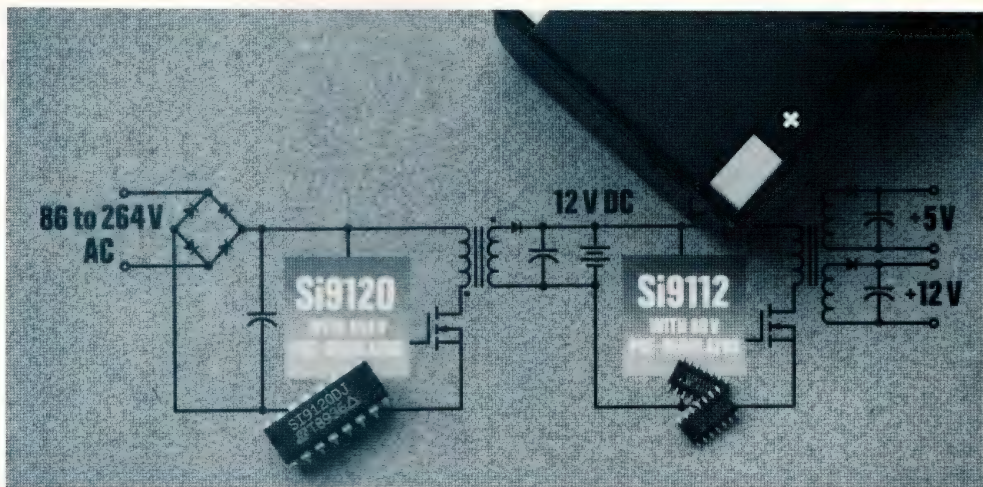
### Learn, don't burn

Even if you decide to relegate most or all of your power-supply design activities to "government jobs," learning more about modern power-supply architecture can be worth your effort: when



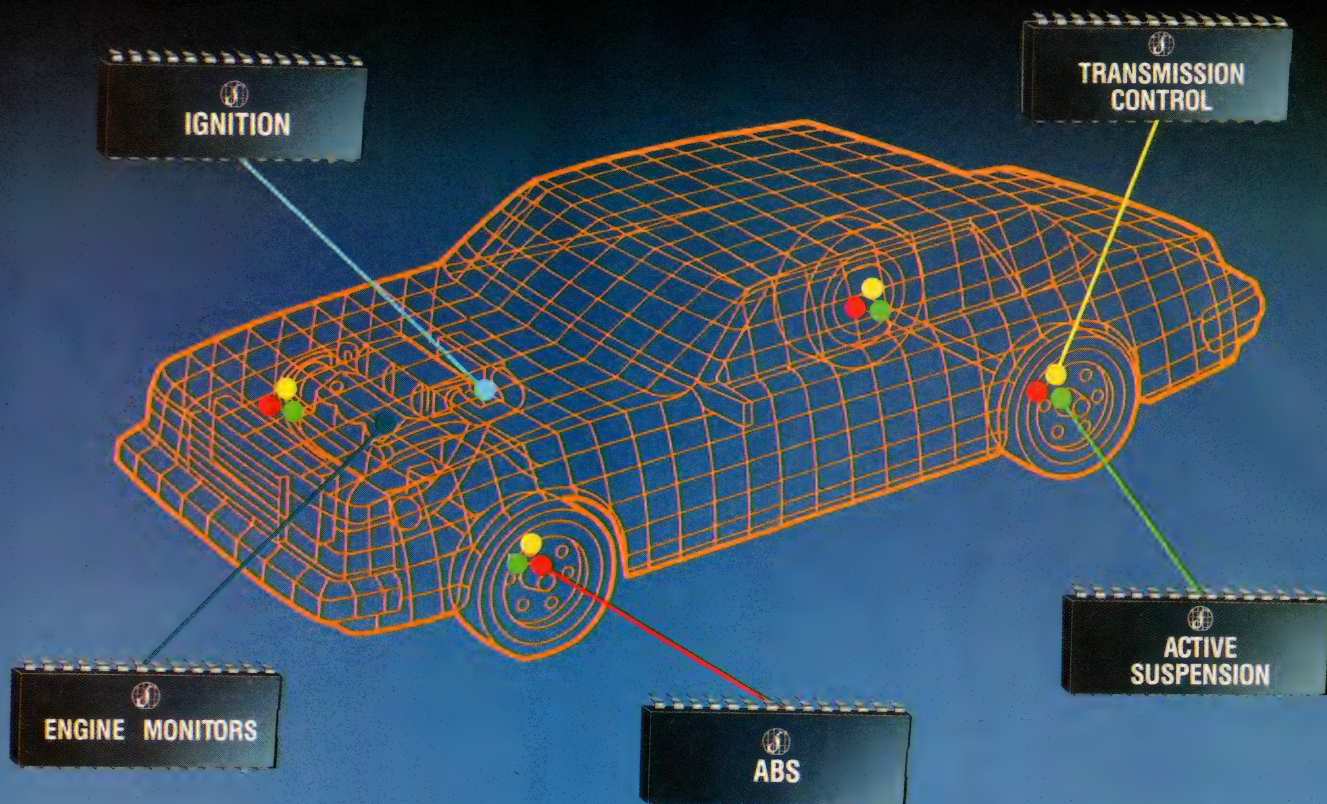A 450V preregulator in Siliconix's Si9120 allows you to create "universal-input" switch-mode supplies that operate from 50-to-450V rectified ac lines without having to reconnect the rectifiers. With an 80V preregulator, the Si9112 is for battery-powered equipment that operates from 9 to 80V dc.





# Send us your mixed signals...we'll give you straight answers.

## Automotive Mixed-Signal ICs From the "MSICs"™ Company

As the industry's most accomplished and innovative mixed-signal integrated circuits (MSICs) company, we can put our expertise in the design and production of complex analog/digital "MSICs" to work for you. We will assign a dedicated team of MSICs engineers to collaborate with you on your automotive electronic control design needs for emission control, ignition, transmission control, active suspension, and anti-lock braking.

Typically, these control systems require the use of complex mixed-signal integrated circuits capable of handling both analog and digital functions. We are your most qualified mixed-signal IC resource for attacking those sensor-to-

MPU or MPU-to-actuator mixed-signal interface problems. Together we can generate MSIC solutions that are both innovative and practical.

Let Silicon Systems place its multifaceted capability in design, process technology, and packaging at your finger tips. We offer both bipolar and CMOS design and manufacturing capability, so we don't need to compromise on system performance. Based on your application, we can meet your needs with our Mixed Signal Arrays, Cell-based Custom, or Full Custom

development capabilities. From design through production, Silicon Systems has the "MSICs Team" to help you solve your problems.

### CALL NOW!

(714) 731-7110, Ext. 3575

For some straight answers on mixed-signals for automotive applications, contact:

#### Silicon Systems, Inc.

14351 Myford Road, Tustin, CA 92680  
Ph: (714) 731-7110, FAX: (714) 669-8814  
European Hdq. U.K. Ph: (44) 7983-2331  
European Hdq. U.K. FAX: (44) 7983-2117

Circle No. 118 for Product Info

*silicon systems®*



# TECHNOLOGY UPDATE

## Switch-mode power-supply ICs


systems misbehave, understanding how a power supply might lie at the root of the problem can save precious troubleshooting time. (For example, a switcher can inject ripple current into the ground reference of a noise-sensitive circuit.) Moreover, in this era of digital techniques, many EEs tend to ignore the physics of the circuits they work on, and few areas of electronics bring home the importance of the physical limitations of circuit layouts and devices as clearly as does switching power-supply design.

If you set out to become a self-taught switching-power-supply expert, you will quickly realize that you've tackled a problem of continuing self education. In switching power supplies, as in most areas of electronics, the only constant is change. Techniques that were mainstays just three years ago appear much less often in today's designs.
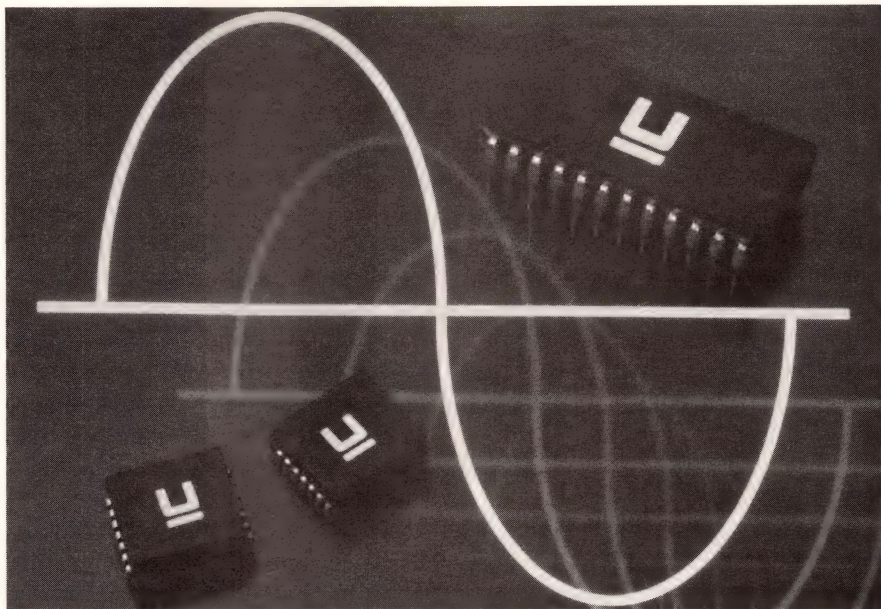
### Switch to the fast track

When most supplies used linear technology, the power-supply field was slow to change. Today, the pace of change is rapid—perhaps too rapid. New design approaches sometimes exhibit new failure modes; the industry can take several years to recognize and correct those modes. Such a situation occurred a decade ago when the first power MOS switches appeared. Unless your requirements are very unusual, because reliability is so important in power supplies, you can frequently justify a wait-and-see attitude toward adopting new approaches.

An area where many observers feel that a go-slow posture will prevail is acceptance of resonant-mode conversion. In supplies that use most of the older pulse-width-modulated (PWM) architectures, the switching frequency remains relatively constant; the percentage




*Surface-mount technology is appearing in more and more switch-mode supplies. Unitrode's UC3860 resonant-mode control chip answers supply designers' demands for packaging flexibility. The vendor provides it in a 28-pin PLCC and a 24-pin DIP.*

of time that the switching elements conduct varies in response to changes in the input voltage and the load current. In resonant supplies, the switches conduct for a constant period of time—determined by the half period of a tank circuit's resonant frequency. These supplies achieve regulation by varying the frequency at which the switches operate (Refs 1 and 2).

If a power-supply design's success depended only on semiconductors, designers would be quicker to

adopt the resonant-mode conversion ICs that have reached the market within the past few years. But there are many elements besides semiconductors in most successful power-supply designs: Magnetic components must have the necessary inductance and distributed capacitance under all operating conditions. Capacitors must be correctly applied (for example, to prevent ripple current from causing them to overheat). Temperature rises must be properly managed and conducted. Radiated interference must be adequately limited. Printed circuits must be laid out and magnetic components must be designed to meet spacing requirements imposed by the agencies that set safety standards.

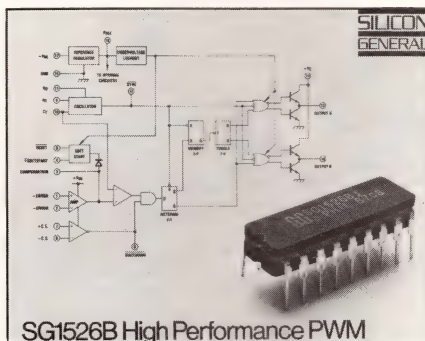Over the years that PWM has dominated the switching-power-supply field, despite the relentless upward trend in switching frequencies, EEs throughout the industry have become familiar with how to select a supply's entire component complement. In resonant supplies, the role of many of the components,



*With a complementary output, soft-start and undervoltage-lockout circuits, a sync pin, and an internal reference, Silicon General's SG1526B incorporates most of a PWM supply's functional blocks.*



# TECHNOLOGY UPDATE

## Switch-mode power-supply ICs

particularly inductors and capacitors, is especially critical. Notwithstanding a growing body of applications literature, designers and component vendors need time to become as familiar with resonant-supply components as they are with PWM-supply components. Therefore, if you're designing your first switch-mode power supply, bear in mind that you stand a better chance of getting the information you need to develop a reliable supply if you choose PWM conversion.

### Know-how yields reliability

If, however, you're convinced that your system should use a resonant-mode power supply (for example, to obtain a power density greater than 20W/in.<sup>3</sup> from a single supply that produces an output below ~200W), you can obtain a supply with the requisite reliability by purchasing it from a vendor with several years' experience building such units. A few power-supply vendors already know a great deal about how to design reliable resonant-mode supplies.

Although its technology is a revolutionary departure from traditional design approaches, in several respects resonant-mode conversion represents a continuation of trends that have dominated the switching-power-supply field since its inception. These trends, toward increased power density and increased switching frequency, affect PWM as well as resonant-mode supplies. Lately, in addition, the power-supply industry has had to meet user demands for greatly improved reliability.

By permitting size reductions in magnetic components and capacitors, increased switching frequency has made possible increased power density. However, if you hold a supply's output and efficiency constant while reducing its size, the operating temperature of the components

will increase and the supply's reliability will decrease—unless you can devise new techniques for thermal management.

Opinions vary on whether further increases in the switching-frequency capabilities of PWM-supply ICs really will make possible additional meaningful reductions in the size of magnetic components and of the supplies themselves. At least in the short run, several factors militate against actually operating supplies at higher frequencies and thus, against realizing the ICs' promise of reductions in supply size:

- Keeping magnetic-core losses low with faster switching requires improved magnetic ma-

terials optimized for higher frequency operation.

- In line-operated supplies, the rules of regulatory agencies, such as Underwriters' Laboratories, govern the spacing between the primary and secondary windings of transformers that provide isolation.
- Simultaneously achieving higher speed and lower on-resistance in power MOSFET switches requires improvements in semiconductor processing technology.

Furthermore, removing heat from high-power-density supplies requires innovative thermal design. In designs that rely on natural con-

**Table 1—Partial list of switch-mode power-supply IC vendors<sup>1</sup>**

Vendor	Voltage mode	Current mode	Circuit types		Power-factor correction	Notes
			Resonant mode	Low standby power		
Cherry	•	•	•			
Gennum		•	•			
Harris	•					2
Hitachi America	•	•				3
Lambda	•					4
Linear Technology	•					
Maxim				•		
Micro Linear	•	•			•	5
Motorola	•	•	•			3
National	•					3, 4
Raytheon				•		
SGS-Thomson	•	•				3
Siemens				•		
Silicon General	•	•				3, 6
Siliconix	•			•		7
Teledyne		•		•		
Unitrode	•	•	•		•	3

#### Notes:

1. This table lists only those circuit types that vendors initially introduced after EDN last surveyed the entire switch-mode IC field in July 1987. Consult vendors for circuit types introduced earlier.
2. Harris supplies a 2-chip set for isolated ac-to-dc supplies and a 1-chip device for building a complete nonisolated ac-line-operated dc supply.
3. This vendor also supplies high-frequency PWM controllers that operate at or above 200 kHz.
4. In addition to monolithic parts, vendor supplies hybrid devices that include both PWM control and medium power switches.
5. Micro Linear's PWM controllers are high-speed devices. The firm also supplies a configurable power-controller array.
6. Silicon General also supplies low-voltage supervisory circuits and switching-regulator power-output stages.
7. Siliconix supplies devices that operate without step-down transformers from rectified ac lines with dc values as high as 450V.



# Experience makes the difference



## Raytheon's experience gives you the winning ECL combination

**Raytheon's ECL array family performs at a fraction of the power of competing ECL technologies. Proven ECL logic arrays are denser than 1.5 micron CMOS arrays.**

☐ **Here now:** ECL arrays with a proven track record. Raytheon's extensive experience in design, prototype and production devices gives you the highest level of confidence.

☐ **Highest density:** CGA 70E18: 12,800 equivalent gates  
CGA 40E12: 7,752 equivalent gates

CGA 1ME12: 4,584 equivalent gates and 1280 bits of RAM.

☐ **Performance:** Superior speed/power performance— $<0.1$  pJ; 300 ps delay; 300  $\mu$ W power dissipation (typical gate).

☐ **Ease of design:** Raytheon's contiguous row array topology provides a superior design approach when compared to fixed position cell-based technologies. This topology offers greater flexibility and ease in macrocell design, placement and routing.

☐ **Interface capability:** I/Os compatible with ECL (10 KH or 100 K), TTL, CMOS, ETL (mixed ECL and TTL), and ETC (mixed ECL, TTL and CMOS).

The extensive experience and support provided by Raytheon mean easy, error-free, and cost-effective ECL design for you.

Raytheon Company  
Semiconductor Division  
350 Ellis Street  
Mountain View, CA 94039-7016  
(415) 966-7611

**Raytheon**

*Where quality starts with fundamentals.*



# TECHNOLOGY UPDATE


## Switch-mode power-supply ICs

vection in air, increased power density is often merely an illusion. Supplies that quote spectacularly high power densities often do so by passing on to you the responsibility for maintaining an acceptably low case temperature. If you want to realize a significant fraction of such supplies' rated output, unless you can use an unconventional cooling technique, such as forced-air, liquid, or vapor-phase cooling, you must attach large, heavy heat sinks to the supplies. Once you have done so, the power density you achieve from the combination of heat sinks and power supplies is usually not spectacular at all.
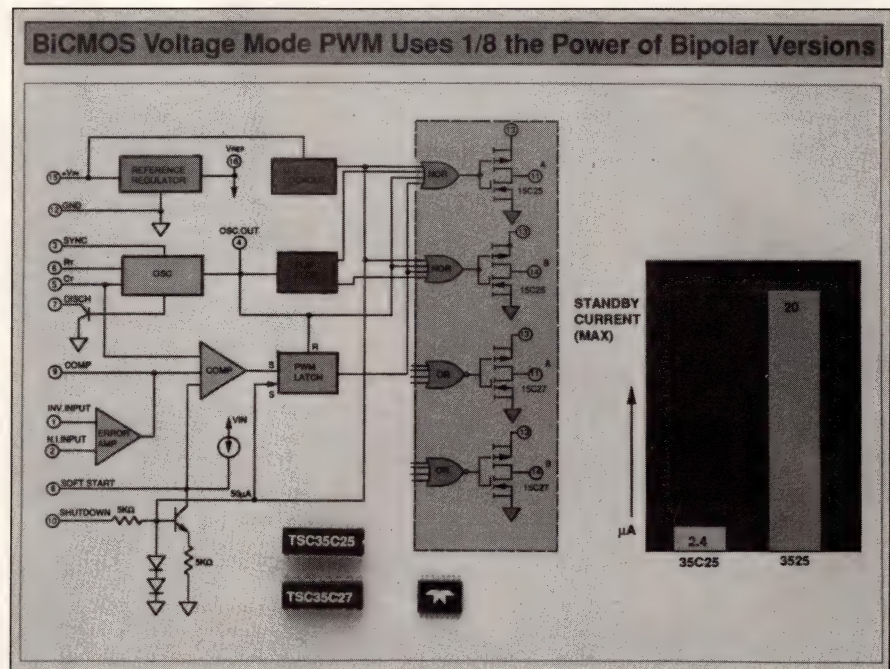
### Factor in the power factor

An area related to efficiency is power factor. A popular misconception has it that the reason most ac-line-operated switching supplies exhibit power factors much below unity is that their input current is out of phase with the line voltage. In fact, the reason is that their input current is highly nonsinusoidal. Because the supplies directly connect the rectified ac line to filter capacitors that store a great deal of energy, the rectifiers only conduct for a short interval every half cycle near the instantaneous line-voltage peak. The resulting input-current waveform is a series of pulses at twice the line frequency. The integral of the product of the instantaneous input current and voltage over one line-voltage cycle represents the energy delivered to the supply during the cycle. That value divided by the cycle's duration is the input power.

The input power is much less than the product of the rms line voltage and the rms input current. To obtain the power factor (PF), you divide the input power by the rms-line-voltage/rms-input-current product. PF values of 0.6 are not uncommon in high-power switching



*Using a BiCMOS process enables Teledyne Semiconductor to cut the standby power consumption of its TSC35C25 and TSC25C27 pulse-width modulators to 1/8 that of the bipolar versions.*

supplies. If a supply operating from an ac line whose nominal rms value is 115V and whose minimum value is 100V produces a dc output of 1000W with an efficiency of 80% and a power factor of 0.6, the supply will draw 20A at low line voltage under a full load. A similar supply with PF of 1 draws only 12A under the same conditions. The standard 3-wire, grounded ac receptacles used in the US are rated for only 15A. Thus, a piece of equipment using the unity PF supply can operate from a building's existing wiring. With the 0.6 PF supply, the unit requires special ac wiring.

### ICs correct power factor

It's clear that there are many instances where a supply's power factor can be important. Until recently, power-factor correction required bulky, expensive, passive components. Now, however, IC vendors have begun introducing power-factor correction ICs. The cost of these devices is justifiable


in many more situations than is the cost of passive power-factor correction networks. The ICs exact a minimal penalty on efficiency and they're much smaller than the passive components you'd have to use to do the same job.

In addition to the trends already discussed, the switch-mode power-supply IC market is seeing trends toward more complete integration of supply functions onto single chips and toward control chips that consume less power. The **box**, "For more information . . .," lists many of the vendors of switch-mode power supply ICs; **Table 1** indicates types of ICs these vendors have introduced since EDN last surveyed the field—July of 1987. The **table** provides an indication of where vendors have placed their power-supply IC development effort for the past 2½ years. The trends toward more complete integration and lower-power control chips reflect a quest for improved reliability.

Supposedly objective data indi-


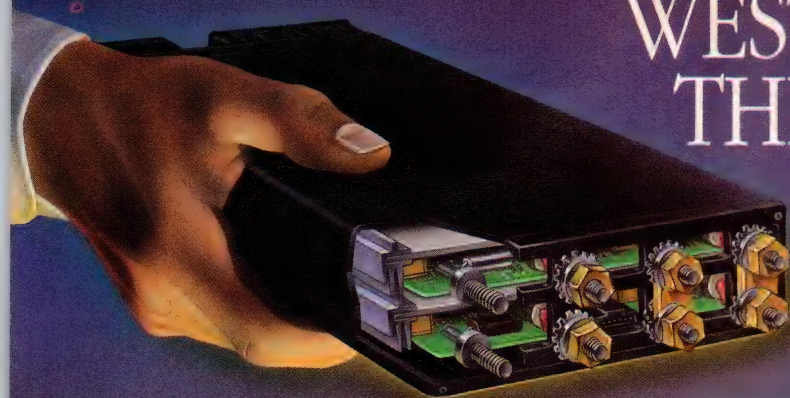
# WESTCOR REDEFINES THE POWER SUPPLY ...AGAIN



**WESTCOR STAKPAKS™. WORLD'S  
SMALLEST SINGLE OR MULTIPLE  
OUTPUT, FAN-COOLED SWITCHERS.  
THE STAKPAK: 1200 WATTS—  
3.2" x 5.5" x 11.5" CASE.  
STAKPAK II: 600 WATTS—  
1.9" x 5.5" x 12" CASE.**

Westcor's compact and low profile StakPaks redefine power packaging with unprecedented power density and output flexibility. Patented megahertz module technology provides up to 6 watts/cubic inch and up to 8 isolated and fully regulated outputs (5 outputs for StakPak II) while at the same time guaranteeing high reliability and reduced time to market.

Consider these standard features:

- Standard or custom outputs (2-95 VDC)
- UL, CSA, VDE (TUV) Safety Agency Approved (StakPak II in process)
- 80% Efficient, typical
- 110/220 VAC, fool-proof strapping
- Full power @ 40°C


Please contact Westcor for datasheets, pricing and additional information.



**WESTCOR CORPORATION**

485-100 Alberto Way  
Los Gatos, CA 95032

(408) 395-7050 • FAX (408) 395-1518

Westcor is a subsidiary of  **VICOR CORPORATION**

## STAKPAK II STANDARD 600 WATT MODELS



**Model Output Voltage (VDC) and Maximum Current (amperes) per Channel**

	#1	#2	#3	#4	#5
Single Output					
ST1-1401	2 @ 120	Total output power may not exceed 600 watts for any model, single or multiple output. Lower power StakPak II models and many other configurations are available. Please contact the factory.			
ST1-1402	5 @ 120				
ST1-1301	12 @ 50				
ST1-1302	15 @ 40				
ST1-1303	24 @ 25				
ST1-1304	28 @ 21				
ST1-1305	48 @ 13				
Dual Output					
ST2-1401	2 @ 60	5 @ 60			
ST2-1402	5 @ 60	5 @ 60			
ST2-1403	5 @ 60	12 @ 33			
ST2-1404	12 @ 33	12 @ 33			
ST2-1405	15 @ 26	15 @ 26			
Triple Output					
ST3-1401	5 @ 60	12 @ 16	12 @ 16		
ST3-1402	5 @ 60	15 @ 13	15 @ 13		
ST3-1501	5 @ 90	12 @ 8	12 @ 8		
Quad Output					
ST4-1401	5 @ 30	12 @ 16	12 @ 16	5 @ 30	
ST4-1402	5 @ 30	15 @ 13	15 @ 13	5 @ 30	
ST4-1403	5 @ 30	12 @ 16	12 @ 16	24 @ 8	
ST4-1501	5 @ 30	15 @ 13	15 @ 13	24 @ 8	
ST4-1502	5 @ 60	12 @ 16	12 @ 8	5 @ 15	
ST4-1503	5 @ 60	15 @ 13	15 @ 7	5 @ 15	
ST4-1504	5 @ 60	12 @ 16	12 @ 8	24 @ 4	
ST4-1505	5 @ 60	15 @ 13	15 @ 7	24 @ 4	
Five Output					
ST5-1501	5 @ 30	12 @ 16	12 @ 16	5 @ 15	24 @ 4
ST5-1502	5 @ 30	15 @ 13	15 @ 13	5 @ 15	24 @ 4

CIRCLE NO. 28

## STAKPAK STANDARD 1200 WATT MODELS



**Model Output Voltage (VDC) and Maximum Current (amperes) per Channel**

	#1	#2	#3	#4	#5
Single Output					
SP1-1801	2 @ 240	Total output power may not exceed 1200 watts for any model, single or multiple output. Lower power StakPak models and many other configurations are available. Please contact the factory.			
SP1-1802	5 @ 240				
SP1-1803	12 @ 100				
SP1-1604	15 @ 80				
SP1-1605	24 @ 50				
SP1-1606	28 @ 42				
SP1-1607	48 @ 25				
Dual Output					
SP2-1801	2 @ 120	5 @ 120			
SP2-1802	5 @ 120	5 @ 120			
SP2-1803	5 @ 120	12 @ 66			
SP2-1804	12 @ 66	12 @ 66			
SP2-1805	15 @ 53	15 @ 53			
Triple Output					
SP3-1801	5 @ 180	12 @ 16	12 @ 16		
SP3-1802	5 @ 150	12 @ 33	12 @ 16		
SP3-1803	5 @ 180	15 @ 13	15 @ 13		
SP3-1804	5 @ 150	15 @ 26	15 @ 13		
Quad Output					
SP4-1801	5 @ 150	12 @ 16	12 @ 16	5 @ 30	
SP4-1802	5 @ 150	15 @ 13	15 @ 13	5 @ 30	
SP4-1803	5 @ 150	12 @ 16	12 @ 16	24 @ 8	
SP4-1804	5 @ 150	15 @ 13	15 @ 13	24 @ 8	
Five Output					
SP5-1801	5 @ 120	12 @ 16	12 @ 16	5 @ 30	24 @ 8
SP5-1802	5 @ 120	15 @ 13	15 @ 13	5 @ 30	24 @ 8
Seven Output					
SP7-1801	5 @ 60	12 @ 16	12 @ 16	24 @ 8	24 @ 8
	#6	#7			
	5.2 @ 28	2 @ 30			



# TECHNOLOGY UPDATE

## Switch-mode power-supply ICs

cates that in real applications, switch-mode power supplies are less reliable than linear supplies. Much of the data has problems, though. Few of the comparisons relate the MTBF of units providing equal outputs under equivalent conditions. Linear-supply efficiency averages around 45%; for switchers, efficiency usually exceeds 70%. So, if you have a linear supply and a switcher each producing a 100W output, the linear supply will dissipate 120W. The switcher will dissipate only about 40W and will therefore exhibit a lower temperature

rise. The switcher's cooler operation will tend to improve its reliability. And, though not related to reliability, the switcher's size and weight will be much lower than those of the linear supply.

Nevertheless, a unit's failure rate does correlate with the number of components it uses, and most switching supplies use many more components than do linear supplies that produce equivalent output power. Placing more of the supply circuits on a single IC chip ought to improve reliability.

Reducing the power dissipated in

a switch-mode power-supply control chip will also improve a supply's reliability, although usually not dramatically. In most supplies, the control chip and the voltage-dropping resistors in series with the chip's power-input pin do not dissipate a significant part of the power the supply consumes. In regulators for battery-powered equipment, though, the situation can be quite different. Moreover, although reliability is often a paramount consideration in such equipment, extending battery life is usually even more important. New control ICs, includ-

## For more information . . .

For more information on the switching-regulator ICs discussed in this article, contact the following manufacturers directly, circle the appropriate numbers on the Information Retrieval Service card, or use EDN's Express Request service. When you contact any of the following vendors directly, please let them know that you read about their products in EDN.

**Cherry Semiconductor**  
2000 South County Trail  
East Greenwich, RI 02818  
(401) 885-3600  
FAX 401-885-5786  
Circle No. 715

**Linear Technology Corp**  
1630 McCarthy Blvd  
Milpitas, CA 95035  
(408) 432-1900  
FAX 408-434-0507  
Circle No. 720

**Raytheon Semiconductor**  
350 Ellis St  
Mountain View, CA 94039  
(415) 968-9211  
FAX 415-966-7620  
Circle No. 725

**Silicon General**  
11861 Western Ave  
Garden Grove, CA 92461  
(714) 898-8121  
FAX 714-893-2570  
Circle No. 729

**Gennum Corp**  
Box 489, Station A  
Burlington, Ontario, Canada L7R 3Y3  
(416) 632-2996  
FAX 416-632-2055  
Circle No. 716

**Maxim Integrated Products**  
120 San Gabriel Dr  
Sunnyvale, CA 94086  
(408) 737-7600  
FAX 408-737-7194  
Circle No. 721

**SGS-Thomson Microelectronics**  
1000 E Bell Rd  
Phoenix, AZ 85022  
(602) 867-6241  
FAX 602-867-6290  
Circle No. 726

**Siliconix Inc**  
2201 Laurelwood Rd  
Santa Clara, CA 95054  
(408) 970-5202  
TWX 910-338-0227  
Circle No. 730

**Harris Semiconductor**  
Box 883  
Melbourne, FL 32901  
(407) 724-3800  
FAX 407-729-5691  
Circle No. 717

**Micro Linear**  
2092 Concourse Dr  
San Jose, CA 95131  
(408) 433-5200  
TLX 275906  
Circle No. 722

**Siemens AG**  
Wittelsbacherplatz 2, D-8000  
Munchen 2, W Germany  
(089) 234-3085  
FAX 089-234-2824  
Circle No. 727

**Teledyne Semiconductor**  
1300 Terra Bella Ave  
Mountain View, CA 94039  
(415) 968-9241  
FAX 415-967-1590  
Circle No. 731

**Hitachi America Ltd**  
2000 Sierra Point Pkwy  
Brisbane, CA 94005  
(415) 589-8300  
FAX 415-583-4207  
Circle No. 718

**Motorola Inc**  
7402 S Price Rd  
Tempe, AZ 85283  
(602) 897-3840  
FAX 602-897-3392  
Circle No. 723

**Siemens Components Inc**  
2191 Laurelwood Rd  
Santa Clara, CA 95064  
(408) 980-7939  
FAX 408-980-4596  
Circle No. 728

**Unitrode Integrated Circuits**  
Box 399  
Merrimack, NH 03054  
(603) 424-2410  
FAX 603-424-3460  
Circle No. 732

**Lambda Electronics**  
515 Broad Hollow Rd  
Melville, NY 11747  
(516) 694-4200  
FAX 516-293-0519  
Circle No. 719

**National Semiconductor Corp**  
2900 Semiconductor Dr  
Santa Clara, CA 95052  
(408) 721-5000  
FAX 408-245-9655  
Circle No. 724

## VOTE . . .

Please also use the Information Retrieval Service card to rate this article (circle one):

High Interest 518  
Medium Interest 519  
Low Interest 520





## SEE WHAT YOU'RE MISSING WITH INTEL'S DEVELOPMENT TOOLS.

### Choices.

All the choices that help you finish your design sooner and get to market faster. That's what Applied Microsystem's development tools give you that Intel® can't.

You can mix or match the emulation and software development tools you need to meet your design requirements—be it an 80X86, 80C18X or 80286.

Choose the debugger you need. Validate®/Soft-Scope®. Validate®/Unison®. Validate®/XEL®. XDB®. Geneprobe®. If you like to debug in C, pick your compiler. We work with them all. Even

Intel's. Or take your choice of other languages, like Ada, Pascal, FORTRAN, PL/M, Assembler or Jovial.

You can work with a PC, Sun®, Vax® or Apollo®. No matter which tools you choose, we'll make sure they all work together.

For more choices, call Applied Microsystems Corporation at 1-800-343-3659. In WA (206) 882-2000. Or write P.O. Box 97002, Redmond, WA 98073-9702 USA.

We just hope you're reading this before you buy an Intel system. And not after.



**Applied  
Microsystems  
Corporation**

\*Call for availability. © 1989 Applied Microsystems Corporation. All rights reserved. AMC 273. Other names indicated by ® are registered trademarks of their respective holders. For the name of your nearest distributor in Europe, call 44-(0)-296-625462. Europe Fax 44-296-623460. Or contact Applied Microsystems Corporation, Ltd., Chiltern Court, High Street, Wendover, Aylesbury, Bucks, HP22 6EP, United Kingdom. In Japan, call 03-493-0770. Japan Fax 03-493-7270. Or contact Applied Microsystems Japan, Ltd., Nihon Seimei, Nishi-Gotanda Building, 7-24-5 Nishi-Gotanda, Shinagawa-KU, Tokyo T141, Japan.





## "The Speech Capital of The World Dictates Lanier."

A speech can be dictated six times as fast as it can be written.

With a Lanier portable, desktop unit, or a large digital system. All Lanier products are backed by the most experienced company in the business. With over 300 offices across America to provide installation, training, and prompt service.

So no matter what city you're in, dictate Lanier. Call 1-800-241-1706.

Or send this ad and your business card for more information on: ☐ Dictation ☐ FaxWriter ☐ Telephones ☐ Copiers

**LANIER**  
VOICE PRODUCTS  
The voice of experience.

HARRIS

Mail to: Lanier, P.O. Box 3064, Cedar Rapids, Iowa 52406-9958. Call 1-800-241-1706. Fax: 404-329-8369.

CN-6

CIRCLE NO. 20

# IN THE YEAR 2000

*This Programmer will still be all you need!*

## ALLPRO™

LIMITLESS DEVICE PROGRAMMING CAPABILITY

### CALL TOLL FREE 1-800-331-7766

## LOGICAL

DEVICES, INC.

FAX (305) 974-8531  
1201 N.W. 65th Place  
Fort Lauderdale, FL 33309

CIRCLE NO. 30

## UPDATE

### Switch-mode power-supply ICs

ing CMOS devices, with low internal dissipation—some low enough to qualify as micropower devices—are tailor-made for creating regulated voltages from batteries.

### The value is outstanding

Although there are exceptions, switch-mode power-supply ICs have become commodity parts. The popular types have several sources and pricing is quite competitive, with some parts available in quantity for under \$1 and many more from \$1 to \$2.50. Though the devices aren't as sophisticated as a  $\mu$ P that contains millions of transistors, when you include the combination of analog and digital circuits and the protection features, the value is outstanding.

However, don't let the value and apparent ease of application become siren songs that entice you into attempting to save your company money by building supplies. If you and your company lack experience in designing and building power supplies, you should make any decision to build switchers—especially small quantities of switchers—very carefully.

**EDN**

### References

1. Sykes, Frederick E, "Resonant-mode design techniques improve switcher performance," *EDN*, November 9, 1989, pg 201.

2. Sykes, F E, "Resonant converters team control theory and circuit design," *EDN*, November 23, 1989, pg 207.

Article Interest Quotient  
(Circle One)


High 518 Medium 519 Low 520



Z I L O G
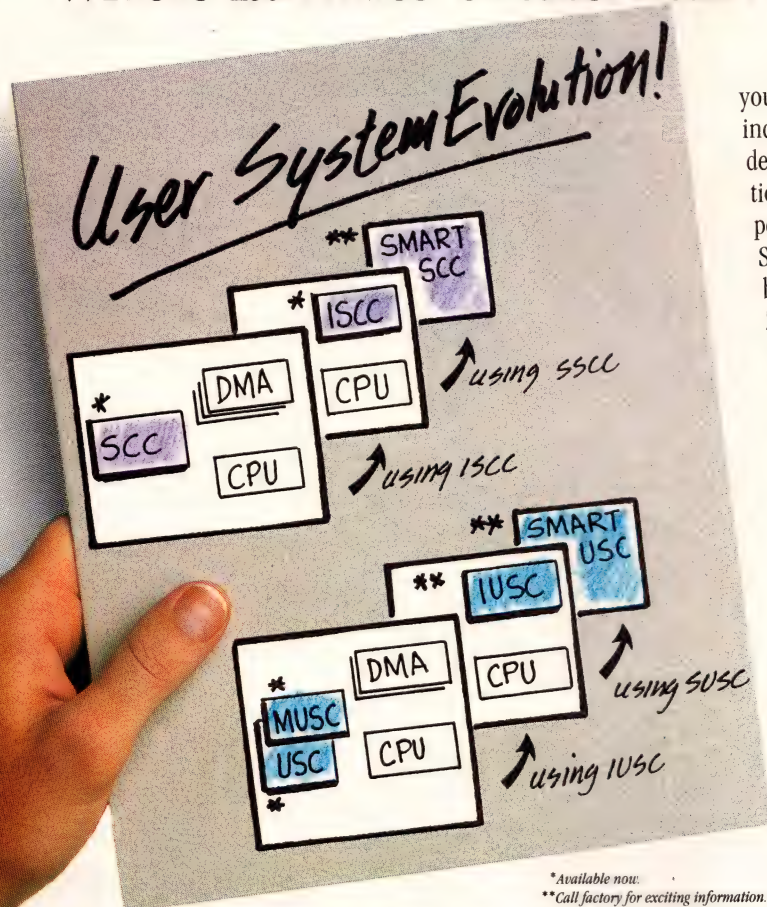
# REAL SCC CHOICES

When you need more than the basic SCC, we give you whole families of alternatives. *Done right!*



At Zilog, we develop products the way you develop systems. Starting with our industry standard SCC, for example, we've developed families of serial communications controllers that give you the system performance your applications call for. Smaller, more integrated systems are fast becoming true "systems on silicon." And Zilog's Superintegration™ technology helps make denser, faster, simpler systems a smooth, natural evolution. With products that are fully upwardly compatible, we solve your systems problems on silicon. As new applications dictate new requirements, you can be sure Zilog will provide the new versions and the new generations you'll need. When you need them. Off the shelf. At a cost that makes sense. Isn't that really the way things should be? Contact your local Zilog sales office or your authorized distributor today. Zilog, Inc., 210 Hacienda Ave., Campbell, CA 95008, (408) 370-8000.

\*Available now.  
\*\*Call factory for exciting information.

**Right product. Right price. Right away.**






**ZILOG SALES OFFICES:** CA (408) 370-8120, (714) 838-7800, (818) 707-2160, CO (303) 494-2905, FL (813) 585-2533, GA (404) 448-9370, IL (312) 517-8080, NH (603) 888-8590, MN (612) 831-7611, NJ (201) 382-5700, OH (216) 447-1480, PA (215) 653-0230, TX (214) 987-9987, WA (206) 523-3591, CANADA Toronto (416) 673-0634, UNITED KINGDOM Maidenhead (44) (628) 39200, W. GERMANY Munich (49) (89) 672045, JAPAN Tokyo (81) (3) 587-0528, HONG KONG Kowloon (852) (3) 723-8979, KOREA (82) (2) 552-5401, TAIWAN (886) (2) 741-3125, SINGAPORE 65-235 7155, DISTRIBUTORS: U.S. Anthem Electronics, Hall-Mark Electronics, JAN Devices, Inc., Schweber Electronics, Vargas Electronics, Western Microtechnology, CANADA Future Electronics, SEMAD, LATIN AMERICA Argentina-Yel.-(1) 46-2211, Brazil-Digibyte (011) 581-1945, Semiconductores Profesionales (5) 536-1312.

CIRCLE NO. 31





# NEW

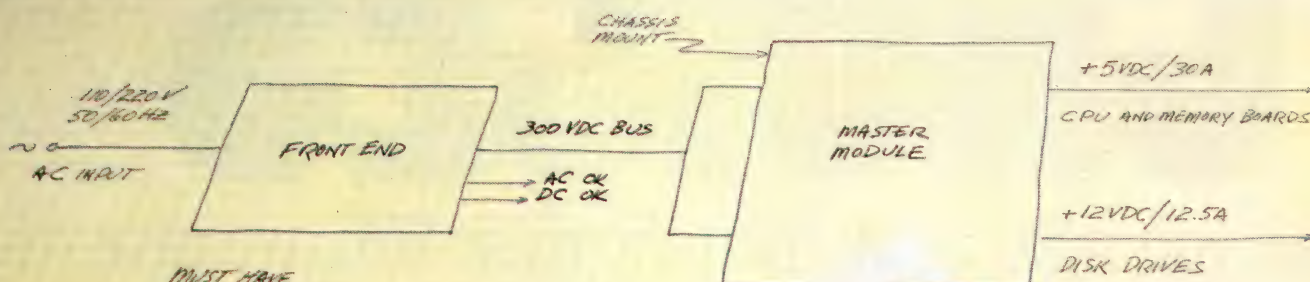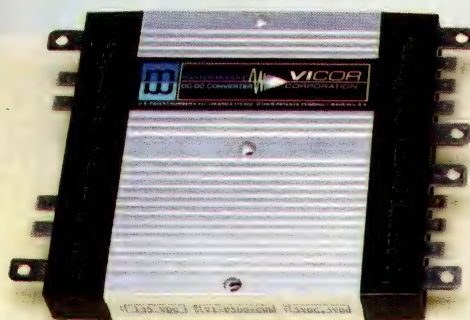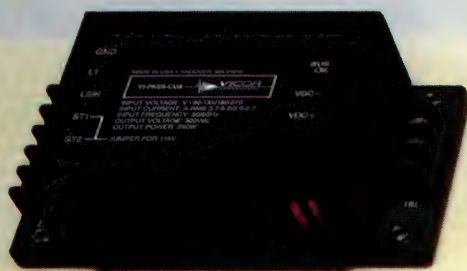

MUST HAVE


- UL, CSA, TUV
- 82% EFFICIENCY
- HIGH RELIABILITY
- POWER OK
- SEQUENCING
- 50 MS HOLD-UP
- FCC CLASS-B
- PROGRAMMABLE OUTPUTS

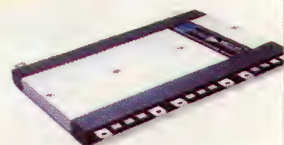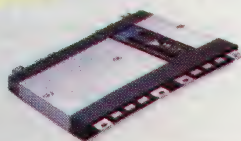*VIC*  
ALSO NEED -5.2 VOLTS  
AT 30 AMPS FOR THE  
ECL.  
CONVERTERS TO BE  
CHASSIS MOUNT.  
SEE ME ASAP




Module Series  
DC-DC Converters  
Triple Output

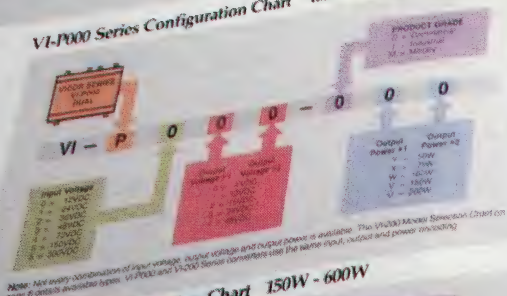VI-P000 Series Configuration Chart 100W - 400W



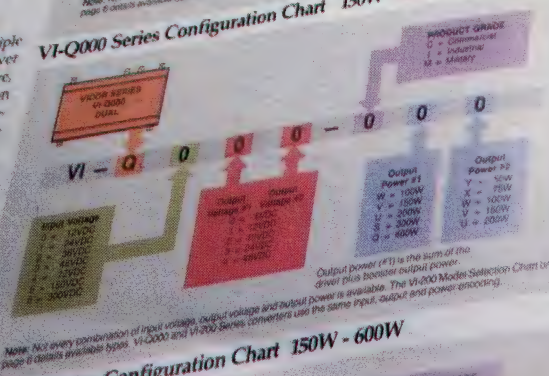VI-Q000 Series Configuration Chart 150W - 600W



## Configuration Steps

- 1 Select Input Voltage
- 2 Select Output Voltage 1
- 3 Select Output Voltage 2
- 4 Select Product Grade
- 5 Select Output Power 1  
(Cannot exceed single module ratings for VI-200 Series drivers.)
- 6 Select Output Power 2  
(Cannot exceed single module ratings for VI-200 Series drivers.)

Example  
48V: VI - P 3  
-5V: VI - P 3 0  
-12V: VI - P 3 0 1 -  
Commercial: VI - P 3 0 1 - C V  
150W: VI - P 3 0 1 - C V X  
75W: VI - P 3 0 1 - C V X

- 1 Select Input Voltage
- 2 Select Output Voltage 1
- 3 Select Output Voltage 2
- 4 Select Product Grade
- 5 Select Output Power 1  
(Cannot exceed single module ratings for VI-200 Series drivers.)
- 6 Select Output Power 2  
(Cannot exceed single module ratings for VI-200 Series drivers.)

300V: VI - Q 6  
+5V: VI - Q 6 0  
+24V: VI - Q 6 0 3 -  
Industrial: VI - Q 6 0 3 - I S  
300W: VI - Q 6 0 3 - I S  
150W: VI - Q 6 0 3 - I S

- 1 Select Input Voltage
- 2 Select Output Voltage 1
- 3 Select Output Voltage 2

24V: VI - R 1  
+5V: VI - R 1 0  
+12V: VI - R 1 0 1  
-12V: VI - R 1 0 1 1



# Chassis-Mount Modular Power From 50 to 600 Watts!


**OFF-LINE**

*In single or multiple output applications, Vicor's family of chassis-mount, power building blocks provide flexible and predictable solutions to virtually any power system requirement.*

Vicor's family of chassis-mount, off-line front ends, combined with the Mega and Master Module families of chassis-mount DC-DC converters, allow the power system architect to quickly and predictably customize expandable single or multiple output power systems with output power from watts to kilowatts. Modular power building blocks get you up and running in less time, at less cost, while Vicor's unprecedented levels of power density and efficiency result in less wasted space and heat.
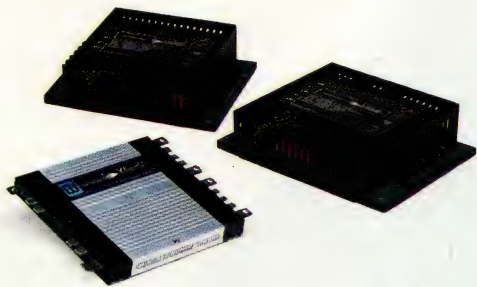
## Off-Line Front Ends

Chassis-mount front ends are available in output power ratings of 250, 500, and 750 watts and are designed for direct connection with Vicor's Mega Module and Master Module Series of DC/DC converter modules.



FRONT END SELECTION CHART

MODEL	OUTPUT POWER		
	250W	500W	750W
VI-FKE6-CUX	✓		
VI-FKE6-CQX		✓	
VI-FKE6-CMX			✓


OPERATING PARAMETERS (ALL MODELS)				
INPUT VOLTAGE (VAC)				
NOM	LOW	HIGH	TRANSIENT (1 SEC)	
110	90	135	150	
220	180	270	300	

Strappable to provide operation from 90 VAC to 270 VAC lines, the front ends feature conducted EMI/RFI filtering to VDE/FCC A & B, 50 msec holdup, active in-rush limiting and a BUS-OK status output. An opto-isolated AC-OK output is provided for advance warning of DC BUS dropout due to AC line failure.

## DC/DC Converter Modules


Vicor's Mega Module and Master Module Series of single and multiple output DC-DC converters provide the power system designer with a cost effective, high performance, off-the-shelf solution for applications that might otherwise require a custom supply. These modules incorporate standard VI-200 Series converters in a rugged, chassis-mount package.

### Single Output

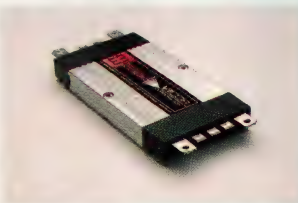


- Single output available from 50 to 200 watts.
- 2.5" x 4.9" x 0.62".

### Single and Dual Outputs

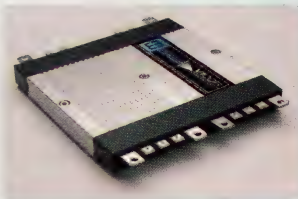

- Single output available from 100 to 400 watts
- Dual outputs from 50 to 200 watts each
- 4.9" x 4.9" x 0.62".

### Single, Dual and Triple Outputs

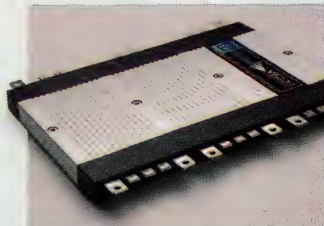

- Single output available from 150 to 600 watts.
- Dual outputs with the first output from 100 to 400 watts, and the second output from 50 to 200 watts.
- Triple outputs from 50 to 200 watts each.
- 7.3" x 4.9" x 0.62".

Specify your configuration by picking any combination of Vicor's standard output voltages (5, 12, 15, 24, 48 VDC) at the power levels you need. Vicor does the rest. If standard output voltages don't meet your needs, Vicor can provide semi-custom outputs anywhere in the range of 2 to 100 VDC! For complete details and applications information, please refer to the Mega Module and Master Module sections of the Vicor Product Catalog.

*To Receive A Complete Catalog, Including Information On Vicor Products, Applications And Accessories, Call Vicor Today At (508) 470-2900, or write to 23 Frontage Road, Andover, MA 01810.*



**Component Solutions  
For Your Power System**





IN THE ERA OF MegaChip<sup>TM</sup> TECHNOLOGIES

# ASIC SOLUTIONS

“My team is hard-nosed about gate array. Our system requires a high-performance solution with no false starts. We must have a supplier who can get us everything we need up front. Our prototype has to be on spec, on time...no surprises.”

You're right to be hard-nosed about your gate array. You're a veteran of high NRE investments, tight market windows, lots of promises, uncertain results. At Texas Instruments, we have anticipated that and have structured an approach to gate arrays which offers you more than a choice of silicon.

As a result, you not only get the solution you need, but you make better use of your time, improve return on investment, lessen the risks, and shorten the design cycle.

**“A clear-cut design process with plenty of support is a necessity.”**

TI's design flow is very straightforward. Areas of control are defined to minimize the possibility of surprises. Our goal is the same as yours — a shortened design cycle time.

When necessary, our design flow can be adapted even more precisely to fit your needs.



# GATE ARRAYS

TI's service and support are comprehensive — and available to you from Texas to Taiwan. Among the highlights: **Our TGC100 Series Design Kit**, operating on Daisy/Cadnetix (DAZIX™), Mentor Graphics™, and Valid™ workstations, provides the necessary information to easily implement your gate-array design.

**Person-to-person advice and counsel** are provided worldwide by ASIC applications specialists in our field sales offices. ASIC design specialists are stationed at ASIC design centers in our Regional Technology Centers, where our design workshop is also conducted regularly.

**Delivery schedules can be tailored** to support your ship-to-stock or just-in-time programs anywhere in the world.

## "We demand high performance in our arrays."

The TGC100 arrays are fabricated in TI's 1-micron EPIC™ CMOS process technology. Typical gate delays are 500 ps with flip-flop toggle rates up to 208 MHz.

## "We prefer a choice of densities plus design options."

TI's TGC100 arrays range in complexity up to 26K gates. You call the shots on pin count, pinout definition, and the package itself by choosing from our variety of pack-

ages having pin counts up to 256 pins (see table below).

TI's gate-array library contains more than 200 macros, many essential to attaining high-performance designs. For example, a clock distribution macro minimizes clock skew. Input/output buffer macros minimize unwanted voltage transients and drive heavy capacitive loads.

In support of the JTAG standard, SCOPE™ macros permit incorporation of design-for-test features.

A path-length criticality parameter allows you to specify the delays on critical nets. This acts to minimize the physical length of the interconnect traces and reduce overall propagation delay.


When you have more demanding requirements, the following options give you maximum flexibility in achieving the exact gate array you need:

- Additional prototypes
- Additional 1-MHz test vectors
- Prototype devices tested over temperature and VCC ranges plus DC parametrics
- Critical-path delay measurements (pin-to-pin)
- "At speed" test vectors
- Nonstandard VCC and ground-pin locations
- Operating temperature range other than 0°C to 70°C
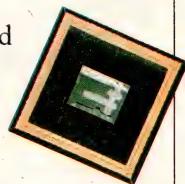
## Tomorrow's outlook

Just as our TGC100 Series gate arrays meet the majority of your needs today, our gate arrays of tomorrow will fill the predominant industry needs for sub-micron densities.

Already, TI has disclosed an array having 106K gates, fabricated with TI's EPIC-II, 0.8-micron BiCMOS technology. High density combines with high performance — ECL speeds at CMOS power levels. This technology is the foundation for an entire family of sub-micron ASIC products from TI.



**For more information** on TI gate arrays, call, fax, or write us. **In Europe** call 44-234-223000, fax 44-234-223459, or write Customer Response Centre, MS 09, Texas Instruments Limited, Manton Lane, Bedford MK41 7PA, England. **In Japan** call 81-3-769-8700, fax 81-3-457-6777, or write Texas Instruments Japan Limited, MS Shibaura Building 9F, 4-13-23 Shibaura, Minato-Ku, Tokyo 108, Japan. **In Hong Kong** call 852-735-1223, fax 852-735-4954, or write Texas Instruments Hong Kong Limited, Market Communications Department, 8th Floor World Shipping Centre, 7 Canton Road, Kowloon, Hong Kong.

## TI's TGC100 SERIES COMMERCIAL GATE ARRAYS

GATE-ARRAY TYPE	TOTAL CELLS	MAXIMUM USABLE (90%)	TOTAL BOND PADS	PRODUCTION PACKAGE OPTIONS															
				PLASTIC DIP				PLASTIC-LEADED CHIP CARRIER				PLASTIC QUAD-FLAT PACKAGE*							
				28	40	28	44	68	84	80	100	120	132	144	160	208	240	100	120
TGC104	3,600	3,240	100	X	X	X	X	X	X	•	••							X	
TGC105A	4,500	4,050																	
TGC106	5,600	5,040	130	X	X		X	X	X	•	••	•	•					X	X
TGC107	6,720	6,048																	
TGC108A	8,340	7,506	158	X	X		X	X	X	•	••	•	•	•	•			X	X
TGC110	10,008	9,007																	
TGC113	12,654	11,389	196				X	X		•	•	•	•	•	•			X	X
TGC115A	14,706	13,235																	
TGC116	15,590	14,022	216							•	•	•	•	•	•			X	X
TGC119	18,620	16,758																	
TGC122	21,854	19,669	256															X	X
TGC126	25,868	23,281																	

™ EPIC, SCOPE, and MegaChip are trademarks of Texas Instruments Incorporated.  
DAZIX is a trademark of Daisy/Cadnetix, Inc.  
Mentor Graphics is a trademark of Mentor Graphics Corporation.  
Valid is a trademark of Valid Logic Corporation.  
® IBM is a registered trademark of International Business Machines Corporation.




# NEWS

ABOUT  
SYNCHRO-CONVERSION  
A/D & D/A CONVERSION  
1553 BUS DEVICES  
POWER & CUSTOM HYBRIDS

**DDC**  
**ILC DATA DEVICE**  
**CORPORATION**
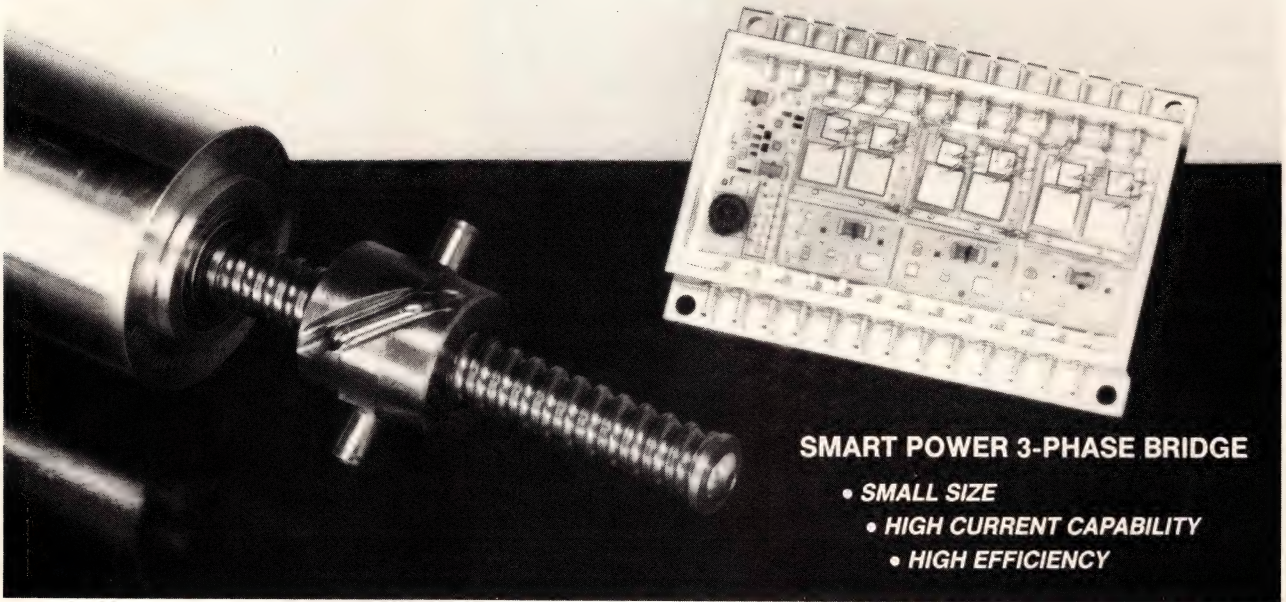
## WE'RE CHANGING THE WAY THE WORLD LOOKS AT MOTOR DRIVERS



**SMART POWER 3-PHASE BRIDGE**

- **SMALL SIZE**
- **HIGH CURRENT CAPABILITY**
- **HIGH EFFICIENCY**

*Motor Courtesy of Inland Motor, Kollmorgen Corporation.*

That's right! The world is changing with the introduction of the PWR-82331, DDC's new family of motor drive products.

The PWR-82331 30A, 200V, 3-Phase bridge power hybrid consists of six N-channel power MOSFETS and six anti-parallel fast recovery diodes connected into a full 3-Phase bridge driver. Each MOSFET bridge is driven directly from a CMOS input through high and low side drivers without the need for external bias voltages.

Internal protection circuitry prevents in-line transistors from simultaneous conduction and eliminates multiple upper or lower conduction. A constant voltage drive to control the MOSFETS is used to ensure uninterrupted performance of the

drivers even in a motor stall situation—performance that cannot be achieved when a boot-strap configuration is utilized.

The PWR-82331 has its own built-in power source which supplies all the required internal biasing and logic supplies. The Vb input to the internal supply can either be hooked directly to the Vcc pin or to an additional external power source.

This highly efficient bridge uses all N-channel MOSFETS to ensure a very low on-resistance of 0.11 Ohm per leg and 50ns fast recovery power rectifiers to clamp inductive flyback. The PWR-82331 is packaged in a thermally efficient copper case with a typical junction-case thermal resistance of 0.5° C/W and measures only 2.1"W x 3.0"L x 0.375"H. This hybrid

is designed to operate from -55°C to +125°C, and is fully processed to MIL-STD-883C.

The PWR-82331 can be driven directly from the commutating logic and when combined with a pulse width modulator creates a Servo Motor Controller, which after proper derating, can drive motors up to 6 hp over the full MIL temperature range.

In addition to the PWR-82331, DDC has introduced the PWR-82333 which can handle a 600V Vcc. Also available are the PWR-82340 and PWR-82342 which are 2-phase bridges in an H configuration.

**For additional product and application information, contact Bob Fryer at 516-563-5390, or contact the DDC office nearest you.** □

**DDC**  
**ILC DATA DEVICE**  
**CORPORATION**

Circle No. 121 for Sales Contact

**HEADQUARTERS AND MAIN PLANT:** ILC Data Device Corporation, 105 Wilbur Place, Bohemia, N.Y. 11716, (516) 567-5600, TLX-310-685-2203, FAX: (516) 567-7358  
**WEST COAST (CA.):** WOODLAND HILLS, (818) 992-1772, FAX: (818) 887-1372;  
SAN JOSE, (408) 236-3260, FAX: (408) 244-9767; GARDEN GROVE, (714) 895-9777, FAX: (714) 895-4988  
**WASHINGTON, D.C. AREA:** (703) 893-7989, FAX: (703) 893-7954  
**NORTHERN NEW JERSEY:** (201) 785-1734, FAX: (201) 785-4132  
**MASSACHUSETTS:** (617) 341-4422 or 3128, FAX: (617) 344-1040; **JAPAN:** (3) 814-7688, FAX: (3) 814-7689  
**UNITED KINGDOM:** 44 (635)-40158, FAX: 44 (635) 32264; **FRANCE:** 33 (1) 4333-5888, FAX: 33 (1) 4334-9762  
**WEST GERMANY:** 49 (8191) 3105, FAX: 49 (8191) 47433; **SWEDEN:** 46 (8) 920635, FAX: 46 (8) 353181

Circle No. 122 for Literature



## THERMAL-ANALYSIS SOFTWARE

# Thermal images provide reliability clues



Thermal analysis, long familiar to mechanical and reliability engineers, can prevent serious thermal problems.

Newer thermal-analysis software, tailored to EEs, can help you pinpoint problems while you can still easily fix them.

**Anne Watson Swager,**  
Associate Editor


An electronic listening device sitting inside a buoy on the Pacific Ocean, a pacemaker in a human heart, and a missile's guidance system are products that can't tolerate unreliability. And reliable product performance is what thermal analysis helps to ensure. Thermal analysis is especially critical for those products that aren't easily serviced, require the utmost in safety, control military equipment, and for designs that are difficult or dangerous to test.

Granted, reliability prediction is tricky. The relationship between temperature and reliability is not determined or fixed. However, you can be sure that if you violate a device's maximum junction temperature, it won't perform very well for very long. Thermal analysis can predict such extreme cases.

Thermal analysis is nothing new to mechanical and reliability engineers. Now, the increasing density of electronic components forces electrical engineers to consider thermal effects early in a design cycle (Ref 1). There isn't time to wait for a dedicated reliability engineer to complete an in-depth analysis. If you wait, you lose the whole advantage of thermal analysis—the ability to evaluate and change a design before you actually build it.

Many thermal-analysis tools are now available. In the last few years, electronic CAD and software companies have introduced packages tailored to pc boards, heat sinks, and electronic enclosures. CAD companies link thermal analysis with their pc-board-layout tools and component libraries so that you can simultaneously design your circuit and perform thermal analysis (Fig 1).

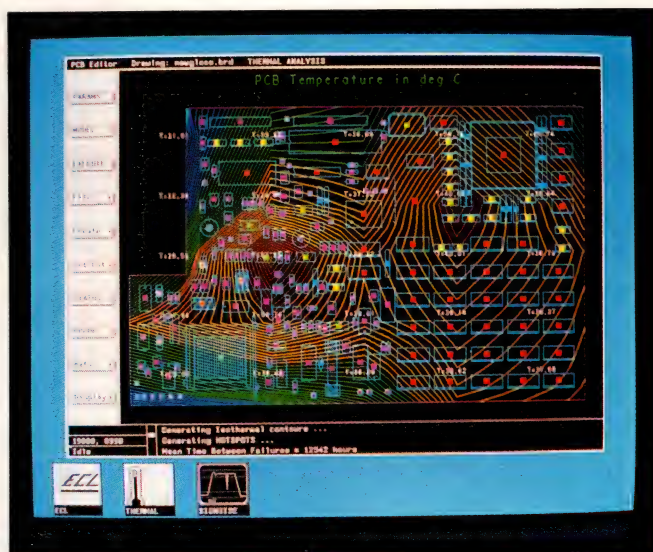The fundamental results of a thermal simulation indicate when your design violates an IC's maximum junction temperature or a component's maximum operating temperature. Basically, the programs use thermal-resistance and power-dissipation data to model junctions and resistors as heat sources. All packages provide you with a steady-



*New thermal-analysis programs tailored to pc boards are available from many CAD vendors. These packages use heat-transfer and fluid-flow equations to solve for steady-state temperatures and in some cases transient temperatures. A common graphical representation displays isotherms, which are lines of constant temperature. (Courtesy Valid Logic.)*





## THERE'S A SURPRISE IN EVERY BOX.

You'll be surprised at what *isn't* included in OrCAD® PCB II. It's missing basic features that any competent layout software needs if it's really going to save you time. Here's a partial list of what's missing:

- No automatic component placement
- No automatic gate and pin swapping
- No partial editing of existing routes
- No on-screen design rule error notification
- No automatic component renaming
- No automatic component or part replacement

MAXI/PC has every one of these features, and more. And while OrCAD charges \$1,495 for PCB II, MAXI/PC

costs just \$995, including everything you need for schematics design, placement, routing, and output of complex boards. With more power for less money, MAXI/PC is simply a better value.

### If You Have OrCAD Schematics...

OrCAD's schematics package outputs directly to MAXI/PC's layout and routing software. So if you were going to buy PCB II because you thought you were locked in, think again. You get a lot more product for a lot less money with MAXI/PC.

### Don't Get Surprised.

You don't need unpleasant surprises when you invest in PCB software. You

need time saving performance. Call today for the details on MAXI/PC. Have boards waiting? Order MAXI/PC and get them started now. Our 30 day, money-back guarantee makes ordering risk-free.

**(508) 692-4900**

**MAXI/PC**  
PCB CAD SOFTWARE

**RACAL-REDAC**

238 Littleton Road, P.O. Box 365  
Westford, MA 01886-9984, USA  
Fax: (508) 692-4725

**RACAL**



# TECHNOLOGY UPDATE

## Thermal-analysis software

state picture of a board's, component's, or object's temperature profile. Some packages also perform transient analysis, which allows you to determine how the temperature changes at start-up. These and other specifications for the packages discussed in this article are listed in **Table 1**.

Before you approach vendors, make sure you have a clear picture of your own objectives. Start by answering a few questions: What types of systems do you want to model? Power transistors mounted on a lone heat sink? A single pc board with components on one side? A board with components on both sides? A whole card cage? A whole enclosure with multiple card cages? Are you well versed in CAE tools, and are you interested in linking the thermal-analysis software with your other tools, such as pc-board-layout tools?

All thermal-analysis software packages solve some set of heat-transfer and fluid-flow equations using a particular numerical scheme. Because each program uses a unique set of equations, comparing different packages is difficult. You may be able to determine a program's accuracy by studying the vendor's test results. Ultimately, the more questions you ask software vendors, the better.


The first criterion for any package you buy is that it accurately models your particular system and produces reliable results. The second most important criterion is how easily thermal analysis inserts into your design flow. In other words, how easy is it for you to implement **Fig 1's** design scenario? Of course, cost is always a factor, so be sure you consider the total thermal-analysis costs. Some of the programs in **Table 1** require additional packages to process and display the data.

To satisfy the accuracy criterion,

you'll need some idea of what's involved in computational heat transfer and fluid dynamics. The numerical technique and set of equations each software package relies upon makes a big difference in the accuracy of your thermal-modeling result. And, the type of numerical scheme that yields the best result depends heavily on the complexity

of your model's component geometries. Modeling air flow in an aircraft engine and around a pc board are quite different tasks.

Both finite-element and finite-difference techniques solve heat-transfer and fluid-flow equations using matrix techniques. Finite-element schemes are typically more accurate for complicated geometries; finite-

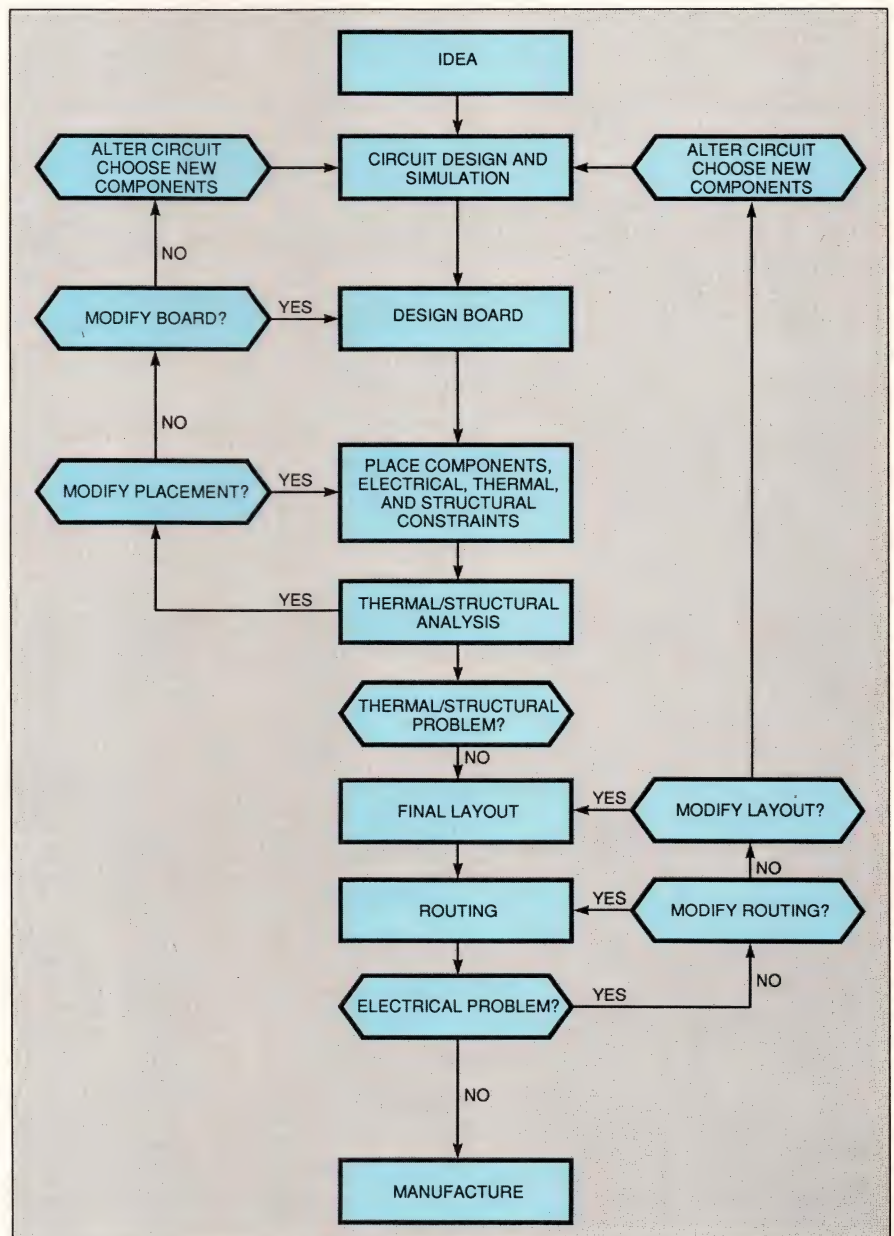

**Fig 1—By integrating thermal analysis into your circuit's design and layout cycle, you can find thermal problems and make changes before your product's physical design is complete.**



# TECHNOLOGY UPDATE

## Thermal-analysis software

difference schemes use simpler algorithms and suit regular geometries. As for the software itself, the major difference between the two

methods lies in the size of the matrices formed and the solver's iteration scheme. According to Fluid Dynamics, the finite-element tech-

nique requires more computer resources per iteration than the finite-difference technique. Thus, it may take more computer power and

**Table 1—Representative thermal-analysis software packages**

Manufacturer (Distributor)	Software package	Price	Program type	Dimensions modeled	Numerical method	Hardware platform	Transient analysis	Comments
BV Engineering Professional Software	STAP	\$125	General purpose	2	Finite difference	IBM PC or compatible, Macintosh		Tailored to heat-sink modeling. Requires Pcpot and Pdp programs to plot and print results. Conduction only.
CAD Software	Pads-thermal	\$975 to \$4000	pc board	3	Finite difference	IBM PC or compatible		Software integrated with Pads-pcb layout tools. Version of Dynamic Soft Analysis' beta soft-pc.
Compuflo	Flotran	\$8000 to \$30,000 (annual license fee)	General purpose	2 and 3	Finite element	Workstation to mainframe		Requires mesh-generation software such as I-deas, Patrans, or Ansys.
Daisix	PCB thermal	\$20,000	pc board	3	Finite element	Sun's Sparc, 386i, or HP workstation	•	Software includes interface to other pc-board-design tools. Version of Pacific Numerix's PCB thermal.
Dynamic Soft Analysis Inc	Betasoft-pc	\$3000	pc board	3	Finite difference	IBM PC or compatible		Latest package upgrade includes reliability calculator.
Flomerics Limited	Flotherm	7500£ to 40,000£ (perpetual license fee) 6000£ to 16,000£ (annual license fee)	General purpose	2 and 3	Finite element	IBM PC or compatible to mainframe	•	Models entire electronic systems and enclosures.
Fluid Dynamics	Fidap	\$3000 to \$26,000	General purpose	2 and 3	Finite element	Workstation to mainframe	•	Includes mesh-generator program, Fimesh, and preprocessor program, Fiprep.
Helios (Management Sciences)	Thermax	\$4500 to \$15,000	pc board	2, 2.5, and 3	Finite difference	IBM PC or compatible, Sun, DEC, or Apollo workstation	•	Interactive, mouse-driven software. Also models radiation effects.
HTRD Software	Tlayers	\$1980	General purpose	3	Finite element	IBM PC or compatible		Tailored to IC hybrids, power supplies, and power hybrids. Conduction only.
Intergraph	PCB thermal	\$20,000	pc board	3	Finite element	Intergraph workstation	•	Features icon-driven user interface that links the thermal model to other pc-board-design tools. Version of Pacific Numerix's PCB thermal.
Mentor Graphics	Autotherm	\$69,000	pc board	2.5	Finite element	Apollo workstation		Price quoted is for the Package Station, which includes Autotherm. Also models radiation effects.
	Prototherm	\$14,900	pc board	2.5	Finite element	Apollo workstation		Thermal package is part of the board station. Also models radiation effects.
Pacific Numerix	PCB thermal	\$15,000	pc board	3	Finite element	Sun, DEC, or Apollo workstation	•	Thermal software (priced separately) operates within the PCB Design Expert System.
Racal-Redac	Visula thermal	\$17,000 to \$19,000	pc board	2.5	Finite difference	Sun, DEC, or Apollo workstation	•	Thermal models rely on both theoretical calculations and real measurements of device performance.
Techna/Soft Systems	T/SNAP	\$985 (8088 version)	General purpose	3	Finite difference	IBM PC or compatible	•	Tailored to analysis of complex thermal networks. Also models radiation effects.
Valid Logic	Thermostats	\$15,000	pc board	2.5	Combined finite element and finite difference	Sun or DEC workstation		Package includes reliability calculator. Also models radiation effects.
Visionics	EE designer III/E	\$5995	pc board	3	Not specified	IBM PC or compatible	•	The EE Designer extended version integrates thermal software with other pc-board design tools. Conduction only.

**NOTE:** All packages model the effects of conduction, and natural and forced convection unless otherwise specified.






# ZAX INVITES YOU TO THE NEXT GENERATION OF MICROPROCESSOR DEVELOPMENT SYSTEMS.

Zax Corporation established its reputation as a leading manufacturer in the Microprocessor Development industry with the introduction of the ICD series of emulators. We expanded upon this technology by unveiling our advanced line of ERX emulators featuring *high performance debugging* for a wide variety of microprocessors including *Motorola, Intel, NEC, Hitachi and Zilog*.

We now invite you to witness the next generation of microprocessor development tools by introducing *high speed 33 MHz support for 68020 and 68030*, and by presenting 'AXIS'; a *revolutionary configuration featuring an ethernet interface for networking ERX-series emulators with Sun*

*workstations*. We've enhanced the ERX configuration without forfeiting the ergonomic features and compact size we've always provided. You now get higher speed and more versatility in addition to features like one million breakpoints, two meg of emulation memory, performance analysis, source level and symbolic debug, enhanced window driven interfaces, and full cross development software, to name a few.

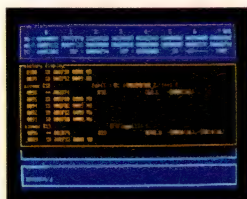Zax is committed to fulfilling all your development needs. Call us toll-free and let the next generation of development systems work for you. Call 1-800-421-0982. In California call 1-800-233-9817. Zax Corporation, 2572 White Road, Irvine, CA 92714.



**ZAX**  
Zax Corporation



# TECHNOLOGY UPDATE

## Thermal-analysis software


processing time. However, Fluid Dynamics claims that the finite-element technique usually requires fewer iterations to converge on a solution than the finite-difference method.

A main difference between these methods, then, is the issue of convergence and convergence time. Finite-difference schemes sometimes use what some call computer "tricks" to speed the computations and ensure convergence. However, one company's trick is another's unique software solution. The "tricks" basically boil down to the software making assumptions to ensure that the solution will always converge.

Another difference between finite-element and finite-difference programs is in the structure of the mesh, which is simply the geometric arrangement of nodes for which the software calculates junction temperatures. To create models that most closely resemble actual components, many finite-element programs use triangular meshes. Meshes composed of triangular shapes can more easily represent circles and other geometric patterns.

Finite-element-based schemes sometimes allow you to create regions of refined mesh. In other words, there may be parts of your board or system that you expect to be more critical than others. You can create a mesh with nodes closer together in those areas and more spread apart in the noncritical areas. A key to producing refined meshes is what Fluid Dynamics calls transition elements. The mesh can't abruptly change from one density to another, and transition elements smooth the transition.

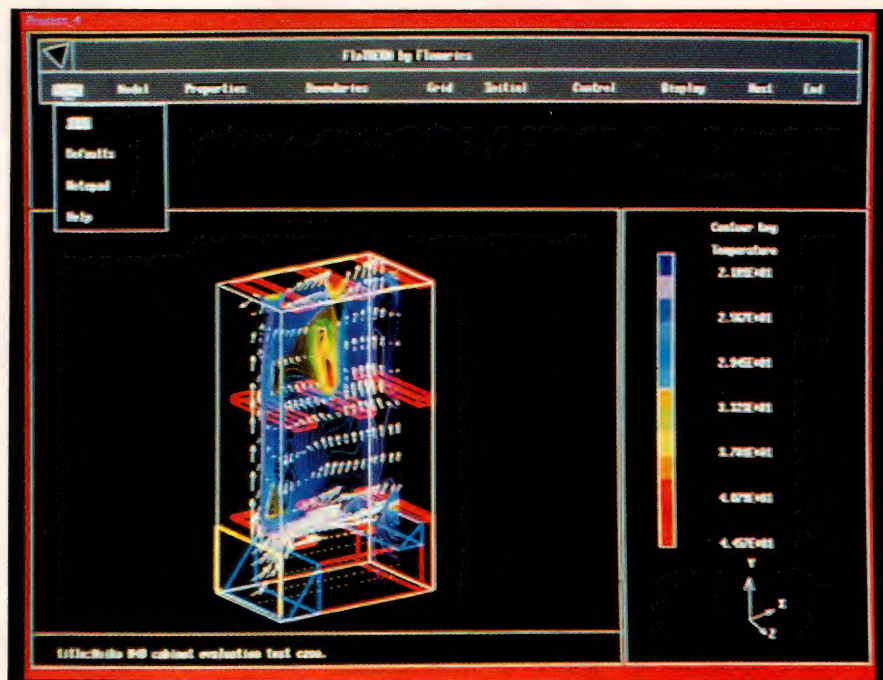Alternatively, most finite-difference-based programs use rectangular meshes, which are adequate for many pc-board layouts. However, rectangular meshes can only ap-



**Modeling temperature inside an enclosure** or any system with multiple heat sources and fans is much more complicated than analyzing a single pc board. Natural, forced, and mixed convection causes complex turbulent effects, which the software must be able to deal with accurately. (Courtesy Flomerics Limited.)

proximate round shapes such as TO power packages. But, according to Dynamic Soft Analysis, the equations of its and CAD Software's packages can correct for mismatches between the mesh and the actual part, so that the rectangular mesh is not a liability.

### Heat travels in three ways

In addition to numerical schemes and equations, there are heat-transfer and fluid-flow considerations to investigate. All of the software packages model the effects of conduction. A few other packages additionally model convection. Since convection involves molecular motion—a kind of fluid flow—programs that calculate the effects of convection are known as computational-fluid-dynamics programs. And a few others also model electromagnetic radiation.


Modeling conductive effects is relatively straightforward, but thermal analysis gets complicated

when you also want to consider convection—especially forced convection. Valid Logic says that an analysis based only on natural convection can often be 99% accurate. However, that accuracy can decrease to 80% with the addition of forced air. High-end packages, such as Fidap, Compuflo, and Flotherm, have elaborate schemes that calculate the effects of turbulent air flow.

Yet another feature you should investigate is the number of dimensions that the software actually simulates. Some packages model in 2-D, 3-D, and even 2.5-D. Vendors use the term 2.5-D to refer to models that aren't purely 3-D, but model more effects than purely 2-D systems.

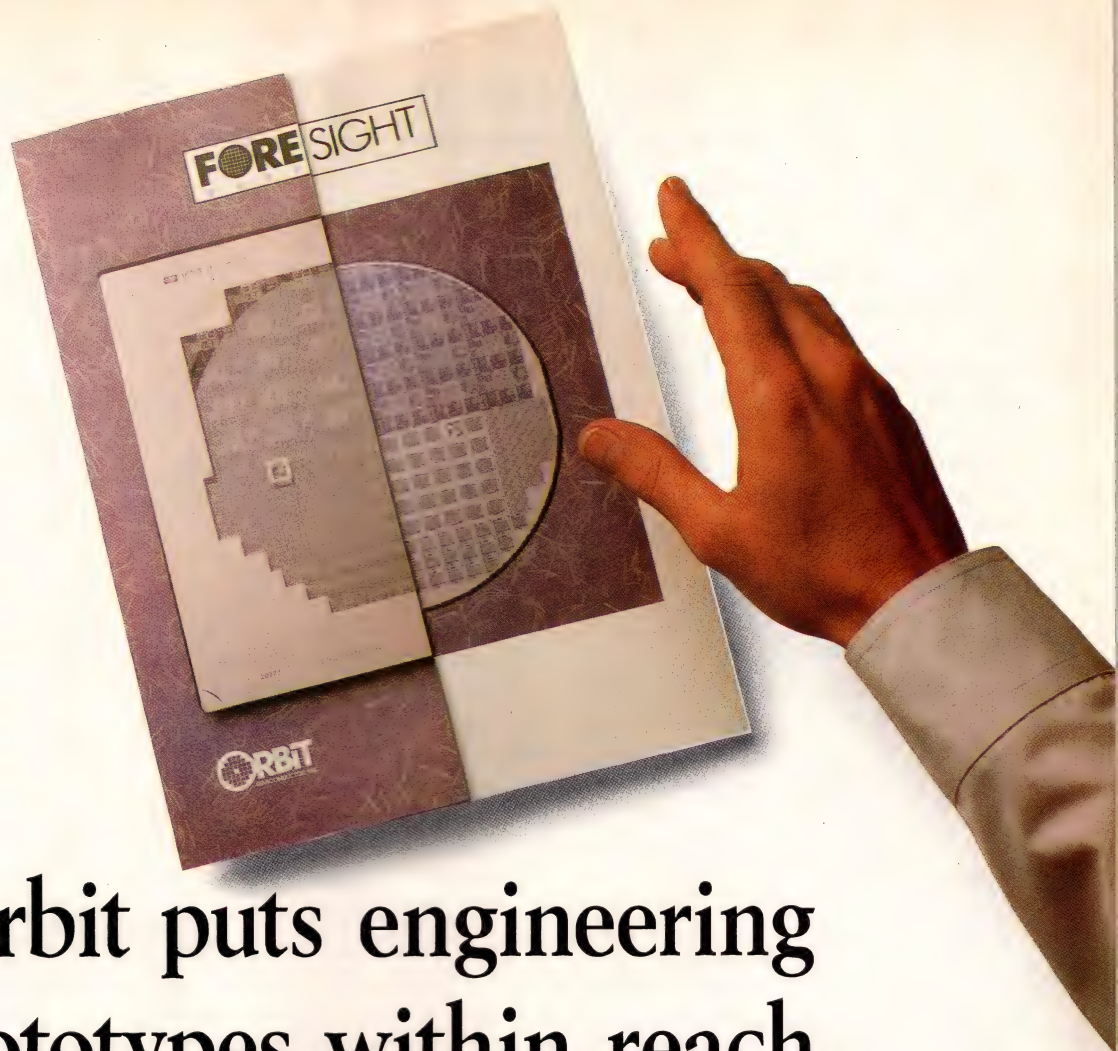Two-dimensional software makes one major assumption: the board or substrate thickness is so thin compared with its surface area that its effects are negligible. More specifically, the temperature through the thickness of the board is uniform.





# Orbit puts engineering prototypes within reach.

Now you can cut NRE expense and save valuable time on engineering prototype runs just by using a little foresight. Foresight, Orbit's new multi-project wafer processing service, puts the engineering prototypes you need within reach. In record time. And at a record low cost.

Orbit's new Foresight accommodates generic CMOS processes with feature sizes down to 1.2 microns with maximum die sizes of 300 mils on a side. Getting in on a run is as easy as supplying a database tape by our monthly start date.

Available processes:

- Single Poly/Single Metal
- Double Poly/Single Metal
- Single Poly/Double Metal
- Double Poly/Double Metal

Don't wait until high NRE costs and slipped deadlines put you in a bind. Design rules and information on Orbit's new Foresight service are within reach today by contacting Foresight Marketing or the international rep nearest you. Orbit Semiconductor, Inc. 1230 Bordeaux Drive. Sunnyvale, CA 94089. FAX (408) 747-1263. Or call (800) 331-4617. In California (800) 647-0222 or (408) 744-1800.



A subsidiary of Orbit Instrument Corporation.

*What others promise, we guarantee.*

CIRCLE NO. 35



# TECHNOLOGY UPDATE

## Thermal-analysis software

Three-dimensional modeling takes all board layers into account, so that you can determine temperatures at each multilayer surface. The definition of 2.5-D is by no means standard. Thermostats, a 2.5-D analyzer from Valid Logic, neglects component height but does account for multiple board layer temperatures.

Mentor Graphics' scheme is substantially different from Valid's. Mentor's Autotherm transforms a 3-D model into a 2.5-D model (Fig 2). The 3-D model includes all the thermal resistances from the semiconductor junction to ambient air and from the junction to the pc board, and it models the junction itself as the heat source,  $Q_V$ . Autotherm transforms the extended model into a simpler model by modifying the power and combining the thermal resistances. According to Mentor, these modifications ensure that the board-surface temperature and the heat flow into the pc board are both completely accurate. Thermax, from Helios, is another program that models so-called 2.5-D effects. The package, an enhanced version of the company's 2-D package, analyzes the effect of air flow over and under a pc board.


Obviously, you'd want to use a 3-D program if you plan to model, for example, a thick block of material. And many CAD vendors say that 3-D is important for pc boards as well, especially when they have multiple layers and components mounted on both sides. Many of the programs in Table 1 are available in both 2-D and 3-D versions.

### Take the right steps


Once you've compared various packages' accuracy, you can examine other features that determine how easy the software is to use. Each thermal-analysis package includes many other features that ac-

complish the basic steps of any thermal-modeling problem (Fig 3). These steps are common to all software programs, but each is implemented in different ways. Many of the steps are automatic. You have to perform other steps manually, or provide additional information to the program.

Software available from CAD vendors who also provide pc-board-layout tools performs the first three steps shown in Fig 3 virtually automatically. During the pc-board-layout stage, you've already essentially defined the entire geometry, and with this information the software automatically creates the mesh. The library you use at the layout stage includes thermal data about the component either in the component's library or a separate thermal library. For example, Mentor's Autotherm extracts board geometry and component placement directly from the company's board-station data. The company's Package Station parts library includes thermal properties such as resistivity, conductivity, and power dis-

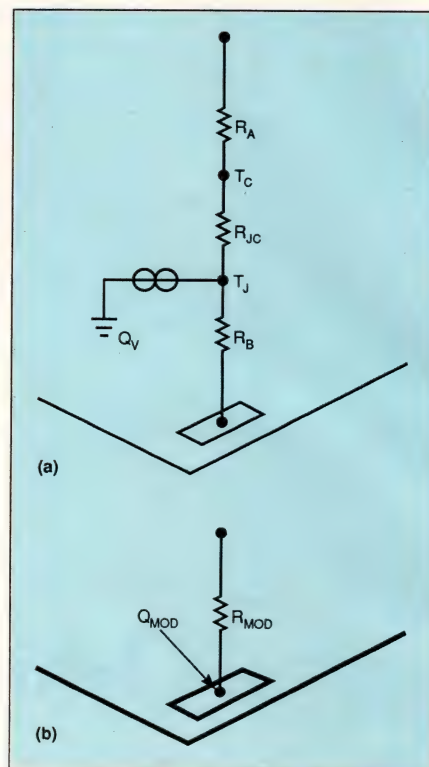


**Fig 2—Software packages that model 2.5 dimensions include 3-D effects in an essentially 2-D analysis. Mentor Graphics' Autotherm package transforms a 3-D model, (a), into its 2.5-D model, (b), by modifying the power and combining the thermal resistances.**

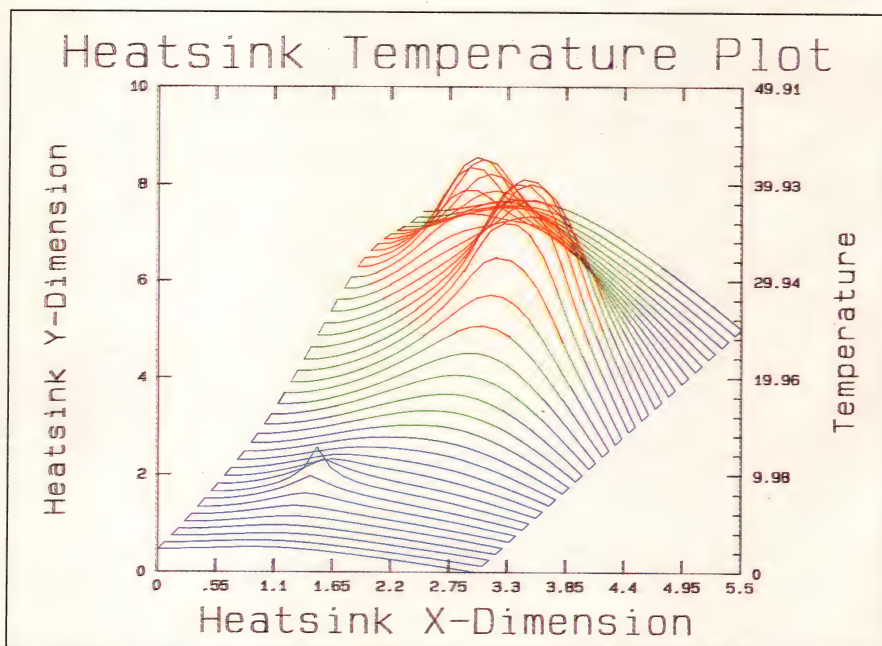

**Two-dimensional software can model simple systems such as 20 transistors and components mounted on a single heat sink. (Courtesy BV Engineering Professional Software.)**



# We've got the guts, you get the glory.

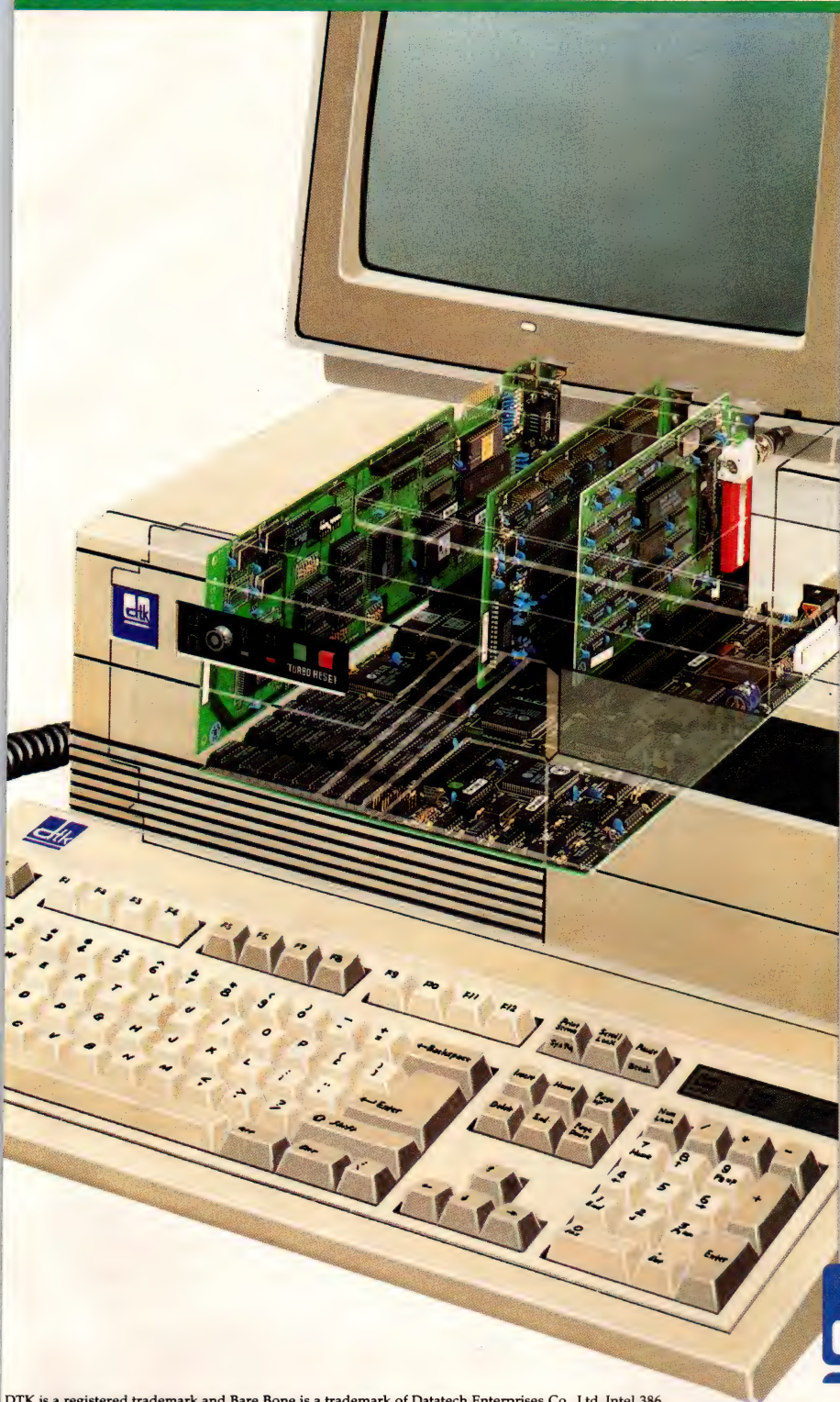

Your product shouldn't be a testing ground for inferior suppliers.

Today's sophisticated systems demand maximum compatibility and reliability. Your reputation depends on it.

DTK offers clearly superior 80386, 80286 and 8088-based Bare Bone™ systems with FCC, UL, CSA and TUV certification. Plus a wide line of motherboards that are fully compatible with AT™, XT™ and Micro Channel™ bus architectures.

They're all built to deliver the performance and reliability you need, even in rigorous manufacturing environments. We'll deliver them when you need them from our state-of-the-art 270,000 square foot manufacturing facility.

**More Guts.** Choose from a dozen Bare Bone systems designed to fit most of your needs. Or select from an extensive line of motherboards, including a 33MHz '386 with cache memory.

We can custom manufacture to your specifications, too. And we'll work hard to bring your projects in on time, and on budget.

**Better Quality.** Our substantial R & D capabilities and stringent QC procedures mean you can depend on us for the most reliable, highest performance products available today. And tomorrow.

Our inspection conforms with MIL-STD-105D, and our boards enjoy an overall reliability rate greater than 98%.

So why take chances? We've got all the guts you need at prices that are hard to beat. Go for the glory.

Call or write DTK COMPUTER, Inc., 15711 E. Valley Blvd., City of Industry, CA 91744.

Tel: (818) 333-7533

Fax: (818) 333-5429

Ask for OEM sales.



**Clearly superior.**

DTK is a registered trademark and Bare Bone is a trademark of Datatech Enterprises Co., Ltd. Intel 386 is a trademark of Intel Corporation. AT, XT and Micro Channel are trademarks of IBM Corporation.



# TECHNOLOGY UPDATE

## Thermal-analysis software

sipation, as well as material properties.

The one exception to this automatic process occurs when a component doesn't appear in the vendor's library. All software vendors provide a way for you to define additional components, but you must supply all thermal data. Obtaining this information may not be so simple. In many cases, semiconductor manufacturers have supplied CAD vendors with data that isn't available on a part's data sheet. For example, Bipolar Integrated Technology (Beaverton, OR) supplied all mechanical and thermal data about its parts directly to Valid so that Valid could include the parts in their library. Also, CAD vendors may have done some testing of their own, and refined their own models. For example, Mentor creates some of its own equivalent models from IC material and die-size information.

To obtain thermal data, which is in many cases not printed on data sheets, you may have to contact manufacturers yourself; however, don't expect them to have all the data you want. If you do get a hold of some data, you need to be quite confident of its validity. Also, some specifications may produce results more erroneous than others. According to Valid, incorrect power-dissipation information is a major source of analysis error.

### Examine the libraries

To date, you'll find that all vendors have standard components in their libraries, such as resistors, capacitors, and digital ICs in both TTL and CMOS. Most libraries also include a variety of package styles, such as DIPs and surface mount, and some include TO power packages. However, you can safely assume that any unique component—a high-speed, wide-bandwidth op amp or a power amplifier—will re-

quire you to create a new model to accompany it.

If you're using a general-purpose thermal-analysis package that isn't linked to other design tools, the mesh description may involve more work, such as specifying X and Y coordinates, for example. Some packages allow you to define the mesh by specifying fine or coarse points. You may need additional software programs for mesh generation. Compuflo's Flotran, a high-end program, requires additional software such as Ansys and Padtrans, which are more familiar to users of mechanical-CAD software.

Defining boundary conditions essentially amounts to giving the pro-


gram certain constraints on ambient temperature, temperatures of any card guides that make contact with the pc board, and air velocities (if your system has a fan). Depending on the package, you may also have to specify heat-transfer and convection coefficients at this stage.

The time required for the next step, solving the equations, can vary tremendously. Depending on your package's numerical scheme, the complexity of your models, the density of the mesh, and the computer you're using, solutions can take anywhere from minutes to hours. Some vendors quote typical simulation times on their brochures. For example, Betasoft-pc and Pads Thermal have typical computation times of 2.5 minutes for a board of 100 components running on an IBM PC/AT with a math coprocessor.

Each vendor uses a variety of methods to display the results. Many packages display isotherms, which are lines of constant temperature. Some packages allow you to zoom in to a particular component to determine its junction temperature. You can plot data and also get a simple listing of temperatures (one of the less useful outputs).

You must interpret and analyze the results, and then make the corresponding design changes. Although some CAD system's layout tools can make simple changes based on thermal results, the design engineer is the best person to oversee such layout changes. You wouldn't want the software to arbitrarily move a component based only on temperature considerations when that component also is part of a sensitive signal path.

Obviously, temperatures that exceed a component's maximum ratings necessitate design changes. But marginal temperatures may or may not lead to component failure. In an attempt to quantify the temperature-reliability relationship,

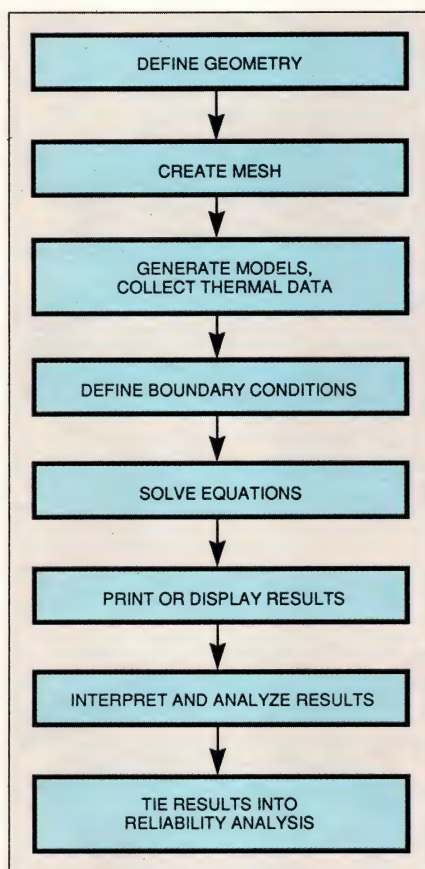

**Fig 3—Some of these basic thermal-analysis steps can occur automatically; others may require additional software or more information from you. The last two steps require you to make decisions about temperature effects and reliability.**





—Fred Molinari, President

## When it comes to high performance data acquisition for the PS/2, we're the only act in town.

A bold claim that happens to be true.

It's our all new DT2901 Analog and Digital I/O Board for the IBM PS/2. We say "all new" because we developed our board from scratch, unlike other developers who have been content to simply modify their "old designs."

So, how does that make our I/O board better?

We built our board around two custom-designed chips. Our data transfer chip permits A/D, D/A and Digital I/O operations to occur simultaneously and

without data gaps. Our custom MCA Interface Chip does the work of several conventional chips, permitting high performance operation while saving valuable space and power.

Add to this its *fast* 50kHz throughput, flexible channel and gain selection, and you've got yourself performance like no other data acquisition board on the market today.

You can get all of this, including our FREE ACQUIRE software.

Think about it, and we think you'll


agree... our *all new* high performance I/O board isn't just the only act in town, it's also the best.

So act now.

**Call (508) 481-3700**

In Canada, call (800) 268-0427

**FREE 1990 Data Acquisition Handbook.**

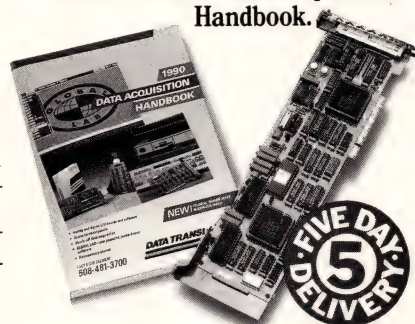

Model	Analog In	Resolution	Programmable Gains	Throughput	Analog Out	Resolution	Throughput	DIO	Pacer Clock
DT2901	16SE/8DI	12 bits	1,2,4,8,16	50kHz	2 chans.	12 bits	50kHz/chan.	16 lines	2
DT2905	16SE/8DI	12 bits	1,2,10,20 100,200, 500,1000	50kHz 2.6kHz	2 chans.	12 bits	50kHz/chan.	16 lines	2

# DATA TRANSLATION®

**World Headquarters:** Data Translation, Inc., 100 Locke Drive, Marlboro, MA 01752-1192 USA, (508) 481-3700 Tlx 951646

**United Kingdom Headquarters:** Data Translation Ltd., The Mulberry Business Park, Wokingham, Berkshire RG11 2QJ U.K. (0734) 793838 Tlx 94011914

**West Germany Headquarters:** Data Translation GmbH, Stuttgarter Strasse 66, 7120 Bietigheim-Bissingen, West Germany 07142-54025

**International Sales Offices:** Australia (2) 662-4255; Belgium (2) 466-8199; Canada (416) 625-1907; China (1) 868-721 x4017; Denmark (42) 274511; Finland (0) 372144; France (1) 69077802; Greece (1) 361-4300; Hong Kong (5) 448963; India (22) 23-1040; Israel (52) 545685; Italy (2) 82470.1; Japan (3) 502-5550, (3) 348-8301, (3) 555-1111; Korea (2) 756-9954; Netherlands (70) 99-6360; New Zealand (64) 9-545313; Norway (2) 53 12 50; Portugal (1) 545313; Singapore (65) 7797621; South Africa (12) 8037680/93; Spain (1) 455-8112; Sweden (8) 761-7820; Switzerland (1) 723-1410; Taiwan (2) 702-0405.

Data Translation is a registered trademark of Data Translation, Inc. All other trademarks and registered trademarks are the property of their respective holders.



# TECHNOLOGY UPDATE

## Thermal-analysis software

Valid's Thermostats and Dynamic Soft Analysis' Betasoft-pc incorporate reliability calculators into their packages. The software uses MIL-HDBK-217 criteria to calculate MTBF. After each analysis run, Thermostats automatically calculates and displays MTBF.

If you believe the military handbook, such reliability calculations can be revealing. For example, the results of a Valid study indicate that a pc board populated with mostly 256k NMOS DRAMs will double in reliability if you reduce the junction temperature from 100 to 90°C. However, the same temperature reduction on a predomi-

nately ECL board improved the reliability by only 22 percent. Also, the results of studies conducted by Dynamic Soft Analysis indicate that the components with the lowest reliabilities are *not* necessarily those with the highest junction temperatures.

Regardless of the unknowns of these relationships, vendors who package reliability and thermal analysis together or provide separate reliability packages linked to thermal analysis are on the right track. Although you may only want to use thermal-analysis software to find a pc board's hot spots, the software can give you much more com-

plete information. Armed with that information, you can design your product with much greater assurance that it will perform as reliably as your customers demand it to.

**EDN**

## References

1. Swager, Anne "Circuit design requires thermal expertise," *EDN*, June 22, 1989, pg 93.

Article Interest Quotient  
(Circle One)

High 515 Medium 516 Low 517

## For more information . . .

For more information on the thermal-analysis software packages discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

**BV Engineering Professional Software**  
2023 Chicago Ave Suite B13  
Riverside, CA 92507  
(714) 781-0252  
Circle No. 700

**CAD Software Inc**  
119 Russell St  
Littleton, MA 01460  
(508) 486-9521  
FAX 508-486-8217  
Circle No. 701

**Compufflo**  
2250 Old Ivy Rd  
Charlottesville, VA 22905  
(804) 977-3569  
Circle No. 702

**Dazix**  
5775 Flatiron Pkwy  
Boulder, CO 80301  
(303) 444-8075  
FAX 303-447-0508  
Circle No. 703

**Dynamic Soft Analysis Inc**  
213 Guyasuta Rd  
Pittsburgh, PA 15215  
(412) 781-3016  
FAX 412-781-3098  
Circle No. 704

**Flomerics Ltd**  
The Kingsgate Business Centre  
12-50 Kingsgate Rd  
Kingston upon Thames  
Surrey KT2 5AA, England  
01-547-3373  
FAX 01-547-2682  
Circle No. 705

**Fluid Dynamics International**  
1600 Orrington Ave  
Evanston, IL 60201  
(312) 491-0200  
FAX 312-869-6495  
Circle No. 706

**HTRD Software**  
Box 909  
Mt Prospect, IL 60056  
(708) 705-8765  
Circle No. 707

**Intergraph Corp**  
One Madison Industrial Park  
Huntsville, AL 35807  
(205) 464-8578  
FAX 205-464-8344  
Circle No. 708

**Management Sciences Inc**  
6022 Constitution Ave NE  
Albuquerque, NM 87110  
(505) 255-8611  
FAX 505-268-6696  
Circle No. 709

**Mentor Graphics Corp**  
1940 Zanker Rd  
San Jose, CA 95112  
(408) 436-1500  
FAX 408-436-1732  
Circle No. 710

**Pacific Numerix**  
1200 Prospect St, Suite 300  
La Jolla, CA 92037  
(619) 587-0500  
FAX 619-459-4081  
Circle No. 711

**Racal-Redac Corp**  
238 Littleton Rd  
Westford, MA 01886  
(508) 692-4900  
Circle No. 712

**Valid Logic Systems**  
Two Omni Way  
Chelmsford, MA 01824  
(508) 256-2300  
FAX 508-250-0087  
Circle No. 713

**Visionics Corp**  
3032 Bunker Hill Lane, Suite 201  
Santa Clara, CA 95054  
(408) 492-1440  
FAX 408-492-1380  
Circle No. 714






## THREE NAMES ARE STACKING UP BIG IN THE BUS BUSINESS.

If you're designing for bus systems, you should know these names: *VIC*, *VAC*, and *ACL*. They're IC building blocks that can drive your system to maximum performance levels.

The VIC068 brings real plug-and-play compatibility to the VME world. It's a complete VMEbus Interface Controller on a single chip. Developed with a consortium of VMEbus International Trade Association (VITA) member firms, it's fast becoming the standard for VME developers, worldwide.

Since it's a single-chip solution, the VIC068 gives VME designers more board space for other features. And, it guarantees compatibility for boards from different suppliers.

The VAC068 is a VMEbus Address Controller, designed as a complementary chip to the VIC. It provides address counters and the necessary hand-shake signals for block transfers. It also provides memory address decoding and, like the VIC chip, is highly programmable. The VIC068 truly raises the level of integration for high-performance systems.

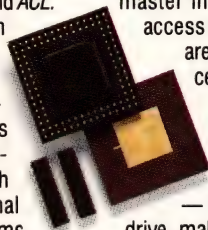

The VIC-VAC architecture provides a complete master interface, with unrestricted memory access to and from the VMEbus. Both chips are packaged in a 144-pin plastic or ceramic PGA.

The VIC and VAC chips drive the bus directly, using the patented output drivers from VTC's ACL (Advanced CMOS Logic) family. Our ACL parts — both FCT and ACT — have up to 64mA drive, making them ideal for *any* high-performance bus system. And, with significantly less ground bounce than competitive products, our FCT gives you better system performance.

VIC, VAC, and ACL are available in commercial grade, or MIL-STD-883C compliant.

And, these three names are just the beginning. There's more to come in the "total VTC bus solution." So, get on board! And start driving *your* system to the maximum.

VTC Incorporated, 2401 East 86th Street, Bloomington, MN 55425 USA. Fax 612/851-5199. Telex 857113. (In Minnesota, please call 612/851-5200.)

**CALL 1-800-VTC-CMOS**




**VTC Incorporated**  
Hard-Driving Bus Solutions.™

See Us at BUSCON WEST, Booth #1001.


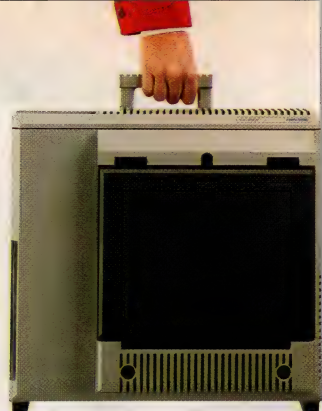
# HIGH-SPEED HARDWARE ANALYSIS MODULES: THE NEWEST PAYOFF TO YOUR PRISM INVESTMENT.




Visualize a logic analyzer that not only acquires microprocessor state and timing data, but adds emulation capabilities... real-time performance analysis... high-speed timing for hardware analysis... and more—all usable in precise, time-correlated combination. All configurable to your needs.

That's the visible edge of the Prism 3000 Series from Tektronix.

## The new dimension of integrated analysis.

<b>MPM/MPX Module</b>	Microprocessor control Real-time performance analysis 200 MHz hardware analysis 8K deep state analysis Multiple Microprocessor support
<b>HSM Module</b>	2 GHz hardware analysis 300 MHz state analysis 1.5 ns glitch capture 12K transitionally-stored memory (up to 120K effective memory)

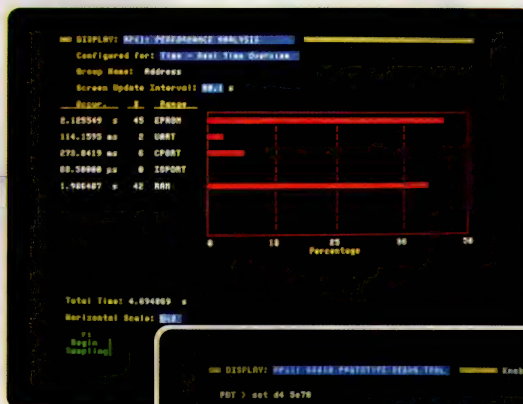Now, just months after introduction, Prism breaks *new* barriers with a module specifically designed for hardware analysis—for detecting glitches, metastability, and the other common problems of state machines, busses, and sequential logic.



Start with up to 96 channels and the exceptional resources of Prism's 8/16/32-bit microprocessor integration modules.

You can view 200 MHz timing and 8K of state data per channel,



(Above, left) Real-time performance analysis as displayed on the Prism color monitor. (Left) The Prototype Debug Tool provides easy access to microprocessor control and debug functions, including the ability to set hardware and software breakpoints, and to patch registers and memory.







(Left) Prism microprocessor and hardware analysis modules are user-installable in minutes. These application modules can be configured in any combination, up to a maximum of ten cards per system.

all time-correlated and integrated on the same display. Set up state and timing sections to cross-

trigger, synchronize and arm each other, so you know exactly when and in what time relationship events occur.

**Push beyond microprocessor observation into microprocessor control.**

With its unprecedented Prototype Debug Tool, Prism lets you easily set breakpoints, patch registers and memory, restart the system—all without an emulator's intrusiveness.

**Use real-time performance analysis to get a true, non-statistical view of system performance.**

Designers of embedded control systems will especially benefit from histograms of uncompromising accuracy.

**Now, with Prism's HSM high-speed hardware analysis module, you can add capabilities like 2 GHz timing and 300 MHz state analysis—and use these tools in tight time-correlation with other Prism modules.**

Detect race conditions, setup and hold time violations, and glitches as small as 1.5 ns. Switch to dual threshold or digitizing modes to get a quick look at intermittent problems like ringing or undershoot.

**Memory constraints are virtually eliminated:** the HSM's 12K of transitionally-stored memory offers the equivalent of as much as 120K of conventional memory!

(Below) The Prism HSM's dual threshold mode triggers on and displays a metastable condition. Middle thresholds are displayed as "M" in the time-correlated state table. Cursors measure the setup time violation that caused the metastable state.



**Choose from a stand-alone Prism, expandable main-frame-and-monitor, even a portable model with fold-up flat panel screen.**

Features like autoloader, split-screen displays, smooth scrolling and on-line help make Prism refreshingly simple to learn and use.

**The clincher?** You can step into this new generation of logic analyzers at prices starting at \$8600.

**Call 1-800-426-2200 for our free video demo and literature packet.** For a hands-on introduction, call your Tek sales engineer soon.



**Tektronix**  
YOUR VISIBLE EDGE


Circle No. 123 for Literature.  
Circle No. 124 for Sales Contact.



**Actual size**

**Actual output**

20 WATTS

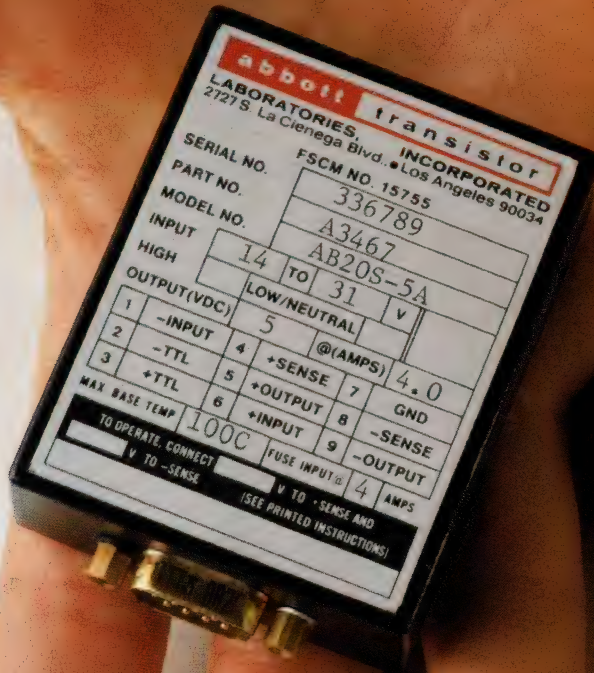

**Actually meets**

MIL-STD-2000  
MIL-STD-810C  
MIL-S-901C  
MIL-STD-461C  
MIL-STD-704D  
NAVMAT GUIDELINES

**Mil/Pac™ high-density military power supplies.**

Introducing NDI DC-to-DC converters that meet an unprecedented combination of military design demands. Plus having the highest power-to-volume ratios of any full-mil qualified products.

Mil/Pacs come in 20W, 35W and 50W configurations, with single (5, 12, 15, 24, 28V) and dual ( $\pm 12V$ ;  $\pm 15V$ ) outputs. They handle a wide 14V to 31V range of input. And

operate at temperature extremes from  $-55^{\circ}\text{C}$  to  $+100^{\circ}\text{C}$ . Mil/Pacs are designed with a field-proven topology that's been verified by rigorous environmental stress screening. They're available with MIL-STD-2000, or without. Either way, the specs are worth reading.

Just write us at 2727 S. La Cienega Bl., Los Angeles, CA 90034. Or call (213) 936-8185.

**abbott**

**WHEN RELIABILITY IS IMPERATIVE.™**



## Integral floating-point unit and caches triple 32-bit $\mu$ P's performance


Marking the processor family's 10th anniversary, the MC68040  $\mu$ P proves that there's plenty of useful life left in "old-fashioned" CISC (complex instruction set computer) architectures. The new 32-bit  $\mu$ P takes advantage of today's million-plus IC transistor budgets to add hardware that triples the chip's performance with respect to its immediate predecessor, the MC68030. Although the company uses a host of optimization techniques to achieve the extra speed, an on-chip floating-point unit (FPU), enlarged cache memories, and additional in-

teger-unit hardware are chiefly responsible for the performance gains.

At a clock rate of 25 MHz, the  $\mu$ P's integral FPU performs 3.5M double-precision flops, executes 8M flops under peak conditions, and retains object-code compatibility with the company's MC68882 floating-point coprocessor IC used with earlier 68000 family members. The FPU's dedicated hardware executes the most commonly used floating-point instructions; more complex instructions such as transcendental functions execute through

microcoded hardware at a rate that still betters the MC68882's speed. A dedicated  $64 \times 8$ -bit hardware multiplier, dual-ported floating-point registers, and register scoreboarding contribute to the FPU's performance.

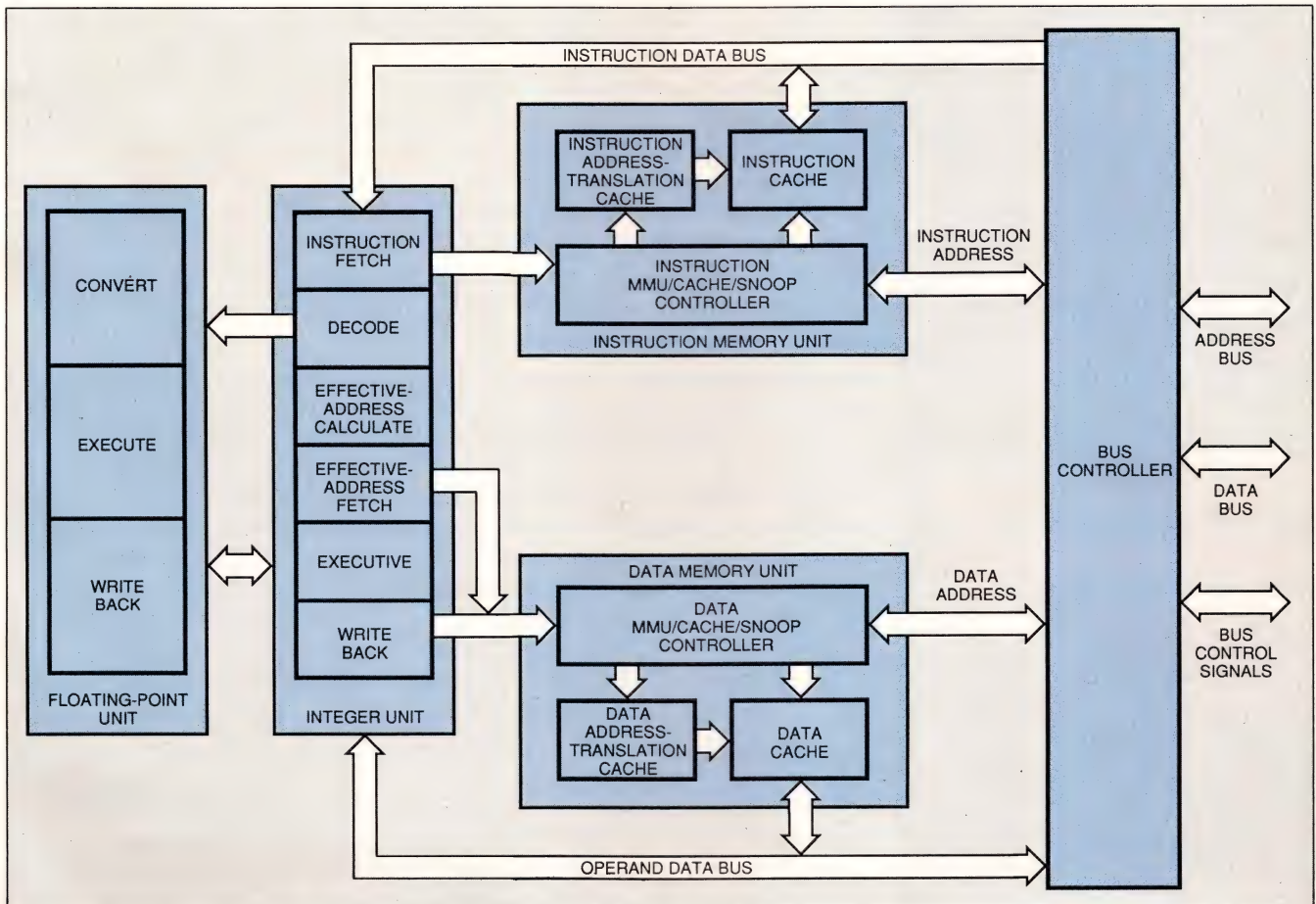To help it optimize the MC68040's integer unit, the company used extensive trace analyses of existing 68000 family code (just as it did with the FPU). The integer unit contains hardware that executes the most commonly used instructions in one clock cycle (thanks to a complex pipeline) so that the hypothetical



*Built with more than 1.2 million transistors, the MC68040  $\mu$ P delivers three times the performance of its immediate predecessor, the MC68030, yet remains object-code compatible with all of its ancestors including the decade-old MC68000.*



# EASY

IOtech includes IEEE 488 device driver software with all of our interfaces. So you'll be up and running fast using our familiar and powerful commands.

We pioneered this easy-to-use device driver technique and we continue to offer the most features and the best performance in the industry.

We also back all of our IEEE 488 products with a 30-day money back guarantee, two-year warranty, and free applications support. So not only are IOtech products easy to use, they're easy to own.

Call us today for your free IEEE 488 Technical Guide: 216-439-4091.

IBM PC, AT, 386, and PS/2 IEEE Products

Macintosh IEEE Products

Sun and DEC Workstation IEEE Products

Serial/IEEE Converters and Controllers

Analog and Digital I/O Converters to IEEE

IEEE Analyzers, Converters, and Extenders

# IOtech

IOtech, Inc. • 25971 Cannon Road  
Cleveland, Ohio 44146  
PHONE 216-439-4091 • FAX 216-439-4093

CIRCLE NO. 40

## PRODUCT UPDATE

"average" instruction executes in 1.3 clock cycles. Therefore, this  $\mu$ P approaches the RISC (reduced instruction set computer) processor's ideal of 1 clock cycle/instruction. The company claims that the integer unit can execute approximately 20 MIPS at a clock rate of 25 MHz.

A separate stage in the integer unit's instruction pipeline calculates effective addresses for operand fetches and has been optimized for the most commonly used addressing modes (again determined by trace analyses). In addition, the instruction-prefetch stage fetches both targets of a branch, thus speeding branch performance while maintaining backwards compatibility with older  $\mu$ Ps in the family and circumventing the need for a delayed-branch scheme. A write-back stage in the integer unit's pipeline schedules operand writes to memory at a lower priority than operand and instruction fetches. This stage helps prevent performance-robbing pipeline stalls.

Separate 4k-byte, 4-way set-associative instruction and data cache memories help to keep the  $\mu$ P's external-bus traffic to an absolute minimum. Each cache has its own paged memory-management unit (MMU), and each cache has its own

64-entry address-translation cache. Dedicated hardware performs address-table searches, thus minimizing the address-translation overhead. The cache MMUs contain snoop circuitry to maintain cache coherency in multiprocessor systems, and the caches support both write-through and copy-back schemes for maintaining cache coherency with external memory. An on-chip bus controller schedules all bus transactions requested by the execution units and the caches, and can perform burst transfers for cache fills and spills.

With all of these hardware features, the company estimates that the MC68040 provides roughly three times the performance of its immediate predecessor, the MC68030. The MC68040 proves that advancing semiconductor technology can enhance the useful life of existing  $\mu$ P architectures by providing substantial performance improvements while retaining compatibility. Samples of the 25-MHz MC68040 cost \$700 to \$800.

—Steven H Leibson

Motorola Inc, Microprocessor Products Group, 6501 Cannon Dr W, Austin, TX 78735. Phone (512) 891-2839.

Circle No. 733

### Coprocessors by any other name

We call Motorola's MC68882 a coprocessor in this article, and we want to be sure that you know precisely what we mean. At EDN, we have decided to adopt and use standard definitions for the terms "coprocessor" and "auxiliary processor." Michael Slater first proposed these terms in his excellent newsletter, the *Microprocessor Report*, published by MicroDesign Resources Inc, 550 California Ave, Suite 320, Palo Alto, CA 94306, (415) 494-2677.

A coprocessor augments a  $\mu$ P's instruction set with special-purpose instructions (such as floating-point, DSP, or graphics instructions) and fetches its instructions from the same instruction stream as its host processor. An auxiliary processor also supplements the capabilities of a  $\mu$ P, but has its own instruction stream, separate from that of its host. Thus, coprocessors are specifically designed to be mated to the bus of a particular  $\mu$ P or  $\mu$ P family, but any  $\mu$ P can serve as an auxiliary processor.



# If you're not interested in second best results...



**Sophia  
systems.**

Universal microprocessor/  
microcontroller emulation systems.

**Just a  
sampling  
of popular  
devices  
covered.**

#### Intel Microprocessors

8086/88/ C86/C88	10 MHz
80186/188/ C186/C188	16 MHz
80286	16 MHz
80386	25 MHz
80386SX/376	16 MHz

#### NEC Microprocessors

V20/30	10 MHz
V40/50	10 MHz
V25	16 MHz
V33	16 MHz
V60	16 MHz



Why use anything but a first-class emulator? When it comes time to prove your design, the tools should be up to the task. And, that's what Sophia emulation systems are about.

Our SA98 is PC based and works with virtually all of the leading 'C' compilers, source level debuggers, and assemblers.

Bus-direct interfacing means code loads fast, and commands execute now. You'll have time to get the most out of your design.

**U.S. Headquarters**  
Sophia Systems  
3337 Kifer Road  
Santa Clara, CA 95051  
Tel: (408) 733-1571  
Fax: (408) 749-8172  
Tlx: 853394

**European Office**  
Sophia Computer Systems, Ltd  
Alpha House  
London Road, Bracknell  
Berkshire RG12 2TJ England  
Tel: 0344-862404  
Fax: 0344-861374

**Corporate Headquarters**  
Sophia Systems Co., Ltd.  
Shinjuku NS Bldg. 8F  
2-4-1 Nishishinjuku  
Shinjuku-ku, Tokyo 163, Japan  
Tel: (03) 348-7000  
Fax: (03) 348-2446

© 1989 Sophia Systems  
Sophia Systems is a registered trademark  
of Sophia Systems Company, Ltd.

**1-800-824-9294**  
OUTSIDE CALIFORNIA

**1-800-824-6706**  
INSIDE CALIFORNIA



## Network interface controller simplifies Ethernet for workstations and bridges

If you're designing LAN bridges or including Ethernet in your workstation design, take a look at the DP83932 network interface controller. Dubbed the SONIC (systems oriented network interface controller), this device can simplify your board design and reduce the network's demands on your CPU.

The DP83932 integrates all of the IEEE-802.3 physical-layer options, including layer network management, into a single device that provides a 10M-bit/sec encoder/decoder, media-access control, and transmit-and-receive FIFO buffers. The device's output stage can drive a 50m cable; all you need add is a pulse transformer to make the device meet the Ethernet AUI (attachment unit interface) standard.

You can connect the device to any 16- or 32-bit  $\mu$ P from Intel, Motorola, or National Semiconductor without additional circuitry. The device offers all necessary data, address, interrupt, and bus-access control I/O signals for the various processors. You use a single control pin to select the proper bus-interface characteristics and to handle byte order correctly during data transfer.

The DP83932 can reduce the demand networking places on your CPU. The device's 32-byte transmit-and-receive FIFO buffers allow it to buffer data while waiting for memory access. By using DMA, the device frees the CPU from handling the data.

When receiving a message, the controller stores status and packet pointers in a description area and the data in a buffer area of system memory. When transmitting, the controller can read and send a series of messages from system mem-



*The DP83932 network interface controller frees your CPU from the tasks of address decoding and data handling. The controller uses DMA to transfer data to and from system memory and features a content-addressable memory that simplifies address decoding.*

ory with a single command. The individual messages need not be contiguous or located at set boundaries.

The DP83932 controller provides the logic for slave access and shared-memory control. The logic permits several devices to share buffer space in your system. By using shared memory, you can pass messages between devices without having the CPU create intermediate copies.

The DP83932 also frees the CPU from the task of address recognition. You can program as many as 16 addresses into the device's content-addressable memory (CAM); a broadcast address is preprogrammed. The CAM will signal if an incoming address has a match

in its list, thus ensuring that the device will handle only those packets it should.

The addresses you program can be physical (single node) or multicast, thus eliminating the need for a hashing algorithm to handle multiple-destination messages. You can also program the device to accept any message, regardless of address.

The DP83932 operates with system clocks from 8 to 20 MHz and can be used in synchronous or asynchronous systems. The device sells for \$55(100).—**Richard A Quinnell**  
National Semiconductor, Box 58090, Santa Clara, CA 95052. Phone (408) 721-5000. TWX 910-339-9240.

**Circle No. 734**



# Engineers Gold.

## When you want to design your life, not just live it.

AND THE ANNUAL FEE IS FREE  
FOR THE FIRST YEAR.

You are first and foremost an innovative planner who shapes, builds and transforms the world. You deserve the credit cards that reflect your own innovative spirit and sophisticated world view. The Engineers Gold Cards® from MBNA®.

MBNA, the number one issuer of the Gold MasterCard®, created these cards for you with features that are extraordinary:

- Worldwide acceptance at over 7 million places.
- Access to cash at over 140,000 locations.
- 24-hour toll-free Customer service 365 days a year.
- Emergency medical and legal assistance when you're travelling away from home.

■ Emergency replacement of cash and airline tickets, based on credit availability.


Request your Engineers

Gold now! The annual fee is free for the first year. Afterwards, it's only \$40 a year for a single card or \$50 a year for both. The APR is just 16.9%. Complete and mail in the application below to:

MBNA, P.O. Box 15464, Wilmington, DE 19885-9440. Or call **1-800-847-7378** toll free. The

Engineers Gold Cards. Because getting the best out of life is what you do best.

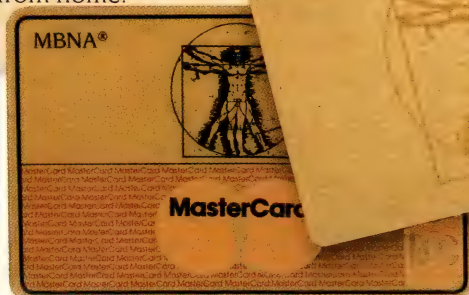Certain restrictions apply to these benefits as outlined in the brochure that accompanies your Access Checks.



**YES!** I wish to apply for the MBNA Gold MasterCard, MBNA VISA Gold or both with a credit line up to \$50,000 and all the other benefits described above. I understand that if I do not qualify for a Gold Card, this constitutes my request for a Silver Card.

(Note: This is not an application for a corporate account.)

- ☐ MBNA Engineers Gold MasterCard® (04:787/16:754)
- ☐ MBNA Engineers VISA Gold® (06:787/17:754)
- ☐ MBNA Engineers Gold MasterCard & VISA Gold (05:788/18:755)

(PLEASE PRINT)

EDN2/1/90 BIIS

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

HOME PHONE ( ) \_\_\_\_\_ BUSINESS PHONE ( ) \_\_\_\_\_

ARE YOU ☐ RENTING ☐ OWN ☐ BUYING MONTHLY PAYMENTS \$ \_\_\_\_\_

SOCIAL SEC. NO. \_\_\_\_\_ DATE OF BIRTH \_\_\_\_\_

NAME OF FIRM \_\_\_\_\_ NATURE OF BUSINESS \_\_\_\_\_

POSITION \_\_\_\_\_ YEARS THERE \_\_\_\_\_

ANNUAL SALARY \$ \_\_\_\_\_ OTHER INCOME \$ \_\_\_\_\_

SOURCE OF OTHER INCOME \_\_\_\_\_

(Alimony, child support, spousal income or separate maintenance income need not be revealed if you do not wish it considered as a basis of repayment.)

MOTHER'S MAIDEN NAME \_\_\_\_\_

(For use when you request special action on your account)

PREVIOUS FIRM \_\_\_\_\_ YEARS THERE \_\_\_\_\_

(If at current firm less than 3 years)

PREVIOUS HOME ADDRESS \_\_\_\_\_

(If at present address less than 3 years)

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CO-APPLICANT NAME \_\_\_\_\_

(Please print)

CREDIT CARD ACCOUNTS

My MasterCard®/VISA® Account # is \_\_\_\_\_

My American Express® Account # is \_\_\_\_\_

I have read the entire application, agree to its terms, and certify the information is correct.

X  
APPLICANT'S SIGNATURE \_\_\_\_\_ DATE \_\_\_\_\_ (SEAL)

I have read this entire application, agree to its terms, and understand that I will be jointly and severally liable for all charges on the account.

X  
CO-APPLICANT'S SIGNATURE \_\_\_\_\_ DATE \_\_\_\_\_ (SEAL)

I (We) authorize MBNA® to investigate any facts, or obtain and exchange reports regarding this application or resulting account with credit reporting agencies and others. Upon request I (We) will be informed of each agency's name and address.

<b>Annual Fees</b> (Fee Waived first year)	\$40 for Gold MasterCard or VISA Gold, \$50 for Combination
<b>Annual Percentage Rate</b>	16.9%
<b>Grace Period For Repayment Of Balances For Purchases</b>	At least 25 Days from statement closing date
<b>Method Of Computing The Balance For Purchases</b>	Average Daily Balance (including new purchases)
<b>Transaction Fee For Cash Advances, And Fees For Paying Late Or Exceeding The Credit Limit</b>	Transaction Fee For Bank and ATM Cash Advances: 2% of each Cash Advance, \$2 Minimum, \$25 Maximum Transaction Fee For Access Check Cash Advances: 1% of each Cash Advance, \$2 Minimum, \$10 Maximum Late Payment Fee: \$15; Over-the-Credit-Limit Fee: \$15

The information about the cost of the card described in this application is accurate as of 6/89. This information may have changed after that date. To find out what may have changed, call us at 1-800-847-7378.


MBNA® is a federally registered service mark of Maryland Bank N.A., an MNC Financial Company.

MasterCard® is a federally registered service mark of MasterCard International, Inc.

VISA® is a federally registered trademark of VISA U.S.A., Inc.



# THE INDUSTRIAL

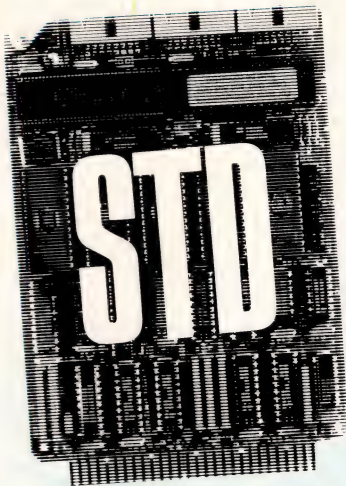

## SOLUTION BUS

From embedded controllers to distributed processing and instrumentation, the STD Bus is the most cost effective industrial bus.

**Why** do so many controller and industrial system designers choose STD Bus solutions?

**Size.** Designed specifically for industrial applications, the small 4.5" X 6.5" cards are easy to package and extremely rugged.

**Performance.** From economical 280s to 286 and 386 systems, the STD Bus lets users choose their performance without sacrificing I/O compatibility or selection.

**Reliability.** Designed from the start with reliability in mind, STD Bus products typically feature an MTBF of 15 to 25 years.

**Selection.** The STD Bus boasts a tremendous variety of CPU, I/O, and specialized board functions.

**Price.** STD Bus industrial solutions come with economy as well. Its price-performance ratio is unbeatable, especially for volume/OEM projects.

**Proof. 312/255-3003.**

Call the STD Bus manufacturers or circle the response number for detailed product information from STD Bus manufacturers.

**STD**  
The Cost Effective  
Industrial Computer

## PRODUCT UPDATE

### Not-dead-yet CISC workstations fight back

Workstation vendors are engaged in a fierce battle for desktops. The Series 9000 Models 345 and 375 are the latest flurry of punches. Both machines derive their CPU power from a 50-MHz 68030 and a 40-MHz 68882. In addition, you can bulk up the Model 375 with the 68040 through a board upgrade when the new CPU becomes available.

The Model 345 provides 12 MIPS starting at \$9000. The system features an optional, 200M-byte SCSI hard disk (\$3250). The hard disk comes with the HP-UX operating system and a graphical user interface based on OSF/Motif; both the OS and the interface are preinstalled to allow you to boot the system into a common, user-friendly environment.

To minimize the likelihood of system crashes due to memory parity errors, the system uses ECC (error correction code) RAM. You can configure the Model 345 with 4M to 16M bytes. This low-end system features the HP-HIL (HP's input interface), RS-232C, HP-IB (IEEE 488), Centronics, and IEEE 802.3/

Ethernet LAN with thinLAN and AUI (attachment unit interface) as standard interfaces. You can optionally add a SCSI.


The Model 375 is a 12-MIPS machine that you'll be able to upgrade with a 25-MHz 68040 for \$2000 in the second half of 1990. The memory in the Model 375 is also ECC memory; you can configure your system with 8M to 32M bytes of RAM. Later this year, when 4M-bit dynamic RAMs are available, you'll be able to run with 128M bytes of main memory. Unlike the Model 345, the 375 is expandable with 12 I/O slots. Starting at \$21,995, the 375 features interfaces equivalent to the 345.

The announcement of the workstations provides HP/UX users with evidence that, contrary to earlier reports, the vendor isn't abandoning the operating system.

—**Michael C Markowitz**

Hewlett Packard Co, 19310 Pruneridge Ave, Cupertino, CA 95014. Phone (800) 752-0900.

Circle No. 735

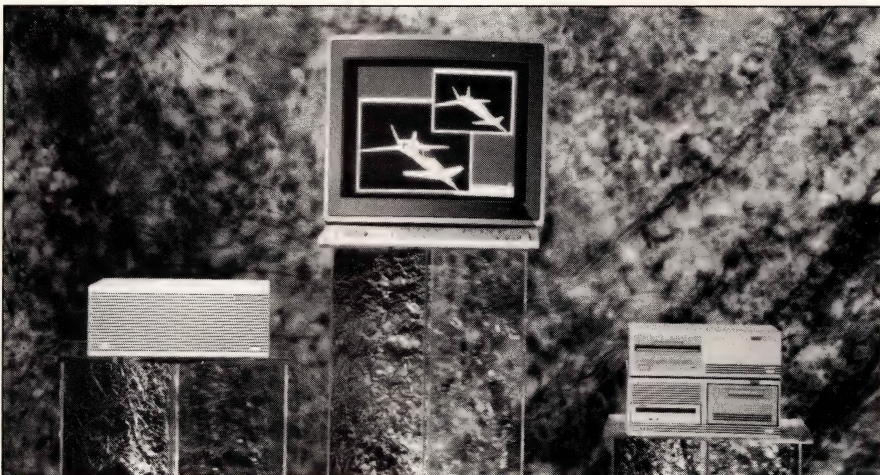

Compatible with previous operating systems, the Series 9000 Models 345 and 375 also provide a path toward the next-generation CPU.



TEXAS INSTRUMENTS

A PERSPECTIVE ON DESIGN ISSUES:

# Beyond VGA



IN THE ERA OF  
**MegaChip**  
TECHNOLOGIES





# TIGA-340 from Texas Instruments

## The open graphics interface standard a clear path for your future.

A ground swell of support is rallying behind TIGA-340™, the Texas Instruments Graphics Architecture. It and TI's TMS340 family are poised to become the next standard beyond VGA as PC users demand higher performance and resolution.




### The PC graphics standard anyone can use

TIGA™ is a high-performance software interface that optimizes communications between industry-standard 340 family processors and the PC host processor.

With TIGA, hardware and software specifications for a PC graphics standard are open and available from inception — one of the reasons why more than 100 companies have already made plans to evaluate TIGA-compatible hardware and software products.
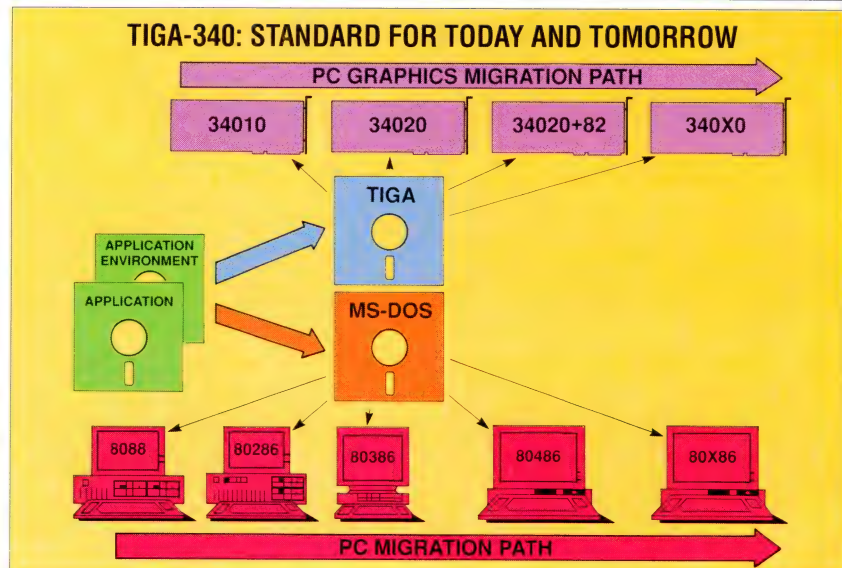
### Lowest cost, highest performance

TIGA's move into the mainstream is being fueled by the price of TMS34010-based boards falling to well below \$1,000. In fact, TI's 34010 processor is the most economical way to implement high-performance 1024 x 768 resolution PC graphics boards. The faster



Just as MS-DOS® allows applications to run on any MS-DOS PC using 80X86 processors, TIGA allows graphics applications to run on any TIGA display system using a 340X0 processor.

speed and greater throughput of the second-generation 34020 result in even higher performance boards.

### Clear migration path

TIGA provides a common platform upon which graphics applications can take advantage of the processing power of the TMS340 family.




Software developers no longer have to rewrite code in order to migrate to higher performance hardware. Software applications

that run through TIGA on the 34010 processor run on the upward-compatible 34020 as well as on future 340 family members.

Hardware developers benefit from wide software support, reduced system development time and costs, and easy differentiation of products.

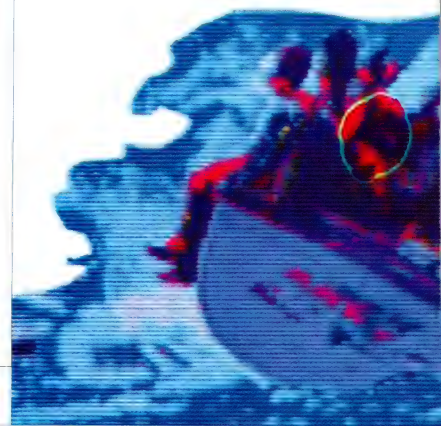At present, TIGA supports DOS-based PCs, with UNIX™ and OS/2 forthcoming.





# Instruments: that defines


## Applications portability

TIGA allows an application to be ported to a wide variety of 340-based graphics systems with a single software driver. Applications will run without modification regardless of resolution, color content, or specific 340 family processor.

For example, the Microsoft® Windows driver, which is part of the TIGA Software Porting Kit (see next page), allows Windows to run without any change on boards having resolutions from 640 x 480 to 4096 x 4096 and color content from monochrome to 256 colors or more.
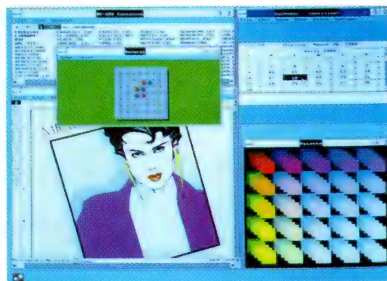
## Speeds time to market

Now hundreds of popular applications can be made available for your new graphics product almost instantly using TIGA and Microsoft Windows. Porting TIGA to a 340-based board typically takes less than one man-week of effort.




More than 150 OEMs have made the TMS340 graphics family their own. That wide acceptance, coupled with open architecture and a defined migration path, makes the future for TIGA-340 and the TMS340 family rich and promising.


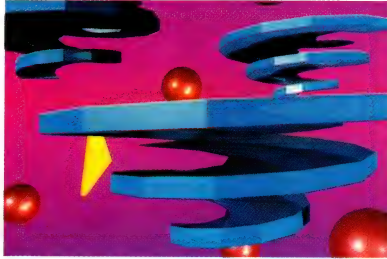
## TI's leadership TMS340 graphics family

No other supplier comes close to TI in the range of cost/performance options for the development of integrated graphics solutions. The widely used TMS34010 processor and other family members are now



being joined by a group of new-generation products that will bring the higher levels of workstation performance to PCs.

Chief among these is the TMS34020, a programmable, 32-bit processor up to 20 times faster than the 34010.


For use with the 34020, the TMS34082 will perform floating-point operations up to 100 times faster than current PC coprocessors. It is the industry's first graphics floating-point coprocessor.

The family's video RAMs, invented by TI, have been augmented by the TMS44C251 1-megabit VRAM. It was designed in conjunction with the 34020 for the high system bandwidths demanded by today's mid- and high-resolution graphics systems.

## TIGA-340 DEVELOPMENT KITS

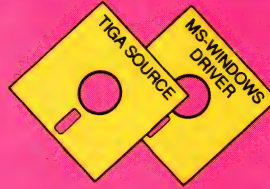
### TMS340SPK-PC SOFTWARE PORTING KIT

is for use by hardware developers to port the TIGA interface to any TMS340-based system.



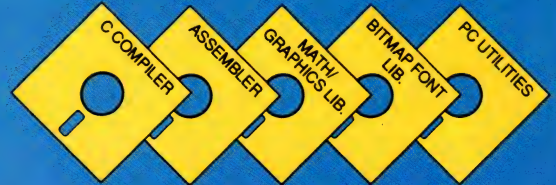
### TMS340SDK-PC SOFTWARE DEVELOPER'S KIT

is designed for those who want to develop direct 34010 code or downloadable extensions to TIGA.


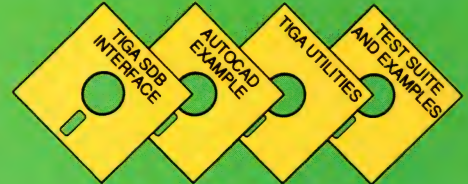
### TMS340DDK-PC DRIVER DEVELOPER'S KIT

allows software developers to make existing software applications run on TIGA-compatible 340-based systems or develop new applications.



## Free user's guide

For more information about the TIGA-340 standard, get your free copy of the *TIGA-340 Interface User's Guide* and the *TIGA-340 Interface Brochure*.

Call 1-800-336-5236, ext. 3526, or write Texas Instruments Incorporated, P.O. Box 809066, Dallas, Texas 75380-9066.

**In Europe** call 44-234-223000, fax 44-234-223459, or write Customer Response Centre, MS 09, Texas Instruments Limited, Manton Lane, Bedford MK41

7PA, England. **In Japan** call 81-3-769-8700, fax 81-3-457-6777, or write Texas Instruments

Japan Limited, MS Shibaura Building 9F, 4-13-23 Shibaura, Minato-Ku, Tokyo 108, Japan. **In Hong Kong**

call 852-735-1223, fax 852-735-4954, or write Texas Instruments Hong Kong Limited, Market Communications Manager, 8th Floor World Shipping Centre, 7 Canton Road, Kowloon, Hong Kong.

TIGA-340, TIGA, and MegaChip are trademarks of Texas Instruments Incorporated. UNIX is a trademark of AT&T Bell Laboratories, Inc. ® Microsoft and MS-DOS are registered trademarks of Microsoft Corporation.

© 1990 TI

08-9254B



**TEXAS  
INSTRUMENTS**





# Power at your command

## Military DC/DC Converters +5, +12, $\pm 12$ , +15, $\pm 15$ V Single and dual output


*AHE Series DC/DC converters from Advanced Analog have the power and reliability needed for military and aerospace systems.*

- -55°C to +125°C and -55°C to +85°C temperature range
- Screened to MIL-STD-883C, Method 5008 in a MIL-STD-1772 certified facility
- 15W and 20W output power
- Hermetically sealed
- Advanced feedback method uses no optocouplers for high reliability and greater radiation tolerance

Now you can get the higher temperature range your system requires. And improved performance. Advanced Analog's AHE Series are built for rugged environments and guaranteed to outperform any other standard DC/DC converter of this type. Other standard Mxx Series converter models are available.

*We've got the experience.* Our PS Series triple-output, 80W converter is serving in the newest attack helicopter.

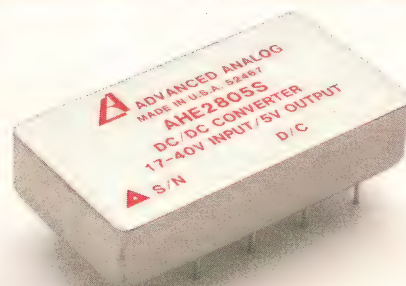Need a special converter or power hybrid? Call us and we'll work with your team to get the best solution for your needs.



### DC/DC Converters

	Output Power	Output Voltage (V) Current (A)
AHE2805S	15	5V, 0 - 3A
AHE2812S	20	12V, 0 - 1.67A
AHE2812D	15	$\pm 12$ V, 0 - 625mA
AHE2815S	20	15V, 0 - 1.33A
AHE2815D	15	$\pm 15$ V, 0 - 500mA

-55°C to +85°C and -55°C to +125°C  
Input voltage range is 17 - 40V

**MIL-STD-1772  
Qualified**



**Advanced Analog**  
a division of Intech


2270 Martin Avenue  
Santa Clara, CA 95050  
(408) 988-4930



# SONY TAKING COMMITMENT TO
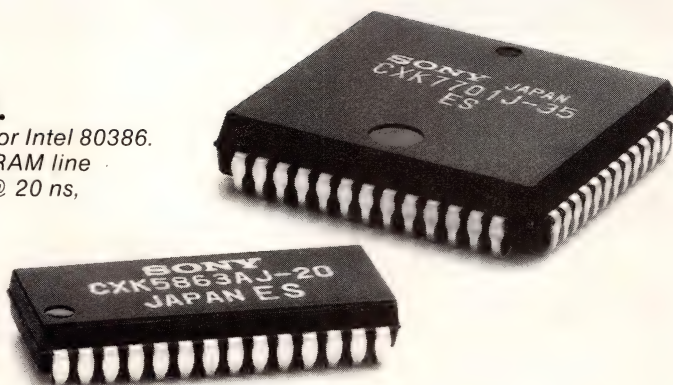
## FAST CACHE.

Cache memory for Intel 80386.  
Also standard SRAM line  
down to 8K x 8 @ 20 ns,  
16K x 4 @ 15 ns.



What you see here is a demonstration of Sony's intense commitment to your each and every SRAM need.

A commitment made even more impressive by the fact Sony's only been engineering and producing SRAMs for just over five years.

And when you consider we're pouring all our resources into SRAM technology—including a new production facility in Nagasaki, Japan—this demonstration merely hints at the Sony SRAM technology yet to come.

## Ultra-high speed cache.

Via a unique 0.8-micron process, Sony covers your fast processor cache-memory needs two distinct ways.

First, there's our Model CXK7701J, designed specifically for the Intel 80386.

This application-specific memory (ASM) combines address

latch, memory and transceiver within one IC. Ready for user

configuration as either an 8k x 16-bit memory or as two 4k x 16-bit memories.

Second, consider our new ultra-high speed SRAM capabilities.

As you scan the chart above, keep in mind even higher speeds will be available soon.


ULTRA-HIGH SPEED CACHE SRAMS			
MODEL	CONFIG.	SPEED (ns)	PACKAGE
CXK7701J*	8K x 16	30/35/45/55	PLCC
CXK5863AP	8K x 8	20/25/35	DIP 300 mil
CXK5863AJ	8K x 8	20/25/35	SOJ 300 mil
CXK5466P	16K x 4	15/20	DIP 300 mil
CXK5466J	16K x 4	15/20	SOJ 300 mil
CXK5467P**	16K x 4	15/20	DIP 300 mil
CXK5467J**	16K x 4	15/20	SOJ 300 mil

\*For Intel 80386.

\*\*0/E



# SITS SRAM THE EXTREMES.

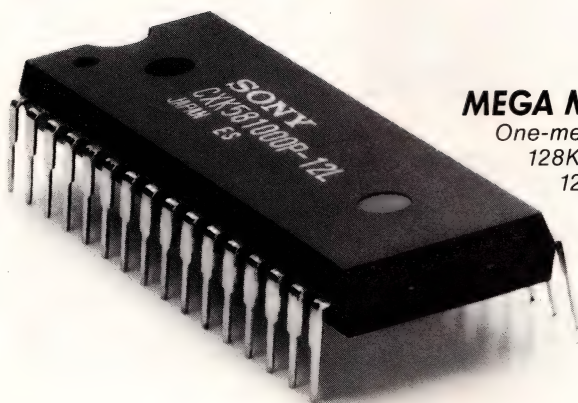

## MEGA MEMORY.

One-meg SRAM line includes  
128K x 8 @ 100/120/150 ns,  
128K x 8 @ 70/85 ns,  
128K x 8 @ 35/45/55 ns.

### Ultra-high density.

Sony solves your board-space problems with three new 1-Mbit SRAMs.

Each is based on our 0.8-micron CMOS technology. Configured as 128K x 8 bits. And available in 32-pin DIP and

surface-mount plastic packages.

And not only do Sony 1-Mbit SRAMs maximize board space, but process speeds as well.

Nowhere else will you find a greater choice: 100/120/150-ns, 70/85-ns and 35/45/55-ns speed figures.

HIGH-DENSITY SRAMS			
MODEL	CONFIG.	SPEED (ns)	PACKAGE
CXK581000P	128K x 8	100/120/150	DIP 600 mil
CXK581000M	128K x 8	100/120/150	SOP 525 mil
CXK581001P	128K x 8	70/85	DIP 600 mil
CXK581001M	128K x 8	70/85	SOP 525 mil
CXK581020SP	128K x 8	35/45/55	DIP 400 mil
CXK581020J	128K x 8	35/45/55	SOJ 400 mil

### Sony SRAMS cover the performance spectrum.

Sony offers well over one hundred SRAM

solutions, covering the entire performance spectrum.

All competitively priced, all shipping now.

So call Sony with your most demanding SRAM spec.

We'll go to the extremes to deliver.

For complete details, call Sony at (714) 229-4190 today. Or write Sony Corporation of America, Component Products Company, 10833 Valley View Street, Cypress, California 90630, Attention: Semiconductor sales. FAX (714) 229-4285.

## SONY®

Sony is a trademark of Sony Corporation. Intel is a trademark of Intel Corporation.




# Top 40 programming. Now



*Mechanical computer-aided engineering*



*Computer-aided imaging and animation*

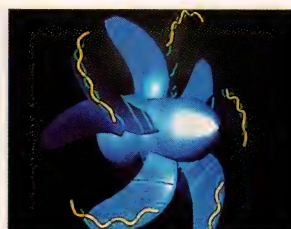


*Computational fluid dynamics*




*Video animation production*




*Video animation*

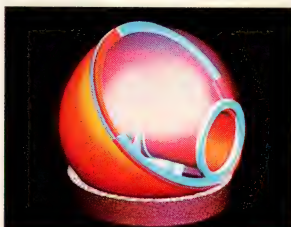

*Computer-aided engineering*

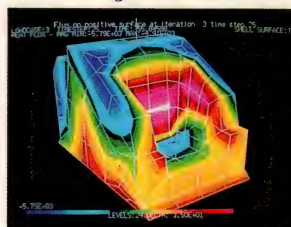

*Finite element modeling and analysis*

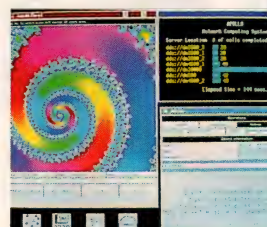


*Network computing and mathematics*



*Computer-aided engineering*




*Aerospace engineering*

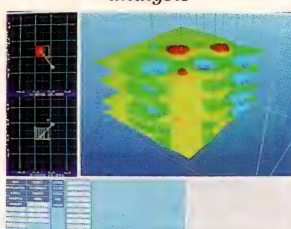


*Seismic analysis*



*Computer-aided design in manufacturing*

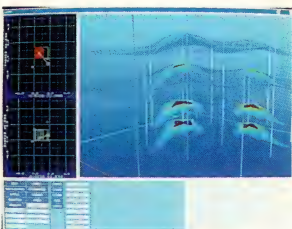

*Reservoir analysis*

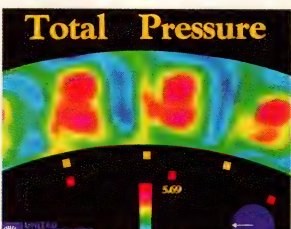

*Computational fluid dynamics*




*Industrial design*




*Computer-aided engineering*



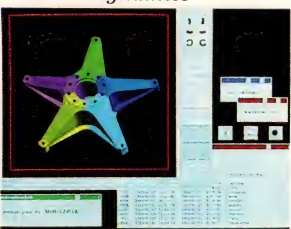*Computer-aided engineering and industrial design*




*Mechanical computer-aided engineering*

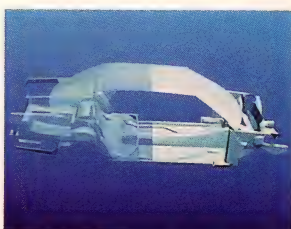


*Automotive industrial design*



*Animation*

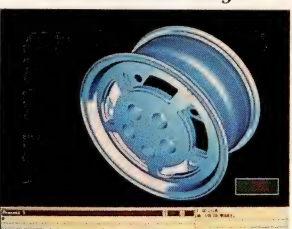


*Mechanical design*

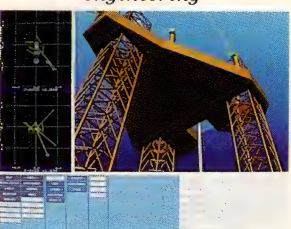

*Scientific visualization*



*Aerospace engineering*

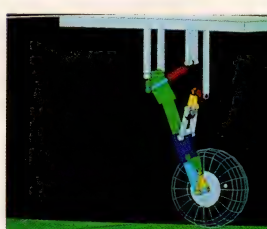


*Kinematics and dynamics*


© 1989 Hewlett-Packard Company. UNIX is a registered trademark of AT&T in the U.S. and other countries. CPWG914



# available for any network.

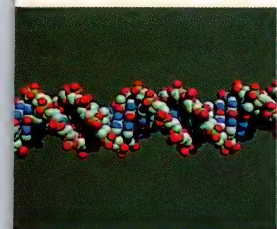

Computer-aided molecular design

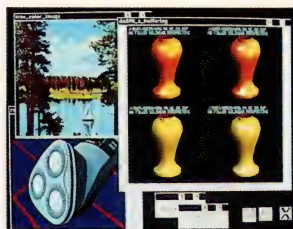


Multi-window industrial design




Computer-aided engineering and design




Industrial design

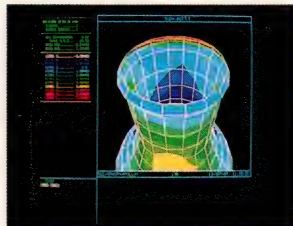

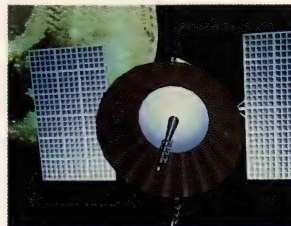Structural analysis using finite element analysis



Aerospace engineering

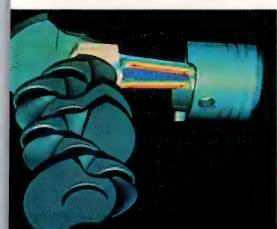


Computer-aided engineering




Automotive engineering



Computational fluid dynamics

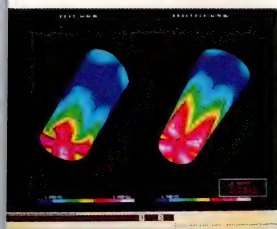

Thermal analysis

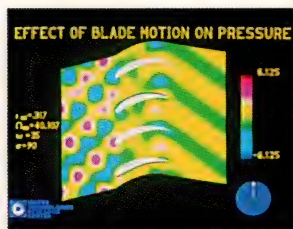

Computational fluid dynamics



Industrial design




Industrial design




Computer-aided engineering




Computer-aided engineering

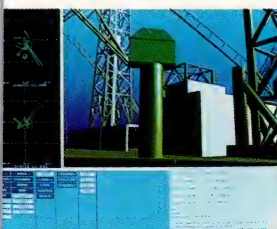

Scientific visualization

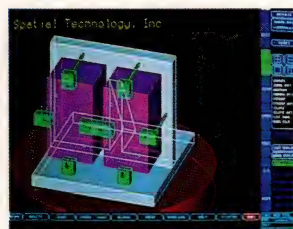

Computer-aided design

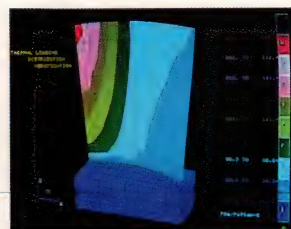

Finite element analysis

## Apollo's Series 10000 now brings supercomputer performance to the desktop.

Your project team can't share its work. Your current system lacks the horsepower for timely solutions. And you can't afford a supercomputer for your network.

Hewlett-Packard has a better way.

It's the Apollo Series 10000. Mini supercomputer performance that can dramatically increase the power of any network. At a fraction of the cost of a supercomputer.

Inside, the remarkable Series 10000 supports up to four amazingly fast processors. Each with its own integer unit, dual floating-point processors, and large cache memory. Which quickly deliver high-resolution, colorful 3D graphics. All of which makes the Series 10000 ideal for analysis, modeling, or imaging.

Even better, the Series 10000 offers the flexibility to attack more than 100 of the leading engineering and design application areas. All, of course, in an industry-standard UNIX® environment that can be linked to a wide variety of networks—including IBM token ring and Ethernet.

The best part is that Apollo's reliable and innovative engineering is now backed by Hewlett-Packard's exceptional worldwide service and support network.


If you'd like more information on how the Series 10000 can help your project team solve its problems better and faster, call 1-800-323-1846 (in MA, call 1-800-847-1011).




The Series 10000

There is a better way.

# apollo

A subsidiary of  
 **HEWLETT  
PACKARD**



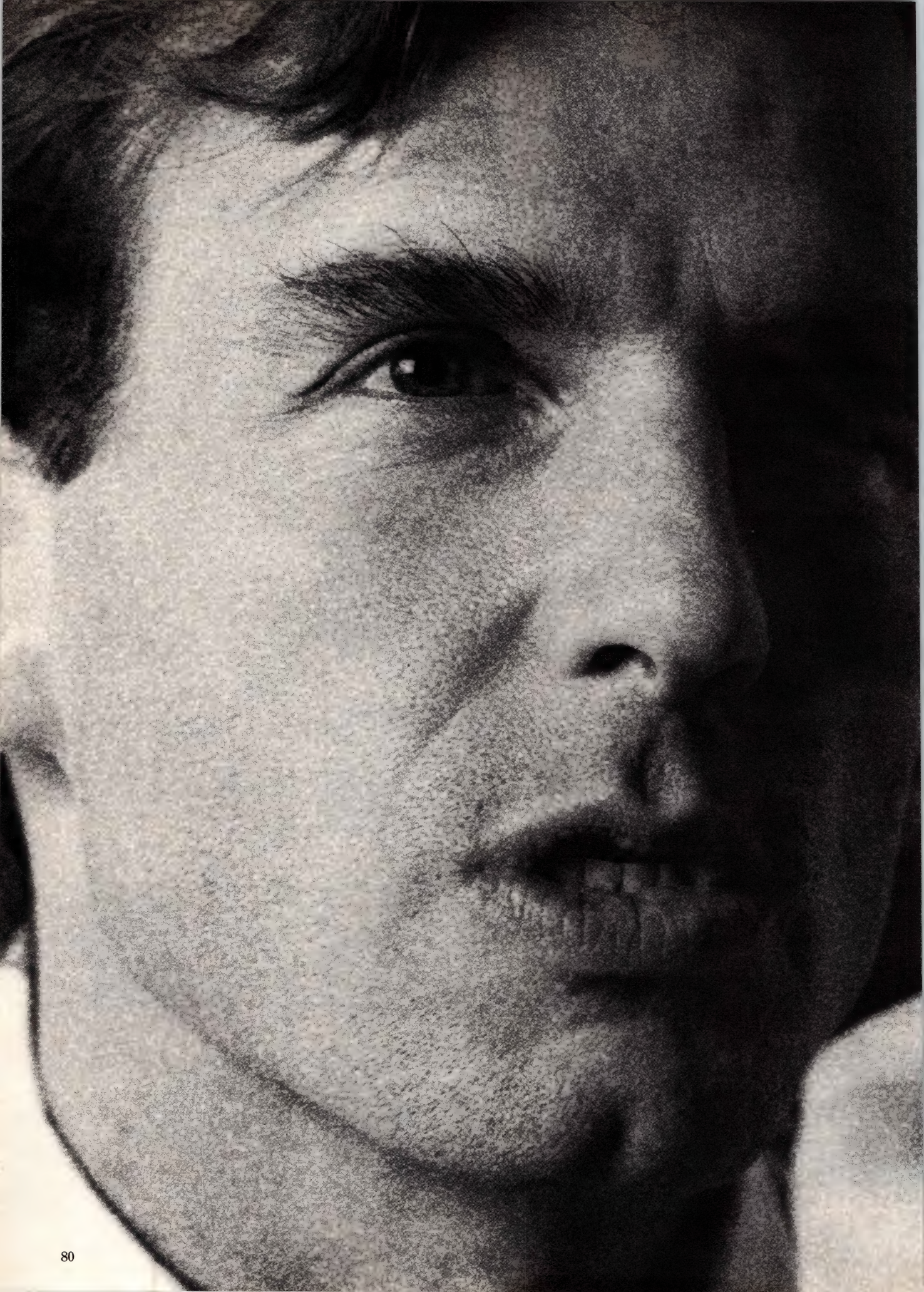



You know how it is. Time's running out. But the company's counting on him to add ISDN compatibility to his T-1 system, and give it all the bells & whistles that mean flexibility, expandability and, above all, total ISDN connectivity.

"Four other guys had worked on this ISDN project. For me, it was do or die time."

He knows Rockwell International's reputation in digital network products with the T-1/PCM-30 R8070 device, the market leader. It's worth a call.

He meets with Rockwell's marketing/engineering team. They quickly understand his ISDN needs and suggest their ISDN Primary Rate solution: R8069, R8070 and R8071/DMI devices. In fact, it looks like this highly integrated system solution can simplify the design from every standpoint he can think of, and deliver performance, quality and cost-savings.

It's the stuff a good night's sleep is made of.

Call the leader in T-1 for innovative ISDN products. Rockwell *is* solutions.



**Rockwell International**


... where science gets down to business

Aerospace / Electronics / Automotive  
General Industries / A-B Industrial Automation

Semiconductor Products Division,  
Rockwell International,  
P.O. Box C, M.S. 501-300, Newport Beach,  
CA 92658-8902 (800) 854-8099.  
In California, (800) 422-4230.

CIRCLE NO. 46



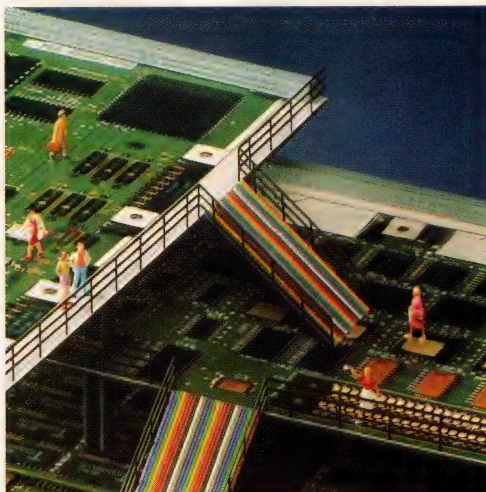

# Add-on BUSES

Jon Titus, *Editor*

*Add-on buses let you attach small I/O boards to your computer at low cost. However, these devices aren't without controversies, which revolve around technical issues, standards, and just how open the architectures of many add-on buses really are.*

**W**hen you think of computer buses, VMEbus, Multibus, and the IBM PC/AT bus probably come to mind first. However, there are many other add-on buses that let you take a basic computer board and expand its use—usually at low cost. The popularity of these add-on buses stems from the need to add special functions to a computer system without occupying an extra slot or without adding expensive and special-purpose boards. Before you look at a specific bus, however, consider the ramifications of adopting a bus that may be supported—at least for now—by only one or two manufacturers.


In defense of add-on buses, Vic Serbe, an applications engineer at Central Data Corp, says that modular I/O connections and boards will always be popular. People want to plug in their boards, write their driver routines, and get the system up and running as quickly as possible, he says.

But not everyone thinks that the add-on boards are a panacea for I/O bottlenecks. Fred Rehhausser, director of strategic marketing at Force Computers (Campbell, CA), believes that gate arrays and ASICs can make board design easier. By adopting such VLSI chips, computer-board manufacturers have more room on their CPU boards for the functions that people need.

Laurent Meilleur, VMEbus product manager at Matrix, doesn't like add-on boards for simple devices such as A/D and D/A converters. He thinks that designers who need such functions should seek boards that connect right to the main bus and that offer those functions. "Overall," he says, "using add-on daughter boards can be more expensive than taking a single-board-computer approach. Some of those daughter boards are expensive!"

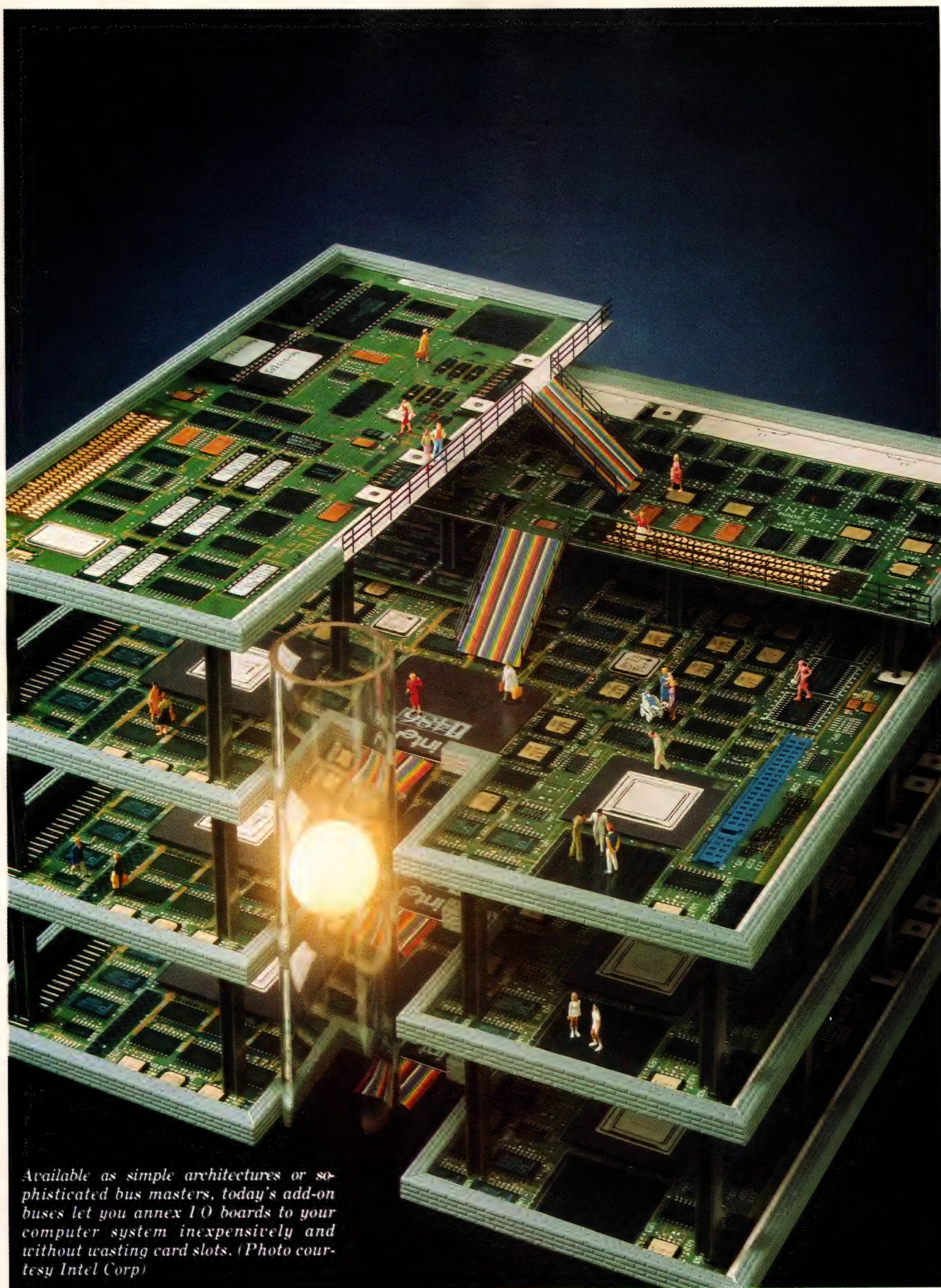Another bus-related topic that comes up frequently is standards. Engineers often wish for standards that





Available as simple architectures or sophisticated bus masters, today's add-on buses let you annex I/O boards to your computer system inexpensively and without wasting card slots. (Photo courtesy Intel Corp)



*Add-on buses offer great flexibility, but you must be willing to deal with only a few suppliers. Some manufacturers offer very few boards.*


would unite the add-on-bus field behind only a few standard buses. However, the issue comes down to standard buses *vs* flexibility for designers. According to Rehhausser, "The add-on buses are an attempt by small companies to defeat standards and to lock in customers. Such manufacturers can get into the market by selling an inexpensive board and forcing customers to buy add-on boards later."

### Markets set standards

"In most cases, the market should set the standards. It's OK for standards to apply to the computer backplanes, but let's put our creativity into the add-on-bus products," says Del Miller, General Micro Systems' vice president of sales and marketing. He adds, "Anyway, why would anyone want to put a Brand-A add-on board onto a Brand-B CPU board? At the add-on-bus level, standards may be an answer to a question that no one is asking."

Kim Rubin of Greenspring puts standards in another light. "You may have a system that doesn't fit a standard—it's not a VMEbus-based system. Maybe it's one board running a piece of equipment, say an automated cash register. You shouldn't have to force someone to use a standard bus. Let them add one small board that customizes the unit to meet the customer's needs."

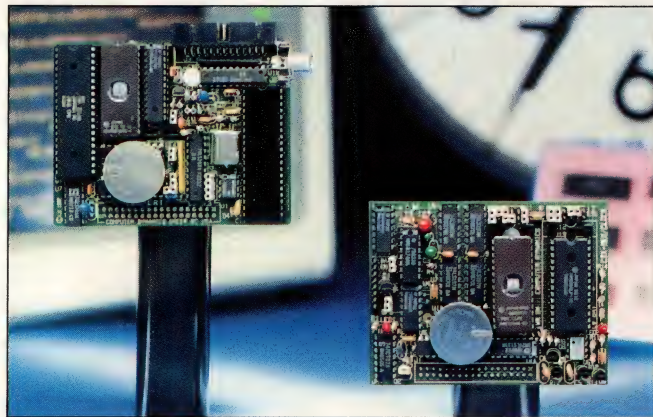Rehhausser says that standard buses are available and that designers and users of VMEbus products should take a careful look at the VMEbus's existing VSB (VME Subsystem Bus), which expands a CPU board's capabilities. He says that communication



**Typical SBX boards** are small, but they can still hold a lot of circuitry. The board on the left is a video controller, and the one on the right is a real-time clock that can accommodate as many as 128k bytes of memory. Because of the SBX bus's limited addressing capability, the clock chip sequences through memory addresses for block-transfer operations.


boards now plug into the VSB and that SCSI-controller boards aren't far from market. Rehhausser stresses that the VSB is a standard now. In fact, Motorola, Radstone, and Ironics all offer VSB boards.

We'll assume that after considering the arguments above, you're still interested in learning more about add-on buses. To give you a better idea of what the add-on-bus world encompasses, we'll examine seven buses, from the simplest to the latest introduction. Our representative sample, including the products in **Table 1**, gives you an idea of what you have to choose from. In some cases, however, your choice may be limited to the products available from only one manufacturer.
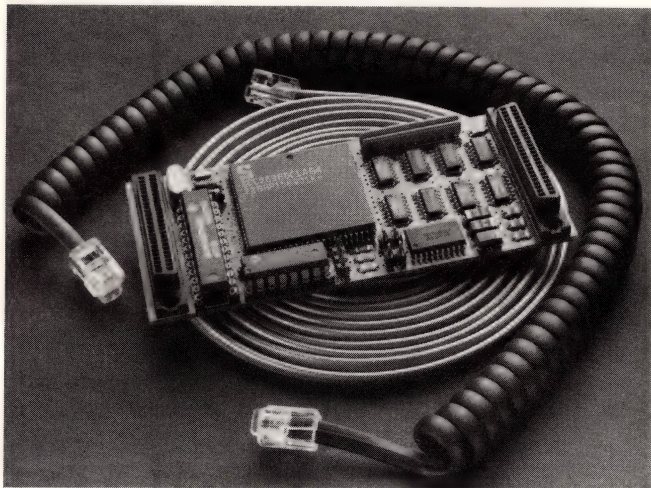
### Start with the SBX

Perhaps the earliest add-on bus arose from Intel's popular Multibus (now Multibus I, or IEEE-796) in the late seventies. Within the Multibus specification, the iSBX (Intel System Bus Extension, or just SBX bus, as it's popularly known), provides a way of adding small I/O boards to a main processor board, or base-board. Many processor boards let you add as many as three SBX boards. If you need to add more SBX boards to a Multibus I system, the CD21/6600 SBX Motherboard (\$710) from Central Data supplies six independent SBX connectors on one Multibus I card. (Unless noted otherwise, all prices are for unit quantity.)

In general, the SBX boards supply a variety of functions and interface circuits for serial communications



**Eight serial ports** are available on Greenspring Computers' IndustryPack add-on board. Two holes on each connector let you use machine screws to fasten the unit to a baseboard.



or for digital and analog I/O. Most SBX manufacturers supply interface circuits on single-wide boards that measure  $2.85 \times 3.70$  in. Manufacturers may also supply double-wide SBX boards that measure  $2.85 \times 7.5$  in. Typical of dual-wide SBX boards is the LSBX Serial/4 board (\$325 (100)) from Computer Modules, which lets you control four serial I/O ports. Keep in mind, though, that the longer boards can hang over the sides of the main board depending upon which SBX connector you plug them into.

Often you have a choice of 8- or 16-bit SBX boards. The 8-bit boards will operate in 8- or 16-bit systems, but you can't adapt 16-bit SBX boards to operate with 8-bit computer boards. The Multibus specification allows two connectors—an 8-bit 36-pin connector and a 16-bit 44-pin connector. A 36-pin SBX-board connector can mate with a 44-pin connector on a baseboard.

#### Boards furnish inexpensive I/O

According to Vic Serbe at Central Data, the SBX is a success because it provides an inexpensive way to get I/O into your computer. However, Serbe cautions that some of the newer buses may avoid incorporating simple add-on buses such as the SBX. Because the SBX provides only a rudimentary bus for I/O devices, SBX boards can't provide much 'intelligence.' As a result, the add-on boards can actually decrease the performance of the system by wasting the CPU's

time. For example, a serial I/O board typically requests service after it sends or receives each byte. In a VMEbus- or Multibus II-based computer, developers must avoid tying up the CPU with such trivial tasks.

SBX boards still have a healthy future. Although each SBX board offers only one or two functions, SBX boards remain popular, and the market is still growing as manufacturers upgrade and expand equipment that relies on Multibus I computers and boards.

Steve Cooper, director of marketing at Radix, notes that although many SBX boards rely on DMA operations to transfer data quickly to and from memory, not all of the baseboards support DMA operations. Thus, if you want to use an SBX board that requires DMA operations, check the baseboard's specs before you design.

Generally, SBX boards cost from more than \$100 to more than \$500. Typical examples of SBX boards include a counter-timer and parallel I/O board from Computer Dynamics (CDX-CTC/PIO, \$300) and an SCSI interface board from Single Board Solutions (SBSx SCSI/CEN, \$195).

In addition to working with Multibus I computers, the SBX offers a way to expand the STD Bus—a bus already known for a wide variety of low-cost I/O boards. One of Ziatech's 80188-based CPU boards for the STD Bus incorporates an SBX connector and interface. Phil Nash, Ziatech's marketing-communications



*Boards for the Dbus-68 fit on either a 6U VMEbus board (left) or a 3U VMEbus board (right). You can choose from a variety of peripheral-control and general-purpose I/O boards for the bus.*



*Today's add-on buses range from simple I/O controllers to sophisticated master/slave control units, but don't buy more flexibility than you need.*

---

manager, says, "Even if the added height of the SBX board means leaving an open slot in the card cage, STD Bus slots are cheap." Nash says that Ziatech will continue to offer SBX connections on new products as the need arises, but they won't be offered on high-end products—on an 80386-based computer, for example.

If the idea of adapting SBX boards to the STD Bus appeals to you, you may want to consider Inovec's STD/SBX card (\$210), which accepts two single-wide SBX boards and occupies one STD Bus slot. The company also supplies several SBX boards.

Kim Rubin, the vice president of engineering at Greenspring Computers, says that Greenspring considered using SBX boards, but the resulting assembly can't fit into one card slot when mated with a VMEbus or Multibus II card. "A wasted card slot in VMEbus or Multibus II systems costs you 5% of a 20-slot enclosure," says Rubin, and he cautions, "Not all SBX boards work in all SBX connectors."

#### **Watch for undefined signals**

Indeed, the SBX specification does show two undefined Option signals that users can connect for their own needs. The specification also describes two Reserved signals that may be defined in the future. The improper use of those signals can lead to confusion, but boards built to the defined signals should operate according to the IEEE-796 specification (Ref 1). However, the specification (Rev 0.6) for Greenspring's IndustryPack boards also lists two Special Function pins

that aren't well defined.

Nevertheless, Rubin claims that his company's interface design is independent of any specific bus or CPU. He backs that claim by pointing to the VIPC310 (\$410), a VMEbus 3U carrier that holds two IndustryPack boards, and to the SupportBoard 1270 (\$295), which puts two IndustryPack boards on the Apple Macintosh's NuBus. The company also sells a VMEbus 6U carrier that holds four IndustryPack boards. Typical IndustryPack boards range from \$240 to \$520 each. Most of the boards are single-wide units, but the carriers also accommodate dual-wide boards that take two single-wide positions.


Unlike some add-on buses, the IndustryPack architecture requires an onboard identification (ID) PROM that may hold as many as 64 16-bit words. The PROM contains a manufacturer ID number, details about the board, and perhaps I/O configuration data. Greenspring furnishes each manufacturer with a free ID number. The PROM helps the main computer system configure the I/O channels and devices. Rubin claims that by storing configuration data in the PROMs, the cards require no jumpers and no installation programs. The company also provides a complete memory map in its specifications booklet.

#### **Some boards suit several $\mu$ Ps**

In the add-on-bus field, the IndustryPack architecture isn't alone in claiming compatibility with many CPU boards. You can adapt Matrix Corp's Dbus-68 (or just Dbus) to other buses, too. However, as it's used by Matrix, the bus lets users add expansion boards to either 3U- or 6U-size VMEbus cards. When you add a Dbus board to a 3U-size card, the complete assembly requires two adjacent VMEbus slots. When you use a 6U-size card, however, the components on both cards face each other, and the assembly requires only one VMEbus slot. The signals and the connectors on the Dbus boards are exactly the same—only the add-on board's mounting position changes.

Besides picking up Dbus signals through a 64-pin connector, the Dbus boards also give you direct access to the signals on rows A and C of the VMEbus's P2 connector. These signal lines help you overcome another serious bottleneck: getting I/O signals to and from your computer boards. The P2 connector lets you route I/O lines out the back of the computer system instead of cluttering the front panel with connectors and cutouts for cables.

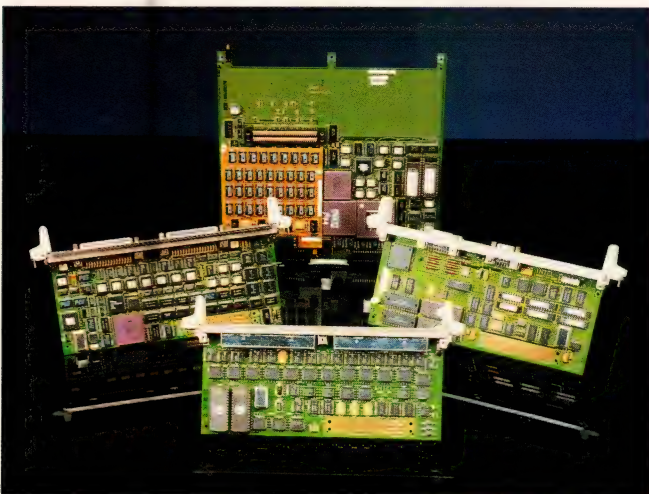For example, Matrix offers a Dbus board that sup-



**Add-on boards for the MIX** attach to a Multibus II baseboard (rear). Each add-on board supplies its own front panel and pads for an SMT board-to-board connector. Connector pads are visible at the bottom right edge of the frontmost board.



## Consider bus selections carefully

Consider the following general guidelines before adopting an add-on bus for a system you're building.

Determine whether an add-on bus supports both master and slave devices. Slave devices are simple I/O circuits that transfer data to and from the computer and I/O devices. On the other hand, if you plan to connect intelligent devices to your add-on bus, you may want them to be able to take control of the bus to transfer information and commands to other devices without having another board intervene. If you need such bus-master capabilities, be sure that the add-on bus supports them.

Also, be sure that the widths of the data and address buses will meet your needs. For example, you can't use the three address lines on the SBX bus to address more than a few I/O locations. Likewise, you may not need all of the addressing capabilities of the Heurikon Corebus unless you plan to greatly expand the memory or use dual-port memories to control a peripheral processor.

Don't let power consumption become a last-minute consideration. A design without enough power or ground pins or insufficient current-carrying capacity at the connectors is an easy trap to fall into. If you're designing your own add-on board, do a power budget after you have a rough design to be sure you aren't facing a brown-out on your board.

Kim Rubin at Greenspring says that a good connector should protect the pins and contacts and

that it should be impossible to mate connectors improperly. Be sure you ask how many insertions a connector's contacts can withstand. Greenspring claims that its connectors can withstand as many as 200 insertion cycles. About 100 insertion cycles is the limit for DIN connectors, and some cheap DIN connectors die after only 25 insertion cycles.

Check the mechanical configuration of the add-on cards you plan to use or design. First, be sure that your circuit will fit on an add-on board; next, be sure that the complete assembly will fit in the space available. Don't assume that an add-on card won't take up an adjacent card slot. Make careful measurements and check them. Also, be certain that the system has space for cables and connectors and that they are readily accessible.

Because add-on cards are part of the overall mechanical system, you should know how add-on boards mount to the baseboard. The connectors and the add-on boards should be mechanically stable. Greenspring's boards fasten to its baseboard with four machine screws. SBX boards usually fasten with one screw. Some users have been known to plug in an add-on board without any mechanical fasteners. Don't rely on the connector's grip to hold your board in place; Fred Rehhausser at Force Computers says that certain add-on boards have a tendency to work out of their sockets. He adds that some designers put the chips so close to other components that heat builds up,

and the circuits become unreliable.

You must demand complete documentation, too. Even though a manufacturer claims that its bus is nonproprietary, or open, you've got to see a complete package of documentation to prove it. Without the proper documentation, a so-called open bus defaults to being proprietary. When you examine the documentation, be sure that you get complete timing diagrams and timing descriptions as well as complete signal descriptions and signal names. Rehhausser also cautions buyers of add-on boards that interoperability of add-on boards can be a problem: "There are good technical people at these companies, but unless you're dealing with a real standard, specs can change—so buyers must beware."

You should also get complete schematic diagrams for the products you buy and for test circuits if you plan to adopt the bus for a product of your own. If a bus-interface design uses PLAs, you must receive complete listings for the PLA circuit. Sample software routines—particularly for the more complex buses—are a must. Don't be shy about asking for such information. You'll have to pay a small amount for some of the bus information, just as you'd have to pay for copies of an IEEE standard.

### Acknowledgment

*Thanks go to Laurent Meilleur at Matrix, who suggested many of the points in this box.*



*If you look far enough, you can probably find an add-on board that meets your needs. Offerings range from a few digital I/O lines to SCSI controllers.*

---

plies an interface to an Ethernet network. When you order one of the DB-ETH cards (\$600), you specify whether you want Ethernet signals brought out to a front-panel connector or to the P2 connector.

#### **Lack of space spurs bus innovation**

The Sambus from General Micro Systems operates in a similar fashion to the Dbus. Del Miller, General Micro Systems' vice president of sales and marketing, says quite frankly that the company developed the Sambus because its main computer boards ran out of space for I/O functions. Therefore, the company's engineers extended all the CPU's pins to an expansion connector. According to Miller, "When you extend the CPU's signals, you get at all of the  $\mu$ P's capabilities."

Miller can't understand why engineers design special add-on buses when a CPU's signals are readily available. He says that some companies may have difficulty designing add-on boards for their own computers because one CPU-board architecture may not adapt to all the various I/O functions and  $\mu$ P chips.

To the designers at General Micro Systems, providing all of the CPU chip's signals on the Sambus meant that the add-on boards would work just as if they were included on the main CPU board. Thus, the Sambus lets you add memory or I/O boards to the main computer board. For example, you can expand the CPU's main memory with a GMS SRAM (static RAM) board (\$2495) that furnishes 1M byte of 35-nsec CMOS SRAM. Similarly, the company's GMS 1553 board (\$1295) lets you add an interface for MIL-STD-1553 applications.

Miller says that General Micro Systems keeps its

CPU boards "lean and mean" so that users can add the capabilities they want as they need them. For example, he says that designers of multiprocessing systems don't necessarily want I/O circuits on each CPU board. But they gain an advantage by building their systems around the same make and model of the base-board CPU cards, because users don't want to learn about the peculiarities of four or five different types of CPU boards.

#### **Add-on boards control VSB, too**

Like the Dbus, the Sambus supplies a 64-pin connector near the P2 bus connector, which gives you access to the P2 connector's row-A and -C signals. The VMEbus's VSB (VME Subsystem Bus) signals aren't supplied on the General Micro Systems CPU board. However, if you need those signals, you can use a Sambus GMS VSB board (\$495) to generate them and put them on the P2 connector.

The VMEbus has gained a large following, but the Multibus II hasn't yet gained widespread popularity. Therefore, it remains to be seen how many third-part OEMs will gravitate toward Intel's MIX (Modular Interface Extension) bus as a way of expanding the I/O capabilities of Multibus II-based computers.

Intel aims its MIX at designers who want a 32-bit bus for the I/O expansion of Multibus II boards. Introduced in the fall of 1989, the MIX includes a baseboard assembly that supplies power connections and mechanical support as well as the hardware, software, and firmware to link MIX boards to the Multibus II.

Because it supplies not only interface logic, but also bus-arbitration logic and shared memory, the MIX

*The MXbus converts 3U VMEbus boards to 6U-size units as it expands the capabilities of the baseboard. Unlike most add-on boards that stack on top of one another, the MXbus adds cards to the side.*





## Manufacturers of add-on buses and bus products

For more information on add-on buses and bus products such as those described in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

**Central Data (SBX)**  
1602 Newton Dr  
Champaign, IL 61821  
(217) 359-8010  
FAX 217-359-6904  
Circle No. 650

**Centralp Automatismes (SBX)**  
16 Rue Gabriel Peri  
92120 Montrouge, France  
33-1-4253-3617  
FAX 33-1-4253-7447  
Circle No. 651

**Computer Dynamics Sales (SBX)**  
107 S Main St  
Greer, SC 29651  
(803) 877-8700  
FAX 803-879-2030  
Circle No. 652

**Computer Modules Inc (SBX)**  
2348C Walsh Ave  
Santa Clara, CA 95051  
(408) 496-1881  
FAX 408-496-1886  
Circle No. 653

**Concurrent Technologies (cCBX)**  
701 Devonshire Dr  
Champaign, IL 61820  
(217) 356-7004  
FAX 217-356-6238  
Circle No. 654

**General Micro Systems (SAM Bus)**  
4740 Brooks St  
Montclair, CA 91763  
(714) 625-5475  
FAX 714-621-4400  
Circle No. 655

**Gespac Inc (MLX)**  
50 W Hoover Ave  
Mesa, AZ 85210  
(602) 962-5559  
FAX 602-962-5750  
Circle No. 656

**Greenspring Computers**  
(IndustryPack)  
1204 O'Brien Dr  
Menlo Park, CA 94025  
(415) 327-1200  
FAX 415-327-3808  
Circle No. 657

**Heurikon Corp (Corebus)**  
3201 Latham Dr  
Madison, WI 53713  
(608) 831-0900  
(800) 356-9602  
FAX 608-831-4249  
Circle No. 658

**Inovec Inc (SBX)**  
115 Wallis St  
Eugene, OR 97402  
(503) 485-7127  
FAX 503-485-4672  
Circle No. 659

**Intel Corp (MIX, SBX)**  
3065 Bowers Ave  
Box 58065  
Santa Clara, CA 95052  
(800) 548-4725  
Circle No. 660

**Ironics Inc (VSB)**  
798 Cascadilla St  
Ithaca, NY 14850  
(607) 277-4060  
FAX 607-272-5787  
Circle No. 661

**Matrix Corp (Dbus-68)**  
1203 New Hope Rd  
Raleigh, NC 27610  
(919) 833-2000  
FAX 919-833-2550  
Circle No. 662

**Mizar Inc (MX)**  
1419 Dunn Dr  
Carrollton, TX 75006  
(214) 446-2664  
FAX 214-242-5997  
Circle No. 663

**Motorola Microcomputer Div (VSB)**  
2900 S Diablo Way, MS DW 283  
Tempe, AZ 85282  
(602) 438-3501  
FAX 602-438-3534  
Circle No. 664

**Omnibyte Corp (Omnimodules)**  
245 W Roosevelt Rd  
West Chicago, IL 60185  
(708) 231-6880  
FAX 708-231-7042  
Circle No. 665

**Pentek (MIX)**  
10 Volvo Dr  
Rockleigh, NJ 07647  
(201) 767-7100  
Circle No. 666

**Performance Technologies Inc (I/O Pak)**  
435 W Commercial St  
East Rochester, NY 14445  
(716) 586-6727  
FAX 716-586-6707  
Circle No. 667

**Radix Microsystems Inc (EXM)**  
19545 NW Von Neumann Dr  
Beaverton, OR 97006  
(503) 690-1229  
FAX 503-690-1228  
Circle No. 668

**Radstone Technology (VSB)**  
20 Craig Rd  
Montvale, NJ 07645  
(201) 391-2700  
(800) 368-2738  
FAX 201-391-2899  
Circle No. 669

**SBE Inc (VSB, SBX)**  
2400 Bisso Lane  
Concord, CA 94520  
(415) 680-7722  
(800) 221-6458  
(800) 328-9900 in CA  
FAX 415-680-1472  
Circle No. 670

**Siemens/Micro Industries**  
(SBX, OME)  
691 Greencrest Dr  
Westerville, OH 43081  
(614) 895-0404  
(800) 446-6762  
FAX 614-882-6357  
Circle No. 671

**Single Board Solutions Inc (SBX)**  
20045 Stevens Creek Blvd  
Cupertino, CA 95014  
(408) 253-0250  
FAX 408-253-8298  
Circle No. 672

**Sun Microsystems Inc (SBus)**  
2550 Garcia Ave  
Mountain View, CA 94043  
(415) 960-1300  
FAX 415-336-3880  
Circle No. 673

**WinSystems Inc (SBX)**  
715 Stadium Dr, Suite 100  
Arlington, TX 76011  
(817) 274-7553  
FAX 817-548-1358  
Circle No. 674

**Zendex (SBX)**  
6700 Sierra Lane  
Dublin, CA 94568  
(415) 828-3000  
FAX 415-828-1574  
Circle No. 675

**Ziatech Corp (SBX)**  
3433 Roberto Ct  
San Luis Obispo, CA 93401  
(805) 541-0488  
FAX 805-541-5088  
Circle No. 676

NOTE: Specific add-on buses are noted in parentheses after each manufacturer's name. Keep in mind that these manufacturers may also offer other types of bus products.

### VOTE...

Please also use the Information Retrieval Service card to rate this article (circle one):

High Interest 488

Medium Interest 489

Low Interest 490



\_\_\_\_\_





Radstone supplies Norden Systems (US) and Marconi Command and Control Systems (UK) with bulk storage memory units developed for the MLRS fire control computer. On time. On budget.

## MIL-Spec. VMEbus

### The Sure-Fire Solution To Cost and Lead-Time Problems In Military Computer Applications

Now there is a new generation of Mil-Spec computer hardware. For systems integrators with tactical computer applications who need a sure-fire solution fast, Radstone has the answer — a complete range of field-proven Mil-Spec, 32-bit VME boards.

All you need to build tomorrow's military systems today, available off-the-shelf, 68020 processors, memory and I/O modules, Multiprocessor capability. On board diagnostics. Real-time Ada and C software support. A choice of Mil-qualified system enclosures.

This total capability is designed for projects where lower development costs, shorter and more predictable timescales are important. Developed by Radstone, one of the world's largest manufacturers of VME boards with leading edge design resources to match. Built by Radstone, in a facility approved to NATO AQAP1 standards. Supported by Radstone, with 30 year's experience of military systems applications.

Call us now for your copy of the new PMV 68 MIL-STD-VME systems guide. Let us show you how we put the sure-fire solution into action.

UK Water Lane, Towcester, Northants, NN12 7JN, (0327) 50312  
USA 20 Craig Road, Montvale, NJ 07645, (201) 391-2700  
France 'Miniparc' 6 avenues des Andes, 91940 Les Ulis, (1) 64.46.04.03  
Germany Bahnhofstraße 38, D-6090 Rüsselsheim (061 42) 6 80 04



**RADSTONE**  
TECHNOLOGY



*Several processor-independent buses lend themselves to original designs, so you can customize your product with existing add-on boards.*

---


suggests that MIX-board designers be very picky about the pc-board fabricator they select. Also, he adds, be sure that you can fit your circuitry on a MIX add-on board that measures  $3.45 \times 7.79$  in.

You can choose from several other buses that let you expand a basic computer system and in which the added boards are designed to occupy card slots. Like the MIX, the cCBX (Concurrent Technologies Bus Extension) from Concurrent Technologies expands Multibus II computers. However, instead of stacking add-on boards on a carrier board, the cCBX uses the Multibus II's P2 connector.

Glen Fawcett, the president of Concurrent Technologies, says that the US Government agencies he deals with favor the Multibus II architecture. Unfortunately, few Multibus II-compatible I/O boards are manufactured. "We designed a basic 80386 CPU board and developed slave boards for it—typically for DSP applications. Our cCBX interface signals go out the P2 connector to our other boards," says Fawcett. The company's basic Multibus II, CPU/cCBX-interface board furnishes an 80386 chip (16 MHz) and as much as 1M byte of memory. Prices start at \$3950.
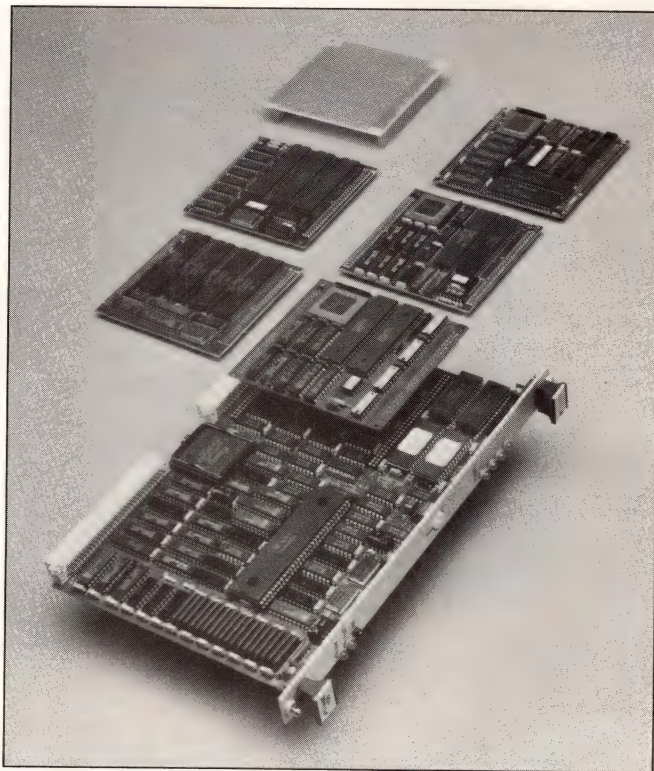
#### **The cCBX controls four slaves**

Bus-timing and bus-termination characteristics limit you to one CPU and to as many as four slave boards on the cCBX bus. However, your system can incorporate other Multibus II boards that communicate with the Concurrent Technologies CPU board over the main Multibus II Processor System Bus (PSB). Concurrent




*The I/O Pak cards access the VMEbus's P2 connector. The add-on boards also offer a variety of functions that you add to Performance Technologies' basic CPU board.*

Technologies sells four types of slave I/O boards for cCBX systems. Complete specifications for the cCBX are available from the manufacturer.

Software isn't a big issue for Fawcett. He says that the cCBX is "nonexistent" to users because their software treats cCBX boards as system resources—it doesn't know that a cCBX bus is there.

Prior to deciding on the cCBX architecture, Concurrent Technologies also examined the IBM PC/AT bus as a candidate for its add-on-bus efforts. But Fawcett says that it wasn't obvious how to put the PC/AT bus into the Multibus II interconnect space. (Both Intel and Siemens/Micro Industries offer PC/AT add-on buses for the Multibus II architecture. Intel calls its extension P2/aPC, and Siemens labels its extension AT96, but these buses are beyond the scope of this article.)

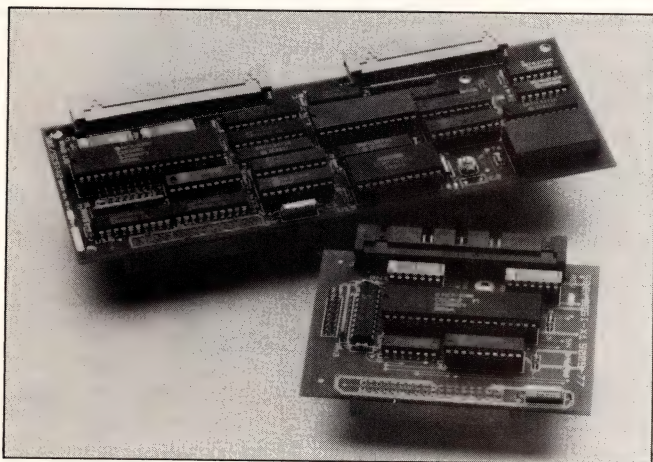However, Radix Microsystems pursued the PC/AT bus and adapted it to the VMEbus. Instead of developing a conversion scheme that fits existing PC/AT boards into a VMEbus-type enclosure, Radix redesigned PC/AT cards to a  $3 \times 6$ -in. size so that two of



*Two sizes of SBX boards let manufacturers put more circuits on one card. These two modules from SBE are SCSI-bus controllers. The smaller board supplies one SCSI port, and the larger one offers two SCSI connectors.*



# Real products for real people.



**ROHM**



*Several manufacturers give you access to the P2 lines on the VSB. This access is vital if you plan to use VSB add-on cards.*

them would fit—one over the other—into a 6U VMEbus slot. The boards don't plug into the VMEbus; instead, they plug into a subplane board that fits on top of the normal VMEbus connectors. In turn, that subplane board mates with the company's EPC-3P CPU board, an 80386SX-based computer board that costs \$2595 (100). The CPU board also connects to the VMEbus so that it can communicate with other

VMEbus boards. The individual PC/AT-like boards are called Embedded-PC Expansion Modules, or EXMs.

You may wonder why anyone would want a PC/AT computer as part of a VMEbus-based computer system. According to Steve Cooper, director of marketing at Radix, many people building VMEbus-based computers want the PC for its I/O functions. Those designers, asserts Cooper, don't want to go out onto the

**Table 1—Representative open add-on bus architectures**

Manufacturer	Add-on bus	Main bus	Data bits	Address bits	Interrupts	License	Comments
Concurrent Technologies	cCBX	MB II	8 or 16	24	8	No	Intended for general-purpose I/O. Bus originates from P2 on the cCBX CPU board.
General Micro Systems	Sambus	VMEbus	32	32	1	No	Dynamic bus sizing. Includes 16,000 I/O addresses. Engineering and manufacturing support, sample software, PLA equations available free.
Gespac	MLX	G-64	8	4	1	No	Intended for general-purpose I/O. Software tools and routines are available free from Gespac.
Greenspring	IndustryPack	VMEbus	16 or 32	22	2 levels	Yes	ID PROM sets up configuration information. Design tools from the manufacturer cost from \$15 to \$545. Includes 64 I/O addresses.
Heurikon	Corebus	VMEbus	64	32	4	Yes	Intended for high-speed memory, general-purpose I/O, and auxiliary processors. Plug-in modules can control baseboard. Two separate buses for I/O and memory devices. Software drivers are available. Source code is available for \$2500. License fee required.
IEEE	SBX	MB I and II	8 or 16	3	2	No	Now covered by IEEE-796 standard. Contact Institute of Electrical and Electronic Engineers (New York, NY).
Intel	MIX	MB II	8, 16, or 32	32	2	No	Intended for general-purpose I/O, and auxiliary processors—not for memory expansion or smart I/O cards. Software tools are available from \$630 (debugger). Includes 4096 I/O addresses.
Matrix	Dbus-68	VMEbus	32	32	2	No	Intended for general-purpose I/O, communications, disks, analog and digital I/O. Dynamic bus sizing. Requires no special software tools.
Mizar	MX	VMEbus	16 or 32	23 to 32	see comments	Yes	Controls as many interrupts as the CPU chip makes available. Based on 680X0 $\mu$ P chips, so users require standard 680X0 software-development tools.
Omnibyte	Omnimodule	VMEbus	16	8 to 12	2	No	Intended for general-purpose I/O. Not recommended for memory extensions or high-speed communications such as Ethernet. Software drivers and debugging software available from manufacturer.
Performance Technologies	E Pak	VMEbus	32	32	2	No	Intended for disk, communications, and general-purpose I/O. Designer's manual and prototype E Pak available for \$200.
	I/O Pak	VMEbus	16	24	2	No	Intended for disk, communications, and general-purpose I/O. Designer's manual available for \$200.
Radix	EXM	VMEbus	8 or 16	24	10	No	Subplane connector lets the baseboard control IBM PC/AT-type cards that supply I/O circuits. Uses standard PC/AT signals. Can access other VMEbus cards over the main system bus.
Siemens/Micro Industries	OME	MB II	32	26	4	No	Intended for general-purpose I/O. Only one master can exist on the bus. Communications between modules occur via multipoint memory and mailboxes, registers, and FIFO memories. Manufacturer supplies tools.
Sun	SBus	None	8, 16, or 32	28	1	No	Intended for general-purpose I/O. Bus supplies 32 virtual address lines and one of seven shared interrupts. Development kit is available for \$300.

**Key:**

cCBX = Concurrent Technologies Bus Expansion  
EXM = Embedded PC Expansion Module  
MB I = Multibus I  
MB II = Multibus II  
MIX = Modular Interface Extension

MLX = Micro Local Extension  
MX Bus = Mizar Expansion Bus  
OME = Onboard Module Expansion  
Sambus = Special Application Module Bus  
SBX = System Bus Extension



# Real help.





**W**hen you're looking for solutions that work *today*, call us. We have products that'll give you some real help.

See, we're a lot like you. Working hard—often late into the night—to make reliable products that meet real needs.

ROHM makes a great line of components—monolithic and hybrid ICs, LEDs, displays, LCDs, discretes, passives, printheads and more. In fact, we're among the world's top 25 semiconductor companies.
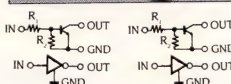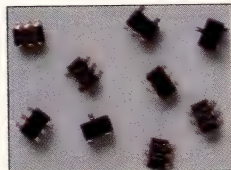
## Dual Digital Transistors

Take our digital transistor series. These combine up to four resistors and two transistors in a SOT-36—a neat little package we developed so we could put more stuff into the same space as the good old SOT-23. And save you a lot of real estate on the circuit board.



You can get  $V_{ce}$  ratings from 11 to 120 volts, and current ranges from 30 to 100 mA. Whichever configuration you choose, they're


all the same size, which sure helps simplify your layout. And their surface-mount packaging makes them popular with the manufacturing folks, too.

If you want to know more, call Lynn Briley, shown in the photo below. (The one with the wide part in his hair.) If Lynn's not in, talk to Sharon Whitmore. She's pictured, too. Either one will have answers for your transistor questions.
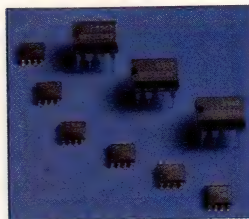
## E<sup>2</sup>PROMs


Maybe you need a PROM with low power consumption and high reprogrammability. If so, take a look at our new CMOS 1024-bit EEPROM, the best alternative to traditional NMOS we know of.

In addition to all the standard features you'd expect, the BR93CS46 operates at a low 2.7 volts, drawing only 20  $\mu$ A. And



you can even run it at a full 1 MHz.

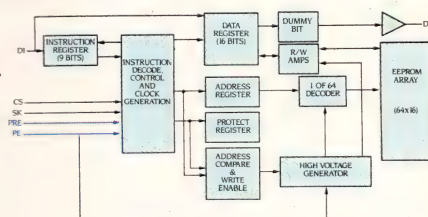The BR93CS46 gives you external read/write memory in sixty-four 16-bit registers, and interfaces with standard microprocessors like Intel's 8048/49/51/96, National's COP4XX, Motorola's 6801/05, TI's TMS1000, and Zilog's Z8. Seven 9-bit instructions control everything.




For more details, call Warren Schoals, the studious guy standing in the

back. (Warren's also known as Mr. Whiteshirt when he's not out in his pick-up.)

Next time you're trying to figure out a solution that works today—or tonight—FAX us an S.O.S. Thank-you.

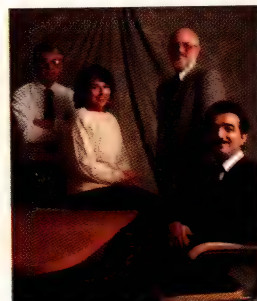Then turn off the light and go home. Your family will thank you, too.



# ROHM

ROHM Corporation ■ 8 Whatney ■ Irvine, CA 92718 ■ (714) 855-2131 ■ FAX (714) 855-1669



*If your application demands standard graphics and I/O, then consider adding a PC/AT to your system. At least one manufacturer puts a PC in VMEbus computers.*

---

VMEbus for disk I/O and for network communications. Instead, they'd rather use peripherals already available for the PC/AT bus. The EXM bus's electrical specifications match those for the PC/AT, says Cooper, so people who develop EXM boards can use the PC/AT-bus information that has been available for some time.

Graphics capabilities are another boost for the embedded PC. "In the industrial market," says Cooper, "there are no graphics standards. On the other hand, the PC display has well-defined standards that most designers can use quickly. Also, people can start with a software standard such as Windows rather than worrying about bashing the display bits."

#### **A VMEbus PC uses standard software**

The PC on the VMEbus appeals to people who want to plug in the boards and have the computer up and running quickly. Cooper stresses that the PC cards come with ready-to-go software. Network boards are already configured and are ready to use with Netware or other standard software packages. The company now offers several EXM units—for example, an Ethernet/CheaperNet Controller (EXM-1), which costs \$380 (100). You can also purchase a solid-state disk with either 1M or 2M bytes of flash EEPROM (from \$590 (100)) and a SCSI and floppy-disk controller board (EXM-3). The disk controller costs \$260 (100).

Workstation vendors are also finding the benefits of providing expansion or add-on buses. Sun Microsystems looked at many buses as candidates for expansion of the company's Sparcstation-1 workstation, but few of the available buses took advantage of today's advanced LSI chips and pc-board technology.

#### **Workstations want buses, too**

The SBus grew out of Sun's search, and the new bus has drawn the interest of 200 companies that represent system vendors, hardware suppliers, and OEMs. Sun's SBus product manager, Steve Furney-Howe, says that 25 third-party suppliers are now working on SBus-based projects. Another indication of interest in the SBus is that LSI Logic Corp (Milpitas, CA) now offers samples of its L64853 DMA-controller chip (\$76 (100)) for the SBus. Also, Sun isn't limiting itself to supporting the SBus on the Sparcstation-1 alone. The company will supply the bus in most of its new products.

Furney-Howe sees software as an important issue in the add-on-bus realm. To him, software drivers are part of the package that hardware manufacturers must deliver to their customers. Sun expects to support load-

able device-driver routines for products that incorporate the SBus so that users don't have to completely reconfigure their systems as they connect add-on boards. Furney-Howe expects that most third-party vendors will write their own device-driver routines, but Sun also has a consulting group that can write drivers.

Sun now offers a 134-page manual of specifications for the SBus, and the booklet is free to interested developers. The company will soon ship its development kit, which will supply device-driver software as well as slave-device interface examples. Sun's SBus Support Group will also offer simulation models, firmware-development tools, and technical seminars.

The seven add-on buses we've discussed here should give you a good idea of the diversity of buses that can answer designers' needs for special add-on devices and circuits. It's impossible to cover all the add-on buses that people have designed over the last few years. For example, many bus adapters change one bus to another, and many adapters let you put one type of card into another bus system. Likewise, you can buy bus extensions that help a bus extend its life by expanding data- and address-bus widths. Look for articles on those units in future issues of EDN.

**EDN**

#### **References**

1. Johnson, J B, and S Kassel, *The Multibus Design Guidebook*, McGraw-Hill, New York, NY, 1984.

---

Article Interest Quotient (Circle One)  
High 488 Medium 489 Low 490

---

## **WHAT'S COMING IN EDN**


EDN Magazine's February 15, 1990, issue will feature a staff-written Special Report on the role of static RAMs in systems with processing speeds exceeding 30 MHz. Part 1 of the designer's guide to Spice-compatible op-amp macromodels will describe a new approach to improving simulation accuracy. And EDN's occasional series about engineering in Europe continues with a report on the UK's Marconi Instruments.

Remember to look for our regular departments, too.

---



# TURNING YOUR IDEAS INTO PRACTICAL REALITIES



SBE technology  
helps your system  
connect in the market-  
place.

When you specify an SBE communications or real-time processing solution, you get more than just a high-quality, highly reliable product—you get a strategic design partner committed to your system's success.

All SBE Multibus I and VMEbus boards, as well as our busless communications processing systems, are modular by design. SBE supports a broad portfolio of technology that can be customized to match your application. The result is extremely fast turnaround in the design of the products you specify.

Our advanced manufacturing, test and inspection techniques utilize surface-mount technology. This ensures that SBE manufactured products will meet your company's stringent quality standards.

You also get a support program that includes comprehensive documentation, access to an extensive software library, and prompt engineering response for your customized OEM requirements.


For more information on how SBE can turn your ideas into practical realities, contact SBE, Inc., 2400 Bisso Lane, Concord, CA 94520 today. Call 1-800-347-COMM.

**SBE**

*Communications & Real-time Solutions*



# .050 centerline shielded I/O.

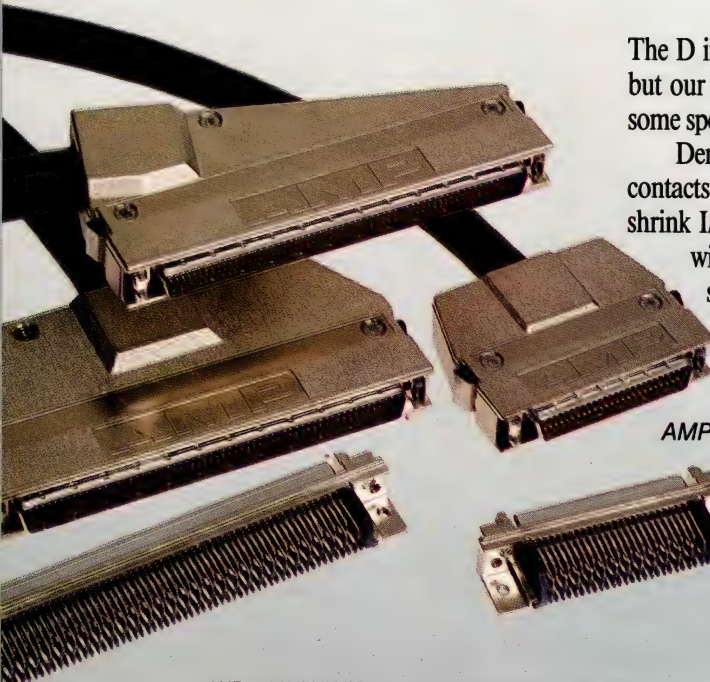

The D interface may look familiar, but our latest I/O connectors have some special temptations all their own.


Density, for instance. Mating contacts in a .050" by .100" pattern shrink I/O real estate dramatically, with sizes to 120 positions. Our staggered .075" by .100" pcb

*AMPLIMITE .050 Series 50 and 68 position connectors were recently selected as the Small Computer Systems Interface (SCSI). The X3T9.2 Standards Committee anticipates approval as an ANSI standard in 1989.*


layout frees up more board, too, but still leaves trace routing uncomplicated.

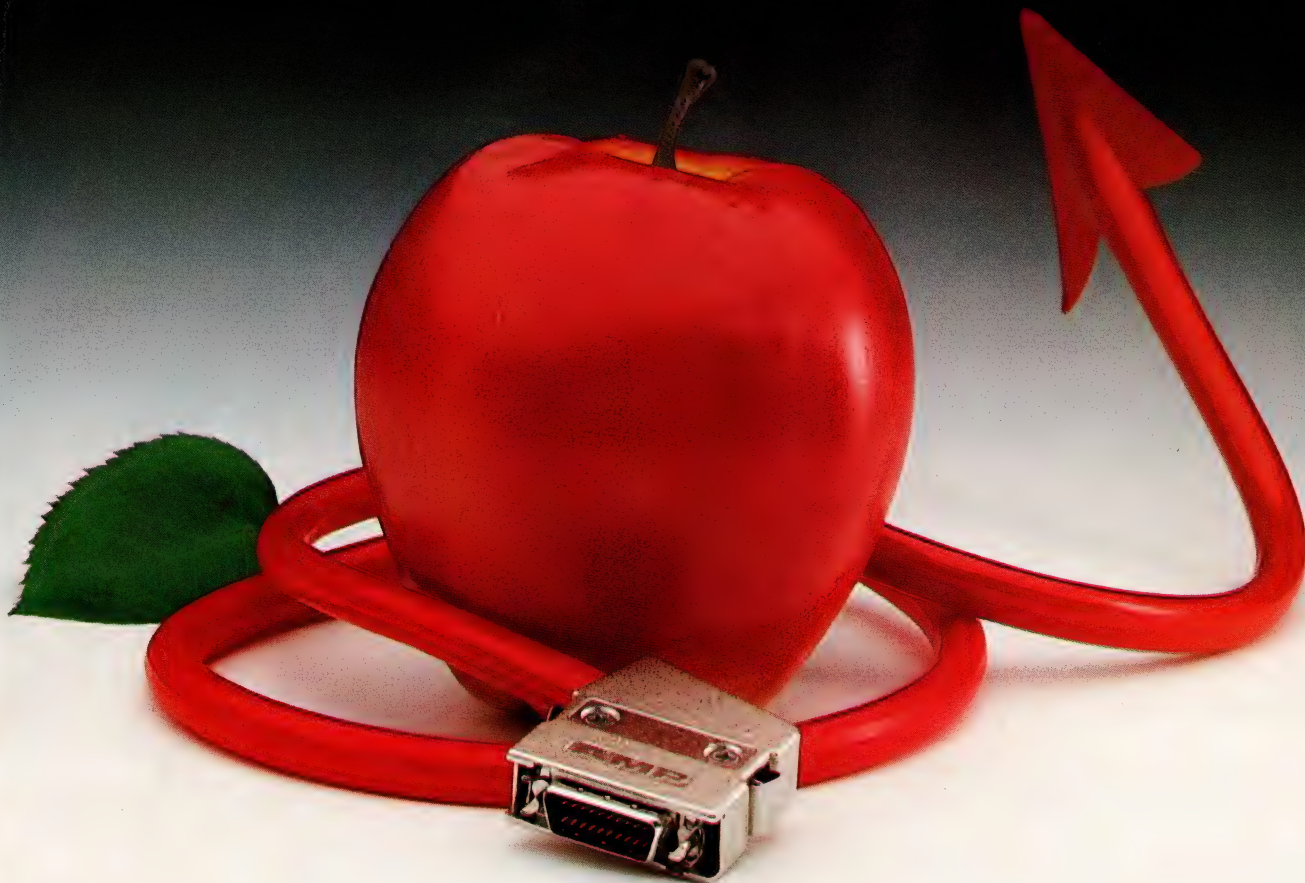And shielding, for another instance. All the effectiveness you expect from steel front shells and AMP engineering—plus our make-first/break-last design to handle electrostatic discharge concerns as well. Add superior strain relief, consider our squeeze-to-release option, and you have a compelling package.





# Very tempting.

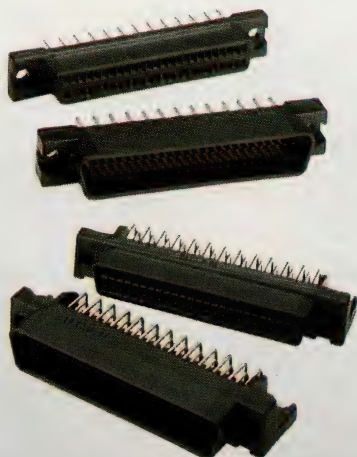

Maximum flexibility with right-angle, stacking, and edge-to-edge configurations. Fork-and-tab contacts minimize insertion/extraction force. Strict polarization, simple interface.

All part of our flexible AMPLIMITE .050 Series Connector line. Board-to-board styles feature the same .050 centerline, gold-over-nickel plated phosphor-bronze contacts. Thermoplastics are 94V-0 rated, and *everything* is compatible in design and material with robotic applications.

And our board-to-board configurations allow parallel stacking with

minimal .472" spacing, plus edge-to-edge, plus right angle configurations with pin or sockets.

**Let us tempt you. Call the AMP Product Information Center at 1-800-522-6752 and ask about AMPLIMITE .050 Series Connectors. AMP Incorporated, Harrisburg, PA 17105-3608.**

## **AMP** Interconnecting ideas




# SNA Systems from 20 Hz to 22 GHz

In Level Measurement we are riding on the crest of the wave.

And our Spectrum and Network Analyzers set the same standard of high performance.

The technical world associates Wandel & Goltermann with peak performance in electronic measurements. In five decades we have become a world leader in measuring-technology for analog and digital transmission systems. Our leadership in experience has been used to particular advantage in our Spectrum and Network Analyzers. You can always expect the best from Wandel & Goltermann. Our SNA Systems offer new dimensions in peak performance. User friendliness and ultrahigh product quality are our hallmarks. Let's take an example: in the realization of our Synthesizers we have made no compromises. The high spectral purity and exceptional stability allow, in conjunction with the 3 Hz bandwidth, measurements of the best quality reproduction and resolution. Return the reply card or write to the following address for full information about the entire SNA-family.

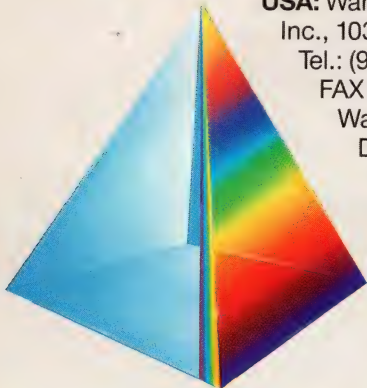


**USA:** Wandel & Goltermann,  
Inc., 1030 Swabia Court, R. T.P., NC 27709,  
Tel.: (919) 941-5730, Telex II: 810-621-0002,  
FAX (919) 941-5751. **Canada:**  
Wandel & Goltermann Inc., 21 Rolark  
Drive, Scarborough, Ontario M1R3B1,  
Tel.: (416) 291-7121. **Worldwide:**  
Wandel & Goltermann,  
VMW, Postfach 1262,  
D-7412 Eningen,  
Tel. + (49) 71 21-86-0,  
Tlx. 7 29 833

CIRCLE NO. 52

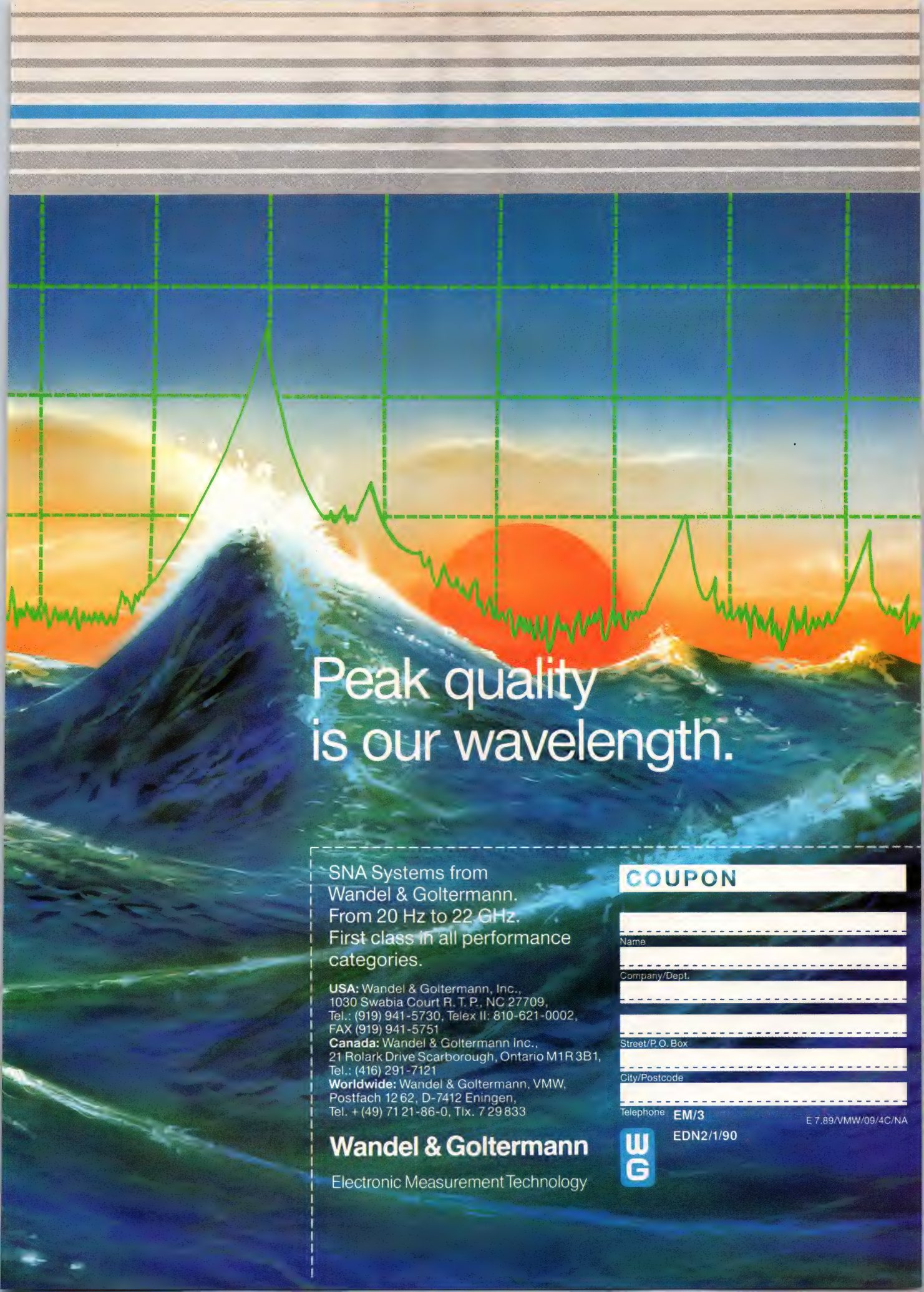Please visit us at CeBIT Hanover, 21.-28.3.90,  
Hall 13, Stand A18/B17.





# Peak quality is our wavelength.

SNA Systems from  
Wandel & Goltermann.  
From 20 Hz to 22 GHz.  
First class in all performance  
categories.

**USA:** Wandel & Goltermann, Inc.,  
1030 Swabia Court R, T. P., NC 27709,  
Tel.: (919) 941-5730, Telex II: 810-621-0002,  
FAX (919) 941-5751

**Canada:** Wandel & Goltermann Inc.,  
21 Rolark Drive Scarborough, Ontario M1R 3B1,  
Tel.: (416) 291-7121

**Worldwide:** Wandel & Goltermann, VMW,  
Postfach 12 62, D-7412 Eningen,  
Tel. + (49) 71 21-86-0, Tlx. 7 29 833

**Wandel & Goltermann**  
Electronic Measurement Technology

## COUPON

Name

Company/Dept.

Street/P.O. Box

City/Postcode

Telephone **EM/3**

EDN2/1/90

E 7.89/VMW/09/4C/NA





# We Believe The World Is Flat...

## or soon will be.

The world is turning to flat panel displays. And Yamaha LSI is there — with the only complete line of single-chip and board-level graphic controllers in the industry. We're the controlling force behind most of the world's portable computer displays. So, if there's a flat panel display in your future, there are many good reasons to turn to Yamaha LSI.

Whether you need CGA, EGA or VGA, our advanced controllers support all leading flat panel display technologies, plus CRTs. They can even control the newest color displays.

Our patented techniques automatically convert color software to gray scale on LCDs and to hatching patterns on EL and plasma displays. Our newest controllers correct aspect ratio problems, so circles look like circles instead of ovals.

Our single-chip solutions are ideal for all new designs, especially laptops and portable devices. With four chips to choose from, you can have the distinct level of control and resolution you need.

Our Display Master® family of auto-initializing IBM compatible board-level controllers is ideal if you need a ready-made solution. These boards are compatible with EL, Plasma, LCD and CRT technologies and support nearly all manufacturers' displays.

### Single-Chip

VGA	V6388
EGA	V6377
CGA, MDA, Hercules	V6366
CGA, MDA	V6355

### Board-Level

Display Master VGA	YDM6448
Display Master EGA	YDM6435
Display Master	YDM6420

And, they're available in a wide range of resolutions. Just plug the card into your PC, set DIP switches and go. No additional hardware or software modification is needed.

We've been building this family of controllers for over six years.

(Optional integrated -24V power supply for LCDs)

Call 1-800-543-7457. Do it today. We'll make you a flat world believer too!

## YAMAHA® LSI

Systems Technology Division  
981 Ridder Park Drive  
San Jose, CA 95131  
(408) 437-3133 FAX (408) 437-8791

CIRCLE NO. 53







## flash-ADC testing Part 3

# Measure flash-ADC performance for trouble-free operation

---

*The first two parts of this series described the subtleties of flash A/D converters and the test methods used to evaluate these devices. Part 3 concludes the series with a discussion of the actual measurements you'll need to fully characterize flash A/D converters.*

---

Walt Kester, *Analog Devices*

Although manufacturers have expanded the number of guaranteed specifications they put on their data sheets, the test conditions often won't match those of your system design. You can use the methods described in Part 2 of this series to test a flash A/D converter, but the measurements you need to perform depend on the converter's primary application. This final part of the series provides information on important measurements you'll need to characterize your converter's performance, including total harmonic distortion (THD), differential and integral nonlinearity, and noise power ratio. You'll probably want to start with the S/N ratio, a measurement that's common to most A/D converter applications.

The S/N ratio is the ratio of the rms fundamental to the rms quantization noise. As described in Part 2,

you can measure this parameter by digitizing a pure sine wave and performing Fourier transformations on the data. The rms energy contained in the fundamental sine wave is equal to the square root of the sum of the squares of the peak value and the values of the appropriate number of samples, or bins, located on either side of the peak. The converter's resolution and its side-lobe roll-off characteristics determine the number of samples you'll need. For a detailed explanation of sampling requirements, see Part 2.

The rms energy in the remaining frequency bins represents the noise due to theoretical quantization, the converter's harmonic distortion and excess noise, and the FFT round-off error. Take the square root of the sum of the squares of the remaining samples (excluding the dc components) to determine the rms energy. The overall S/N ratio of the A/D converter is

$$\text{S/N ratio} = 20 \log(\text{rms signal level/rms noise level}).$$

You can measure harmonic distortion in a similar manner. The test program (described in Part 2) examines the FFT frequency spectrum for the proper location of the desired harmonic (harmonics above  $f_s/2$  will be aliased into the baseband) and determines the rms energy in that harmonic. The following equation calculates the harmonic distortion:

$$\text{Harmonic distortion} = 20 \log(\text{rms signal level/rms harmonic level}).$$



---

## *The S/N ratio and harmonic distortion are key specifications in evaluating the performance of A/D converters.*

---

The total harmonic distortion (THD) is the root-sum-square of the first five harmonics of the fundamental. Use this number in place of the rms harmonic level in the above formula.

### Two-tone intermodulation tests using FFTs

In many applications, you don't have the simple case of a single input frequency. For example, in communication applications that multiplex several frequencies onto a single carrier, you need to measure intermodulation products. You determine this parameter by applying two sine waves of different frequencies ( $f_1$  and  $f_2$ ) to an A/D converter. You then measure the amplitudes of the third-order intermodulation products, which occur at frequencies  $2f_1 + f_2$ ,  $2f_1 - f_2$ ,  $2f_2 + f_1$ , and  $2f_2 - f_1$ .

Although it's possible to filter out most intermodulation distortion if the two tones are of similar frequencies, the third-order products will be very close to the fundamental frequencies and thus difficult to remove.

To avoid clipping-induced distortion, the amplitudes of the individual tones should be at least 6 dB below the full-scale range of the flash converter. In addition, the frequency separation of the two tones should be consistent with the resolution of the FFT. As discussed in Part 2, the spectral resolution of the FFT is a function of record length  $M$ , coherence vs noncoherence, and the properties of the windowing function that you choose.

In receiver applications, you often want to know the maximum ratio between the amplitude of a single-tone input signal and the amplitude of its maximum spurious

component. For an ideal A/D converter, this ratio occurs for a full-scale input sinusoid. In a practical A/D converter, however, spurious content is a function of slew rate. Therefore, the maximum spurious-free dynamic range for a given input frequency will probably occur at a level somewhat below full scale. Because the spurious-free dynamic range is slew-rate dependent, it's a function of input frequency and amplitude.


Fig 1 is a plot of the typical maximum spurious level vs input signal level. Also shown is a plot of the corresponding spurious-free dynamic range. The plot demonstrates that the maximum spurious-free dynamic range of 38 dB occurs for an input signal that's about 3 dB below full scale.

The data you need to generate these plots is readily available from the family of FFTs calculated for the different input amplitudes. By knowing the input signal level that gives the highest spurious-free dynamic range at frequencies close to the Nyquist frequency, it's possible to set the gain of the system to take maximum advantage of the A/D converter's spectral characteristics.

### Histograms are helpful

Differential and integral nonlinearity are also important measurements of converter performance. Try a histogram test to obtain these measurements. To make a histogram analysis, digitize a known periodic input at a rate that's asynchronous relative to the input signal. To gather the sample data for the histogram, you'll need a buffer memory and a test system, as described

**Fig 1—**These dynamic-range plots show the power levels of spurious frequencies and the maximum spurious-free dynamic range. In this example, the maximum spurious-free dynamic range occurs at an input signal level that's 3 dB below full scale.

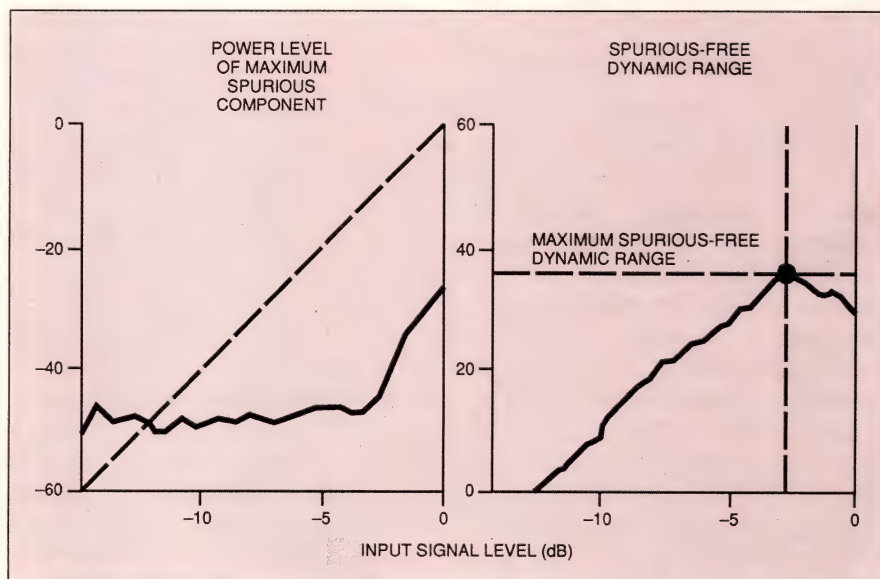



in Part 2. The buffer memory will probably be too small to hold a statistically significant number of samples from a single run (several hundred thousand are usually required). For this reason, run several tests to acquire the data and load the contents of the buffer into the main memory of your test system after each run. Benchtop test systems from Hewlett Packard and Tektronix also provide histogram test capability.

After the test system accumulates a statistically significant number of samples, it can determine the relative number of occurrences of each digital code (the code density). This test routine then normalizes the data based upon the input signal and analyzes the results for linearity errors.

For an ideal A/D converter with a full-scale triangular-wave input, you'd expect an equal number of codes in each bin. The number of counts in the  $n$ th bin,  $H(n)$ , divided by the total number of samples taken,  $M$ , is the bin width as a fraction of full scale. The ratio of the actual bin width to the ideal bin width,  $P(n)$ , is the differential linearity. Ideally, this ratio should be unity. Subtracting 1 LSB gives you the differential nonlinearity.

You can determine integral nonlinearity with a cumulative histogram; the cumulative bin widths are the transition levels. However, the cumulative effects of errors can make the integral-nonlinearity measurement inaccurate. Histograms are used more often in evaluating differential nonlinearity.

High-speed, high-accuracy triangular waves are difficult to generate, so use a sine wave. All codes aren't


equally probable with a sine-wave input, however, and you should normalize the histogram data using the probability density function for a sine wave, as shown in Fig 2.

To obtain accurate results, you need to take a large number of samples. For example, to determine the differential nonlinearity for an 8-bit flash converter to within 0.1 bit with 99-percent confidence, you'll need 268,000 samples. You can use hardware to count these samples, thus speeding up the software processing time. For high-speed sampling, decimate the output data to clock rates that are compatible with a slower-speed memory.

### Using noise-power-ratio tests

You can use noise-power-ratio (NPR) tests to measure the transmission characteristics of frequency-division-multiplexed (FDM) communications links. In a typical FDM system, 4-kHz-wide voice channels are "stacked" in frequency for transmission over coaxial, microwave, or satellite equipment. At the receiving end, the FDM equipment demultiplexes the data and returns it to individual, 4-kHz baseband channels. In an FDM system that has 100 channels or more, Gaussian noise with the appropriate bandwidth approximates the FDM signal.

The test setup of Fig 3 measures an individual 4-kHz channel for quietness by using a narrow-band notch (bandstop) filter and a tuned receiver (Ref 4), both of which measure the noise power inside this 4-kHz notch. The NPR measurements are straightforward. With the

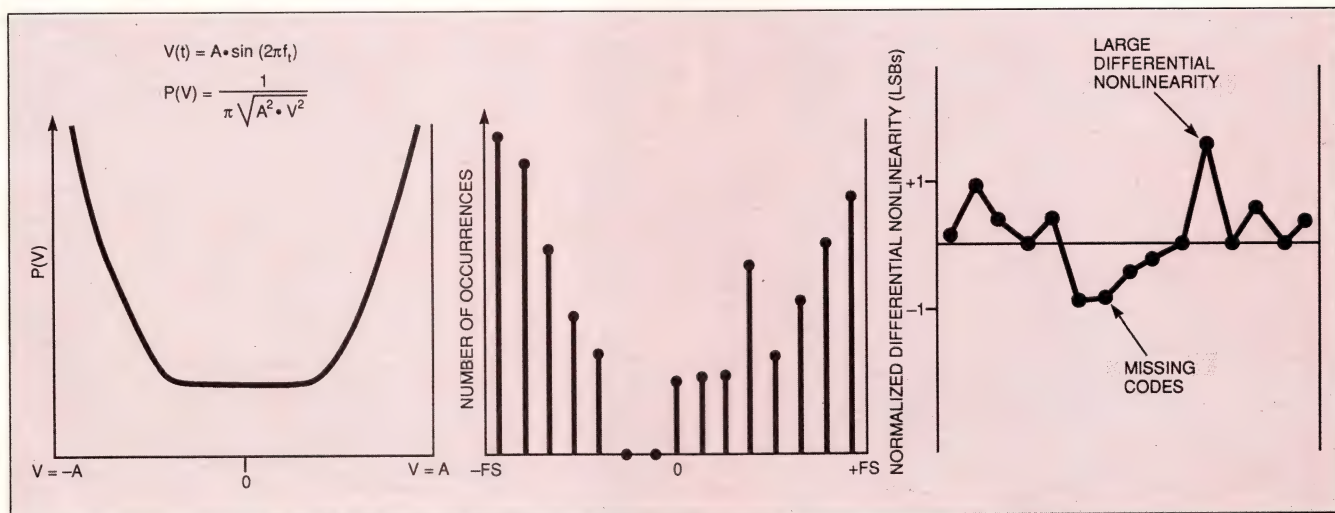

**Fig 2—Histograms are often used to plot differential nonlinearity.** Shown here is a curve for the probability density function of a sine wave, which is used to normalize histogram data to produce a plot of differential nonlinearity.



*Where multiple frequencies exist on a single carrier, you need to measure intermodulation distortion as well as harmonic distortion.*

notch filter out, the receiver determines the rms noise power of the signal inside the notch. The notch filter is then switched in, and the receiver determines the residual noise inside the 4-kHz slot. The ratio of the two readings, expressed in dB, is the NPR. You should test several slot frequencies across the noise bandwidth—low, midband, and high.

The NPR is usually plotted on an NPR curve as a function of rms noise level referred to the peak range of the system. For very low noise levels, the undesired noise is primarily thermal noise and is independent of the input noise level. Over this region of the curve, a 1-dB increase in the noise level causes a 1-dB increase in the NPR. As the noise level increases, the amplifiers in the system begin to overload, creating intermodulation products that cause the noise floor of the system to rise. As the input noise increases further, the effects of overload noise predominate, reducing the NPR dramatically. FDM systems are usually operated at a noise-loading level a few decibels below the point of maximum NPR.

In a digital system containing an A/D converter, the noise within the slot is primarily quantizing noise when low values of noise input signals are applied. The NPR curve is linear in this region. As the noise input level increases, the hard-limiting action of the converter causes clipping noise to dominate.


In a practical A/D converter, any dc or ac nonlinearities cause a departure from the theoretical NPR. Although the peak value of NPR occurs at a fairly low input noise level (rms noise =  $1/4 V_0$ , where  $\pm V_0$  is the range of the A/D converter), the broadband nature of the noise signal stresses the device, and the test provides a good indication of its dynamic performance.

Theoretically, NPR readings should be independent of any particular slot frequency. However, because of increased nonlinearities for the higher input frequencies, the NPR readings in the higher slots tend to be lower.

#### NPR testing using DSP techniques

Using FFT analysis techniques, you'll find NPR measurements a real challenge. Consider the case where the record length is 1024 and the sampling rate is 20 MHz. The FFT of 1024 contiguous time samples would place a spectral component every 19.53 kHz (20 MHz/1024). Because the notch-filter slot width is approximately 4 kHz, the probability of a spectral component falling within the notch is very low.

To achieve reasonable data stability in the FFT NPR analysis, a number of samples must fall within the notch. If ten samples are within the 4-kHz notch, then the resolution of the FFT would need to be 400 Hz, necessitating a record length of 50,000 for a sampling

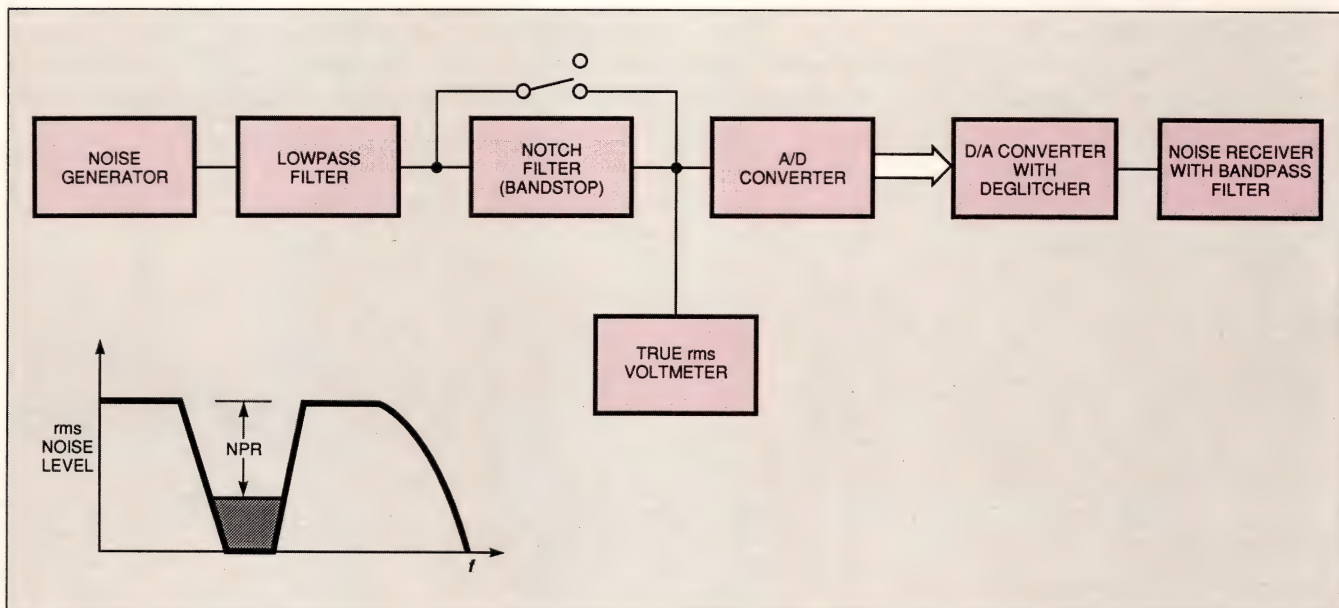

**Fig 3—You can use this test setup to measure noise power ratio (NPR). With the notch filter out, the receiver determines the noise power of the signal inside the notch. With the notch filter switched in, the receiver measures the residual noise inside the typical 4-kHz slot. The ratio of the two readings (in decibels) is the NPR.**



rate of 20 MHz. To avoid an extremely large buffer memory (and hence more demands on the FFT processor), you need to make the notch filter wider. For 20-MHz sampling and a 1024-word buffer memory, a notch filter that has a width of 200 kHz will provide ten frequency bins inside the notch. Even under these conditions, however, you should average the NPR calculations for several records to provide reasonable data stability.

### Transient-response testing

The response of a flash converter to a transient input such as a square wave is often critical in radar applications. The major difficulty in implementing this test is obtaining a flat pulse that's commensurate with the converter's resolution.


A test setup for measuring the transient response of an A/D converter is shown in Fig 4. If you mount the Schottky-diode flat-pulse generator as close as possible to the analog input of the A/D converter, you can apply a signal to the A/D converter that's flat to at least 10-bit accuracy a few nanoseconds after it reverse biases the Schottky diodes.

You can use the same test setup to measure overvoltage recovery time. The amount of overvoltage is generally specified as a percentage of the A/D converter's range. For a converter with a 2V input range, 50% overvoltage corresponds to 1V above or below the nominal 2V input range. You make the starting point of the flat pulse correspond to the desired overvoltage condition. The actual recovery time is referenced to the time the input signal re-enters the A/D-converter

input range. As in the transient-response test, you must consider the sampling (aperture) time delay when making this measurement.

The aperture-time and -jitter specifications of video A/D converters have probably been the least understood and most misused specifications in the entire field. The original concept of aperture time is centered around the classic S/H circuit of Fig 5. In an ideal S/H circuit, the switch has zero resistance when closed and opens instantly on receipt of an encode command. In practice, the sampling switch changes from a low to a high resistance over a certain finite time interval. An error occurs because the circuit tends to average the input signal over the finite time interval required to open the switch. As a result, the sampled voltage varies from the voltage at the instant the switch starts to open. The time required to open the switch is the aperture time. The error is determined by  $E_a = t_a \, dV/dt$ , where  $E_a$  is the aperture error,  $t_a$  is the aperture time, and  $dV/dt$  is the rate at which the input signal changes.


A simple first-order analysis, which neglects non-linear effects, shows that no real error exists for such a switch. As long as the switch opens in a repeatable fashion, there is an effective sampling time that will cause an ideal S/H amplifier to produce the same hold voltage. The difference between this effective sampling point and the leading edge of the sampling clock is a fixed delay, which doesn't constitute an error. This effective aperture delay is the period from the leading edge of the sampling clock to the instant when the input signal equals the hold value. This specification

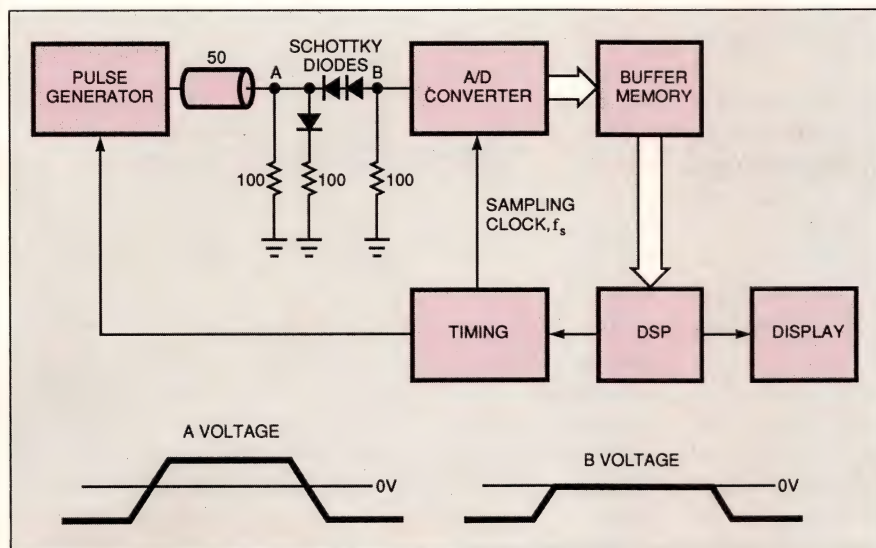

**Fig 4—This test setup measures the transient response of an A/D converter. The Schottky-diode network, located between points A and B in the circuit, generates a flat pulse for the input of the converter.**



*In a practical A/D converter, the spurious-free dynamic range is a function of the converter's slew rate and can occur at a level below full scale.*

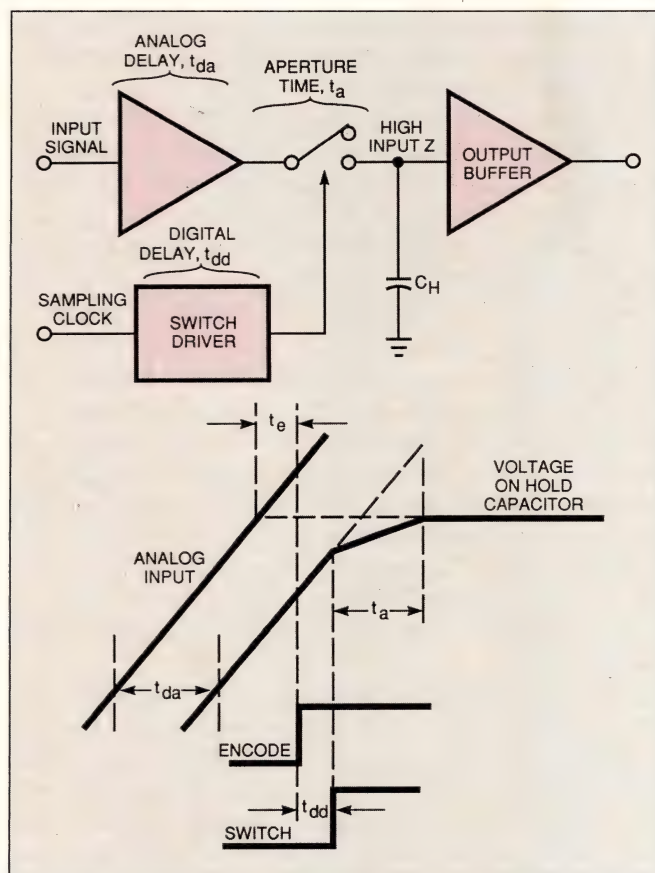

**Fig 5—The concept of aperture time centers around the S/H circuit. In practice, the sampling switch generates an error because of input-signal averaging over the finite time interval needed to open the switch. The aperture time is the time needed to open the switch.**

is important because it helps you determine when to apply the sampling clock with respect to the input signal timing.

The variation in effective aperture delay is important in simultaneous S/H applications. For example, in both I (in-phase) and Q (quadrature) radar receivers you may have to provide adjustable delays in the sampling clock to match the effective aperture delay times of several A/D converters. You should also consider delay-time tracking over a range of temperatures, especially in military systems where the specified operating temperature ranges from  $-55$  to  $+125^{\circ}\text{C}$ .

True aperture errors, however, do result from variable time delays. In a practical A/D converter, the sampling clock is often phase-modulated by some unwanted source; the source can be wideband random noise, power-line frequency, or digital noise due to poor grounding techniques. Phase jitter on the input

sine wave can produce the same effect as jitter on the sampling clock. The resulting error is called aperture jitter. The corresponding rms voltage error caused by the rms aperture jitter qualifies as a valid aperture error.

The aperture-jitter specification is sometimes interpreted as a measure of the converter's ability to accurately digitize rapidly changing input signals. An A/D converter with an impressive aperture-jitter specification still may lose effective bits when digitizing a sine wave that has a maximum slew rate calculated from the aperture formula  $E_a = t_a \, dV/dt$ .

For example, assume that a 20-MHz, 8-bit flash converter has a bipolar input range of  $\pm V_0$  ( $2V_0$  p-p) and an aperture jitter specification of 20 psec rms. To calculate the maximum aperture-jitter error, convert the rms aperture jitter into a maximum value. If you consider that aperture jitter follows a Gaussian distribution similar to white noise, the rms aperture jitter,  $t_a$ , corresponds to the sigma ( $\sigma$ ) of the distribution. The  $2\sigma$  point on the distribution is a good place to set the maximum value, and the maximum aperture jitter becomes is  $2t_a$ .

If the corresponding maximum voltage error ( $\Delta V$ ) at the zero crossing of a full-scale sine wave is set to  $\frac{1}{2}$  LSB ( $\frac{1}{2}$  LSB  $= 2V_0/2^{N+1}$ , where  $N$  equals the resolution of the A/D converter), then you can calculate the maximum full-scale sine-wave frequency,  $f_{\text{max}}$ , which will produce the  $\frac{1}{2}$  LSB aperture error, by using the following equations:

$$V(t) = V_0 \cdot \sin(2\pi f t),$$

$$\frac{dV}{dt} = 2\pi f V_0 \cdot \cos(2\pi f t),$$

$$\left. \frac{dV}{dt} \right|_{\text{max}} = \frac{\Delta V}{2t_a} = 2\pi V_0 f_{\text{max}}, \text{ and}$$


$$f_{\text{max}} = \frac{\Delta V}{4\pi V_0 t_a} = 2\pi t_a \cdot 2^{N+1}.$$

For  $t_a = 20$  psec rms and  $N = 8$ ,  $f_{\text{max}}$  is 16 MHz. These calculations imply that a 20-MHz flash converter can accurately digitize a full-scale sine wave of 16 MHz. In actual practice, however, the device may begin to suffer from skipped codes, decreased effective bits and S/N ratio, and ac nonlinearities at much lower frequencies.

You can calculate the effects of aperture jitter on



# **SPEED** **DEVELOPMENT**

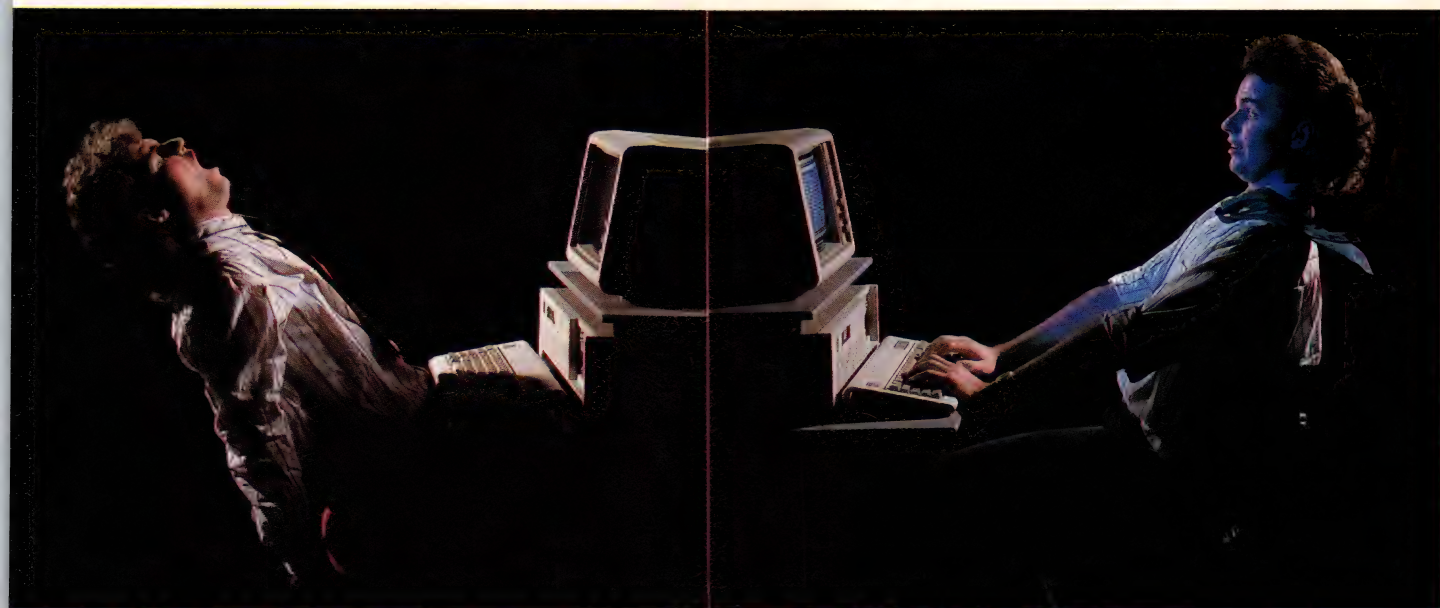

## **VSDS** the Power to Perform

At Stag we figured that microprocessor software development should be exciting rather than a chore.

Which is why we insure our Versatile Software Development System (VSDS) will produce code for all popular processors and fast – very fast.

So much so it makes other development methods appear positively uninspiring.

A view which is shared by EDN and contained in an independent article, June 8, 1989.

Being a truly integrated system, VSDS so outdistanced the competition it leaves people asking . . . what competition?

So if you would like to read what they said, just call us Toll Free at (800) 222-STAG (East) or (800) 227-8836 (West) and we'll send you a copy.

At the same time you might like to discuss your particular application with one of our engineers who will explain precisely where VSDS really scores.

You'll quickly discover what life is like back in the fast lane – which is where you'll want to stay.

CIRCLE NO. 54

**Versatile Software**  
**VSDS**  
**Development System**

West Coast:  
1600 Wyatt Dr, Santa Clara, CA 95054  
Tel: (408) 988-1118 Fax: (408) 988-1232

East Coast:  
3 Northern Blvd, Amherst, NH 03031  
Tel: (603) 673-4380 Fax: (603) 673-1915

**stag**  
microsystems





*Histograms are useful in evaluating the differential nonlinearity of an A/D converter.*

the full-scale sine-wave S/N ratio as follows:

$$V(t) = V_0 \cdot \sin(2\pi f t),$$

$$\frac{dV}{dt} = 2\pi f V_0 \cdot \cos(2\pi f t), \text{ and}$$

$$\frac{dV}{dt}_{\text{rms}} = \frac{2\pi f V_0}{\sqrt{2}}.$$

For an rms error voltage,  $\Delta V_{\text{rms}}$ , and an rms aperture jitter of  $t_a$ ,

$$\frac{\Delta V_{\text{rms}}}{t_a} = \frac{2\pi f V_0}{\sqrt{2}}, \text{ and}$$

$$\Delta V_{\text{rms}} = \frac{2\pi f V_0 t_a}{\sqrt{2}}.$$

The rms-signal to rms-noise ratio, expressed in decibels, is


$$\begin{aligned} \text{S/N ratio} &= 20 \log \left[ \frac{V_0/\sqrt{2}}{\Delta V_{\text{rms}}} \right] \\ &= 20 \log \left[ \frac{1}{2\pi f t_a} \right] \text{ dB.} \end{aligned}$$

The S/N ratio that's due exclusively to aperture jitter in the above equation is plotted in Fig 6 as a function of the full-scale input-sine-wave frequency for various values of aperture jitter.

Consider an 8-bit, 20-MHz A/D converter with an rms aperture jitter of 20 psec. For an 8-MHz full-scale input, the S/N ratio due only to aperture jitter is 60 dB, as calculated from the equation. The theoretical S/N ratio due to quantizing noise in an 8-bit flash converter is 50 dB. When you combine the S/N ratio of 60 dB with the S/N ratio of 50 dB, you obtain a theoretical S/N ratio of 49.6 dB, which encompasses both the ideal quantizing noise and the noise due to aperture jitter. A practical 8-bit device that has an rms aperture-jitter specification of 20 psec may, however, only achieve an S/N ratio of 40 dB under these conditions.

Therefore, to accurately evaluate the A/D converter's dynamic performance, you must carefully examine the S/N ratio, effective number of bits, and aperture-jitter specifications.

Try measuring the aperture jitter of an A/D converter using the test setup shown in Fig 7. The low-

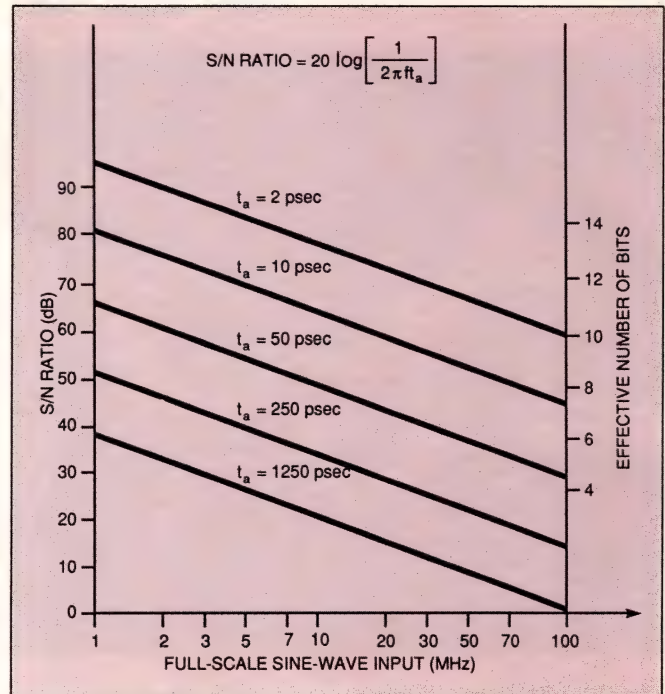

**Fig 6—This plot compares the S/N ratio to the full-scale sine-wave input frequency for various values of aperture jitter.**

jitter pulse generator produces both the sampling clock and the analog input signal to minimize the phase jitter between them. Adjust the phase shifter until the A/D converter repetitively samples the sine wave at its point of maximum slew rate at midscale. Then take a histogram on the digitized A/D-converter output data.

An ideal A/D converter with no aperture jitter would have only one code present on the histogram. A practical converter gives a distribution of codes that you can fit to the normal distribution. The sigma ( $\Sigma$ ) of the distribution corresponds to the rms error voltage,  $\Delta V_{\text{rms}}$ , produced by the rms aperture jitter. Calculate the aperture jitter,  $t_a$ , from the formula

$$t_a = \frac{\Delta V_{\text{rms}}}{\frac{dV}{dt}}$$

where  $dV/dt$  is the rate-of-change of the sine wave at zero crossing.


If you sufficiently attenuate the input sine wave, any spreading of the distribution around the nominal code is due to intrinsic A/D-converter noise. As the input sine wave increases in amplitude, the slew rate,  $dV/dt$ , becomes proportionally greater, and the distri-



# OPEN SYSTEMS::OPEN TOOLS™
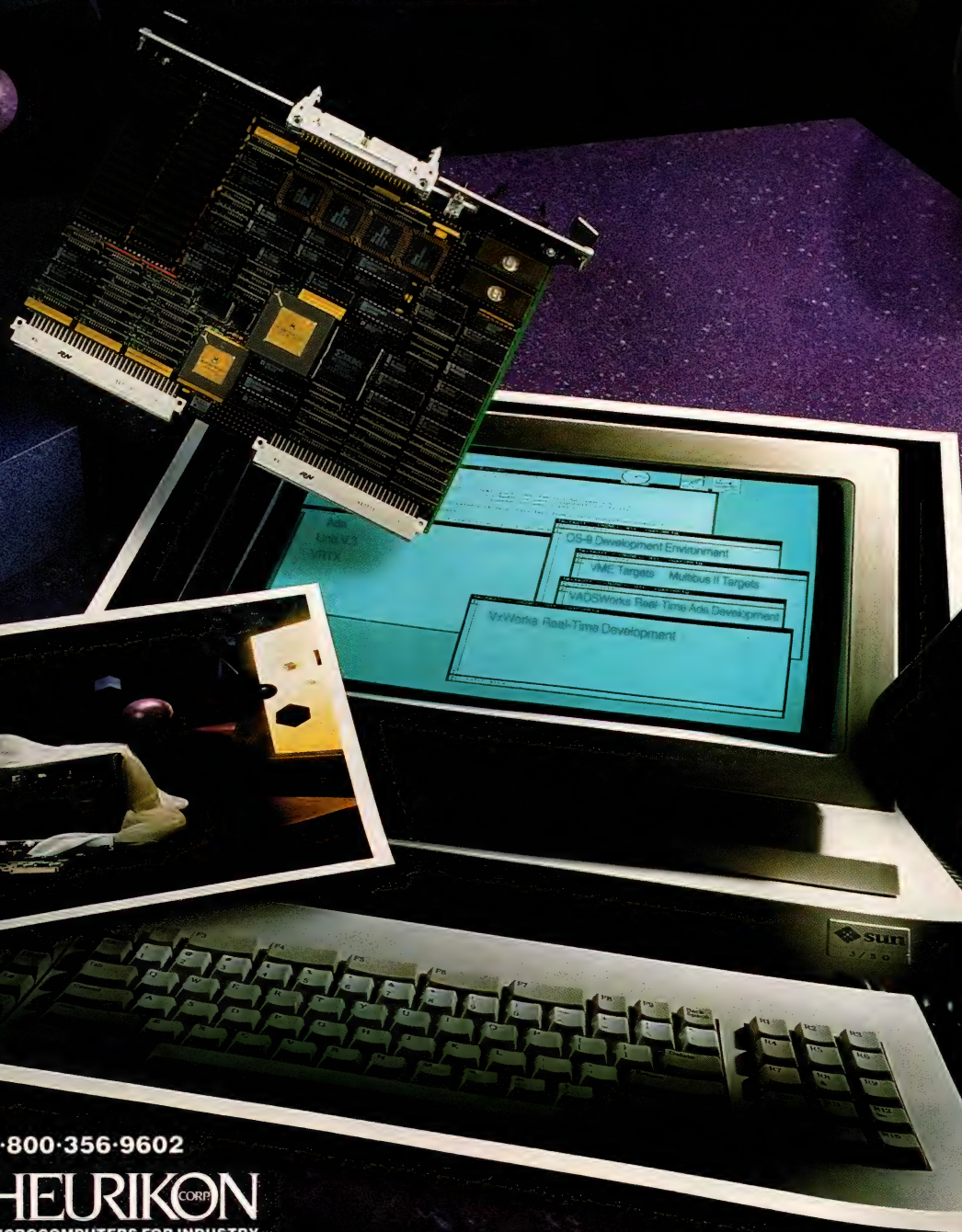
## MAXIMUM POWER FOR REAL-TIME DEVELOPMENT

Whether over the backplane or network, Heurikon has your VME and Multibus targets. VxWorks • VADSWorks • OS-9 • VRTX • Ada • Unix V.3 • Network solutions • Just a few of the Open Tools™ Heurikon has to speed your application to market. Call now for real-time response.



1-800-356-9602

**HEURIKON**  
CORP.  
MICROCOMPUTERS FOR INDUSTRY

VxWorks is a trademark of Wind River Systems, Inc. VADSWorks is a trademark of Wind River Systems, Inc. and Verdex Corporation. VRTX is a trademark of Ready Systems, Inc. OS-9 is a trademark of MicroWare Systems, Inc. Unix is a trademark of AT&T Bell Laboratories, Inc. Multibus is a trademark of Intel Corporation. Open Systems, Open Tools is a trademark of Heurikon Corporation. Open Tools is a trademark of Heurikon Corporation.



---

*Noise-power-ratio tests are useful in determining the transmission characteristics of frequency-division-multiplexed communications links.*

---

bution begins to spread because of the aperture jitter. Because high slew rates can affect the ac differential linearity of the converter, you should exercise caution when interpreting the histogram for high slew-rate inputs.

The offset adjustment shown in Fig 7 lets you position the sine wave at different points on the A/D-converter range. In this way, you can see variations attributed to range-dependent differential-linearity characteristics. When offsetting the sine wave, make sure you don't exceed the A/D converter's input range.

It's also possible to measure effective aperture delay by using the locked-sine-wave technique. Adjust the phase shifter until the output reads midscale. Use a dual-trace scope to determine the difference between the leading edge of the sampling-clock pulse and the actual zero crossing of the sine-wave input. This difference is the effective aperture delay, which can be either negative or positive, depending on the values of the internal analog and digital delays in the S/H portion of the A/D converter.

At present, no industry standard exists for either the definition or the test for A/D-converter error rates. In flash converters, comparator metastable states can occur for low- or high-frequency input signals. At high frequencies, bubbles in the thermometer code of the comparator-bank output can also produce erroneous output codes.

Because error rates less than  $1 \times 10^{-16}$  are typical for well-behaved A/D converters, you need to take a large number of samples to properly measure the error rate. You must also take great care in the test-set

layout, grounding, shielding, and power-supply decoupling so that 60-Hz, EMI, or RFI glitches don't create erroneous errors.


Use the circuit in Fig 8 to measure the error rate for low-frequency input signals. Apply a low-frequency, full-scale sine wave (or triangle wave) to the A/D converter so that its rate of change is less than 1 LSB/sample. This step ensures that the transition zones between codes are all adequately exercised. An error amplitude of X LSBs is established as the lower limit for the definition of a qualified error. Usually, you select X to be several LSBs so that random noise doesn't produce errors. The software or hardware then examines the difference between each adjacent sample and records the number of times this difference exceeds the error threshold, X. If NQ is the number of qualified errors that occur, and NT is the total number of samples taken, then the error rate, ER, is given by the equation  $ER = NQ/2 \cdot NT$ .

As an example, consider an 8-bit, 100M-sample/sec flash converter designed to take at least ten samples at each code level. For one slope of the triangle-wave input, the number of samples required is  $10 \times 256 = 2560$  samples. The frequency of the triangle wave is

$$f_t = \frac{1}{2560 \cdot 2 \cdot 10 \text{ nsec}} = 19.5 \text{ kHz.}$$

At a 100-MHz sampling rate, the average time required to make an error for an error rate of  $1 \times 10^{-9}$  is 10 seconds.


**Fig 7—In this test setup for measuring aperture jitter, you adjust the phase shifter until the A/D converter repetitively samples the sine wave at its point of maximum slew rate. You then take a histogram of the digitized A/D-converter output data. The offset adjustment lets you position the sine wave at different points on the converter's range.**

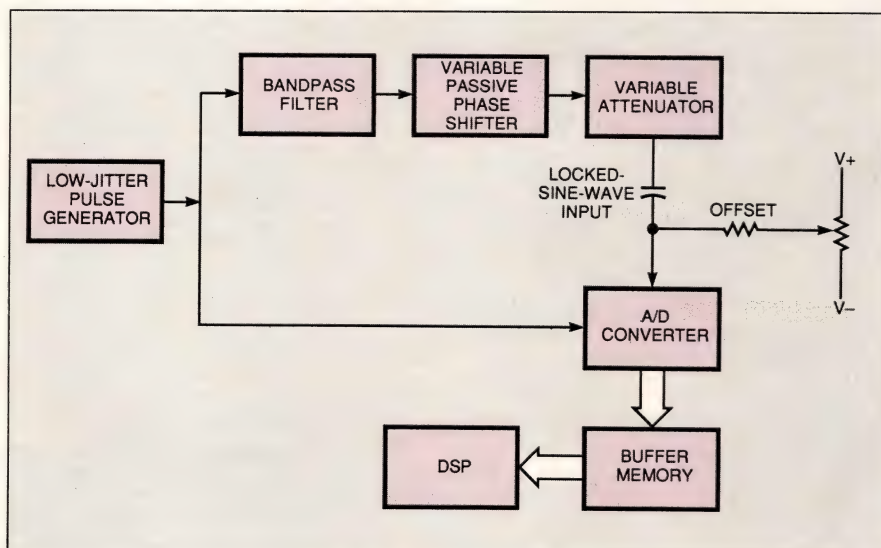



# SOLUTIONS IN PERFECT PROPORTION

F R O M E P S O N O E M

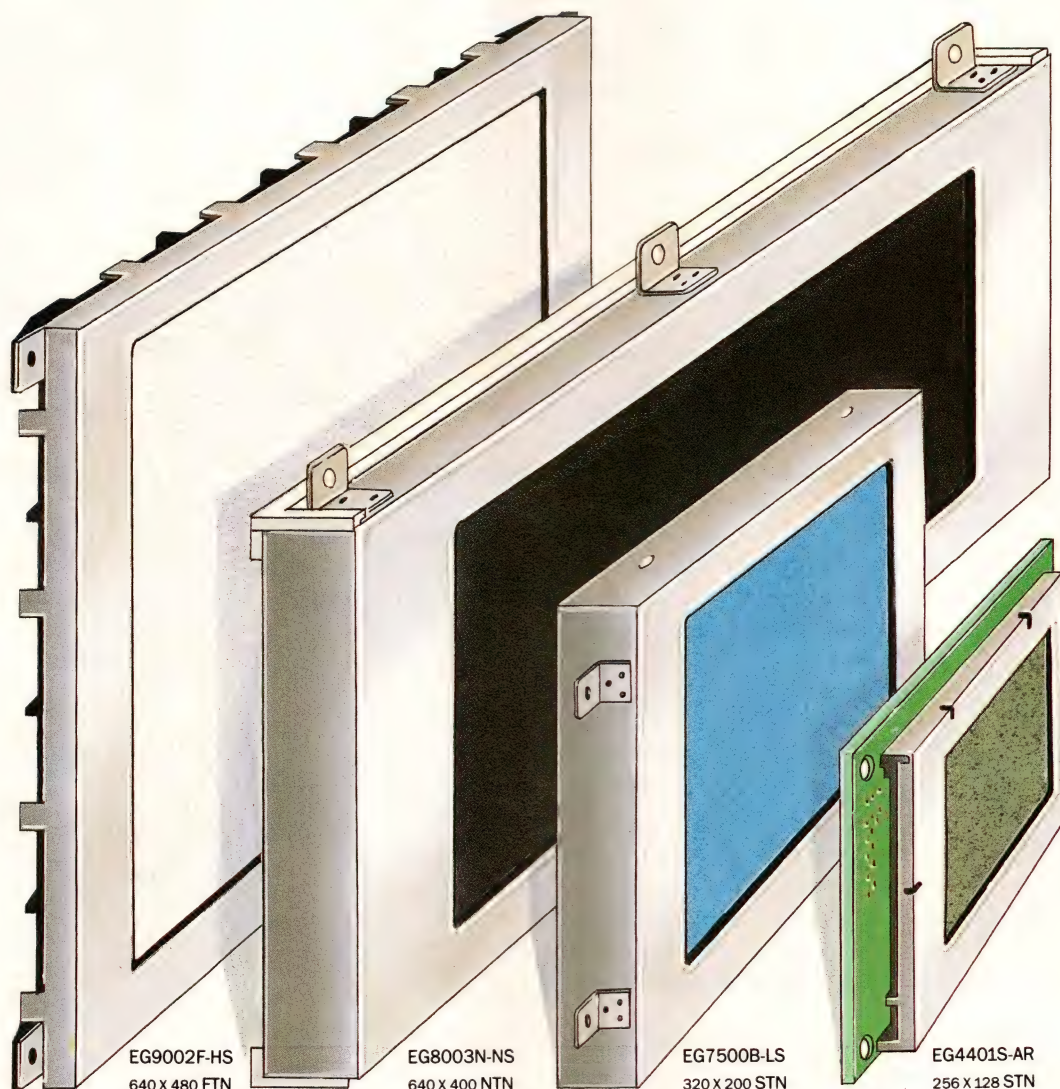

From large VGA resolution **L C D M O D U L E S** to small alphanumeric displays, Epson has a solution in perfect proportion for your newest product application. The EG series of graphics display panels are available in 92 configurations ranging from 640X480 dots to 128X64 dots. A choice of super-twisted STN, page-white NTN or the latest in single film FTN technologies provides high-contrast and wide-angle viewing that rival the more traditional CRT. The popular EA-D series of alphanumeric modules come in 8 sizes from two lines of 40 characters to one line of 16 characters with a choice of EL or LED backlighting. Featuring low power consumption and unique chip-on-flex drivers in a compact, lightweight design Epson LCDs are ideal for applications ranging from handheld and lap- and telecommunications terminals. For additional product information and detailed specifications, please contact your nearest Epson OEM sales office.

San Francisco 408/257-6730 ■ Los Angeles 714/768-7474 ■ Chicago 815/455-7630 ■ Atlanta 404/552-1150  
Boston 617/245-8007 ■ Vancouver 604/421-8008 ■ Toronto 416/479-8866 ■ Montreal 514/331-7534

Visit us in Booth 111 at Systems USA


CIRCLE NO. 56



---

## Aperture time and aperture jitter for A/D converters are probably the most misunderstood and misused specifications.

---

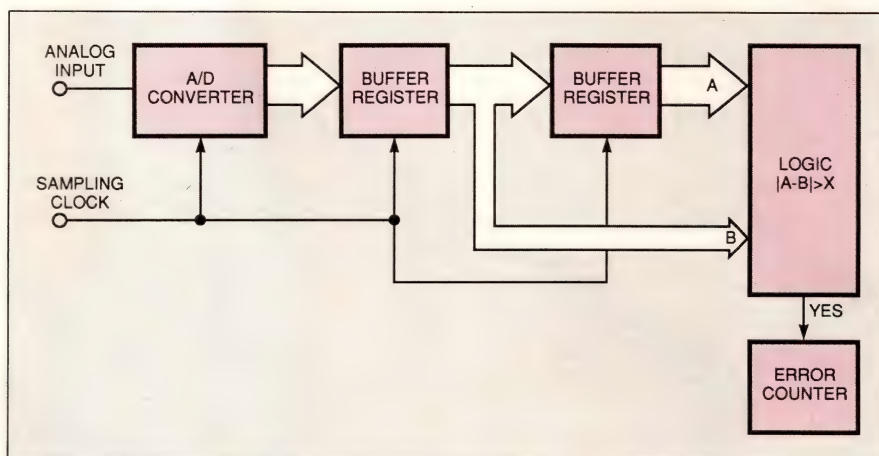

**Fig 8**—The effective aperture delay is the time difference between the leading edge of the sampling-clock pulse and the actual zero crossing of the sine-wave input.

In a similar manner, you can measure dynamic errors caused by fast input signals by using the beat-frequency approach. You choose the low-frequency beat frequency to give the proper number of samples per code level, and then you examine the decimated digital outputs for adjacent sample differences that exceed the allowable error amplitude.

In summary, determining appropriate error-rate criteria for an A/D converter depends upon both the application and the characteristics of the converter under consideration. Flash converters that use straight binary decoding with no additional correction logic are most subject to large metastable errors at midscale. For this situation, a low-amplitude dither signal centered on the midscale code transition might be an appropriate stimulus. In a more well-behaved flash converter, a full-scale signal that exercises all codes might be desirable.

If you plan to digitize composite video signals, you'll need to measure the differential-gain and -phase performance of the flash A/D converter. Differential gain is the percentage difference between the digitized amplitudes of two signals. Likewise, differential phase is the phase difference between the digitized values of the same two input signals. The input signals are typically a high-frequency low-level sine wave representing the color subcarrier frequency, superimposed on a low-frequency sine wave. Distortion-free processing of the color signal requires that the flash converter alters neither the amplitude nor the phase of the chrominance signal as a function of the luminance-signal level.

The best method for performing composite video tests is to use an A/D converter back-to-back with a D/A converter. Connect a TV test signal to the A/D converter and use the output of the D/A converter to drive a vectorscope. To ensure that the test accurately

measures the A/D converter's performance, use a low-glitch D/A converter followed by a track-and-hold deglitcher. In addition, the dc accuracy of the D/A converter should exceed that of the A/D converter. When testing an 8-bit flash converter, use a D/A converter with at least 10 bits of accuracy.


**EDN**

## References

1. Andrews, James R, Barry A Bell, Norris S Nahman, and Eugene E Baldwin, "Reference Waveform Flat Pulse Generator," *IEEE Transactions on Instrumentation and Measurement*, Vol IM-32, No. 1, March 1983, pg 27.
2. Schoenwetter, Howard K, "A Programmable Voltage Step Generator for Testing Waveform Recorders," *IEEE Transactions on Instrumentation and Measurement*, Vol IM-33, No. 3, September 1984, pg 196.
3. Gray, G A, and G W Zeoli, "Quantization and Saturation Noise Due to Analog-Digital Conversion," *IEEE Transactions on Aerospace and Electronic Systems*, January 1971, pg 222.
4. Tant, M J, *The White Noise Book*, Marconi Instruments, July 1974.
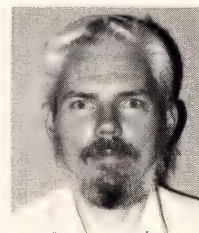
## Author's biography

Walt Kester is a technical-support manager for the Computer Labs division at Analog Devices. Walt has been with the company for 20 years and supports the development of high-speed ADCs, DACs, S/H amplifiers, and op amps. He has a BSEE from North Carolina State University and an MSEE from Duke University. In his spare time, Walt enjoys carpentry and travel.



---

Article Interest Quotient (Circle One)  
High 497 Medium 498 Low 499



**Signetics 68070**  
**Moto dives into RISC chip pool**  
 NEW YORK—Motorola finally takes its plunge into the RISC pool today, announcing its long-awaited 68070 chip set. More than 100 semiconductor manufacturers are expected to find a place in the computer and workstation world. Major system companies are pushing the RISC theme with own architectures, shutting the door on standard products.

**Advanced Micro Devices positions its 29K for the embedded micro market**  
 AMD, with its new 29000 microprocessor, is probably the most recent entrant in the embedded micro market.

**Intel unveils long-awaited 80386SX micro now supported by fast coprocessor control chip**  
 Intel Corp. of Santa Clara unveiled on Thursday its long-anticipated 'P-9' computer chip, which will create less expensive personal computer systems that run more sophisticated software. Introduction of the new 80386SX chip, which analysts say eventually will supplant Intel's widely used 80286 chip as the "brain" of certain IBM PC and compatible computers, essentially is a marketing move that allows computer makers to offer lower-cost alternatives in their high-powered 80386-based product line.

For example, prices of computers—like the IBM 80286—range from \$4,500. Systems based on the IBM Model 701 chip—start at about \$10,000. The 80386SX, although more powerful, is all the software of the 80286. The new chip also will support 8086 software, Intel said. While analysts said they expect National Semiconductor's NS32532 microprocessor has a dedicated math coprocessor (the NS32381), its 1-MFLOPS floating-point calculation speed is deemed too slow for many tasks. To meet speed demands, National came up with the NS32580, a dedicated coprocessor-control chip that ties Weitek's WTL3164 fast floating-point data path in the 32-bit 32532 microprocessor. The combination yields a peak floating-point performance of 15 MFLOPS for single- and double-precision tasks.

## Now, what about the other 95% of your design?

### Signetics We've got the guts!

It takes more than a microprocessor to improve product performance.

At Signetics, we haven't developed proprietary MPUs. Instead we've concentrated on the other 95% of your system. We call it "the guts."

That's why we're known as your dependable, worldwide supplier of quality ICs. Producers of devices that are processed with leading-edge technology and supported with customer-oriented service.

We provide everything essential to the total performance of your design. And we make it easy for you to get it. From one vendor. In less time. With less paperwork. For less cost.

We're Signetics. We've got the guts! Make us prove it. Call (800) 227-1817, ext. 982D and ask for our new capabilities brochure.

© 1988 NAPC


**Signetics**

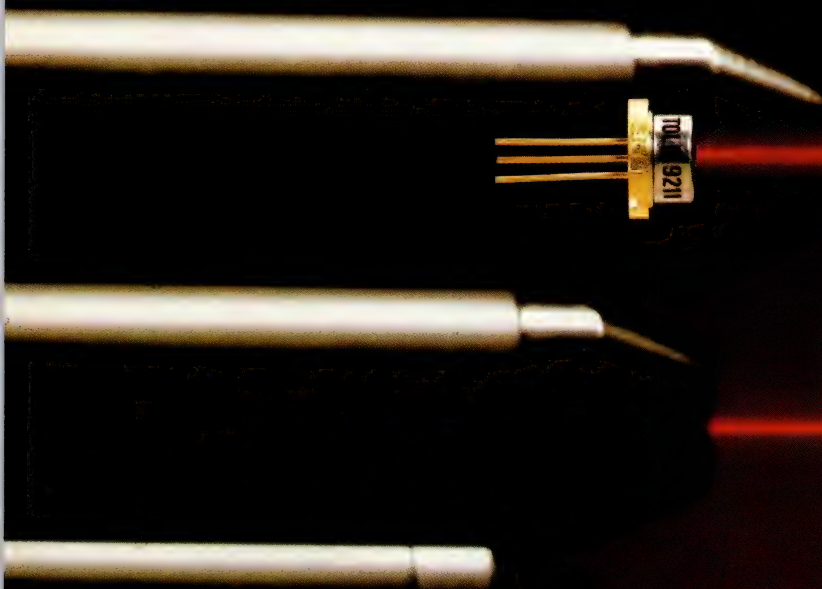**Philips Components**





*"You can see why we chose 670nm index-guided visible laser diodes."*



HSD series "Spot"™ collimated laser sources, Holo-Spectra, Inc. Van Nuys, CA  
Laser Beam is artist's representation.

ALABAMA, Marshall Electronics Group, (205) 881-9235, Milgray Electronics, Inc., (404) 393-9666, Repton Electronics, (404) 446-1300; ARKANSAS, Marshall Electronics Group, (214) 233-5200, Milgray Electronics, Inc., (214) 248-1603, Sterling Electronics-Dallas, (214) 243-1600; ARIZONA, Marshall Electronics Group, (602) 496-0290, Sterling Electronics-Phoenix, (602) 268-2121; CALIFORNIA, Sterling/Image Electronics, (619) 271-6555, (714) 259-0900, (818) 407-8850, Marshall Electronics Group, (818) 407-0101, (714) 458-5395, (408) 942-4600, (916) 635-0700, (619) 578-9600, Mart Electronics, Inc., (408) 434-0800, Western Microtechnology, (619) 453-8430, (714) 637-0200, (408) 725-1660, (818) 707-0377; COLORADO, Marshall Electronics Group, (303) 451-8383, Sterling Electronics-Denver, (303) 792-3939; CONNECTICUT, Cronin Electronics, Inc., (203) 265-3134, Marshall Electronics Group, (203) 265-3822, Milgray/Milford (203) 878-5538, Sterling Electronics-Wallingford, (203) 265-9535; DELAWARE, General Components, Inc., (609) 768-6767, Marshall Electronics Group, (301) 840-9450, Milgray/Delaware Valley, Inc., (609) 983-5010, (800) 257-7808, (800) 257-7111, Sterling Electronics-Sterling, (703) 450-2373; DISTRICT OF COLUMBIA, Marshall Electronics Group, (301) 840-9450, Milgray/Washington, Inc., (301) 621-8169, (800) 638-6666, Sterling Electronics-Sterling, (703) 450-2373; FLORIDA, Marshall Electronics Group, (813) 570-1399, (305) 977-4880, (305) 757-8585, Repton Electronics-Tampa, (813) 855-4656, (305) 735-1112; GEORGIA, Marshall Electronics Group, (404) 923-5750, Milgray Electronics, Inc., (404) 446-9177, Repton, (404) 446-1300; IDAHO, Marshall Electronics Group, (801) 485-1551, Western Microtechnology, (509) 629-2082, Milgray Electronics, Inc., (801) 272-4999; ILLINOIS, Gould Electronics, (312) 860-7171, Marshall Electronics Group, (312) 480-0155, (314) 291-8554, Milgray Electronics, Inc., (913) 236-8800, (312) 350-0490; INDIANA, Gould Electronics, (312) 593-3220, Marshall Electronics Group, (317) 297-0483, Milgray/Chicago, Inc., (312) 350-0490; IOWA, Marshall Electronics Group, (612) 559-2211, Milgray Electronics, Inc., (913) 236-8800; KANSAS, Marshall Electronics Group, (913) 492-3121, Milgray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 492-5406; KENTUCKY, Marshall Electronics Group, (513) 898-4460, Milgray/Cleveland, Inc., (216) 447-1520, (800) 321-0006; LOUISIANA, Marshall Electronics Group, (214) 233-5200, Milgray Electronics, Inc., (214) 248-1603, Sterling Electronics-Dallas, (214) 243-1600; MAINE, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 858-0810, Sterling Electronics-Boston, (617) 938-6200, Western Microtechnology, (617) 938-6200; MICHIGAN, Marshall Electronics Group, (313) 525-5850, Repton Electronics, Inc., (313) 525-2700; MINNESOTA, Marshall Electronics Group, (612) 559-2211, Repton Electronics, (612) 938-0000, Sterling Electronics, (612) 851-2666; MISSISSIPPI, Marshall Electronics Group, (205) 881-9235, Milgray Electronics, Inc., (404) 393-9666; MISSOURI, Marshall Electronics Group, (913) 492-3121, (314) 291-8554, Milgray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 236-5589; NEBRASKA, Marshall Electronics Group, (913) 492-3121, Milgray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 236-5589.



***"I see the Toshiba index-guided VLD reduces astigmatism —by up to two-thirds."***

***"And with a simpler collimating lens system and no auxiliary light source necessary, it optimizes design and reduces cost."***

***"But is this 670nm diode a prototype?"***

***"No way. Our shipment of these new Toshiba Laser Diodes is in the stock room right now."***



Move over, gain-guided VLDs and IRLDs. Toshiba has the first index-guided visible laser diode, the TOLD 9211, in production today. And what a difference it makes.

The TOLD 9211 has the lowest astigmatism of any 670nm visible laser diode. In fact, index guiding cuts astigmatism by over 67%, dramatically reducing the complexity and cost of a collimating lens. Output power is increased by 67% to 5mW, giving you a brighter red color at 670nm. Higher density and greater visibility even makes color code and thermal printed code reading possible. And that opens up a whole world of applications, from portable scanners to precision measuring and survey instruments to laser printers.

Threshold current has been reduced to just 50mA so you get top performance with a smaller power supply—even battery operated. And the clearly visible light eliminates the need for an LED aiming beam. So no matter what your application, it'll come in smaller, lighter and less costly to produce.

The solid state construction of the TOLD 9211 makes it more durable and less susceptible to shock. It has life expectancy of over 100,000 hours and the TOLD 9211 can be operated at temperatures of up to 50°C. Plus you're assured of the consistently high level of reliability you've come to expect of Toshiba, the company that was first to develop the visible laser diode, and first to deliver it to you in volume quantities.

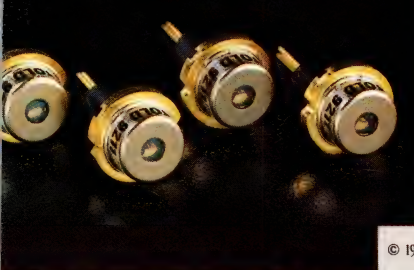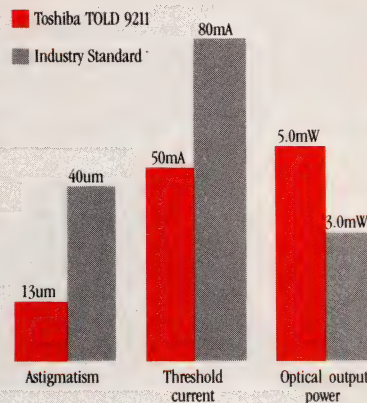See for yourself the difference that index guiding can make. For technical literature on the Toshiba TOLD 9211, call 1-800-888-0848 ext. 517 today. *Service is our key component.*



In Touch with Tomorrow  
**TOSHIBA**

**TOSHIBA AMERICA ELECTRONIC COMPONENTS, INC.**

© 1989 Toshiba America Electronic Components, Inc.

SPD-89-019

Milgray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 236-5589; **NEVADA**, Marshall Electronics Group, (916) 635-9700, (602) 496-0290, Sterling Electronics, (602) 268-2121, Western Microtechnology, (408) 725-1660; **NEW HAMPSHIRE**, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 658-0810, Sterling Electronics-Boston, (617) 938-6200, Western Microtechnology, (617) 273-2800; **NEW JERSEY**, General Components, Inc., (609) 768-6767, Marshall Electronics Group, (201) 882-0320, (609) 234-9100, Milgray Electronics, Inc., (516) 420-9800, Sterling Electronics-So. Plainfield, (201) 769-7000; **NEW MEXICO**, Marshall Electronics Group, (602) 496-0290, Sterling Electronics-Albuquerque, (505) 884-1900; **NEW YORK**, Marshall Electronics Group, (516) 273-2424, (607) 738-1611, (716) 235-7620, Milgray Electronics, Inc., (516) 420-9800, (716) 235-0830, Rome Electronics, (315) 337-5400; **NORTH/SOUTH CAROLINA**, Marshall Electronics Group, (919) 878-9882, Milgray Electronics, Inc., (404) 393-9666; **NORTH/SOUTH DAKOTA**, Marshall Electronics Group, (612) 559-2211, Repron Electronics, (612) 938-0000; **OHIO**, Marshall Electronics Group, (513) 888-4480, (216) 248-1788, (614) 891-7580, Milgray/Cleveland, Inc., (216) 447-1520, (800) 321-0006, Repron Electronics, (814) 436-6675, (216) 349-1415; **OKLAHOMA**, Marshall Electronics Group, (214) 233-5200, Milgray Electronics, Inc., (214) 248-1603, Sterling Electronics-Tulsa, (918) 863-2410; **OREGON**, Marshall Electronics Group, (503) 644-5050, Western Microtechnology, (503) 629-2082; **PENNSYLVANIA**, General Components, Inc., (609) 768-6767, Marshall Electronics Group, (609) 234-9100, (412) 963-0441, Milgray/Cleveland, Inc., (216) 447-1520, (800) 321-0006, Milgray/Delaware Valley, Inc., (609) 983-5010, (800) 257-7808, (800) 257-7111; **RHODE ISLAND**, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 938-6200, Western Microtechnology, (617) 273-2800; **TENNESSEE**, Marshall Electronics Group, (205) 881-9235, Milgray Electronics, Inc., (404) 393-9666; **TEXAS**, Marshall Electronics Group, (214) 233-5200, (915) 583-0706, (713) 895-9200, (512) 837-1891, Milgray Electronics, Inc., (214) 248-1603, Sterling Electronics, (713) 623-6600, (512) 836-1341, (214) 243-1600, Western Microtechnology, (214) 248-3775; **UTAH**, Marshall Electronics Group, (801) 485-1551, Sterling Electronics, (801) 972-5488; **VERMONT**, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 658-0810, Sterling Electronics-Boston, (617) 938-6200, Western Microtechnology, (617) 273-2800; **VIRGINIA**, Marshall Electronics Group, (301) 840-9450, Milgray/Washington, Inc., (301) 621-5189, (800) 638-6656, Sterling Electronics, (703) 742-9400, (804) 226-2180; **WASHINGTON**, Marshall Electronics Group, (206) 458-5747, Western Microtechnology, (206) 881-6737; **WISCONSIN**, Gould Electronics, (312) 593-3220, Marshall Electronics Group, (414) 797-8400, Milgray/Chicago, Inc., (312) 350-0490, Marsh, (414) 475-6000, Repron Electronics, (612) 938-0000; **CANADA**, Marshall Electronics Group, (416) 458-0406, ITT Multicomponents, (604) 291-8666, (403) 253-8575, (204) 786-8401, (416) 736-1144, (613) 226-7406, (514) 335-7679, (902) 465-2350, Active Components, (514) 697-8676, (416) 638-8814, (613) 596-5340, (604) 294-1166.



***The last thing you need from your  
DC/DC converter is a surprise!***






# The Magic Module™ — the ultimate in proven performance, power capability, size and features...

When designing a DC/DC converter into your system, you want the assurance that a surprise is not going to pop up. With Electronic Measurements' EMQ Series of Magic Modules, you have the assurance of dependable performance, since the design incorporates proven fixed frequency, forward converter technology with current mode control and a nominal frequency of 250 kHz. Another good reason to choose the Magic Module is size. The EMQ series also offers the highest power rating for any self contained 5-V output, high density, board mounted unit available.

For example, the EMQ48-05-40, rated at 200 W, occupies a footprint of only 2.4" x 4.6" with a 0.625" profile, and a nominal input of 48VDC.

For a pleasant surprise, check these MAGIC MODULES features:

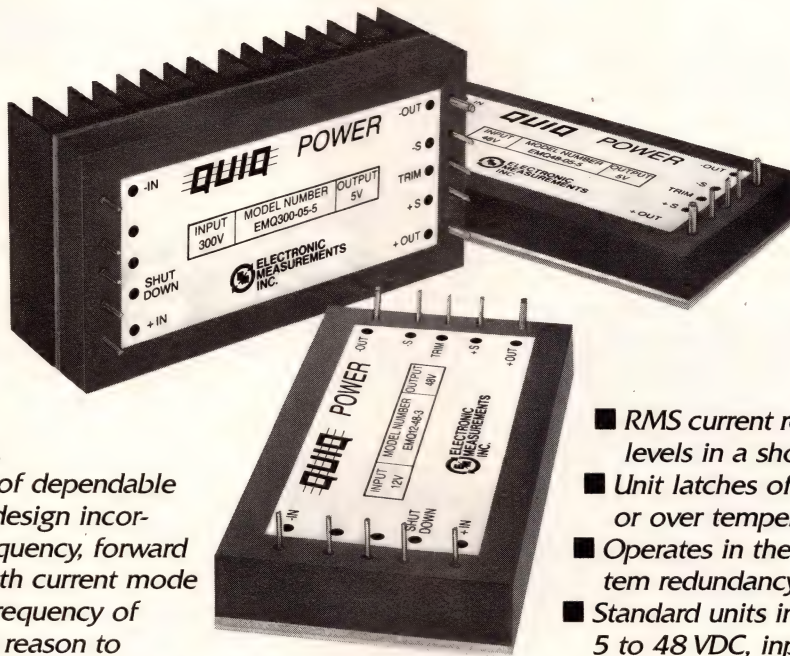- More watts per cubic inch than any other 40 Amp. converter
- Forward converter topology for proven reliability




- Fixed frequency (250 KHz) for EMI reduction and stability
- 6 sided RFI shielding available

- RMS current reduced to negligible levels in a short circuit mode
- Unit latches off in an overvoltage or over temperature condition
- Operates in the N+1 Mode for system redundancy
- Standard units include outputs from 5 to 48 VDC, inputs from 10 to 300 VDC, 50 to 200 Watts power out

- Thermal characteristics allow for PC board mount with only natural connection up to 50 watts

Best of all, you have the assurance that THE MAGIC MODULE comes from Electronic Measurements, a company with over 40 years of power conversion experience.

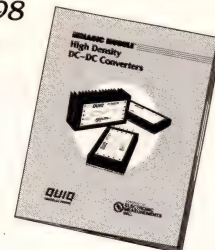THE MAGIC MODULE brochure is yours for the asking. If you need information immediately, call TOLL FREE 1-800-631-4298 (In NJ, HI, AL and Canada 201-922-9300).



A PRODUCT OF

## ELECTRONIC MEASUREMENTS INC.

405 Essex Road, Neptune, NJ 07753 • CALL TOLL FREE 800-631-4298 • Fax: 201-922-9334  
(In NJ, Alaska, Hawaii & Canada Call: 201-922-9300)



# News from Philips



THE COMPLETE COMPONENT COMPANY

Philips Components  
5600 MD Eindhoven  
The Netherlands

## Philips enters SRAM market with ultra-low-power 64-kbit CMOS SRAMs

Philips Components is entering the byte-wide SRAM market with a high performance 8kx8 CMOS device offering ultra low-power consumption down to 1  $\mu$ A both in 5 V standby and in the battery backup mode ( $V_{dd} = 3$  V). Access times range from 55 ns to 70 ns. The 8kx8 CMOS SRAM is fully pin-compatible with devices presently on the market.



Philips Components' 64 kbit SRAMs suit many demanding applications.

The new devices are manufactured in MOS-3, Europe's most advanced wafer fab based in Nijmegen, the Netherlands. The 1.2  $\mu$ m, double-metal technology together with the full-CMOS six-transistor cell design account for the very low power consumption, very low sensitivity to alpha particles and wide operating temperature range. The FCB61C65 operates from a single 5 V supply; inputs


and outputs are directly TTL- and CMOS-compatible. Two chip-enable pins are provided for maximum flexibility, easy memory expansion and controlling the standby mode. The address activated devices feature combined data input and output interfaces and can also be three-state controlled with a separate output enable pin.

The FCB61C65 normal and low power devices with an access time of 70 ns are available now in a 600 mil 28-pin DIL package and will be available in a 330 mil SO28XL package early 1990. The 55 ns part and the ultra low-power part will be offered in the near future.

Circle 14
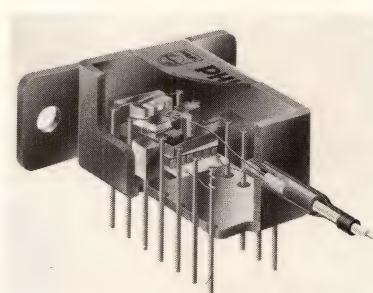
## InGaAsP laser diode for high bit-rate fibre-optic communications

Philips Components is introducing an ultra-fast DIL-packaged InGaAsP laser diode for extremely high bit-rate fibre-optic communications. The CQF60 incorporates internal electrical compensation that allows operation at up to 2.4 Gbits/s, a unique feature for a DIL-packaged laser diode. The LC compensation network counteracts the effects of the inductance and capacitance of the encapsulation and feed-through connections, provides perfect 50- $\Omega$  line impedance matching, and avoids electrical reflections.



1.3 and 1.55  $\mu$ m wavelength lasers in user-friendly DIL package.

The 14-pin DIL package is both cost-effective and user friendly.

The CQF60 forms part of a new and comprehensive range of DIL-packaged InGaAsP lasers which covers the 1.3  $\mu$ m and 1.55  $\mu$ m wavelengths.

Circle 15

## New ferrite helps lift SMPS operating frequency

Philips Components' 3F3 ferrite helps boost the operating frequency of switched-mode power supplies to 1 MHz, thus making the supplies smaller and lighter. The new ferrite will be attractive for EDP, aerospace, and telecom equipment, where size and weight are at a premium. It will work particularly well in new resonant-converter designs, which can further reduce switching losses, increase operating frequencies, and cut EMI.

ICs □ SEMICONDUCTORS □ DISPLAY COMPONENTS

Philips Components




By reducing high-frequency losses, the ferrite reduces the core size without sacrificing power throughput. Replacing a conventional core with a 3F3 and simultaneously increasing the operating frequency from 50 kHz to 500 kHz leads to a threefold reduction in core volume and weight, and a tenfold reduction in the size of the output choke and capacitor.

#### Circle 16
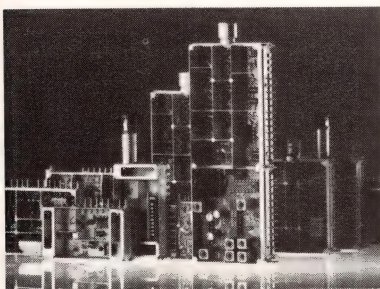
### TV tuners incorporate PLL tuning system

Philips Components has added two new series of TV tuners with built-in phase-locked loop (PLL) tuning systems to their range of VHF/UHF TV tuners. The UV-800 and UV-900 TV tuner series' advanced PLL tuning system contains all channel and function information necessary to control the tuner. In this way, a sizeable portion of external circuitry is made redundant, making CTV design both simpler and cheaper.



*These PLL TV tuners make CTV design simpler and cheaper.*

The PLL tuning system takes instructions from a microcomputer via the I<sup>2</sup>C Bus. The new ranges share the pinning and electrical configuration of the established

Philips UV-600 and UV-700 series TV tuners, thus guaranteeing total compatibility throughout the range.

These tuners. They cover the entire TV broadcast spectrum in just three bands (VHF high, VHF low and UHF) in place of the four required for earlier tuner designs (VHF1, VHF3, Hyperband and UHF).

To further simplify system design, Philips also produces complete front-end modules. Housed in screened boxes slightly larger than those used for the tuners, these front-ends contain a tuner plus IF amplification and demodulation circuits, providing baseband video output with either quasi-split stereo or demodulated mono sound.

#### Circle 17


### Clock-timer IC has low power consumption

The compact PCF8583 CMOS clock/timer/static RAM IC provides a wide range of timing functions, including a real-time clock with alarm functions, a calendar, and a timer or event counter.

Drawing typically just 10  $\mu$ A from a 2.5 V to 6 V supply, the device is particularly attractive for normal telephones as well as for battery-operated and portable equipment such as pagers, remote handsets, and cordless telephones. A programmable timer or alarm interrupt allows the PCF8583 to reduce system power consumption by waking a processor from an idle mode at pre-programmed intervals.

With a resolution of 0.01 s, the PCF8583 works as a real-time 12- or 24-hour clock/calendar, keeping

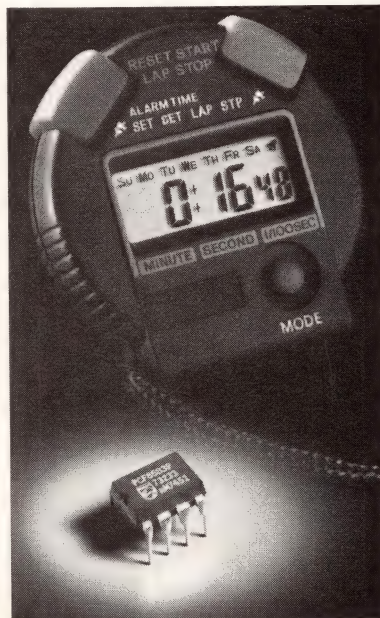track of the year (with compensation for leap years), month, date, day of week, hour, minute, and second. As a timer, the PCF8583 provides elapsed time information in either days, minutes, seconds, or hundredths of a second.



*The low-power PCF8583 provides a wide variety of timing functions.*

The PCF8583 also has an on-chip 256-byte SRAM to store alarm, status or time information as well as telephone numbers, access codes, and other application-related information. The IC can connect to any microprocessor, and is controlled via the two-line I<sup>2</sup>C-bus. Its operating temperature range is -40 °C to +85 °C. Naked-chip versions are available, as well as versions in small outline and DIL packages.

#### Circle 18

**PASSIVES □ PROFESSIONAL COMPONENTS □ MATERIALS**



# PHILIPS



# Born Prepared for Any Game.

## 286

### Industrial Computer

As you face the changing demands of today's industrial environments, Qualogy's 286, 12.5MHz industrial computers will keep you prepared for any game. Our 286 system comes in a rugged rackmount chassis including:

- 10-slot passive backplane
- 200-Watt switching power supply
- Positive airflow cooling
- 1M DRAM, 2 serial/1 parallel port
- Hard disk, 1.2M floppy, 1:1 controller
- EGA card, 101 keyboard, DOS 3.3

The 286, 12.5MHz system comes with a 20Mbyte drive, for only:

**\$3,595**



## 386


### Industrial Computer

When you need both super speed and ruggedness, Qualogy's 386, 20MHz industrial computers give you the winning edge in the game of your choice. Our 386 system comes in a rugged rackmount chassis including:


- 10-slot passive backplane
- 200-Watt switching power supply
- Positive airflow cooling
- 1M DRAM, 2 serial/1 parallel port
- Hard disk, 1.2M floppy, 1:1 controller
- EGA card, 101 keyboard, DOS 3.3

The 386, 20MHz system comes with a 40Mbyte drive, for only:

**\$4,795**

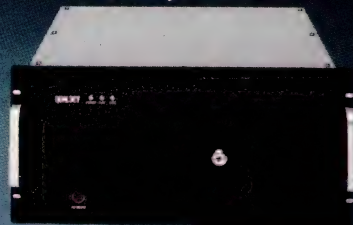

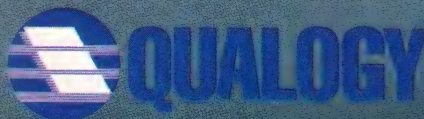*Industrial PC/AT computers and peripherals.*



1751 McCarthy Blvd. Milpitas, California 95035 408-434-5200 Fax 408-434-5242 Telex 4993489

Qualogy is a trademark of Qualogy, Inc. IBM PC/AT is a trademark of International Business Machines, Inc. Copyright © Qualogy, Inc., October 1989. All rights reserved.



It's one thing to know  
where you're going  
– another is to get there.



Investment calculations, marketing strategies, plans for tomorrow. A lot of thought goes into preparing a company to face the future.

But what happens when all those grandiose plans have to be put into practice? Take CIM, for example – Computer Integrated Manufacturing. Everyone is talking about it, but what does it mean to your company in reality?

How far have your competitors come? What does the market offer?

There's only one way to prepare yourself, and that is with knowledge.

In Sweden and many other parts of Europe, companies are moving well ahead. That's why the CIM 88 fair was such a success. Representatives from knowledge-hungry Swedish and foreign industries attended the fair to gain information and make business contacts.

Now comes the follow-up: CIM 90, a fair which will run consecutively with Machine Tools 90. This will increase interest and considerably broaden your customer base. At CIM 90, products and methods will be presented, as well as all-inclusive and partial solutions. Why not show the world what you have to contribute? Welcome as an exhibitor at CIM 90! 2 – 6 April, 1990.

Please send me exhibitor information

Company \_\_\_\_\_

Name \_\_\_\_\_


Address \_\_\_\_\_

City, Zip code \_\_\_\_\_

Tel \_\_\_\_\_

Fax \_\_\_\_\_

CIM -90 \_\_\_\_\_

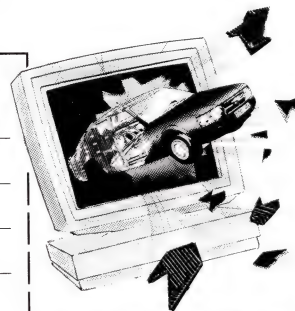

**CIM-90**  
**2-6 APRIL**

You can also telephone +46 8 749 41 00.



**STOCKHOLMSMÄSSAN**  
STOCKHOLM INTERNATIONAL FAIRS


Mailing address: S-125 80 Stockholm, Sweden. Telex 10660. Telefax +46 8 99 20 44.

**SHOW WHAT YOU HAVE TO CONTRIBUTE AT CIM 90**

For information circle 21


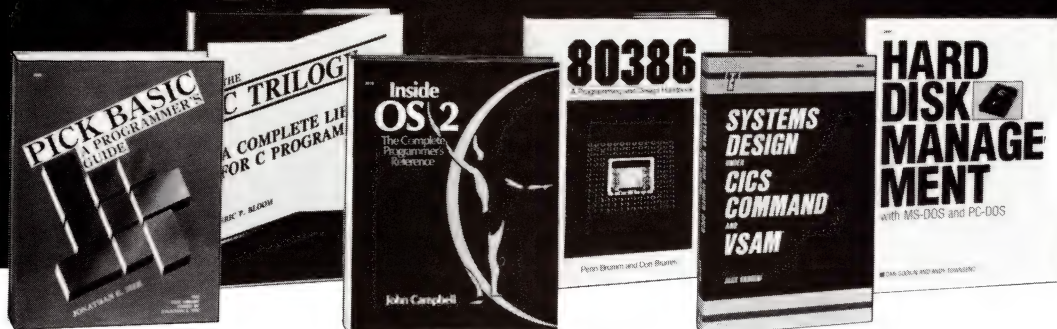
# Solutions to Your Computer and Management Problems from **TAB** Professional and Reference Books



**ORDER  
NOW**

## **80386—A PROGRAMMING AND DESIGN HANDBOOK.**

**P. Brumm and D. Brumm.** Preview everything Intel's 386 has to offer including: memory paging, debugging applications, the Virtual 8086 Mode, and 32-bit instruction enhancements. Features actual software applications for entering into the protected mode. *"The Brumms have produced a thorough reference for the 80386. Programmers and hardware designers alike should find it a valuable addition to their technical libraries."* —Leo J. Scanlon, bestselling author

**\$19.95**

## **DATABASES IN THEORY AND PRACTICE.**

**J.A. Jones.** Obtain maximum efficiency in all aspects of data storage with this practical guide to mainframe database management. Using case studies to illustrate successful techniques, Jones walks you through the process of designing, applying, and analyzing a database.

**\$28.95**

**PICK®/BASIC: A PROGRAMMER'S GUIDE.** **J.E. Sisk.** *"a straightforward, plain-English approach to learning the sophisticated PICK/BASIC programming language. A must for every PICK professional."* Frank Petyak, VP Sales & Marketing, Pick Systems (developers of Pick/BASIC).

**\$34.95**

## **MICRO TO MAINFRAME DATA INTERCHANGE.**

**M.S. Bodner, Ph.D.** This problem-solving reference features standards and protocols needed for conversions . . . a sophisticated menu-driven conversion program . . . plus an overview of the latest products on the market including Focus, ORACLE, and DataFlex.

**\$26.95**

## **THE C TRILOGY: A COMPLETE LIBRARY FOR C**

**PROGRAMMERS.** **E.P. Bloom.** This 3-in-1 volume provides you with the theory and commands you need to effectively and efficiently program in C on your IBM PC or compatible. Includes nearly 200 ready-to-run functions and subroutines.

**\$34.95**

## **WORKING WITH ORACLE®.**

**J.L. Hursch, Ph.D. and C.J. Hursch, Ph.D.** Tap the communication power of ORACLE with this user-oriented guide. Explains and illustrates the full range of system applications of version 5.0 . . . including how to use ORACLE's query language, SQL.

**\$19.95**

## **HARD DISK MANAGEMENT WITH MS-DOS® AND PC-DOS®.**

**D. Gookin and A. Townsend.** This treasury of disk management commands and ready-to-use software applications will take you from day one to your system's most advanced capabilities. Includes invaluable data recovery solutions and optimization techniques.

**\$28.95**

## **INSIDE OS/2: THE COMPLETE PROGRAMMER'S REFERENCE.**

**J. Campbell.** With this guide, you can start taking advantage of the new features of OS/2 including multitasking, using the protected mode, the Presentation Manager, and more. Complemented by actual examples, it explains the added commands and functions as well as how to convert DOS programs to run on OS/2.

**\$39.95**

## **WORKING WITH FOCUS®: AN INTRODUCTION TO DATABASE MANAGEMENT.**

**C.A. Schaffer.** Harness the applications potential of FOCUS on your mainframe or microcomputer. Featuring fully developed systems that you can customize to handle your own business needs, this indispensable guide taps FOCUS's power and efficiency.

**\$22.95**

## **SQL: THE STRUCTURED QUERY LANGUAGE.**

**Dr. C.J. Hursch and Dr. J.L. Hursch.** User-friendly, powerful, convenient, and now easy-to-learn—SQL is rapidly emerging as the leader of programming languages for relational databases. This reference illustrates all of its features including "embedded SQL," data definition, manipulation, and control statements, and more.

**\$17.95**

## **SYSTEMS DESIGN UNDER CICS® COMMAND AND VSAM®.**

**A. Varsegi.** Equivalent to a course in programming and systems design with CICS, this invaluable source includes: detailed program examples . . . "inside" tips . . . state-of-the-art instruction . . . plus in-depth application examples.

**\$28.95**

## **C PROGRAMMER'S UTILITY LIBRARY.**

**F. Whitsell.** All tested and proven reliable, this invaluable collection of system control functions aids you in developing high-quality C programs. Includes programs for turning an IBM PC into a communications terminal, modules for your video display and keyboard, routines for tapping the power of DOS and more.

**\$16.95**

**TO ORDER** — Circle the books you want and mail this ad with payment to: **TAB Books, Inc. c/o Mike Tucker, Cahners Publishing Company, Inc., 275 Washington St., Newton, Mass. 02158 U.S.A.** All orders must be prepaid. Include \$5.00 for shipping & handling. Send check or money order payable in U.S. funds to TAB Books, Inc. Credit cards accepted — VISA, Mastercharge, American Express — include expiration date.



# Path-distribution analysis simplifies logic-circuit timing

---

---

*Whereas logic simulators let you prove your circuit does what you want it to, timing-analysis CAD tools provide a more detailed examination of delay paths. Building a design from the results of a simulator without using a timing analyzer is like reading only the beginning of a story—you can't be quite sure how it will turn out.*

---

Chi-Lai Huang and Marek Ryniejski, *Advanced CAE Div, Cadence Design Systems Inc*

Adding sophisticated timing-analysis capability to your logic simulator can help ensure that you have eliminated timing problems from your design before you commit to silicon. However, timing analyzers cannot automatically correct timing violations that exist in your design. Correcting violations requires engineering know-how and, often, considerable time. Nevertheless, a good timing analyzer does provide the tools to guide you quickly toward the optimum solution to timing-violation problems.

The path-distribution analyzer is an important tool in the timing-analyzer arsenal. When employing path-distribution analysis, you create a histogram of the

number of arriving paths versus time for a given circuit. These plots give you a global view of the path timing and suggest the difficulty you'll face in attempting to improve circuit speed. You can use the path-distribution feature along with other timing-analysis tools to pinpoint specific changes that will improve circuit performance.

## Definition of paths through gates

A review of path basics is in order before considering the use of path-distribution analysis. **Fig 1a** shows a simple inverter chain. You can use several different models to represent the output delays caused by input transitions on the inverter chain (**Fig 1b**). **Fig 1c** shows the output waveform for the simplest model, which assigns equal values to both the rise and fall delays. For example, assign each inverter a delay value of four units for both rising and falling output transitions. Here, the inverter chain's output transitions always trail input transitions by 12 time units (four time units for each of the three inverters).

A model allowing you to assign distinct delays for rising and falling output transitions provides more information than the simple 1-delay model. As an example, such a representation would allow assignment of a rise delay of six time units and a fall delay of two time units for each inverter in **Fig 1a**. These values would yield the output response in **Fig 1d**. For a 3-inverter chain, the total delay between a rising input transition and a falling output transition,  $t_{\text{FALL}} = 10$ , is



*Gates can have the same rise and fall times, different rise and fall times, or else they can use minimum and maximum values for their rise and fall times.*

the sum of the fall delays for inverters  $G_1$  and  $G_3$  (two time units each) and the rise delay of  $G_2$  (six time units).

Similarly, the total delay between a falling input and a rising output change for the inverter chain,  $t_{RISE} = 14$ , is the sum of the rise delays of  $G_1$  and  $G_3$  (six time units each) and the fall delay of  $G_2$  (two time units).


A representation that lets you assign either minimum or maximum delays for rising and falling transitions provides still more information. Consider, for example, assigning the following values for each inverter in **Fig 1a**:  $t_{RISE(MIN)} = 3$  time units;  $t_{FALL(MIN)} = 1$  time unit;  $t_{RISE(MAX)} = 7$  time units; and  $t_{FALL(MAX)} = 3$  time units.

**Fig 1e** shows a minimum total fall time of five time units (fall delays of one time unit each for  $G_1$  and  $G_3$  plus a rise delay of three time units for  $G_2$ ). The minimum total rise time for **Fig 1e** is seven time units (rise delays of three time units each for  $G_1$  and  $G_3$  plus a fall delay of one time unit). **Fig 1f** shows a maximum total fall delay of 13 time units (fall delays of three each for  $G_1$  and  $G_3$  plus a rise delay of seven units for  $G_2$ ). The maximum total rise delay is 17 time units (rise delays of seven each for  $G_1$  and  $G_3$  plus a fall delay of three for  $G_2$ ).

The full adder in **Fig 2** illustrates timing analysis for

a more complex circuit. Assume, for this circuit, that the NAND gate has minimum and maximum fall delays of one and three time units, respectively, and rise delays of two min and four max time units. The XOR gate, on the other hand, has fall delays of three min and five time units max and rise delays of four min and six time units max. The possible paths and delay times are

PATH	$t_{(MIN)}$	$t_{(MAX)}$
A-D-COUT(FALL)	3	7
A-D-COUT(RISE)	3	7
B-D-COUT(FALL)	3	7
B-D-COUT(RISE)	3	7
CIN-F-COUT(FALL)	3	7
CIN-F-COUT(RISE)	3	7
A-E-F-COUT(FALL)	6	12
A-E-F-COUT(RISE)	7	13
B-E-F-COUT(FALL)	6	12
B-E-F-COUT(RISE)	7	13
A-E-SUM(FALL)	6	10
A-E-SUM(RISE)	8	12
B-E-SUM(FALL)	6	10
B-E-SUM(RISE)	8	12
CIN-SUM(FALL)	3	5
CIN-SUM(RISE)	4	6

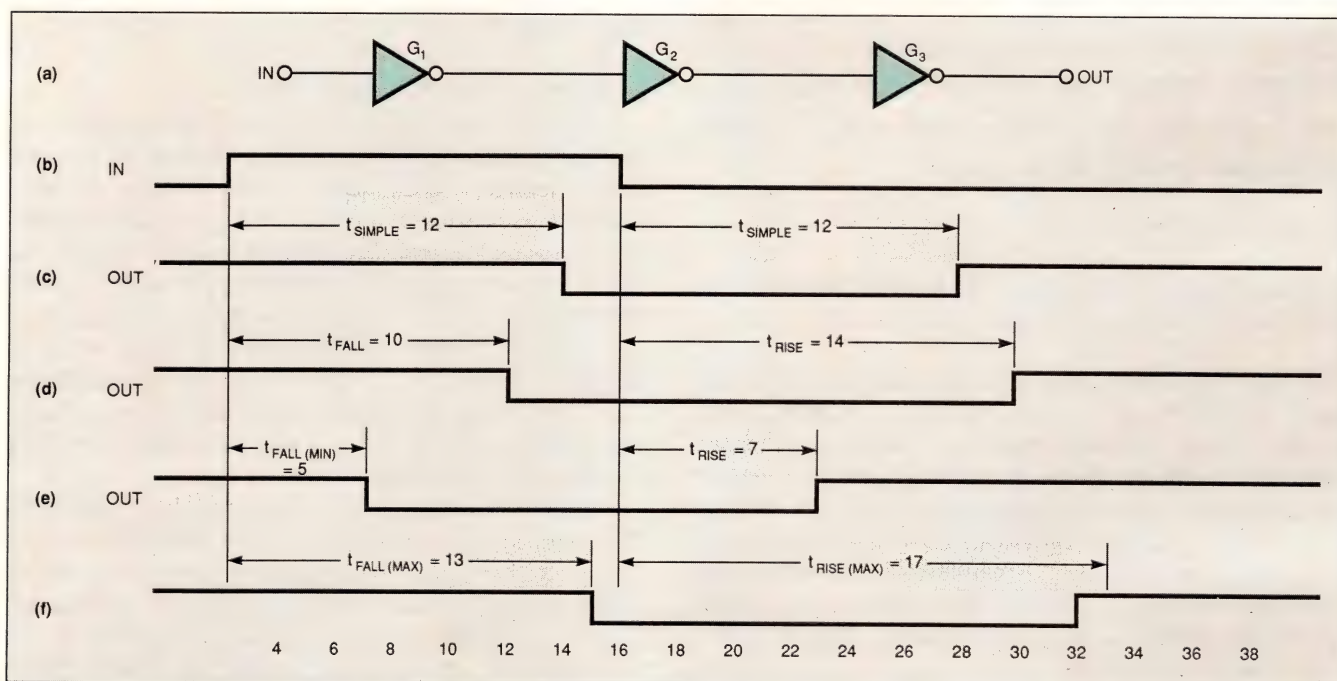

**Fig 1**—For an inverter chain (a) driven by an input waveform (b), a timing analyzer can represent delays in any of three forms: as a single, typical delay value for both rising and falling outputs (c); as different delay values for rising and falling outputs (d); and, for both rising and falling outputs, as minimum (e) and maximum (f) delay values.



## The hybrid timing analyzer

Gateway's Veritime timing analyzer serves all logic-design applications—from integrated circuits to systems. It handles asynchronous as well as synchronous circuits. It can help users detect timing problems such as setup, hold, and minimum-pulse-width timing violations. The software also helps to correct these violations, in addition to predicting circuit performance before layout and tuning delay values to enhance circuit performance.

Veritime is a hybrid timing analyzer. The software gives you the option of combining static timing analysis with logic simulation. For circuitry with simple clocking schemes, you can use the static analyzer to find critical paths; whereas you can use the software's hybrid mode for designs with more complex timing.

For static timing analysis, you define begin and end points. You also specify the number of longest or shortest critical paths for the software to find and enumerate in one pass. Limiting the number of critical paths lets you isolate that part of the circuit where design changes can produce the greatest improvements in circuit performance.

### KISS—Keep It Simple, Stupid

Complex clocking schemes often restrict your ability to perform static timing analysis. If your circuit uses multiple or multiphase clocks, then hybrid path tracing may be more helpful. With this feature, you employ your functional simulation pat-

terns to exercise the clocking and control portions of the circuit.

You also enable "timing checks"—that is, you specify nets at which the analyzer should check for timing violations. For example, you could specify the clock and data inputs of a flip-flop as the location of a potential setup violation.

When stimulus patterns cause value changes to propagate to clock/control inputs for which you've enabled timing checks, the software automatically initiates static analysis. For the flip-flop example, the software would find the critical paths to the data input and to the clock input. The software then compares the delay values to determine whether a setup violation exists.

An overly pessimistic analysis is one that would signal a timing violation based on theoretical worst-case analysis—even though actual conditions would prevent those worst-case conditions from occurring.

For example, consider two paths with stringent setup requirements with respect to each other passing through the same circuit component (a condition called reconvergent fanout). When looking for a setup violation, an overly pessimistic analyzer would assign a minimum delay to the component when calculating one path and a maximum delay to the same component when calculating the other path. The more realistic approach recognizes that a component can be either fast or slow; but not both.

Therefore, a better analyzer restricts the delay-assignment range when reconvergent fanout exists.

Similarly, the software correlates gate delays on a substrate. The software won't assign the worst-case delay to some gates and the best-case delay to others when all the gates are on one chip. While there is likely to be some variability, to mix best- and worst-case delays on a single chip wouldn't reflect the relative consistency of IC processing. On the other hand, you can override this correlation for system-level timing checks.

In addition to this correlation, Veritime minimizes the adverse effect of feedback paths by automatically halting the tracing of loops that contain more than a user-specified number of logic gates. A default value of 10 allows the analyzer to exhaustively trace most common latches (which constitute "local" loops) while not tying up CPU time with exhaustive tracing of larger, "global" loops.

The vendor integrates the timing analyzer with their Verilog-XL logic simulator and Verifault-XL fault simulator. The timing analyzer shares the same hardware-description language of the Verilog family of products, which make up a complete range of verification and test tools, including libraries of software models as well as hardware-modeler support.



*The number of possible paths through a circuit grows logarithmically as the number of gates increases, causing the analysis to become more complex.*

The number of paths for this adder demonstrates how time consuming path-distribution analysis is for circuits of even moderate complexity. Consider that whereas a 2-bit multiplier contains  $9.8 \times 10^1$  rising and falling paths from multiplicand to product, a 4-bit multiplier contains  $3.6 \times 10^4$  such paths. Worse, the number of paths grows logarithmically so that a 28-bit multiplier contains  $2.4 \times 10^{38}$  rising and falling paths.

Clearly, exhaustive listing of circuit paths is not practical. Complete cataloging of even relatively simple circuits would yield more information than you could use. Consider that even an 8-bit multiplier has more than five billion paths.

#### Critical-path analysis provides micro view

Contrast the path-distribution analyzer with another timing-analysis tool, the critical-path analyzer. This tool finds and reports only a specified number of the slowest (or fastest) paths in a circuit, or region of a circuit. Some critical-path analyzers incorporate algorithms—called breadth-first—that quickly locate and report critical paths. Such analyzers are much faster than depth-first algorithms. (For more information on breadth- and depth-first algorithms, see box, "Timing-analysis algorithms.")


Nevertheless, breadth-first analyzers, too, can be inconveniently slow to use early in the design cycle. They can be inefficient because they may not indicate the severity of your timing problems. If you find paths with unacceptable delays, you cannot tell whether there are only a few or thousands of them. It may take hours before you determine that too many unac-

ceptable delay paths exist. After investing this time, you may find that a complete redesign, or substitution of higher-speed parts throughout the design, is necessary.


Consider, for example, the full adder in Fig 2. Suppose you approach the problem without benefit of a path-distribution analyzer; you don't know how slow the slowest path is. A 1-path, critical-path search for the longest path would provide the delay and would note that the longest path could be A-E-F-C<sub>OUT</sub>(RISE). To find out that B-E-F-C<sub>OUT</sub>(RISE) exhibits the same delay, you'd have to start a second 1-path search. You could also conduct a multiple-path search, at the expense of CPU time, to find more than one of the slowest paths. At the fast end of the adder's performance, you'd have to conduct seven single-path searches—or one 7-path search—to uncover all seven paths with a minimal path delay of three.

Graphical display of path distribution, however, can quickly provide you with an overview of circuit timing. You can use standard workstations that incorporate the appropriate algorithms to generate such distributions in a reasonable amount of time.

A path-distribution histogram for the full adder shown in Fig 2 would illustrate that two paths exhibit the longest delays of 13 time units. Furthermore, it would show that a total of six paths have delays of

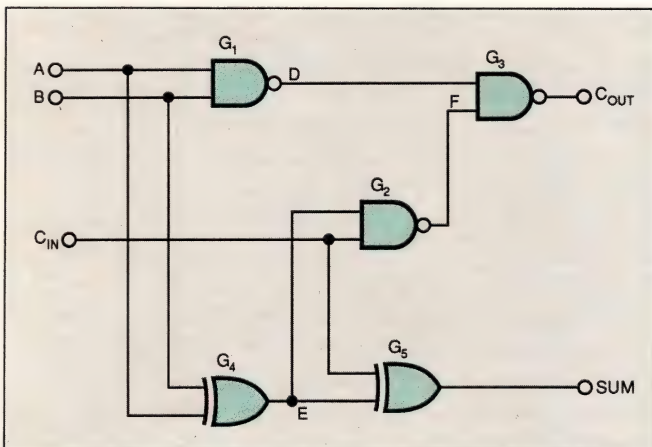


**Fig 2**—This simple adder has 16 paths from its three inputs to its two outputs, demonstrating the difficulty of performing timing analysis for circuits of even moderate complexity.

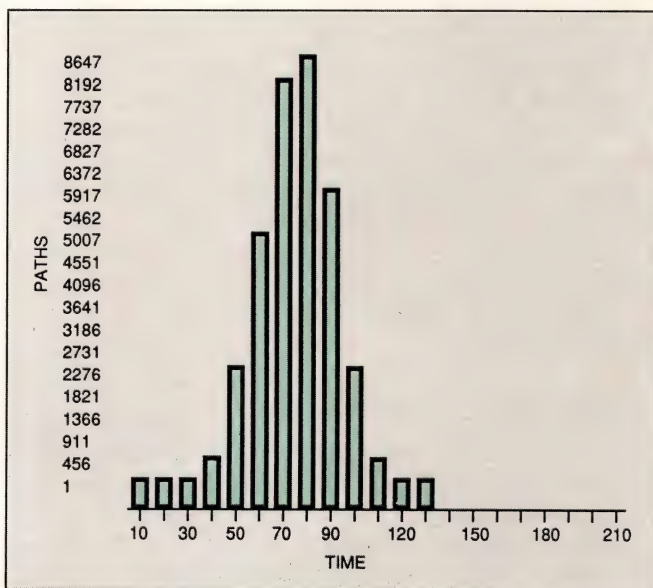

**Fig 3**—The path-distribution histogram for a 4-bit multiplier suggests that it might be possible to eliminate all paths with delays of 120 time units or greater—if there are a reasonable number of such paths.


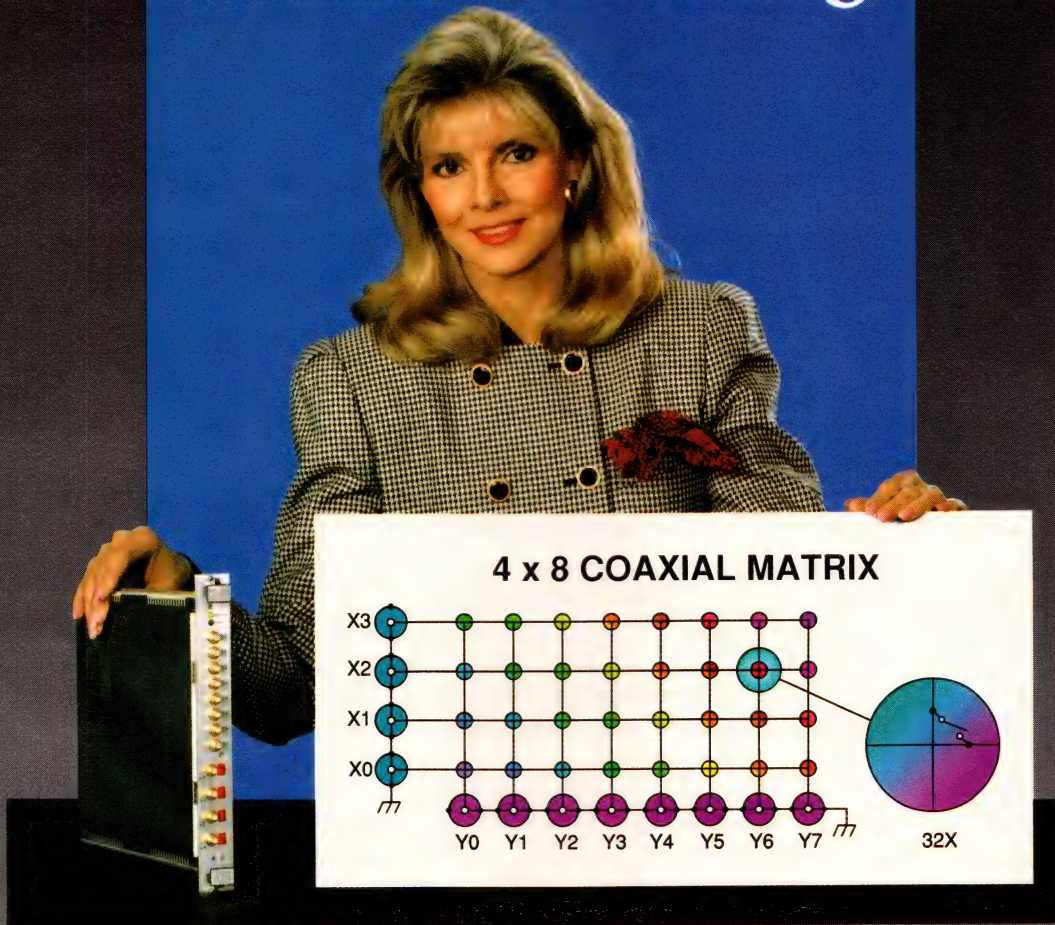
# "For VXIbus Users... The First 4x8 Coaxial DC to 625MHz Switching Matrix"



**Here's great news for VXIbus users.** It's the first VXIbus compatible 4x8 coaxial fully shielded message based switching matrix.

Model 10081 comes in a C-size package, and has a frequency range of DC through 625MHz, making it ideal for use in Automatic Test Equipment (ATE) systems where instruments such as frequency counters, signal generators, oscilloscopes, pulse generators, RF analyzers and other broad band devices are to be interconnected using the VXIbus



(Revision 1.3) specifications.

Available in 50 and 75 ohm configurations, Model 10081 has twelve front panel SMA signal connectors to provide



**MATRIX**  
SYSTEMS CORPORATION

5177 North Douglas Fir Road  
Calabasas, California 91302  
(818) 992-6776 • FAX (818) 992-8521

access to the bi-directional coaxial matrix at a switching speed of one milli-second.

Our matrix module also has a handy seven-segment display next to each of the four "X" axis signal connectors to provide front panel indication of any crosspoint with verification.

It's new products such as the VXIbus compatible 10081 switching module that makes Matrix Systems the leader in broad band matrices.

The price is right, too. \$2750 with quantity discounts available.



*Breadth-first timing algorithms tend to be faster than depth-first algorithms because the breadth-first approach avoids multiple tracing of a path.*

more than 10. A user might then invoke a critical-path analyzer to search for the six longest paths, yielding the following results:

PATH	$t_{(MIN)}$	$t_{(MAX)}$
A-E-F-C <sub>OUT</sub> (FALL)	6	12
A-E-F-C <sub>OUT</sub> (RISE)	6	13
B-E-F-C <sub>OUT</sub> (FALL)	6	12
B-E-F-C <sub>OUT</sub> (RISE)	6	13
A-E-SUM <sub>(RISE)</sub>	8	12
B-E-SUM <sub>(RISE)</sub>	8	12

In this simple case, notice that the XOR gate,  $G_4$ , is common to all of the slowest paths. Therefore, you can enhance circuit performance by using a faster XOR gate. This example shows the advantage of using both timing-analysis tools.

#### A histogram shows what is practical

Fig 3 shows a path-distribution histogram for a 4-bit multiplier. It illustrates that of more than 36,040 total paths, no path delay exceeds 140 time units. Note too that between one and 456 paths have delays greater than 130 time units, suggesting that you should further

## Timing-analysis algorithms


Timing analyzers typically use one of two algorithmic approaches: depth-first or breadth-first. To gain a basic understanding of how these approaches work, consider the two representations of a 12-node circuit shown in Fig A.

For the tree-like network, the depth-first algorithm explores a branch of the tree until the branch's termination; it then backtracks to the base of an unexplored branch and proceeds from there. For example, the depth-first algorithm first calculates the

path A-B-C-D. Then it backtracks to node C to calculate path A-B-C-E; and then it backtracks to node B to calculate paths A-B-F, A-B-F-G, and A-B-F-H. From node H, it proceeds through nodes I, K, and L and then through nodes J, K, and L.


Note that the depth-first algorithm explores the path segment from K to L twice; once as part of path segment H-I-K-L and once as part of H-J-K-L.

The breadth-first algorithm improves analysis speed by avoiding such duplicate path explorations. It does not proceed from a node until it has calculated all paths to that node. For example, after calculating the delay to node K via node I, the breadth-first algorithm does not proceed to node L until it first calculates the delay to path K via node J. If the algorithm were searching for a longest critical path, it would add the delay of path segment K-L to the longer of the two delays (via node I or node J) to node K. The algorithm would discard the shorter delay to node K and the algorithm would not have wasted time performing an irrelevant calculation.

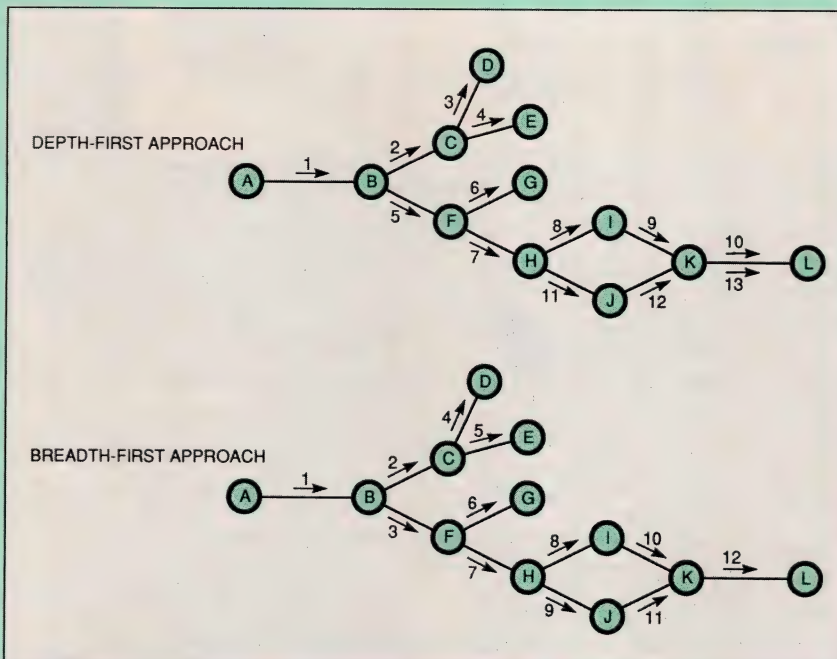

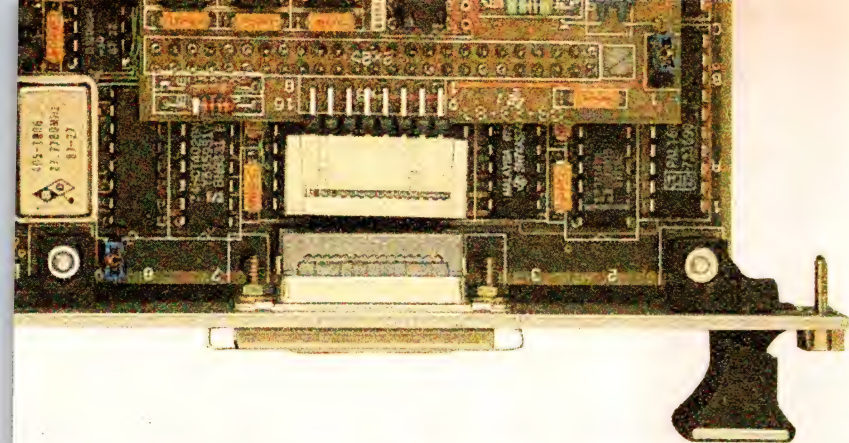**Art A—Depth-first and breadth-first algorithms take different approaches to finding critical paths.** The circuit nodes (labeled A through L) illustrate the differences. The numbers along each path segment show the order in which the respective algorithms perform path-delay calculations.






# NETWORKING SOLUTIONS

## ETHERNET SOLUTIONS FOR VMEbus

Ethernet can be frustrating. No one likes putting up with an Ethernet link that has low throughput. And for the system or network designer, the real price of a slow network is staggering. Just think about the productivity lost when almost every node is idly waiting for the network.

Often, the culprit is not the network itself, but slow, poorly-designed node controllers. Now, Interphase gives you solutions that are measurably better.

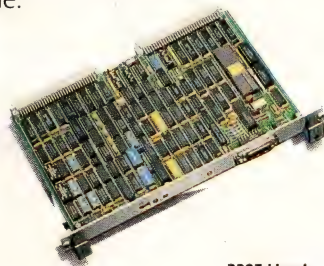Interphase has a connectivity strategy for a wide range of VMEbus-to-Ethernet applications. The solution is two new products: the V/Ethernet 3207 Hawk and V/Ethernet 4207 Eagle.



3207 Hawk

## HIGH-PERFORMANCE NODE CONTROLLERS

An elegantly partitioned architecture and powerful 16 MHz 68020 processor give the Eagle plenty of power


for on-board protocol processing, yet provide outstanding throughput in link level applications. In fact, the Eagle is able to continuously saturate the Ethernet cable even with packets as small as a few hundred bytes. The other side of the performance question is the VMEbus interface. Here the Eagle has Interphase's exclusive BUSpacket Interface<sup>SM</sup> which transfers data over the VMEbus at more than 30 megabytes per second.

## LOW COST-PER-NODE SOLUTION

Our V/Ethernet 3207 Hawk offers a cost-effective approach to network access and node control. The Hawk has high-speed, dual-ported memory, innovative memory mapping capabilities, and a set of pipeline registers which prevents the bus from being monopolized during network access. For link-level performance at a surprisingly low cost, the Hawk can't be beat.
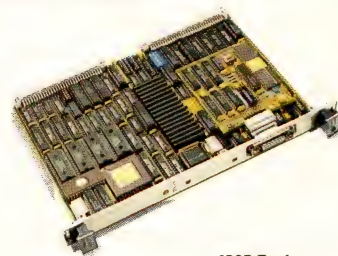
## NETWORK LEADERSHIP

Interphase has consistently led the industry in high-performance peripheral controllers. It should be no surprise that our advanced technology has been applied to these two Ethernet controllers.



4207 Eagle

## NETWORKING SOLUTIONS

Interphase provides the high-performance Ethernet solutions you need today. And just as we have for our first 15 years, we continue to set trends in technology and standards for performance that others follow. With Interphase as your technology partner, you gain a valuable member of the team that always keeps you...

...A Step Ahead.



**INTERPHASE**  
CORPORATION

OPEN SYSTEMS CONTROLLERS<sup>SM</sup>

Disk • Tape • Networking

13800 Senlac Drive • Dallas, Texas 75234 • (214) 919-9000 • FAX: (214) 919-9200 • NASDAQ-NMS: INPH


Interphase International

Astral House, Granville Way • Bicester, Oxon OX6 0JT • (01144) 869-321222 • FAX: (01144) 869-247720

Interphase is a registered trademark of Interphase Corporation. Open Systems Controllers is a trademark of Interphase Corporation. Virtual Buffer Architecture and BUSpacket Interface are service marks of Interphase Corporation.



*Path-distribution analysis gives a macro view of your circuit's timing whereas critical-path analysis provides the micro view.*

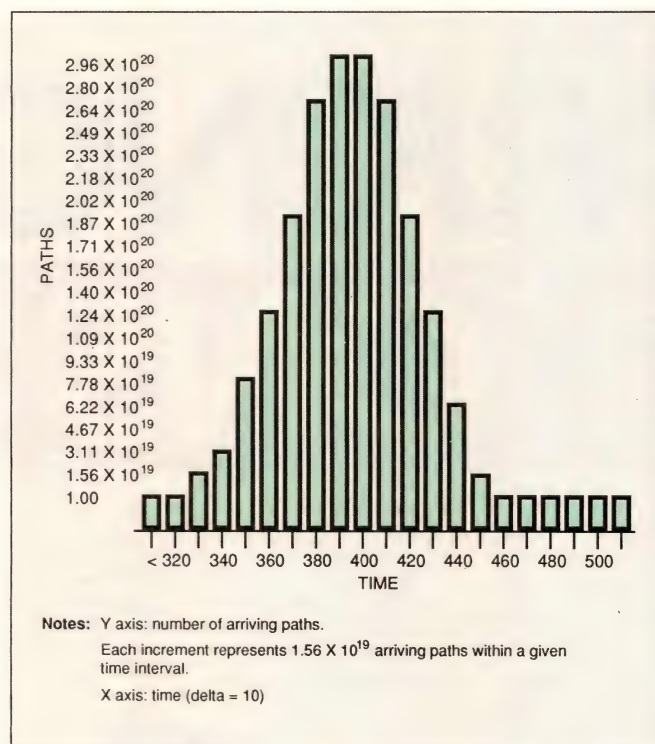

**Fig 4—Although a 16-bit multiplier circuit contains more than  $2 \times 10^{21}$  paths, the path-distribution software required only 227 seconds on a Sun workstation to provide a global picture of circuit timing.**

investigate whether you can reduce the maximum path delay to less than 130 time units. You would need to rerun the analysis with increased resolution to determine the feasibility of cutting the maximum path delays. Note, however, that it isn't practical to reduce the maximum path delay below 100 time units because of the existence of more than 2734 paths with delays longer than 100 units.

Timing analysis of a 16-bit multiplier illustrates the benefits of path-distribution capability in timing analysis. The alternative approach, using Gateway's Veritime critical-path tracer (running on a Sun 3/260 workstation), required 32 sec to run a 1-path trace, whereas a 4-path trace did little more than double the run-time to 66 sec. However, without benefit of the path-distribution analysis, you'd just be guessing at the number of paths to analyze.

Searches for additional critical paths would take increasingly more time. Worse, you wouldn't know how much of the potential timing problem you'd analyzed, even after completing 10 or 20 path searches. Addi-


tional searches could yield many more paths with delays nearly as long as those of the paths already traced. Moreover, an exhaustive enumeration of such a circuit wouldn't be practical because the total number of paths from one operand to the 32-bit result exceeds  $10^{20}$ .

In short, critical-path tracing alone can be time consuming and provides no information about circuit paths that you haven't traced. In contrast, path-distribution analysis provides global information about circuit delays in far less time. Veritime, for example, running on a Sun 3/260, generated the Fig 4 histogram in 227 seconds.

The Fig 4 histogram reveals the potential value of a 5- or 6-path trace to enumerate the few longest paths. The histogram also illustrates that additional traces to enumerate paths in the 450- to 460-time-unit range would be neither useful nor practical, thereby illustrating that path-distribution analysis is a powerful tool that complements critical-path tracing. **EDN**
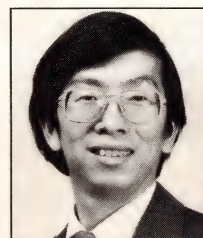
## Authors' biographies

*Chi-Lai Huang has been with Gateway for 5 years. He earned his PhD in computer science at the State University of New York at Binghamton. Chi-Lai enjoys playing bridge and gardening.*




*Marek Ryniejski is a senior software engineer who is responsible for maintaining and enhancing Gateway's timing-analysis tool. He has a BA in computer science from Boston University. In his spare time, Marek enjoys cycling.*



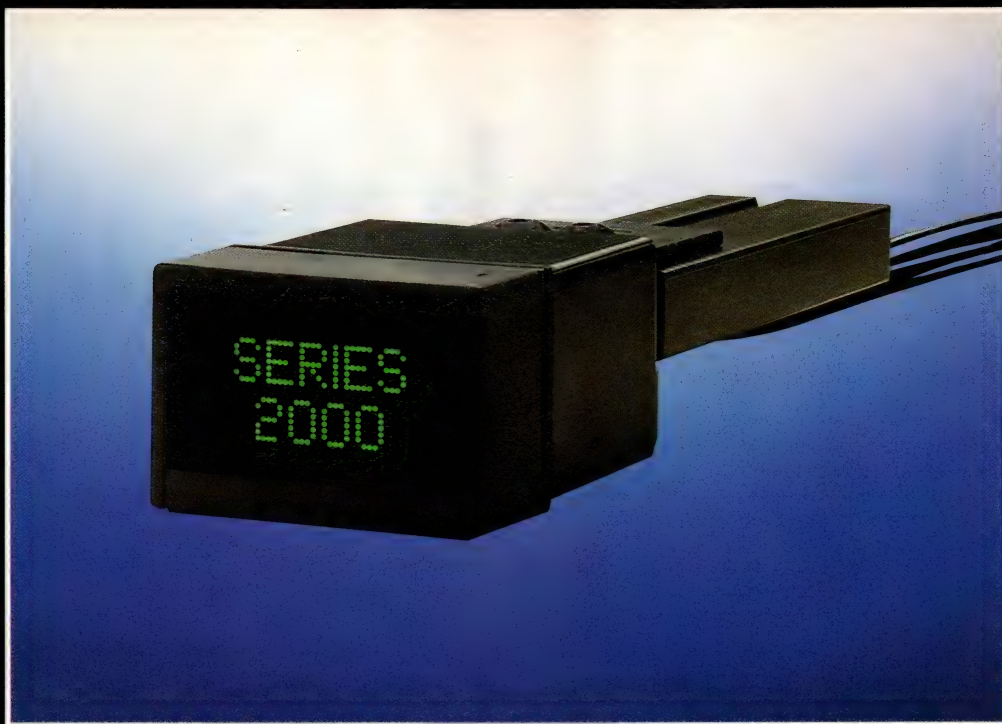**Article Interest Quotient (Circle One)**  
High 491 Medium 492 Low 493





# The program in a switch.

Introducing Vivisun Series 2000, the programmable display pushbutton system that interfaces the operator with the host computer. The user friendly LED dot-matrix displays can display any graphics or alpha-numerics and are available in green, red or amber. They can efficiently guide the operator through any complex sequence, such as a checklist, with no errors and no wasted time.

They also simplify operator training as well as control panel design. Four Vivisun Series 2000

switches can replace 50 or more dedicated switches and the wiring that goes with them. In short, Vivisun Series 2000 gives you more control over everything including your costs.

Contact us today.



**AEROSPACE OPTICS INC.**

3201 Sandy Lane, Fort Worth, Texas 76112  
(817) 451-1141 • Telex 75-8461 • Fax (817) 654-3405

SERIES  
**VIVISUN 2000**™



*Programmable display switches. Making the complex simple.*



# Revolution.

Now there's a new plotter that makes output bottlenecks disappear. With the ColorStation D™ from Raster Graphics you can now generate wide-format color plots in minutes instead of hours. All for a starting price of \$18,500.

The ColorStation has been designed from the ground up to be the ideal high speed, full-color output device for the workstation environment. It utilizes a revolutionary writing technology called the "Silicon Imaging Bar™" to produce hardcopy at up to 400 dpi. It's HP-GL compatible and produces dazzling color output without the frustration of pen plotters or the expense of the high-end electrostatics and thermals.

## Give Your Plots A Whole New Image.

With the ColorStation D from Raster Graphics you'll create beautiful, full-color plots in minutes, and, you have complete shading and solid fill capabilities as well. It's even compatible with the newest 3-D rendering software from AutoDesk and others.

Plus, plots come out into the convenient paper catch tray. So there's no need to stand around feeding paper into a pen plotter, or unrolling your plot from a take-up reel. You can pick them up as soon as they




The ColorStation handles AutoCad, AutoShade, AT&T Targa and just about any other popular CAD software.

are done or get them later. Iterations are quick and easy, speeding up design cycles.
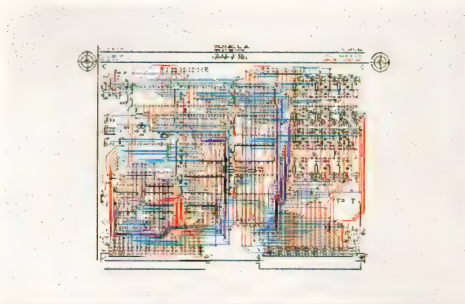
## Plug And Play.

Raster Graphics' ColorStation is engineering D-size (22x34), and comes standard with both RS-232 and Centronics interfaces. That means it's no problem to connect to just about any CAD workstation environment.




You'll get full, rich color and black & white hardcopy from our Silicon Imaging Bar. This revolutionary technology offers up to 400 dpi and a palette of up to 16 million colors.

## Plots For Pennies.

The other good news is price per plot. Literally pennies. In fact, each plot only costs about 50 cents. You won't find a more efficient wide-format color output device.
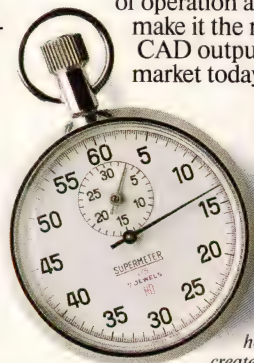
## Picture Perfect Plotter.

What this all adds up to is an incredible new option for your design system. The ColorStation offers all the speed and capability of the high-end electrostatics with pen plotter affordability. The unique design, ease of operation and beautiful output make it the most revolutionary CAD output solution on the market today.



You'll get plots in minutes instead of hours. The unique design creates no paper waste and produces plots for about 50 cents each.

## Get Your Plots In Minutes.

A built-in vector-to-raster converter processes your HP-GL or raster plot files at high speed. Our patented paper transport system takes over from there. The paper gets vacuum-anchored in place for absolute accuracy. We've completely eliminated the take-up spool mechanism of older (and more expensive) electrostatics.

The ColorStation's Silicon Imaging Bar plots each color pass at an impressive 2 inches per second to achieve full-color output. You can even make multiple copies of your finished plots at the push of a button.



If you would like to see some actual plot samples, or get more information about Raster Graphics' ColorStation, call our toll-free number: 1-800-441-4788.

Raster Graphics, Inc., 285 North Wolfe Rd., Sunnyvale, CA 94086-3820

**RASTERGRAPHICS**

*ColorStation* The World's First Full Color D-Size Electrostatic Plotter Starting At \$18,500.

© 1990 Raster Graphics, Inc. ColorStation and Silicon Imaging Bar are trademarks of Raster Graphics, Inc. HP-GL, AutoCad, AutoShade, AT&T Targa are all trademarks of their respective manufacturers.



# Revolutionary.





# Announcing the 1990 EDN Caravan Tour

## *"The Electronic Trade Show on Wheels"*

**Tektronix®**

**YOUR  
VISIBLE  
EDGE**

CAHNNERS

**CAPS**

Computer Aided  
Product Selection

**BURR-BROWN®**  
**BB**

**OrCAD**



**MITSUBISHI  
ELECTRONICS**



**Basler Electric**

**DURACELL®**

Batteries

**Speedy  
Circuits  
Inc.**

**Metro  
Circuits  
Inc.**

**Amphenol**

BENDIX CONNECTOR OPERATIONS

**CAROL**

**WAVETEK**

**EAGLE EPICHER**




**zitel**

*Memories of the Future*



**BUSSMANN**

**LORD** Lord Corporation

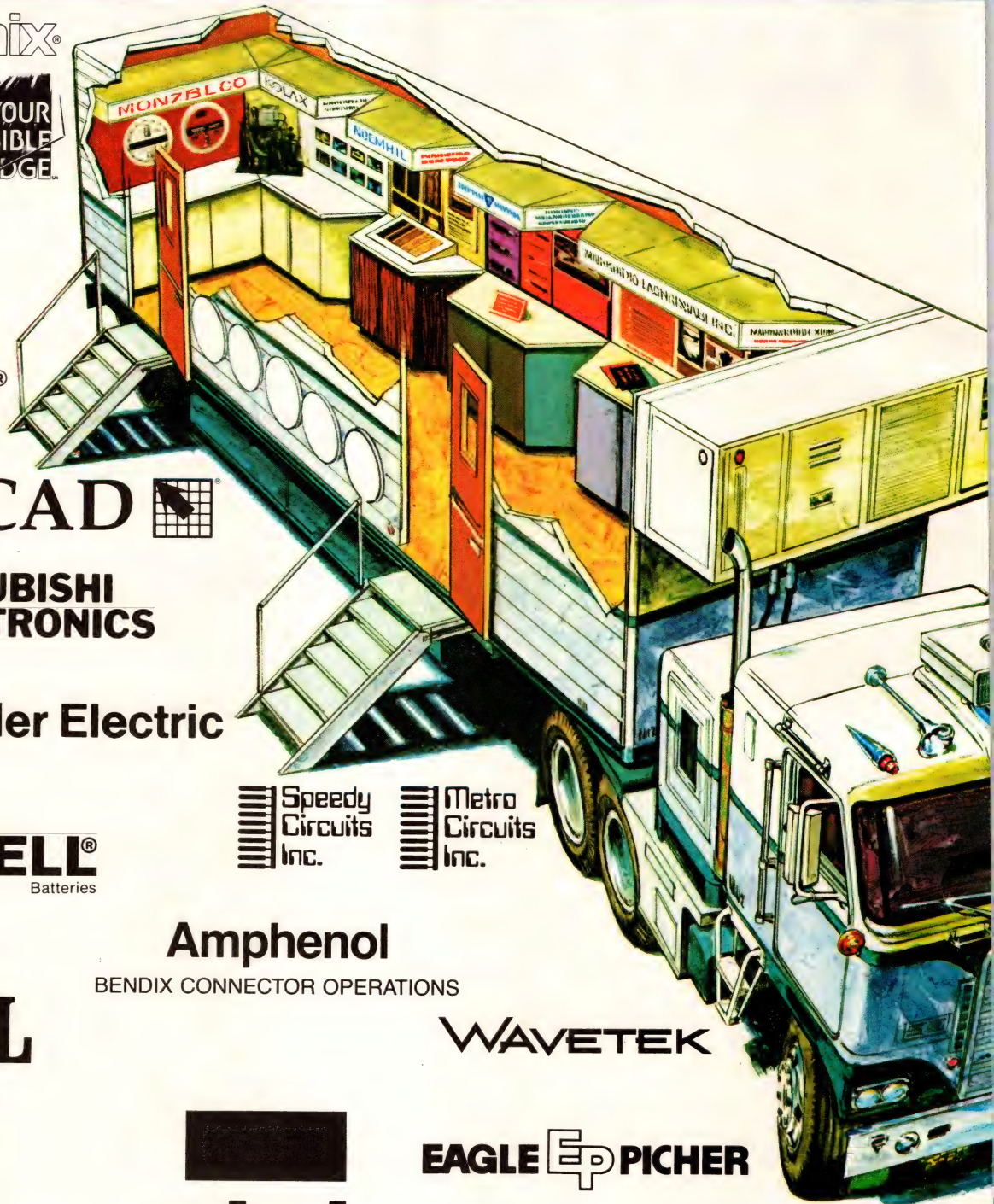

*Bringing New Products and Ideas to Your Business Doorstep*



# 1990 EDN STAVAN SHOW TOUR SCHEDULE (First Half)

DATE	TIME	SITE
February 19	9:00-11:00	SCI TECHNOLOGY
Monday	AM	5000 Technology Drive, Huntsville, AL
February 19	11:45-1:15	SCI TECHNOLOGY
Monday	AM-PM	8600 So. Memorial Parkway, Huntsville, AL
February 19	2:30-4:30	INTERGRAPH CORPORATION
Monday	PM	Highway 20 - Intergraph Way, Huntsville, AL
February 20	8:30-10:00	PENTASTAR ELECTRONICS INC.
Tuesday	AM	5021 Bradford Blvd., Huntsville, AL
February 20	10:30-12:00	UNIVERSAL DATA SYSTEMS
Tuesday	AM	5000 Bradford Drive, Huntsville, AL
February 20	2:00-4:00	ACUSTAR, INC., Huntsville Electronics Div.
Tuesday	PM	100 Electronics Blvd., Huntsville, AL
February 21	8:00-10:30	BOEING AEROSPACE
Wednesday	AM	499 Boeing Blvd., Huntsville, AL
February 21	11:30-1:30	TELEDYNE BROWN ENGINEERING
Wednesday	AM-PM	Sparkman Avenue, Huntsville, AL
February 21	2:30-4:00	AVEX ELECTRONICS
Wednesday	PM	4807 Bradford Drive, Huntsville, AL
February 22	8:00-10:00	SCIENTIFIC-ATLANTA, INC.
Thursday	AM	4311 Communications Drive, Norcross, GA
February 22	11:00-1:00	AT&T Network Systems
Thursday	AM-PM	2000 Northeast Expressway, Norcross, GA
February 22	2:30-4:00	BELL NORTHERN RESEARCH
Thursday	PM	5555 Spalding Drive, Norcross, GA
February 23	9:00-11:00	NORTHERN TELECOM INC.
Friday	AM	1555 Roadhaven Drive, Stone Mountain, GA
February 23	1:00-2:30	HARRIS/LANIER, Voice Products
Friday	PM	1704 Chantilly Drive NE, DeKalb, GA
February 26	10:00-1:00	HARRIS CORPORATION, Electronic Systems
Monday	AM-PM	Palm Bay Road, Palm Bay, FL
February 26	2:30-4:00	HARRIS CORPORATION, Controls & Composition
Monday	PM	John Rode Boulevard, Melbourne, FL
February 27	8:30-10:00	IBM CORPORATION
Tuesday	AM	1626 S. Congress Avenue, Del Ray, FL
February 27	11:30-3:30	IBM CORPORATION
Tuesday	AM-PM	1000 NW 51st Street, Boca Raton, FL
February 28	8:30-10:00	MODULAR COMPUTER SYSTEMS (plant 8)
Wednesday	AM	3101 S.W. 10th Street, Pompano Beach, FL
February 28	10:45-12:00	HARRIS CORPORATION, Computer Systems Div.
Wednesday	AM	2101 W. Cypress Creek Road, Ft. Lauderdale, FL
February 28	2:00-4:00	RACAL-MILGO INC.
Wednesday	PM	1601 N. Harrison Parkway, Sunrise, FL
March 1	8:30-11:00	ALLIED SIGNAL AEROSPACE, Bendix/King ATAD
Thursday	AM	2100 N.W. 62nd Street, Ft. Lauderdale, FL
March 1	1:00-3:00	ENCORE COMPUTER CORPORATION
Thursday	PM	1801 N.W. 66th Avenue, Ft. Lauderdale, FL
March 2	9:00-11:00	LORAL DATA SYSTEMS
Friday	AM	6000 Fruitville, Sarasota, FL
March 2	1:30-4:00	E-SYSTEMS INC., ECI Division
Friday	PM	1501 72nd Street No., St. Petersburg, FL
March 5	10:00-1:00	HONEYWELL, INC., Space & Strategic Avionics
Monday	AM-PM	13350 Highway 13 So., Clearwater, FL
March 5	2:00-4:30	AT&T PARADYNE CORPORATION
Monday	PM	8545 126th Avenue No., Largo, FL
March 6	8:00-10:30	MARTIN MARIETTA CORPORATION
Tuesday	AM	12506 Lake Underhill Drive, Orlando, FL
March 6	12:00-2:30	MARTIN MARIETTA CORPORATION
Tuesday	PM	East Sandlake Road, Orlando, FL
March 7	9:00-11:00	NCR CORPORATION
Wednesday	AM	3325 Platt Springs Road, W. Columbia, SC
March 7	2:00-4:00	IBM CORPORATION
Wednesday	PM	1001 WT Harris Blvd. West, Charlotte, NC
March 8	9:00-11:00	ALCATEL NETWORK SYSTEMS
Thursday	AM	2912 Wake Forest Road, Raleigh NC
March 8	2:30-4:30	NORTHERN TELECOM INC.
Thursday	PM	Perimeter Park Drive, RTP, NC
March 9	8:00-11:00	IBM CORPORATION
Friday	AM	Research Triangle Park, NC
March 9	12:00-2:00	NORTHERN TELECOM INC.
Friday	PM	Research Triangle Park, NC

DATE	TIME	SITE
March 9	2:30-4:00	NORTHERN TELECOM INC.
Friday	PM	Northern Telecom Plaza, RTP, Inc.
March 12	9:00-11:30	AT&T TECHNOLOGIES
Monday	AM	204 Graham-Hopedale Road, Burlington, NC
March 12	1:00-3:30	AT&T TECHNOLOGIES
Monday	PM	I 85 & Mt., Hope Church Rd., McKleinsville, NC
March 13	9:00-11:00	GENERAL ELECTRIC COMPANY
Tuesday	AM	1501 Roanoke Blvd., Salem, VA
March 13	1:30-3:30	GENERAL ELECTRIC COMPANY
Tuesday	PM	Mountain View Road, Lynchburg, VA
March 14	9:00-11:00	GENERAL ELECTRIC COMPANY
Wednesday	AM	US Route 29 North, Charlottesville, VA
March 14	1:30-4:00	IBM CORPORATION
Wednesday	PM	9500 Godwin Drive, Manassas, VA
March 15	8:30-11:00	E-SYSTEMS INC., Melpar Division
Thursday	AM	11225 Waples Hill Road, Fairfax, VA
March 15	1:30-4:00	E-SYSTEMS INC., Melpar Division
Thursday	PM	7700 Arlington Blvd., Falls Church, VA
March 16	9:00-10:30	RACAL COMMUNICATIONS
Friday	AM	5 Research Place, Rockville, MD
March 16	12:00-2:00	FAIRCHILD COMMUNICATIONS & ELECTRONICS CO.
Friday	PM	20301 Century Blvd., Germantown, MD
March 16	2:30-4:00	HUGHES NETWORK SYSTEMS
Friday	PM	11717 Exploration Lane, Germantown, MD
March 19	9:00-11:00	LITTON SYSTEMS INC., Amecon Division
Monday	AM	5115 Calvert Road, College Park, MD
March 19	1:00-3:00	ALLIED SIGNAL AEROSPACE
Monday	PM	9140 Old Annapolis Road, Columbia, MD
March 20	8:30-11:00	ALLIED SIGNAL AEROSPACE
Tuesday	AM	1300 E. Joppa Road, Baltimore MD
March 20	12:30-3:00	MARTIN MARIETTA AEROSPACE
Tuesday	PM	103 Cheseapeake Park Plaza, Baltimore, MD
March 21	9:00-11:30	WESTINGHOUSE ELECTRIC
Wednesday	AM	Intl' Airport, Baltimore, MD
March 21	1:00-3:30	MARTIN MARIETTA CORP., Ocean Systems
Wednesday	PM	6711 Baymeadow Drive, Glen Burnie, MD
March 22	9:00-11:30	WESTINGHOUSE ELECTRIC COMPANY
Thursday	AM	111 Schilling Road, Hunt Valley, MD
March 22	2:00-4:00	AAI CORPORATION
Thursday	PM	York Road & Industry Lane, Cockeysville, MD
March 23	9:30-12:00	UNISYS CORPORATION, Tredyffrin
Friday	AM	Swedesford Road, Paoli, PA
March 23	1:30-3:30	LEEDS & NORTHROP
Friday	PM	Summeytown Pike, North Wales, PA
March 26	9:00-11:00	GENERAL ELECTRIC
Monday	AM	Market & Delaware St., Camden, NJ
March 26	1:30-4:00	GENERAL ELECTRIC, Astrospace
Monday	PM	Jct. Rt. 571 & Rt. 535, East Windsor, NJ
March 27	8:30-11:00	AT&T BELL LABORATORIES
Tuesday	AM	200 Laurel Avenue, Middletown, NJ
March 27	2:00-4:00	AT&T BELL LABORATORIES
Tuesday	PM	Whippany Road, Whippany, NJ
March 28	9:00-11:00	ITT Defense Communications
Wednesday	AM	492 River Road, Nutley, NJ
March 28	12:30-2:00	ALLIED SIGNAL AEROSPACE, Test Systems
Wednesday	PM	Route 46, Teterboro, NJ
March 28	2:30-4:00	ALLIED SIGNAL AEROSPACE, Flight & Guidance
Wednesday	PM	Route 46, Teterboro, NJ
March 29	9:00-11:00	AIL SYSTEMS INC.
Thursday	AM	Comac Road, Deer Park, NY
March 29	12:00-1:30	AIL SYSTEMS INC.
Thursday	PM	1 Walt Whitman Road, Melville, NY
March 29	2:30-4:00	NORDEN SYSTEMS
Thursday	PM	75 Maxess Road, Melville, NY
March 30	8:00-10:00	GRUMMAN CORPORATION, Aircraft Systems
Friday	AM	Stewart Avenue, Bethpage, NY
March 30	11:00-1:00	GRUMMAN CORPORATION, Aircraft Systems
Friday	AM-PM	Maxess Road, Melville, NY
March 30	2:00-3:30	NORDEN SYSTEMS
Friday	PM	500 Bi-County Blvd., Farmingdale, NY

**Check the site itinerary above for the date and time we visit your company. Make a point to attend this unique "hands on" exhibit and see the very latest in new products and services from this years' exhibitors.**

(ITINERARY SUBJECT TO CHANGE)



# Linear's family of choppers lays the competition to rest.



## No drift. No offset. No competition.

Introducing LTC1150. For the first time, a  $\pm 15\text{V}$  chopper with capacitors on-chip has the performance you've come to expect from LTC:  $5\mu\text{V}$  max offset,  $0.05\mu\text{V}/^\circ\text{C}$  max drift and low noise ( $0.6\mu\text{V}$  p-p 0.1 to 1Hz). You can plug the LTC1150 into your favorite  $\pm 15\text{V}$  precision bipolar op amp socket and eliminate offset voltage and drift with time or temperature as sources of error. No more annoying offset voltage changes with temperature cycling. The LTC1150 buries the competition.

Other members of the Linear family operate on lower supplies. The LTC1050 is the new industry standard for low cost precision

Part Number	Description	Max Vos (25°C)	Max TcVos	Typical 0.1 Hz to 10 Hz Noise	External Caps Req.	Max Supply Voltage
LTC1049	Single, Micropower	$10\mu\text{V}$	$0.10\mu\text{V}/^\circ\text{C}$	$3.0\mu\text{Vp-p}$	No	$\pm 9\text{V}$
LTC1050	Single, Low Power	$5\mu\text{V}$	$0.05\mu\text{V}/^\circ\text{C}$	$1.6\mu\text{Vp-p}$	No	$\pm 9\text{V}$
LTC1051	Dual, Low Power	$5\mu\text{V}$	$0.05\mu\text{V}/^\circ\text{C}$	$1.5\mu\text{Vp-p}$	No	$\pm 9\text{V}$
LTC1052	Single, 7652 Upgrade	$5\mu\text{V}$	$0.05\mu\text{V}/^\circ\text{C}$	$1.5\mu\text{Vp-p}$	Yes	$\pm 9\text{V}$
LTC1053	Quad, Low Power	$5\mu\text{V}$	$0.05\mu\text{V}/^\circ\text{C}$	$1.5\mu\text{Vp-p}$	No	$\pm 9\text{V}$
LTC1150	Single, $\pm 15\text{V}$ Operation	$5\mu\text{V}$	$0.05\mu\text{V}/^\circ\text{C}$	$1.8\mu\text{Vp-p}$	No	$\pm 18\text{V}$

choppers. When multiple op amps are needed, the new dual LTC1051 (8-pin DIP) and the new quad LTC1053 (14-pin DIP) match the LTC1050's performance and provide lower cost, space saving alternatives. The LTC1049 runs at only  $200\mu\text{A}$  supply current with slightly higher noise.

All devices are available in surface mount packages and perform to the same specifications as standard product. Pricing starts at \$2.25 in 100 piece quantities. For more details contact Linear Technology Corporation, 1630 McCarthy Blvd., Milpitas, CA 95035. Or call 800-637-5545.



TOUGH PRODUCTS  
FOR TOUGH APPLICATIONS.



## EDITED BY ANNE WATSON SWAGER

## 139



## DESIGN IDEAS

form to the input signal, you can calculate the mean of a number of samples that occur within one or more sawtooth-wave cycles. The cost of the increased resolution time is a longer conversion time.

The circuit in Fig 2 connects to the input of a M68HC11. The analog-input signal must lie between 0 and 1V, and the input impedance is 10 k $\Omega$ . IC<sub>1A</sub> integrates and filters the input signal; this stage's cut-off frequency is 37 Hz. By adding a small input offset voltage at the input to IC<sub>1A</sub> through R<sub>1</sub>, the circuit prevents the final output from ever going negative. IC<sub>1B</sub> adds the filtered input signal to the sawtooth wave and inverts the result. The output signal of the circuit, and thus the input to the MC68HC11, ranges from 0.05 to 4.95V.

You should set the value of the sawtooth wave's amplitude to around 20 times the smallest level difference of the converter. For example, an 8-bit, 5V converter would require 20(5/256), or 0.39V, as the p-p amplitude. The amplitude of the waveform at IC<sub>1B</sub>'s input is 5.9(10k/150k), or 0.393 V<sub>p-p</sub>.

You can write code for the MC68HC11 that calculates the mean of a number of consecutive samples using the flow diagram in Fig 3. Or you can write the authors at the following address for a listing of their M68HC11 interrupt-based resolution-extender program: Data-Guider Oy Inc, Visakoivunkuja 12 D 25, 02130 Espoo, Finland. The authors' program uses an algorithm that takes 128 consecutive samples, and uses them to calculate a 12-bit mean result. For a 12-bit result, the input-frequency-range limit is 0.78 Hz.

EDN

To Vote For This Design, Circle No. 748

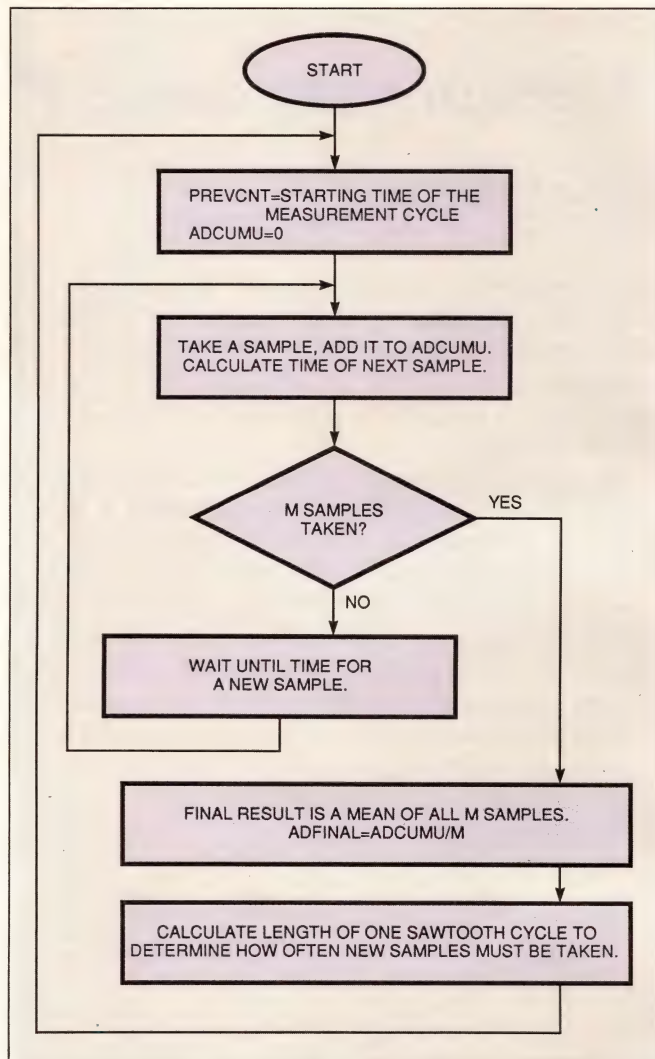


Fig 3—By writing code based on this flow diagram, you can implement a resolution extender for the MC68HC11.

## Precision amplifier turbocharges buffer

Charles Kitchen and Fred Benkley  
Analog Devices, Wilmington, MA


By combining a high-current buffer amplifier with a precision BiFET op amp, you can build a precise, high-current buffer amplifier (Fig 1). Because the LM675 power op amp is inside the feedback loop of the AD711 BiFET op amp, the circuit exhibits the low input offset, low bias current, and low distortion characteristics of the AD711. With 10-kHz inputs, this circuit achieves a THD of less than 0.003% and a maximum offset voltage of 1 mV. The two op amps work well together

because the AD711 has twice the slew rate of the LM675. Thus, the AD711 can quickly damp out any overshoots by the LM675.

You can configure the circuit as the high-input-impedance, unity-gain follower shown in Fig 1. Or, you can add a resistor to the overall feedback, add the input through a resistor to the inverting pin, and ground the noninverting pin of the AD711 to achieve a low-input-impedance inverting amplifier. The inverting-amplifier configuration has approximately 10 dB less distortion than the follower configuration; grounding the positive input eliminates the large amount of



# Super Amplifier

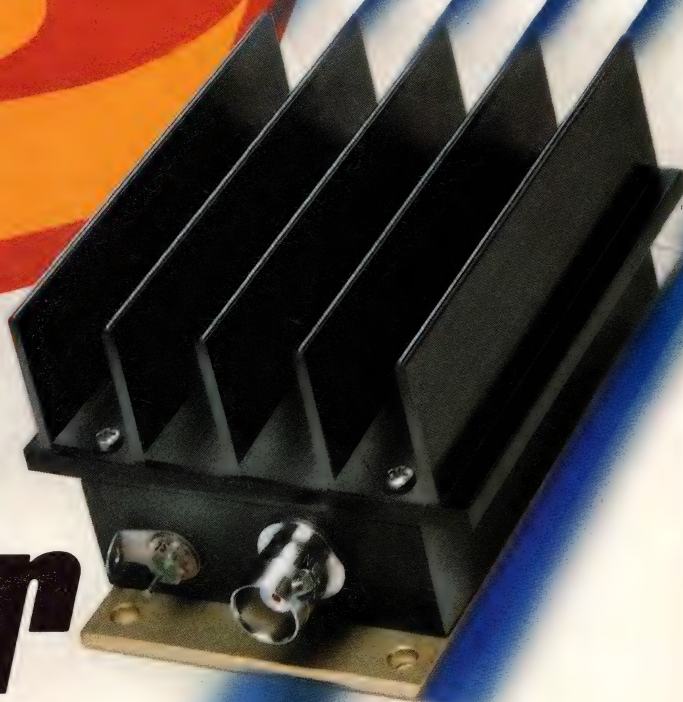

**2.5KHz to 500MHz 250mW only \$199**

**POWERFUL** up to +23dBm undistorted output

**FLAT** within 1dB over the entire band. 2.5KHz to 500MHz

**UNCONDITIONALLY STABLE** regardless of load

**DAMAGE-RESISTANT** built-in current regulator; supply voltage 24V, 0.35A

**RUGGED** operates from -55 to +85° C, withstands shock and vibration, ground equipment

**COMPACT** only 3.75 by 1.8 by 2.6 in.

Packed with these super performance features, 22dB flat gain and a typical VSWR of 1.3 to 1, the ZHL-6A amplifier is ideally suited for your latest broadband systems designs. And where space is critical, its height can be cut in half, to only 0.9 in., by removing the heat sink and attaching the unit to your chassis.

Running tests in your lab or on the production line covering all or segments of the 2.5KHz to 500MHz range and need more output from sweep or signal generators? It's not necessary to purchase and connect/disconnect an assortment of amplifiers when the ZHL-6A does it all...at an attractive price of only \$199.

For a super price/performance amplifier, order a ZHL-6A, available for immediate delivery with a one-year guarantee.

finding new ways ...  
setting higher standards

**Mini-Circuits**

A Division of Scientific Components Corporation  
P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500  
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156



F127 Rev A



# DESIGN IDEAS

common-mode voltage that appears across the input terminals of an AD711 connected in a follower configuration.

The phase-lead network comprising  $C_1$ ,  $R_3$ , and  $R_4$  provides the necessary compensation to stabilize the response of the AD711 and LM675. You can tailor this network for your particular circuit application by trading bandwidth for phase margin (Table 1). The inverting circuit with a phase margin of  $61^\circ$  is stable when driving coaxial cable loads 100-ft long and resistive loads as low as  $10\Omega$ .

You can achieve the full 20W rms rating of the LM675 by running the LM675 from  $\pm 21V$  supplies and the AD711 from  $\pm 18V$  supplies. When you power both op amps from  $\pm 18V$  or  $\pm 15V$  supplies, the circuit can respectively provide 15 or 10W rms to an  $8\Omega$  load. Always include a 2- to  $5\text{-}\mu\text{F}$  electrolytic capacitor on


**Table 1—Buffer-amplifier performance**

$R_3$	$R_4$	$C_1$	Connection	Small-signal -3-dB bandwidth	Phase margin
4.02k	200	30 pF	Follower	1.77 MHz	$35^\circ$
4.02k	100	68 pF	Follower	1.58 MHz	$70^\circ$
4.02k	64.9	100 pF	Follower	1.34 MHz	$86.3^\circ$ *
4.02k	400	30 pF	Inverter	1.8 MHz	$24^\circ$
4.02k	200	68 pF	Inverter	1.6 MHz	$61^\circ$
4.02k	80	100 pF	Inverter	890 kHz	$89.5^\circ$ *

\* Preferred connection for best transient response and highest stability

each power-supply line, and  $0.1\text{-}\mu\text{F}$  capacitors at each amplifier's power-supply input. **EDN**

To Vote For This Design, Circle No. 749

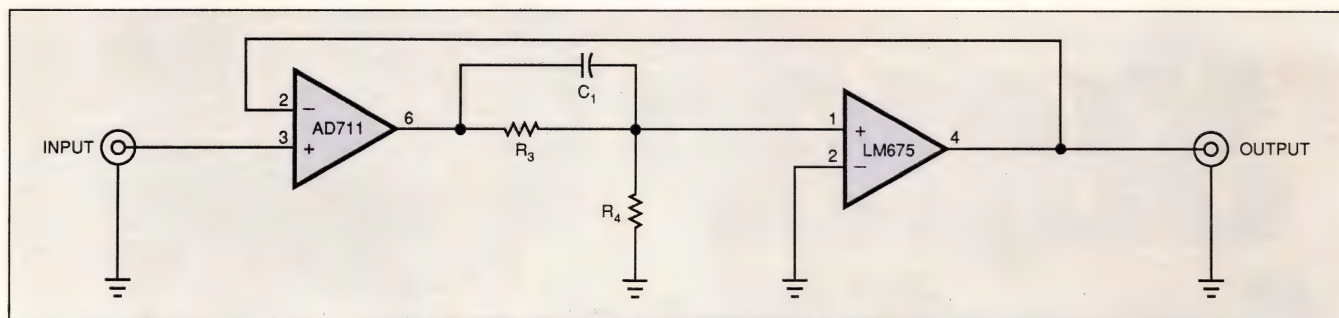

**Fig 1—By matching the talents of two op amps, this circuit can precisely drive high-power loads.**

## Feedback enhances thermometer accuracy

T G Barnett

*The London Hospital Medical College  
London, UK*

**Fig 1's** circuit measures body temperature by sensing both the temperature inside the ear's auditory meatus and the temperature of a heating pad inside an external heatset. By means of servo control, the circuit holds the heating pad's temperature approximately  $0.2^\circ\text{C}$  below the temperature of the auditory meatus. Thus, the heating pad minimizes the effects of the temperature outside the ear. The circuit implements a simple proportional controller, which operates in a slightly underdamped mode. Underdamping leads to small overshoots of pad temperature, which allow the circuit to reach the required temperature more quickly than if it were critically damped.

$R_{T1}$  and  $R_{T2}$  are interchangeable R-T curve-matched thermistors with tolerances of  $\pm 0.05^\circ$  over the 32 to

$42^\circ\text{C}$  temperature range.  $R_{T2}$  comprises a probe that you insert 10 mm into the auditory meatus.  $R_{T1}$  sits on the heating pad. Both thermistors are part of a Wheatstone bridge, whose output voltages differentially drive two LM363 precision instrumentation amplifiers. These amplifiers,  $IC_1$  and  $IC_2$ , both have preset gains of 10.  $IC_1$ , the ear-probe amplifier, receives its signal from  $R_{T2}$ .  $IC_2$ , the heating-pad amplifier, receives its input signal from  $R_{T1}$ . Switch 1 feeds either amplifier output to a 20V full-scale digital panel meter so that you can read the ear-probe and heating-pad temperatures. You can trim the meter's gain to indicate a  $100\text{ mV}/^\circ$  change in the thermistor-sensed temperature.

Two different voltage dividers feed the two instrumentation amplifiers' sense pins. The dividers include  $2\text{-k}\Omega$  potentiometers, which are buffered by two op amps,  $IC_{3A}$  and  $IC_{3B}$ . You can adjust the potentiometers to offset the instrumentation amplifiers' outputs



# WIN AN ALL EXPENSE PAID TRIP INTO THE FUTURE.



## Up to one-half million dollars in prizes.

RTX™ is the wave of the future in embedded control. It's the only microcontroller optimized for the unique demands of real-time, offering 10 MIPS of predictable performance in low-power CMOS.

And to show you how easy it is to develop your vision of the future on the RTX, we'll help pay your expenses along the way. Announcing the *Harris/Embedded Systems Programming Magazine* Real-Time Design Competition.

## 1,000 Free RTX Development Kits.

The Harris/ESP Real-Time Design Competition begins with nothing but ideas. Simply send us your application ideas for the RTX. And if your entry qualifies, we'll give you a free RTX development kit.

Up to 1,000 free RTX development kits will be given away. The kit includes a Euro-card size RTX development board, with 16K of PROM, 4K of SRAM, serial port and

development software.

Once you've qualified for a development kit, you've already won a \$500 value. But there's lots more to win.

## \$10,000 Grand Prize

The grand prize winner, as chosen by Harris and *Embedded Systems Programming Magazine*, will win a \$10,000 prize, so you can continue your trip into the future, all expenses paid.

## Send for your entry kit today.

The Harris/ESP Real-Time Design Competition is happening in real time. Initial proposals must be received by April 16, 1990. Send for an entry kit with complete rules and regulations. Call 1-800-4-HARRIS, ext. 1008 (in Canada, 1-800-344-2444, ext. 1008).



What your vision of the future demands. Today.



# DESIGN IDEAS

so that the meter reads the required temperature. For example, you can hard wire the meter's decimal point and adjust the potentiometer so that the meter reads 37.1°C when it senses 3.71V.

IC<sub>3C</sub> and IC<sub>3D</sub> together form a high-impedance differential amplifier with an overall gain of 23. The outputs of IC<sub>1</sub> and IC<sub>2</sub> drive the inputs to IC<sub>3D</sub> and IC<sub>3C</sub>, respectively. Note that a divider network, which includes a 5-k $\Omega$  potentiometer, attenuates the output of the heating-pad amplifier. By adjusting the potentiometer, you can adjust the set differential between the pad and the ear. The differential amplifier's output drives IC<sub>4</sub>, a high-power op amp with a gain of 11 and a frequency response limited to 3.3 Hz.

The output of IC<sub>4</sub>, in turn, drives the heating pad,

which consists of a form of conductive rubber and has between 25 and 35 $\Omega$  of resistance. The parallel LED indicates when power is on. For safety, the design attaches the pad to a thermal switch, which is set to open at 50°C.

You can power this circuit from a 12V rechargeable NiCd battery as shown in Fig 2. The 12V battery output directly powers IC<sub>4</sub>, but the other op amps receive their power from three low-power precision reference sources. Fig 2 includes a 50-mA antisurge protector to limit current under fault conditions.

EDN

To Vote For This Design, Circle No. 750

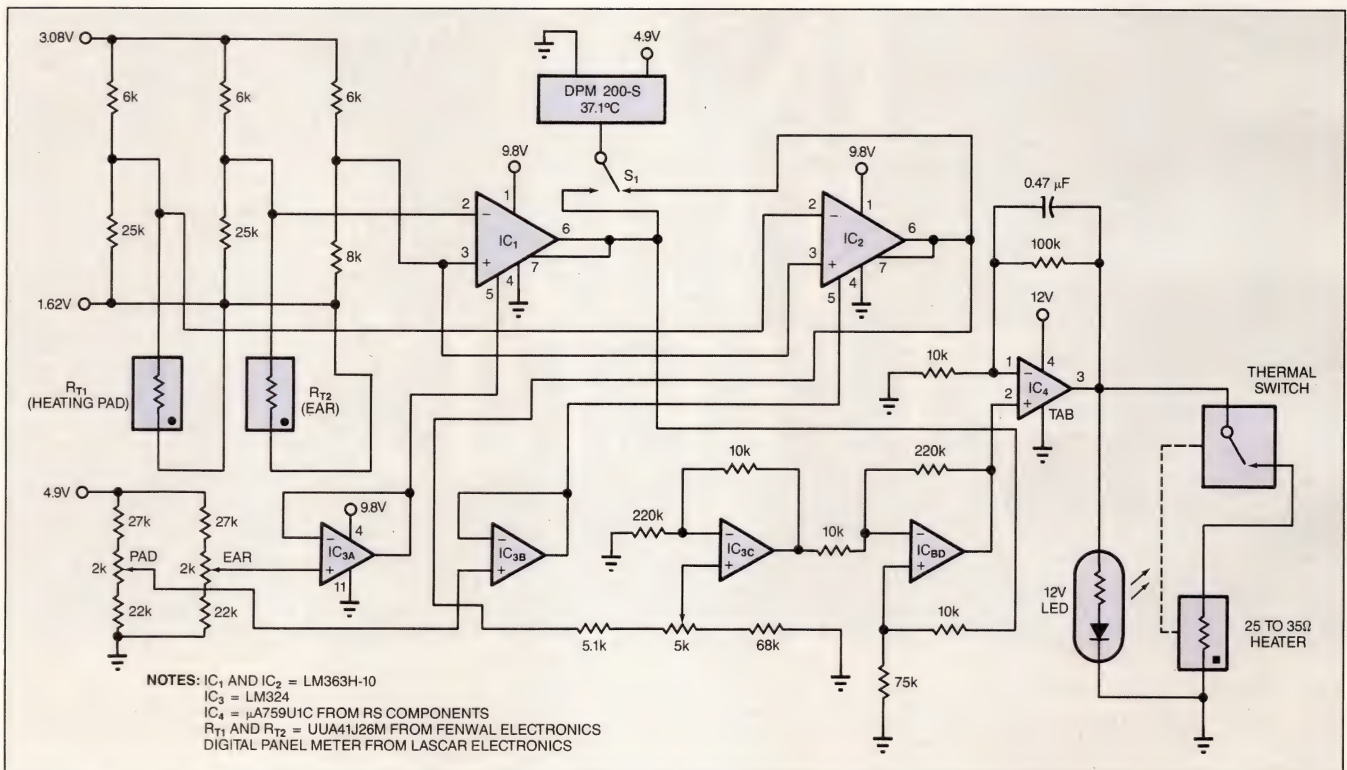


Fig 1—To accurately measure body temperature, this control circuit maintains a small temperature difference between an ear probe and an over-the-ear heating pad. The heating pad minimizes the effects of external temperature conditions on the thermometer's measurement.



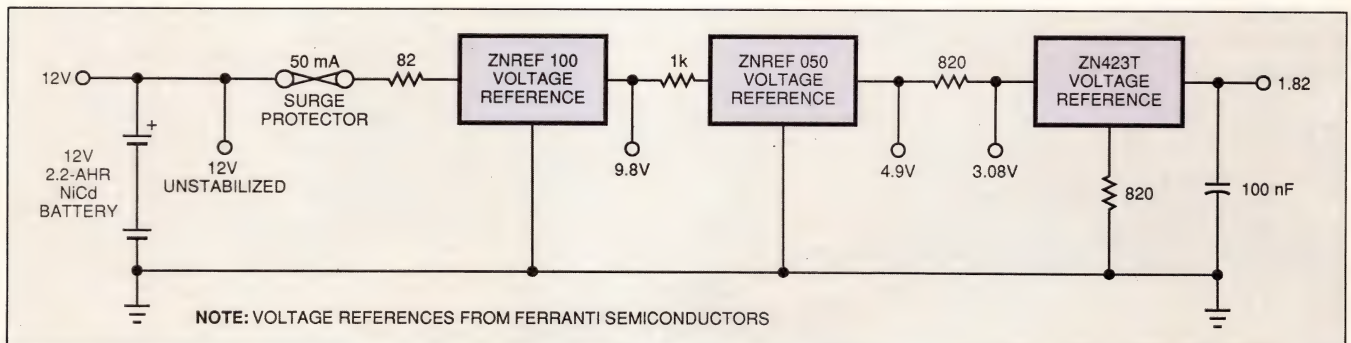


Fig 2—A 12V battery drives the output power amp, but precision references power the circuitry used for actual temperature measurement.

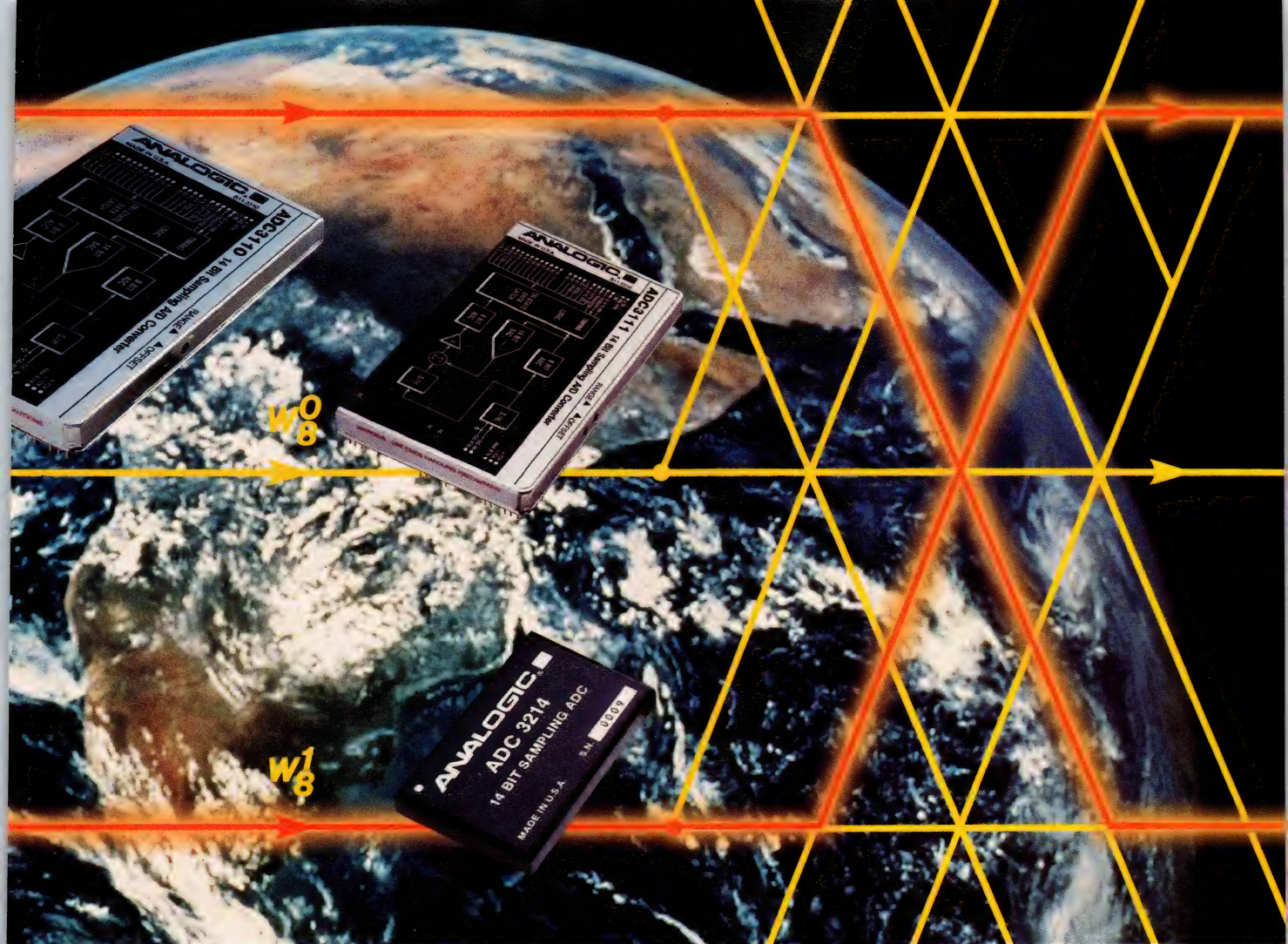

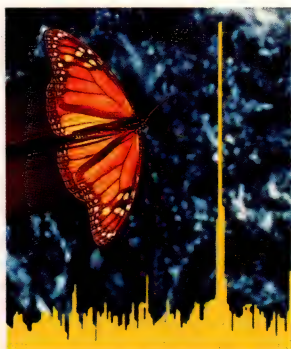

# Our A/D's Were Designed to Give You Butterflies!\*



\* The illustrated flow graph of the Cooley-Tukey algorithm is known in the industry as a butterfly computation.

*True 14-Bit Performance at 1 & 2 MHz Sampling Rates*

Analogic's new, ultra stable 14-bit sampling A/D converters make the most of your post-processing computations. Using advanced hybrid and surface mount technology, these sampling A/D's provide the most cost-effective solution to your high speed, high resolution applications.

This new family of sampling A/D's, designed for low noise and low distortion, provides 14 bits of resolution with true 14-bit performance. An 84 dB signal-to-noise ratio and our guarantee of no missing codes over an operating temperature range of 0°C to 60°C make these units unique. The ADC3110 in the frequency domain and the ADC3111 in the time domain will digitize signals up to 1 MHz at a 2 MHz rate, thus achieving unprecedented speed vs. accuracy performance. The ADC3214 has a 1 MHz sampling rate and is packaged as a compact 2" x 3" hybrid.

Our new sampling A/D's will perform superbly in your most demanding OEM applications. Digital oscilloscopes, waveform analysis, high speed data acquisition, sonar and digital signal processors. Whatever your DSP needs, Analogic has a sampling A/D to help you catch the butterflies...fast.

We even pledge it in writing. Unlike other manufacturers, Analogic puts all our sampling A/D's through exhaustive tests on our proprietary automatic test systems. The test data shipped with each product is our proof that it meets or exceeds our published specifications. What else would you expect from the world resource for A/D converter technology?

For Application Assistance: Richard Lentini  
Analogic Corporation, 360 Audubon Road,  
Wakefield, MA 01880 (508) 977-3000 X2170  
Telex: 466069, Fax: (617) 245-1274

CIRCLE NO. 71

**ANALOGIC**

*The World Resource  
for Precision Signal Technology*



# DESIGN IDEAS

## Design Entry Blank

**\$100 Cash Award** for all entries selected by editors. An additional **\$100 Cash Award** for the winning design of each issue, determined by vote of readers. Additional **\$1500 Cash Award** for annual Grand Prize Design, selected among biweekly winners by vote of editors.

To: Design Ideas Editor, EDN Magazine  
Cahners Publishing Co  
275 Washington St, Newton, MA 02158

I hereby submit my Design Ideas entry.

Name \_\_\_\_\_

Title \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Division (if any) \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Design Title \_\_\_\_\_

Home Address \_\_\_\_\_

Social Security Number \_\_\_\_\_  
(Must accompany all Design Ideas submitted by US authors)

**Entry blank must accompany all entries.** Design entered must be submitted exclusively to EDN, must not be patented, and must have no patent pending. Design must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_

Date \_\_\_\_\_

### ISSUE WINNER


The winning Design Idea for the September 28, 1989, issue is entitled "Transistors boost difference amp," submitted by R Mark Stitt and Rod Burt of Burr-Brown Co (Tucson, AZ).

**Your vote determines this issue's winner.** All designs published win \$100 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize. **Vote now**, by circling the appropriate number on the reader inquiry card.


## The World's Fastest Quad Comparator...
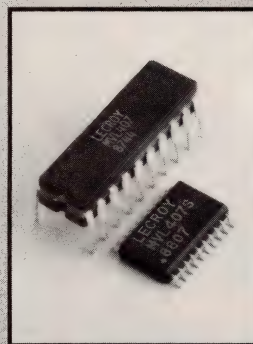
### LeCroy's MVL407

**... For Only \$2 Per Channel\***  
**... Now Available In SOIC Packaging†**  
**... When Performance Makes The Difference!**



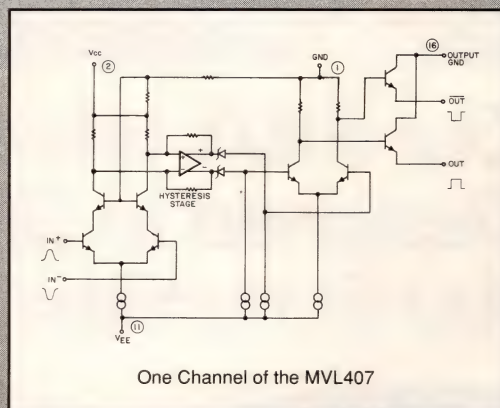- 400 MHz Operation
- 3.5 nsec Propagation Delay
- 4.8 mV Hysteresis
- 100 mW/Comparator Typical
- Complementary ECL Outputs
- 4 Comparators in 20-pin DIP or SOIC



One Channel of the MVL407

#### Applications:

- |                          |                              |
|--------------------------|------------------------------|
| ■ ATE                    | ■ Robotics                   |
| ■ Disk Testing           | ■ Remote Sensing             |
| ■ Communications         | ■ Precision Timing           |
| ■ High Speed Interfacing | ■ Physical Sciences Research |

\* quantity 10,000 parts



† for surface mount, specify MVL407S

Corporate Headquarters  
700 Chestnut Ridge Road  
Chestnut Ridge, NY 10977-6499  
Telephone: 1-800-5-LECROY  
or (914) 578-6013

**LeCroy**  
Innovators in Instrumentation



# TAILORED OPTICAL POWER

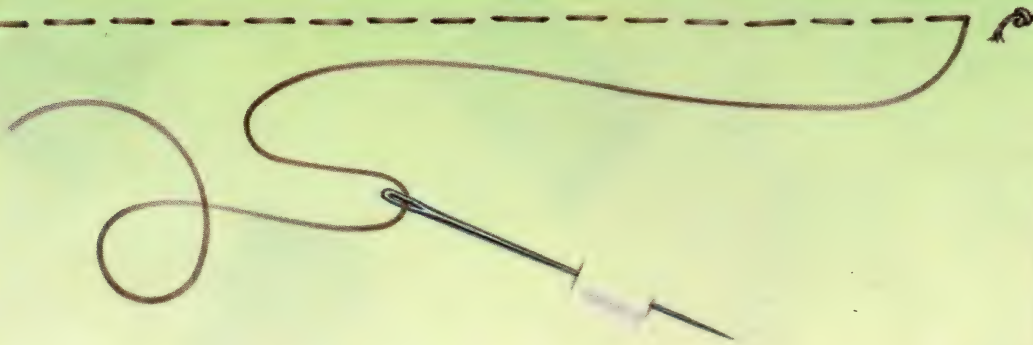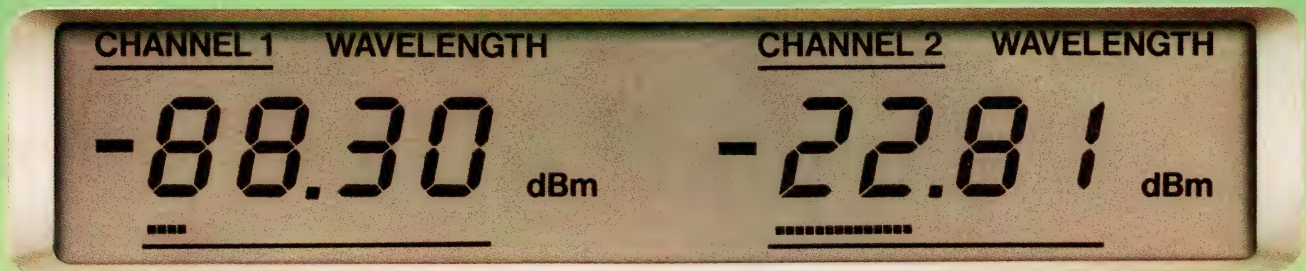


## From The Laboratory To The Field... Choose The Fit That's Best For You

- Highest Accuracy, Stability, Linearity
- Interchangeable Optical Connectors
- Power Range:  
-100 dBm to +10 dBm
- Wavelength:  
380 nm to 1800 nm
- Automatic Wavelength Correction

Accurate, reliable and repeatable optical power measurement is assured with Anritsu. Featuring a broad range of possible configurations,

Anritsu offers the total solution for all your optical power measurement requirements. Tailor your optical power with: the dual channel ML910B or single channel ML9001A in the lab and match the same performance in the field with the ML9002A.

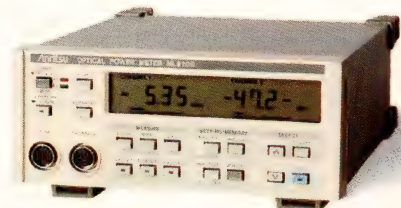Suit yourself ... for a demo, literature or application assistance, contact ... Anritsu America, Inc., 15 Thornton Road, Oakland, NJ 07436. Call 800-255-7234 or (in NJ) 201-337-1111. FAX 201-337-1033.




# Anritsu



**Compatible solutions  
for industry**
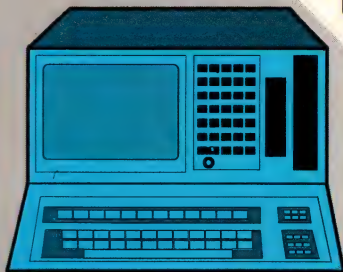
# Process Controllers

...galore!  
but one giving  
complete solutions  
is a rarity indeed



## We offer

- Expertise and experience in system solutions
- Support from a single source
- AT compatibility
- Programming languages and user interfaces
- Worldwide support from highly trained staff

D-8000 München 80  
Postfach 80 14 69  
Telex 523 703 (rs d)  
Telefax (0 89) 41 29-21 64  
Tel. internat. +(49 89) 41 29-0



**ROHDE & SCHWARZ**

An independent concern, founded in 1933.  
5000 employees, represented in 80 countries.  
Design and turn-key installation  
of systems with software and servicing.  
Calibration, training and documentation.



# NEW PRODUCTS


## COMPONENTS & POWER SUPPLIES

### Modular Power Supplies

- 600W max output
- Available in single and multiple output versions

StakPak II off-line switching power supplies are available with anywhere from one to five outputs. Maximum output capability equals 600W, and fully regulated output-voltage options range from 2 to 95V. Housed in a package measuring 1.9×5.5×12 in., the supplies are self cooled and offer full output at 40°C. Efficiency measures 85% max. A paralleling option allows you to share current among as many as four outputs. The supplies carry UL and CSA safety approvals. 600W model, \$980.

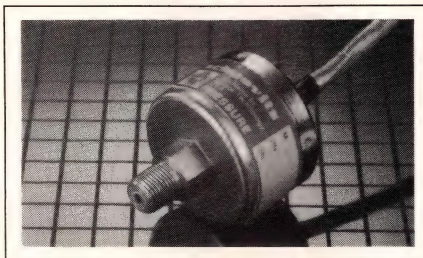**Westcor Corp.**, 485-100 Alberto Way, Los Gatos, CA 95030. Phone (408) 395-7050. **Circle No. 369**



### 2-Wire Pressure Transmitter

- Has  $\pm 1$  FS-output accuracy
- Has a 4- to 20-mA output

The Model 5081 2-wire pressure transmitter is compatible with data loggers and other instrumentation used in process control applications. The unit provides a 4- to 20-mA output from a 12 to 45V dc excitation; it offers both vented and sealed-gauge measurements over ranges of 0 to 5000 psi. Combined non-

linearity, hysteresis, and nonrepeatability are rated at  $\pm 1$  FS output. Stainless-steel construction allows you to operate the unit in corrosive media. The unit is also water resistant. From \$300.

**Schaevitz Engineering**, 7905 N Rte 130, Pennsauken, NJ 08110. Phone (609) 662-8000. FAX 609-662-6281. **Circle No. 370**

### Bulk Power Converter

- Has built-in power-factor correction
- Delivers 2100W

The PM2958-6 bulk power converter uses 0.99 power-factor correction to meet stringent international safety and EMI standards. The unit operates from inputs of 90 to 264V ac and delivers an output

## Crystal Clear LCD Modules

CRYSTAL CLEAR  
HANTRONIX LCD

Hantronix, Inc. has for immediate delivery, a large variety of high-resolution LCD modules. Our wide selection of formats include:

1 x 8	1 x 16	1 x 20	1 x 24	1 x 32	1 x 40	1 x 80
	2 x 16	2 x 20	2 x 24	2 x 32	2 x 40	
	4 x 16	4 x 20			4 x 40	

#### Also available are:

- Super Twist Models
- E/L or LED Backlight
- Extended Operating Temperatures (-20°C - 70°C)
- Positive or Negative Types
- Wide Viewing Angles
- Various Character Heights
- Custom Models
- Graphic Modules

For more information on our high-quality and moderately priced LCD modules, call or write:



**HANTRONIX, INC.**

250 Santa Ana Court  
Sunnyvale, CA 94086  
Tel: (408) 736-3191 • Telex: 880165 • Fax: (408) 749-0477

CIRCLE NO. 76


## Sampling A/Ds

DATEL's video speed sampling A/D converters give superior dynamic performance, to bring both harmonic distortion and signal-to-noise ratios to new lows.

For complete information call (508) 339-3000

Model	Sampling Rate	Effective Bits at Nyquist Frequency	THD* at Nyquist Frequency	Power Dissipation	Package
ADS-112	1MHz	11.0	-73 dB	1.3 watts	24-pin DDIP
ADS-132	2MHz	11.0	-73 dB	2.9 watts	32-pin TDIP
ADS-131	5MHz	10.6	-69 dB	4.2 watts	40-pin TDIP
ADS-130	10MHz	10.6	-69 dB	4.5 watts	40-pin TDIP

\*THD (Total Harmonic Distortion)

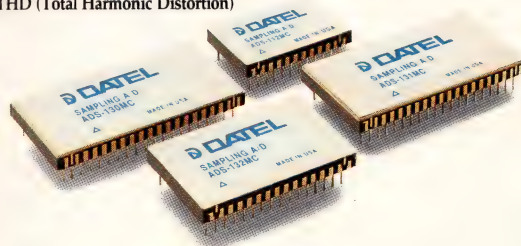

**DATEL**

INNOVATION AND EXCELLENCE IN PRECISION DATA ACQUISITION  
DATEL, Inc., 11 Cabot Boulevard, Mansfield, MA 02048 (508) 339-3000

CIRCLE NO. 77



of 375 to 390V, which can be delivered to a PWM power supply or a distributed dc bus network. Depending on input voltage, the single-output converter will deliver a 1680 or 2100W output. Weighing 10 lbs, the unit is housed in a forced-air-cooled enclosure measuring 4×8×11 in. Operating range meas-

ures 0 to 50°C at full load. MTBF is calculated at 200,000 hours. Over-voltage and overtemperature protection are standard. \$600 (OEM qty).

**Pioneer Magnetics**, 1745 Berkeley St, Santa Monica, CA 90404. Phone (800) 233-1745; in CA, (800) 848-1745. **Circle No. 371**

## Common-Mode Filter

- Meets FCC requirements
- Provides 20-dB attenuation

The TRF-2000 tip-and-ring filter helps you meet FCC Part 68 requirements in 2-wire telecomm applications. The unit attenuates common-mode noise by 20 dB over a 30- to 250-MHz frequency range. Attenuation equals 15 dB to a frequency of 300 MHz. The filter has a 1500V isolation figure between windings, and dc resistance/winding equals 40 mΩ. Housed in a package measuring 0.4 in. square and 0.55 in. high, \$1.50 (5000).

**Coilcraft**, 1102 Silver Lake Rd, Cary, IL 60013. Phone (708) 639-6400. **Circle No. 372**

## 4-Quadrant PWM Servo Amplifier

- Has 100A current rating
- 90% min efficiency

The AD5020 4-quadrant PWM servo amplifier can drive servo motors with ratings as high as 50V. Continuous current ranges from 10 to 100A, and output ripple equals 140 mV max. Efficiency is 90% min, and standby power is 6.7W. Optocouplers and Hall sensors are used for isolation. Rotary switches with 10 positions ease the set-up process. A jumper allows you to configure the amplifier for either speed-loop or current-loop operation. A thermistor provides thermal protection. \$446.

**Zahn Electronics Inc**, 2200 Northwestern Ave, Racine, WI 53404. Phone (414) 634-4300. **Circle No. 373**

## 4-Digit Programmable Displays

- Available in three colors
- Operate to 100°C

The IPD 4-digit, dot-matrix programmable displays are available in red (2545), green (2547), and yellow (2548). An 8-bit data word on the bidirectional bus supervises the



**Our CODE switches stand out in a crowd.**

**Industry's Largest CODE Switch Selection**


- Rotary DIP & Pushwheel switches
- Hundreds of code, actuation and termination combinations
- Largest choice of PC terminations for pushwheels
- PC or wire lug card edge connectors

**AUGAT/ALCOWITCH** offers a full product line including...

For your free catalog, product samples, applications help, or a quotation, call or write **AUGAT/ALCOWITCH**, 1551 Osgood Street, No. Andover, MA 01845 USA.  
Tel: (508) 685-4371, TLX: 275423, FAX: (508) 686-9545

**AUGAT® ALCOWITCH®**

Quality and Innovation

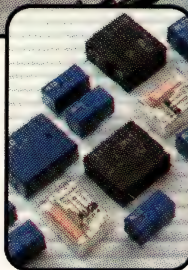

Relays



Toggles, Rockers, Pushbuttons



Industrial Controls

### AUGAT INTERNATIONAL SALES OFFICES

**AUGAT LIMITED - ENGLAND**  
**AUGAT SA - FRANCE**  
**AUGAT GMBH - WEST GERMANY**  
**AUGAT AB - SWEDEN**  
**AUGAT SRL - ITALY**  
**AUGAT ISRAEL**  
**AUGAT ELECTRONICS INC. - CANADA**  
**AUGAT RTY LTD. - AUSTRALIA**  
**AUGAT KK - JAPAN**

(011) 4490676655  
(011) 33146683090  
(011) 49896129090  
(011) 468960270  
(011) 3939654100  
(011) 9723492173  
(1) 4166771500  
(011) 6129050533  
(011) 810550897911



CMOS controller chip; the ASCII data and attribute data are word driven. Additional features include internal memory, decoders, multiplexers, and drivers. Viewing angle measures  $\pm 40$  and  $\pm 75^\circ$  for the X and Y axes, respectively. The TTL-compatible devices have a built-in character-generator ROM, read/write capability, and are easily cascaded to create larger displays. Software-controlled features include memory-clear function, lamp test, display-blank function, single- or multiple-character blinking, and three brightness levels. Operating range spans  $-55$  to  $+100^\circ\text{C}$ . \$100 (100).

**Siemens Components Inc.**, 19000 Homestead Rd, Cupertino, CA 95014. Phone (408) 725-3544.

Circle No. 374

## Solid-State Thermostat

- Monitors at the board level
- Has a  $\pm 1^\circ\text{C}$  accuracy

Housed in a  $0.48 \times 1.20$ -in. SIP, the TP Series solid-state thermostat monitors temperature at the board level. Designed for parallel or perpendicular mounting, the unit can trip at either one or two specified temperatures with  $\pm 1^\circ\text{C}$  accuracy. The unit operates over a 2 to  $65^\circ\text{C}$  range and is available in normally open or normally closed versions for 5 to 24V dc operation. Compatible with most logic, relays, and indicators, the thermostat employs an open-collector npn transistor for the output. From \$6 (5000).

**Cambridge Aeroflo Inc.**, 900 Mt Laurel Circle, Shirley, MA 01464. Phone (508) 425-2346. FAX 508-425-2338.

Circle No. 375

## Single-Turn Open-Frame Trimmers

- Resistance values range to 1 M $\Omega$
- Have a carbon element


Model 3319 9-mm, single-turn open-frame trimmers have standard resistance values ranging from 100 $\Omega$

to 1 M $\Omega$ . Housed on a ceramic substrate, the carbon resistive element is enclosed with a contaminant-resistant dust cover to increase life. The trimmers come with a choice of rotor colors (white is standard) and are available in side- or top-adjust models. Rated for 200 mW at  $70^\circ\text{C}$ , the units operate over a

$-25$  to  $+100^\circ\text{C}$  range. Contact-resistance variation equals 3% max, and temperature coefficient measures  $\pm 1000$  ppm/ $^\circ\text{C}$ . \$0.20 (1000). Delivery, stock to 12 weeks ARO.

**Bourns Inc.**, 1200 Columbia Ave, Riverside, CA 92507. Phone (714) 781-5500. TLX 676423.

Circle No. 376

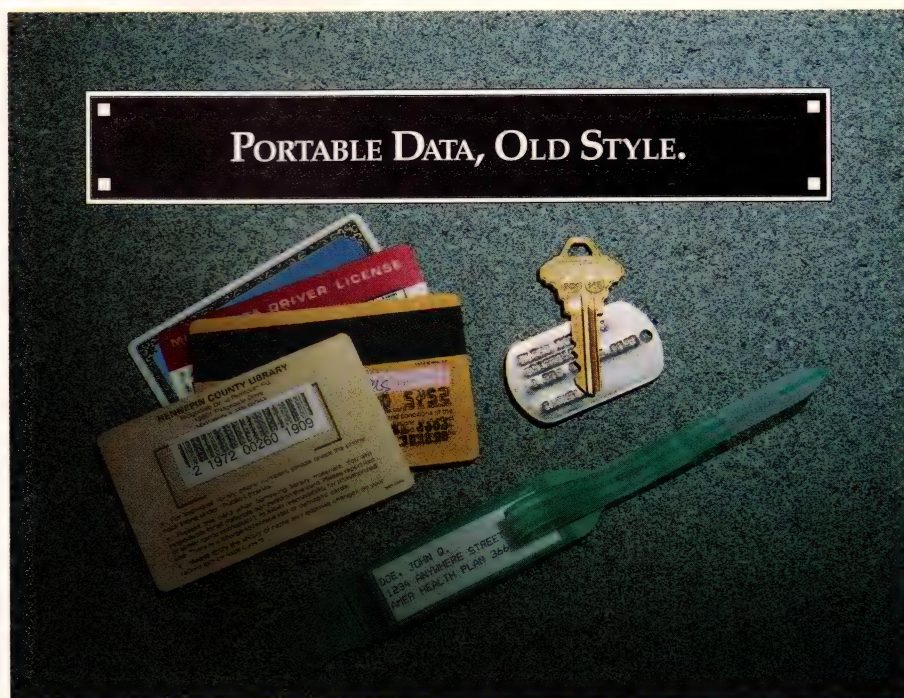

## PORTABLE DATA, OLD STYLE.

You've seen them all before. Everyday items you may not think about much. But, they have something in common: they all carry "data." Information that's important to you. And their size makes it easy for you to transport that data from place to place. In your pocket, your wallet, your briefcase, on your person, whatever's convenient.

Data that opens things up...identifies you to others...accesses machines, services, and physical areas...allows you to do repetitive tasks faster and easier...and more.

The need for new "portable data carriers" in today's world of miniaturization and convenience is growing all the time.

What does all this mean to you as an electronics design professional?

We'd like to tell you. Read on...

# Datakey®

Datakey, Inc. • 407 West Traveler's Trail, Minneapolis, MN 55337 U.S.A. • Phone (612) 890-6850 • Fax (612) 890-2726



# NEW PRODUCTS

## COMPUTERS & PERIPHERALS

### 3½-In. Hard-Disk Drive

- Has an IBM PC/AT Type 17 intelligent interface
- Transfers data at a burst rate of 4.5M bytes/sec

The KL343 3½-in. half-height hard-disk drive provides 42.5M bytes of formatted data storage. Its data-

transfer rate is 4.5M bytes/sec in burst mode and 720k-bytes/sec rate in sustained operation. The drive employs an IBM PC/AT Type 17 intelligent interface and has an average seek time of 33 msec. The drive features independent DMA channels, error correction, sector-



### VMIC's ANALOG I/O PRODUCTS JUST GOT SMARTER!

Our INTELLIGENT ANALOG I/O PRODUCTS feature a 68000 CPU for processing all inputs into user specified data formats and engineering units. The CPU also supports board and system level calibration; and non-volatile storage eliminates offset and gain potentiometers. Each board features dual port data registers, 13-bit digitizing of eight differential input channels, and accepts multiple input types simultaneously.

Our intelligent RTD/STRAIN GAGE BOARD provides excitation, lead compensation and linearization for RTD inputs, and accepts full and half-bridge strain gage inputs. The THERMOCOUPLE BOARD features fully isolated

inputs, and provides linearization and cold junction compensation for 11 thermocouple types; or a high level version can be used for current loop inputs.

So, when your project requires intelligent processing on VMEbus, call VMIC.



VMIC MICROSYSTEMS INTERNATIONAL CORPORATION  
12090 South Memorial Parkway, Huntsville, Alabama 35803-3308  
(205) 880-0444 or 1-800-322-3616 EXT. 2089 FAX: (205) 882-0859

INTERNATIONAL DISTRIBUTOR: Diamond Point International, Inc., 9 Enterprise Close, Medway City Estate, Rochester, Kent ME 24LY, U.K. (44) (634) 722390 FAX: (44) (634) 722398  
CANADIAN DISTRIBUTOR: Tracan Electronics Corp., 1200 Aerowood Drive, Unit 4, Mississauga, Ontario L4W 2S7 (416) 625-7752 FAX: (416) 625-4986

level defect handling, track and cylinder skewing, and a head autosleep mode. The device also contains an 8k-byte buffer between the host and the drive, which is expandable to 32k or 64k bytes. The MTBF is 40,000 power-on hours. The drive operates over a temperature range of 10 to 55°C. \$495.

**Kalok Corp.**, 1289 Anvilwood Ave, Sunnyvale, CA 94089. Phone (408) 747-1315. **Circle No. 358**

### Bitbus Interface

- Controls 250 devices for ISA bus computers
- Contains a 12-MHz 8044  $\mu$ C and two 28-pin sockets

The PC-Bitboss is a Bitbus interface board for the short slot in an ISA bus computer. The board can operate either as a master or as a slave. Operating as a master, it can control as many as 250 slave devices. The Bitbus Workbench software lets you control the Bitbus network using a windowed menu-driven format. You can send and receive messages, using the keyboard without writing code. The software drivers come in linkable source code that lets you incorporate them into an application program. The software also lets you download application programs to a specific node. A free application note and demo disk is available describing the software package. \$372.

**Computer Dynamic Sales**, 107 S Main St, Greer, SC 29650. Phone (803) 877-8700. **Circle No. 359**



## Memory Card

- *Plugs into the ISA bus*
- *Has access time of <160 nsec*

The PCard memory card plugs into the ISA bus and provides from 64k to 1024k bytes of storage with access times of <160 nsec. The product is available with static RAM, EPROM, or EEPROM storage devices. The PCard features dual-lithium batteries that can maintain data integrity as long as 10 years. Optional NiCad batteries are available for situations that require recharge. The card draws <55 mA from the host system and draws a maximum of 18  $\mu$ A from the battery during standby mode. A battery-management system continually checks and reports on the battery condition. The board operates over -20 to +60°C and is available with an RS-232C interface. 64k-byte version, \$98; 256k-byte version, \$244.

Plus 5, 1640 5th St, #224, Santa Monica, CA 90401. Phone (213) 395-6076. **Circle No. 360**

## 1553 Bus Adapter

- *Includes a 68020 or 68030  $\mu$ P*
- *Contains as much as 1M byte of dual-ported SRAM*


The Vx7-1553 adapter board for the VMEbus provides a communications path to the MIL-STD-1553 data bus. The board contains either a 68020 or a 68030  $\mu$ P operating at speeds as high as 33 MHz. Options include either a 68881 or a 68882 coprocessor. In addition, the board has as much as 1M byte of zero-wait-state dual-ported static RAM (SRAM), two multiprotocol serial ports, and a configuration controller with timers. The 6U board can implement the bus controller, bus monitor, and remote terminal modes of the MIL-STD-1553 specification. The adapter can also accept special applications modules that allow you to add a VSBbus, SCSI, or Ethernet interface. Monitor and mailbox interrupts permit real-time

processing. The single-slot board draws 3.1A from the 5V supply and a maximum of 50 mA from the  $\pm$ 12V supply. \$3793.

**General Micro Systems Inc.**, 4740 Brooks St, Montclair, CA 91763. Phone (714) 625-5475. FAX 714-621-4400. **Circle No. 361**
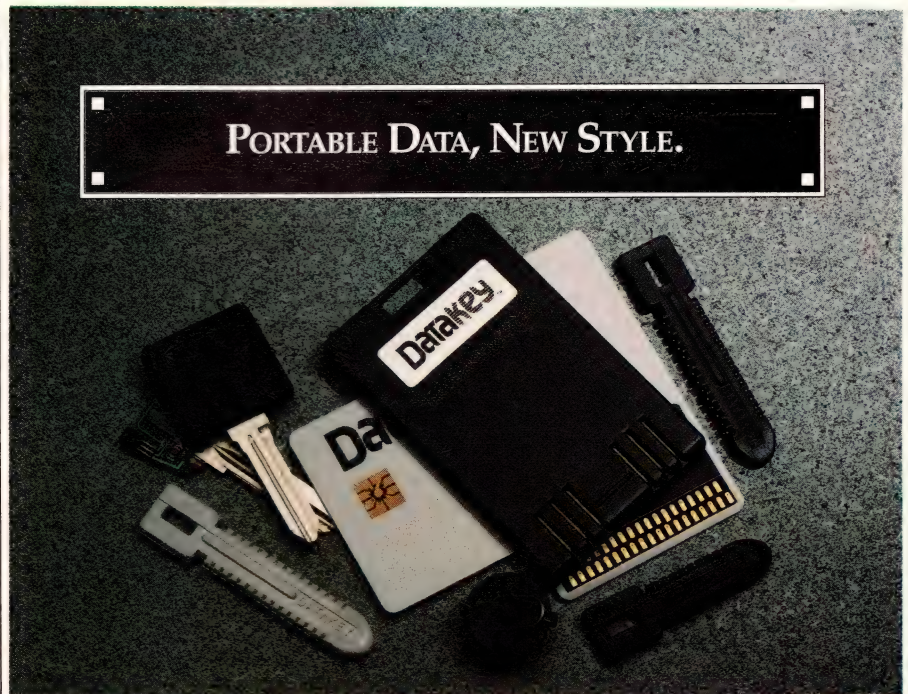
## Display Controller

- *Has 1280  $\times$  1024-pixel resolution*
  - *Provides 256 simultaneous colors*
- The VX8 graphics display controller card for the VMEbus provides 1280  $\times$  1024-pixel resolution for color X Windows applications. The



Welcome to the new world of portable data carriers. Small, pocket-sized devices that carry electronically recorded information so it's convenient to retrieve and use. For a variety of real-world applications.

They're made of tough, static-resistant, specially formulated plastic—to withstand rough handling and retain your data even when exposed to dust, dirt, moisture, magnetic fields, and other environmental hazards. In other words, to survive in your pocket—and in even more rugged environments.

Our expertise in packaging semiconductor memories and microprocessors has led to many advances in transportable data. Including the access device for the U.S. government's secure phone system. Hundreds of thousands of these data carriers are already in use. Today, our line of *standard products* includes several types of portable data carriers:

- *Serial EEPROM Keys:* with 1, 2, or 4-kbit capacity.
- *Parallel EEPROM Keys:* For high speed or direct microprocessor interface, from 16 to 512-kbit capacity, 8-bit word length.
- *Memory Cards:* credit-card type devices, with up to four Mbytes storage including chip-on-card or edge-connect.
- *Low-Cost Personal ID Tokens:* ideal for many office or industrial uses, each with 67 million unique, user-definable IDs.
- *And more:* including combination mechanical/electronic keys, and mil-spec type plug-in devices.

They're machine readable, smaller than floppy disks, require less power and cost less than disk drives, can store more data than mag-stripe cards...and they're much more rugged.

To learn more about the new wave in data portability, call toll-free today. (For custom applications, read on...)

# Datakey®


Advanced Solutions  
in Portable Data  
Technology,™

Datakey, Inc. • 407 West Traveler's Trail, Minneapolis, MN 55337 U.S.A. • Phone (612) 890-6850 • Fax (612) 890-2726

**Call 1-800-328-8828**  
Need it fast? We'll fax it.

See us at  
SYSTEMS/USA  
Booth # 340



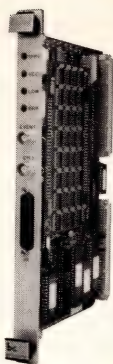

PC03V

- SYNCHRONIZE PROCESSORS
- TIME TAG DATA

#### IMMEDIATE SOLUTIONS TO YOUR TIMING PROBLEMS

Our off-the-shelf VMEbus time code translators and generators are a convenient, accurate means of synchronizing data processing systems to each other or to standard time of day satellite transmissions.

#### IMMEDIATE DATA SHEETS

Call or FAX a request to us for any of these FAX SPECS:

VMEbus boards:

PC03V Time Code Processor

PC05V Time Code Generator

PC26V Time Display

Model 9390 GPS Satellite Receiver



BANCOMM  
DIVISION OF DATUM, INC.  
6541 Via del Oro, San Jose, CA 95119  
CALL: (408) 578-4161 FAX: (408) 578-4165

CIRCLE NO. 82

## DSP Data Acquisition VMEbus - MULTIBUS I & II

### Floating Point Processor Boards

DUAL Texas Inst. TMS320C30's

### Fixed Point Processor Boards

TRIPLE Texas Inst. TMS320C25's

### Analog I/O Boards

- 10 MHz, 12-bit A/D with Buffer
- 32 Channel, 500 kHz, 16-bit A/D
- 16 Channel, 160 kHz, 12-bit A/D
- 16-bit, 50 kHz A/D & D/A with Filters
- 8 Channel, 12-bit, 160 kHz A/D with Filters
- Custom Designs to Fit Your System

Call one of our application engineers today to discuss your system requirements!

# PENTEK

10 Volvo Drive Rockleigh, NJ 07647  
(201) 767-7100

CIRCLE NO. 84

# PULSE-GUARD™

Providing Solutions for:

## ESD LIGHTNING HANEMP

Fast Acting • Low Capacitance  
High Energy

PULSE-GUARD™ is a Moldable,  
Flexible, Solderless Super-Varistor™  
that is available in:


**CONNECTORS • COAX  
CUSTOM APPLICATIONS**

For More Information, Call, Write or Fax - Today:  
750 W. VENTURA BLVD., CAMARILLO, CA 93010  
(805) 484-0543 • FAX: (805) 987-5062

**G&H Technology, Inc.**  
A UNIT OF PENN CENTRAL CORPORATION

CIRCLE NO. 83


## LOW POWER 80C88 BOARD

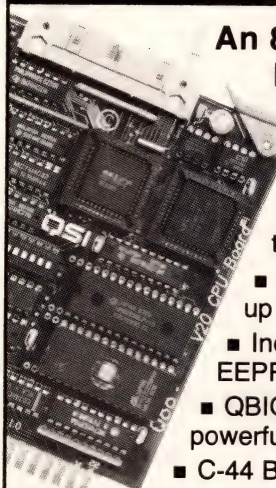

### An 80C88 (V20) CPU Board For Remote and Harsh Environments

- 5 MHz V20 CPU board; 21 mA active, 2 mA sleep.
- -40° to 85° C operating temperature range.
- Up to 256K memory on-board; up to 32M memory off-board.
- Includes: UART, real-time clock, EEPROM, and 22 digital I/O lines.
- QBIOS support software and a powerful monitor/debugger included.
- C-44 Bus compatible; 4.5x4.7" (114x 120 mm); 5 to 18 VDC supply; peripherals available include A/D, D/A, memory, data storage, IEEE-488, and others.

Q88 Unit  
Price  
\$495

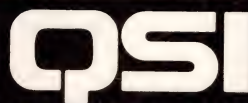

QSI Corporation  
1740 Research Park Way  
Logan, UT 84321  
CORPORATION (801) 753-3657


CIRCLE NO. 85 EDN February 1, 1990



card has 256 simultaneous colors from a palette of 16 million, and it refreshes a noninterlaced display at 60 Hz. Its graphics processor operates at 25 MIPS and can draw primitives as fast as 25M pixels/sec. In addition, the VX8 provides direct access to the frame buffer at a data-transfer rate of 20M bytes/sec for the host CPU or any bus master. The board translates 12-bit image data to 8-bit data before storage in the frame buffer and lets you view any quadrant of the frame buffer on a full-screen display. Other features include depth cuing and Gouraud shading for 3D applications. Optional X Server software for SunOS and VxWorks operating systems is available. \$4950.

**Jupiter Systems**, 1100 Marina Village Pkwy, Alameda, CA 94501. Phone (415) 523-9000.

Circle No. 362

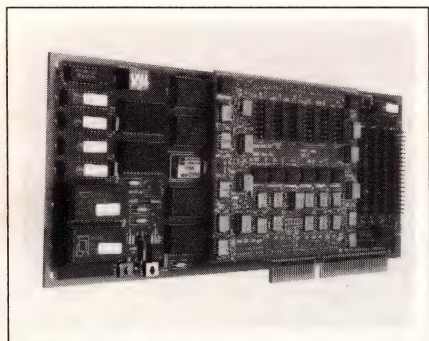

## NTDS Interface Card

- Connects to standard Navy computers
- Transfers 8-, 16-, or 32-bit data and half- or full-duplex devices


The IOC I/O controller card for ISA bus computers provides a Naval Tactical Data System (NTDS) port for connection to standard Navy equipment. The card lets the computer simulate Navy computers such as the AN/UYK-7, -20, -43, and -44. The NTDS port conforms to the MIL-STD-1397A specification. Under program control, the card can transfer 8-, 16-, or 32-bit data and either half- or full-duplex devices. The card automatically

configures itself to either the host's 8- or 16-bit bus. The IOC can execute either DMA or programmed I/O data transfers over the bus, and it can operate in either a polled or interrupt mode. In addition, the IOC has separate 512-byte FIFO buffers on the NTDS input and output ports as well as separate con-

trol, status, and word-count registers. \$2900, including driver and diagnostic software.

**Rockwell International Corp.**, Interface Products Group, Autonetics Marine Systems Div, BB44, 3370 Miraloma Ave, Anaheim, CA 92803. Phone (714) 762-1476.

Circle No. 363

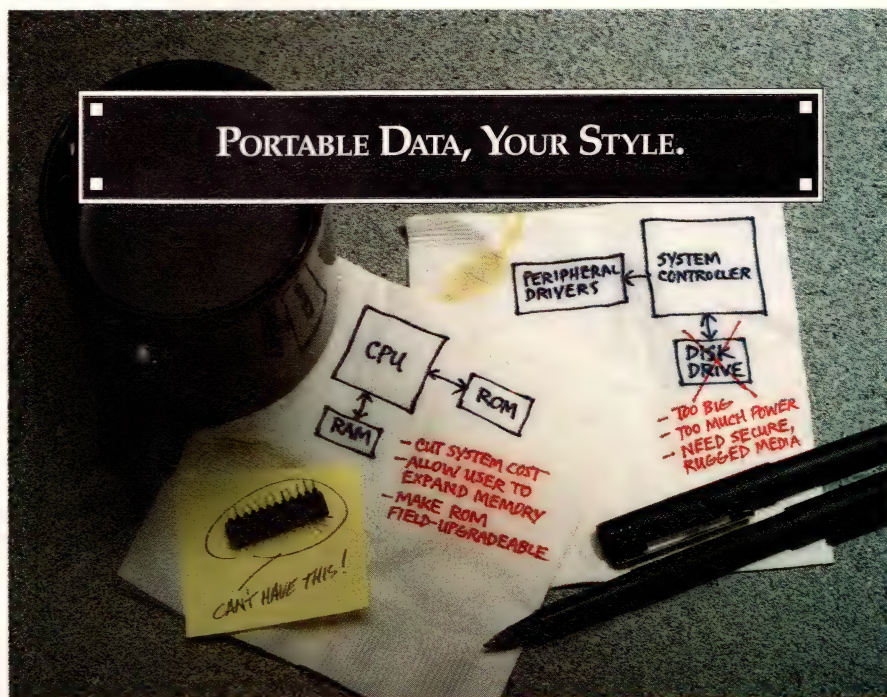

To meet your unique system design needs, we also manufacture custom portable data devices. For applications with limited system space, limited power availability, and other tough requirements. With end-uses as diverse as computer and communications system security, industrial process control, automotive, and medical electronics, to name a few.

Anywhere a simple, reliable, easy-to-use data carrier can help you improve user or system convenience...save keystrokes...reduce operator errors...improve security...load and transfer equipment operating parameters...collect data at remote sites...you name it.

Portable data is a proven, expanding technology that you as an electronics design professional should know about. So, we've written a booklet. In it, we describe some of the many benefits you can realize by adopting portable data technology in your system

designs, no matter what your volume needs:

- ☐ Save valuable system space
- ☐ Reduce system power requirements
- ☐ Cut costs... low-cost memory expansion
- ☐ Improve system security
- ☐ Speed data transfer, with more convenient data handling
- ☐ Make ROM upgrades quicker, easier
- ☐ Simplify your system
- ☐ Ruggedize your I/O device
- ☐ Reduce I/O device size, weight
- ☐ Differentiate your product competitively

For a free copy of the booklet, call us toll-free. The sooner you do, the sooner you can start putting portable data to use your way.



**Datakey**  
Advanced Solutions  
in Portable Data  
Technology,™

Datakey, Inc. • 407 West Traveler's Trail, Minneapolis, MN 55337 U.S.A. • Phone (612) 890-6850 • Fax (612) 890-2726

**Call 1-800-328-8828**  
Need it fast? We'll fax it.

See us at  
**SYSTEMS/USA**  
Booth # 340

CIRCLE NO. 81



# NEW PRODUCTS

## CAE & SOFTWARE DEVELOPMENT TOOLS

### Screen Generator


- Lets you design data-entry and custom screens
- Can provide data validation for 17 types of data

QuickScreen 3.0 is a screen designer for QuickBasic programmers. The program lets you draw text and backgrounds, define entry fields, and manage screen libraries that contain many screens in a single file. The package includes routines for field-by-field editing with full data validation of 17 different types of data. The program uses the same keystrokes as QuickBasic. You can store the screens that you create in any of three ways: as individual compressed-binary screen files; as object files that you can link with your application program; or in a screen-library file. The pro-

gram gives you complete control over colors and highlights, and you can incorporate a variety of video effects such as horizontal or vertical wipes, dissolves, opening curtains, or roll-aways. \$99.

**Crescent Software Inc.**, 11 Grandview Ave, Stamford, CT 06905. Phone (203) 846-2500.

Circle No. 364

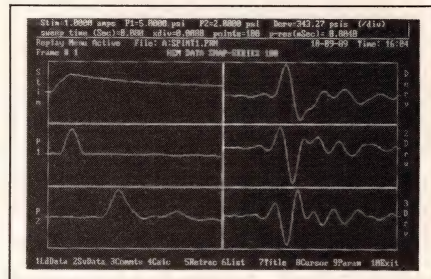

### Screen-Printing Utility

- Produces hard copy of a graphics screen display
- Can capture waveform displays to a disk file

Snap-Print works with most data-acquisition or other application software that displays images on the screen and captures a screen display either to a disk file or to a


hard-copy device such as a dot-matrix or laser printer. You can customize the printed-screen image by specifying the left and top margins on the page, the horizontal and vertical image size, draft or quality print, and whether black and white are to be reversed during printing. If you direct the output to a disk file, you can later merge the image into text generated by a word processor. The program is compatible

Text continued on pg 160

# ANNOUNCING . . .

## WORLD'S FIRST
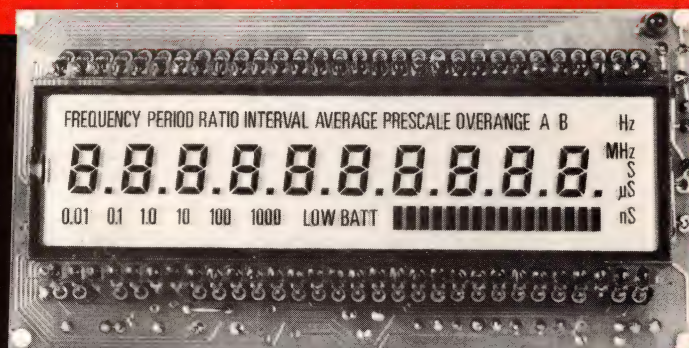
### High Performance Universal Counter Timer Module/Panel Meter



ACTUAL SIZE

#### INTRODUCTORY PRICING

Quantity	Price
1-10	189.00
11-99	159.00
100+	129.00

#### ENGINEERING EVALUATION KIT \$250.00

### OPTOELECTRONICS INC.

5821 N.E. 14th Avenue • Fort Lauderdale, Florida 33334  
(800) 327-5912 • FL (305) 771-2050 • FAX (305) 771-2052

- 10 Digit (120 Segment) LCD Display with Gate, Function, and Input Annunciators.
- .1 Hz to Over 150 MHz Direct Count (1 Hz resolution in 1 Sec).
- Single Shot Time Interval 100 ns, .1 ns averaged.
- Functions Include: Frequency, Period, Ratio, and Time Interval and Average.
- 16 Segment Analog Input Bargraph is driven by an 8 Bit A to D and Can Be Used for Signal Level Display.
- Low Power (250 mw) with Single 5v Supply.
- High Accuracy, 1 ppm 10 MHz Crystal Time Base with Cal Adjust on Board.
- Economical to Use in Custom OEM Applications.



# AT YOUR COMMAND.



## Data Acquisition and Instrument Control at Your Fingertips

With the CEC genie your wishes come true. You can control any IEEE-488 (HP-IB, GP-IB) instrument, printer, or plotter from your PC.

CEC's plug-in cards come with a software library of example programs and utilities that let you spend more time solving problems than programming. CEC provides software support for BASIC, Pascal, C, and FORTRAN.



If your wish is for a custom program, CEC also offers software that writes '488 programs. Simply pop up our software over your program editor and select a control function or library for your instrument. Code is automatically generated from your choices. Press a key and the magic begins. The code appears where you want it in your program.

Now, make your wishes come true by calling 800-234-4232 for your FREE demo disk.



**Capital Equipment Corp.**

99 South Bedford Street  
Burlington, MA 01803

Tel: 617-273-1818 Fax: 617-273-9057




with IBM CGA, IBM EGA, IBM VGA, and AT&T 6300 monochrome graphics boards. \$195, if purchased separately; \$150, if purchased with one of the vendor's other products.

**HEM Data Corp.**, 17336 Twelve Mile Rd, Suite 201, Southfield, MI 48076. Phone (313) 559-5607. FAX 313-559-8008. **Circle No. 365**

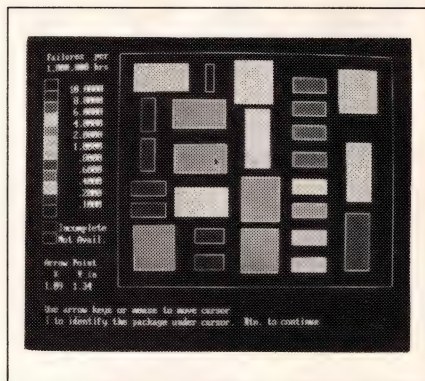
## Thermal-Reliability Analyzer

- Can evaluate boards of irregular shape
- Can interface with any CAD system

The BETAsoft software package runs on IBM PCs and compatibles and predicts the thermal perform-



## Are you looking for trouble ...?

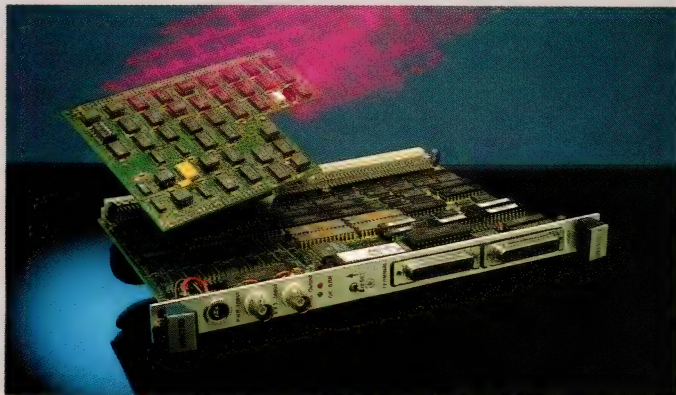


The VBT-321 Advanced VMEbus Analyzer concept has now been expanded with the new VBAT-321-Peggy-back module that automatically screens for violations of the VME specification.


You have come to the right place. VMETRO offers Bus Analyzers for VMEbus, VSB, Multibus II, PC AT/XT bus, NuBus and the MC680XX family of microprocessors. These easy to use instruments provide real-time logic state and performance analysis from a standard ASCII terminal or PC, saving you both time and money.

**Your trouble is our business.**


PMA-030680xx Program Analyzer

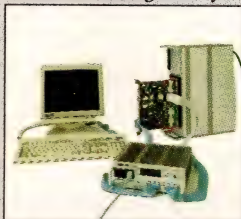

M2BT Multibus II Analyzer

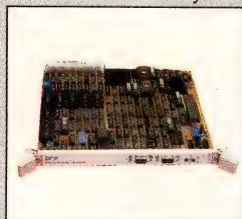

PCbus/NuBus Analyzers

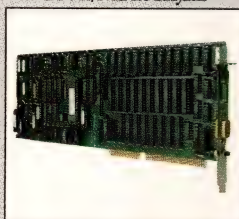

# VMETRO

*The Bus Analyzer Specialist*

VMETRO INC.  
2500 Wilcrest #550 Houston, TX 77042  
TEL: (713) 266-6430 FAX: (713) 266-6919

VMETRO AS  
Sognsvien 75, 0855 Oslo 8, Norway  
TEL: 47-2-394690 FAX: 47-2-183938

See us at Buscon West '90 Booth #630

ance of a pc board, using parameters contained in a library of more than 2500 ICs and heat sinks. The program creates a 3-D thermal model of the board and can handle as many as 800 components (including surface-mount types) on each side of the board; the maximum number of types/board is 400. The program can handle natural or forced cooling, or a combination of both. The finite-difference algorithm takes into account the complex airflow and thermal fields caused by components of different sizes and heights, and incorporates reliability predictions. Upon completion of the initial calculations, the program displays the board temperature and the individual temperatures of components and IC junctions; you can relocate overheated components or add heat sinks, and then obtain a new display. You can direct any display to a plotter for hard copy, and obtain a reliability analysis that's compatible with the MIL-STD-217E standard. To run the program you need an IBM PC, PS/2, or compatible that has at least 320k bytes of memory (640k bytes recommended), an EGA-compatible display, and a hard disk. A math coprocessor is not required but will increase the computation speed. With one CAD-system interface (P-CAD, AutoCAD, PADS-PCB, Racal-Redac, or other), \$2995.

**Dynamic Soft Analysis Inc.**, 213 Guyasota Rd, Pittsburgh, PA 15215. Phone (412) 781-3016. FAX 412-781-3098. **Circle No. 366**



## CAE & SOFTWARE

### Logic Compiler For PLDs

- Accepts input from schematic-capture program
- Compiles complete design rather than individual elements

The Schema-PLD logic compiler runs on IBM PCs, PS/2s, and compatibles. The compiler accepts input from the vendor's schematic-capture software and compiles the design to use PLDs. When compilation is complete, the program displays the PLD resources needed so that you can then select appropriate PLDs on the basis of performance, availability, and cost. The program generates output in the form of a standard JEDEC file and comes with libraries that include most mainstream PLDs. \$495.

**Omaton Inc.**, 801 Presidential Dr, Richardson, TX 75081. Phone (800) 553-9119. FAX 214-783-9072.

Circle No. 367

### Op-Amp Macromodels For Spice


- Disk provides new macromodels for six op amps
- Spice net lists included on disk

The PMISpice library contains new, improved macromodels of the vendor's OP-42, OP-61, OP-64, OP-260, OP-400, and MAT-03 op amps. These macromodels provide much greater accuracy than the standard Boyle macromodel, especially at frequencies above 1 MHz. They are modular in structure and allow you to include any number of poles and zeros to shape the frequency response of your design. The macromodels include Spice-compatible net lists. A 2-part article scheduled for the next two issues of *EDN* will show you how to adapt these models to your own op-amp designs. PMI customers can receive the disk at no charge.

**Precision Monolithics Inc.**, Box 58020, Santa Clara, CA 95052. Phone (408) 727-9222. FAX 408-727-1550.

Circle No. 368

## TO GET FROM HERE TO HERE

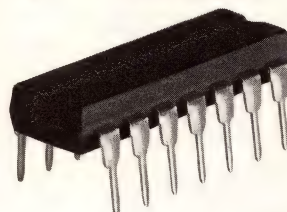

### You need a really good guide.

And this is it. The only transformer guide available that can help you get from wall plug to semiconductor chip circuit requirements with the least possible trouble.


Common mode inductor. Microprocessor power. DC-to-DC converter. F.E.T. driver. Telephone-interconnect series of transformers—that can be critical to your electronics design.

Board level. Total systems.

In short, everything associated with plug-to-chip energy management. And communications signals from "wet circuit" to "dry circuit". Along with the expertise you need to design it right the first time.

Plug into a good thing. Simply write us at East Bridgewater, MA 02333. Or call 1-800-422-1107. In Massachusetts, call (508) 378-5260.

**Foxboro/PCG**

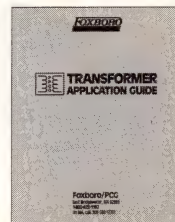

**FOXBORO**

CIRCLE NO. 89



### ICs For Telephones? Talk To Us!

For subscriber sets, cordless and cellular telephones, AEG has the Amplifiers, Tone Ringers, Speech Circuits, Programmable Filters, Charger Control ICs—virtually any customer specific circuit—We have information and products available for evaluation and use.

Contact: AEG Corporation, 3140 Rte. 22, PO Box 3800, Somerville, NJ 08876-1269, (201) 231-8493; Fax: (201) 231-8353.




**TELEFUNKEN electronic**  
Creative Technologies

CIRCLE NO. 90


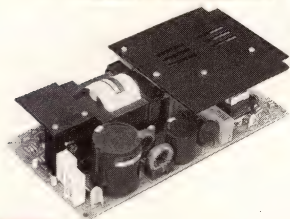
# IN-STOCK! UNIVERSAL INPUT VOLTAGE 100 WATT SWITCHERS



## FEATURES

- Universal input voltage 85-265 VAC
- 0% Minimum load on auxiliary outputs
- Meets UL, CSA, VDE and IEC standards
- VDE/FCC Class "B" onboard filter
- Indefinite short circuit protection
- Overvoltage protection
- Minimum 165,000 hours M.T.B.F.
- Compact size 4" x 8" x 2.2"

MODEL NUMBER	OUTPUT VOLTAGE/CURRENT
FLU4-100-1AD	+5V@15A, +12V@7.5A, -12V@0.75A, -5V@0.25A

Six models are available with voltage combinations of +5, -5, +12, -12 & +24 VDC.

## PRICE & DELIVERY

- \$159 for singles and \$121 each for 100 quantity. (For FLU4-100 Series)
- Delivery-Stock to 2 weeks


POWER GENERAL'S FLU3-100 & FLU4-100 series are families of triple & quad output 100 watt switching power supplies for Disk drive subsystems, Data communications, CRT terminals, & Microprocessor based systems.

These products are machine inserted, auto-tested and monitored under statistical process control on our JIT production line.

Power General utilizes the latest technology to provide complete, innovative solutions to your power needs.

**FREE HANDBOOK!**  
Call or Fax for detailed specifications and a free Power Supply Handbook.

**LET  
POWER GENERAL  
WORK FOR YOU!**

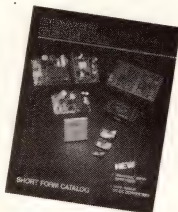


# POWER GENERAL

A SUBSIDIARY OF UNITRODE CORPORATION  
152 Will Drive, Canton, MA 02021  
TEL: (617) 828-6216 FAX: 617-828-3215

CIRCLE NO. 91

## NEW PRODUCTS

### INTEGRATED CIRCUITS

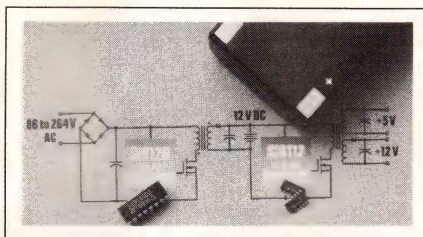

## Switch-Mode Controllers

- *Handle high voltages*
- *Use current-mode PWM*

The Si9112 and Si9120 are current-mode PWM controllers for use in switching power supplies. Both monolithic ICs include high-voltage start-up circuitry, an oscillator, an error amplifier, a voltage reference, and a noninverted output stage for direct drive of an external power MOSFET. The Si9112 is optimized for use in dc/dc converters that operate from 12V batteries or from dc voltages in the 9 to 80V range. The Si9120 has an input-voltage capability of 50 to 450V, which makes it suitable for use in power supplies operating from 110 or 220V ac power lines. Both devices are fabricated in CMOS, which reduces the quiescent current to less than 1.5 mA. The Si9112 comes in a 14-pin DIP and in a 14-pin SOIC package; the Si9120 comes in a 16-pin DIP. \$4.28 to \$4.90 (100).

**Siliconix Inc.**, 2201 Laurelwood Rd, Santa Clara, CA 95054. Phone (408) 988-8000. **Circle No. 351**

## 16-Bit Bus Interface With Several Functions


- *Transceiver and latched multiplexer/demultiplexer*
- *Interfaces to popular backplane buses*

The SN74BCT2423 16-bit bus interface integrates four octal bus transceivers and its control circuitry in a single BiCMOS IC. Manufacturers of computers and add-in boards can use the cascable device to interface to any popular backplane

bus including the Nubus, MCA (Micro Channel Architecture) bus, and AT bus. With an available drive current of 48 mA on the multiplexed side, the interface also supports the VMEbus and Multibus. Outputs on the demultiplexed A and B buses are rated at 24 mA. The device draws only 190 mA max when enabled and 50 mA max when disabled. The SN74BCT2423, which comes in a 68-pin PLCC (plastic leaded-chip carrier), operates from a 5V supply and is characterized over the 0 to 70°C temperature range. \$6.48 (1000).

**Texas Instruments Inc.**, Box 809066, Dallas, TX 75380. Phone (800) 232-3200, ext 700.

**Circle No. 352**

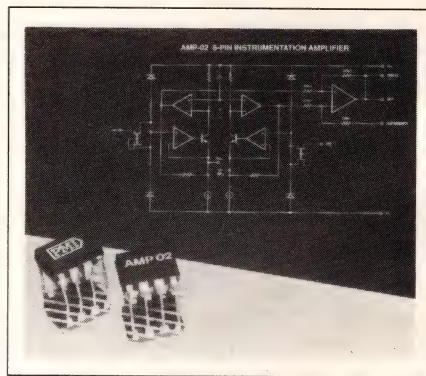

## Instrumentation Amplifier

- *Comes in an 8-pin package*
- *Features high accuracy*

The Amp-02 is a complete instrumentation amplifier in a space-saving 8-pin miniature DIP. The device, which needs only a single external resistor to set the gain, also offers internal overvoltage protection. Key specifications include an offset voltage of only 100  $\mu$ V max, temperature drift of less than 2  $\mu$ V/°C, a gain range of 1 to 10,000, and a minimum common-mode rejection of 115 dB. Because of its transimpedance input stage, the Amp-02 does not suffer a dramatic decrease in bandwidth as gain is increased.



# Micro Channel Bus Master Mastered.



**Just \$9.85**

Get your Micro Channel adapter boards to market fastest with the PLX MCA 3200 Bus Master Chip Set.

This two chip set supplies the bus master timing, control and local arbitration logic necessary to get you up and running at data transfer rates of 20Mb/sec.

Best of all, they're on the shelf right now, volume priced at only \$9.85.

## \$10 Fast-Start Design Kit Offer.

Get the jump on your competition. Order our MCA 3200 Fast-Start Design Kit today. Simply fill out this coupon and mail it to PLX Technology, 625 Clyde Ave., Mountain View, CA 94043. Or, for same-day shipment, call 1-800-759-3735.

Kit includes one MCA 3200 Chip Set, complete product specifications, and an application note with example circuits.

**PLX Technology, please rush me:**

- ☐ One MCA 3200 Fast-Start Design Kit.  
Package Type: ☐ PLCC or ☐ DIP  
☐ Payment Enclosed ☐ Bill Me

- ☐ Free literature only.  
☐ MCA 3200 Data Sheet  
☐ MCA 3200 Application Note

NAME \_\_\_\_\_ TELEPHONE \_\_\_\_\_  
COMPANY \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_




EDN2/1/90

Micro Channel is a trademark of International Business Machines Corporation.


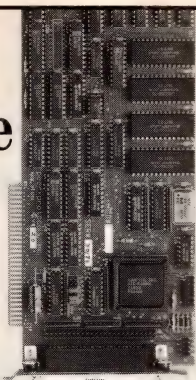
# Introducing the Great Boardware Protection Co.<sup>TM</sup> you may already know as the Great Software Protection Co.<sup>TM</sup>




SentinelChip protects the Peer-4000 SCSI Test System board for Peer Protocols, Inc.

**I**t didn't take long for people to start calling us The Great Software Protection Company. And we don't think it will take very much time for some more people to start calling us The Great Boardware Protection Co.

That's because of our new security device for printed circuit boards—the SentinelChip.<sup>TM</sup> It's the perfect finishing touch for your nothing-like-it, finally-on-the-market PCB that stops anyone from copying your one-of-a-kind electronic design or firmware.

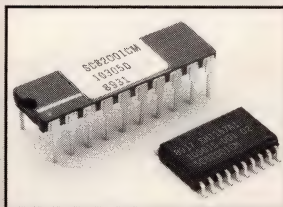The SentinelChip from Rainbow Technologies is a custom-designed, board-mounted ASIC security device that's built from the heart of our proven, best-selling, virtually unbreakable SentinelPro<sup>TM</sup> software protection key.



Without the "correct" dialog between your board's firmware and the SentinelChip's impen-

etrable algorithmic code, the board won't work and its design can't be copied. It's that simple.

The "never-say-copy" SentinelChip from the Great Boardware Protection Co. The simple, sure-fire protection you and your PCBs can stop looking for. For more information, call Rainbow Technologies today.

## SentinelChip<sup>TM</sup>

■ Protects electronic design and board software against copying ■ Protects revenues for designers/developers ■ For any pc board, including those used in computers, peripherals, test equipment, and arcade games

**Technical features include:** ■ High-security algorithm technique, never a fixed response ■ SentinelChip must be in-place at all times for board operation ■ Simple clocked interface ■ CMOS design for low power consumption ■ Single 3.5 to 5.5 VDC supply voltage ■ Surface mount (SOIC-20) or thru-hole (DIP-20) packaging

EVALUATION KITS AVAILABLE



**RAINBOW TECHNOLOGIES**

18011-A Mitchell South, Irvine, CA 92714  
(714) 261-0228 • TELEX: 386078 • FAX: (714) 261-0260  
Outside California: (800) 852-8569

Europe: Shirley Lodge, 470 London Rd., Slough, Berkshire,  
SL3 8QY, U.K. TEL: 0753-41512 FAX: 0753-43610

## INTEGRATED CIRCUITS

At unity gain, the AMP-02 has a bandwidth of 1.2 MHz; at a gain of 1000, the bandwidth is 200 kHz. In two offset-voltage grades, \$5.25 and \$8.75 (100).

**Precision Monolithics Inc.**, Box 58020, Santa Clara, CA 95052. Phone (408) 727-9222. FAX 408-727-1550. **Circle No. 353**

## 10-Bit D/A Converter

- Has 30-nsec settling time
- Contains on-chip data registers

The TDC1041 is a 10-bit, 20-MHz D/A converter with a  $\pm 0.5$ -LSB settling time of 30 nsec. On-chip data registers eliminate the need for external registers. The outputs can directly drive 50 $\Omega$  loads or complex filters, thus eliminating the need for additional amplifiers. Other features include a peak glitch area of only 25 pV/sec, differential and integral linearity errors of 0.5 LSB, and a 60-dB spurious-free dynamic range. You can operate the TTL-compatible TDC1041 without a clock signal. In a 28-pin plastic chip carrier, from \$9.75 (1000).

**TRW LSI Products Inc.**, Box 2472, La Jolla, CA 92038. Phone (619) 457-1000. FAX 619-455-6314.

**Circle No. 354**

## 3-Chip Modem Set

- Handles 2400 bps
- Complies with V.42 standards

The SSI 73D2420 3-chip modem IC set, which can handle data rates to 2400 bps, lets designers develop products that comply with the internationally recognized V.42 LAP-M error-control standard. The set includes the 73D680 controller, 73D681 K-series interface, and 73D682 ROM. When used with one of the company's K-series single-chip modem ICs, the devices combine to provide V.42 error control, LAP-B error control, Asynchronous Framing Technique (AFT) error control, adaptive data-compression, automatic feature negotiation,



flow control, and other Hayes-compatible features. The three devices, which are available in a variety of package options, are sold as a set. \$40 (10,000).

**Silicon Systems**, 14351 Myford Rd, Tustin, CA 92680. Phone (714) 731-7110, ext 3575.

Circle No. 355

## Power Supply Control IC For Automotive Use

- Provides current-mode PWM
- Has high-current totem-pole output

Specially trimmed and tested for automotive applications, the CS-2841B provides fixed-frequency, current-mode PWM control for switch-mode power supplies. A variation of the company's CS-2843A, the CS-2841B has a typical start-threshold of 8.0V and the ability to withstand 42V automotive load-dump transients. The maximum start-threshold of 8.4V enables low-battery operation. Other features include a totem-pole output rated at  $\pm 1A$  max, double-pulse suppression, and pulse-by-pulse current limiting. In an 8-pin DIP, \$1.09 (10,000).

**Cherry Semiconductor Corp**, 2000 South County Trail, East Greenwich, RI 02818. Phone (401) 885-3600. FAX 401-885-5786.

Circle No. 356

## Lowpass Filters

- Fourth- and sixth-order types
- Operate from 0.1 Hz to 30 kHz

The LMF40 and LMF60 are fourth- and sixth-order lowpass filters, respectively. The filters use switched-capacitor circuitry to obtain a Butterworth response that provides an 80-dB/decade roll-off for the LMF40 and a 120-dB/decade roll-off for the LMF60. Other key specifications include a wide center-frequency range of 0.1 Hz to 30 kHz (40 kHz for the LMF40), a maximum offset voltage of 100 mV, and a typical


dynamic range of 88 dB. The filters feature a clock-tunable cutoff frequency set by an internal or external clock, and a maximally flat frequency response over the passband. The devices operate from supplies of 4 to 14V or 2 to 7V. Package options include 8- and 14-pin DIPs and a 14-pin small-outline package.

\$2.19 to \$17.20 (100), depending on temperature range and package options.

**National Semiconductor Corp**, Box 58090, Santa Clara, CA 95052. Phone (408) 721-2273.

Circle No. 357
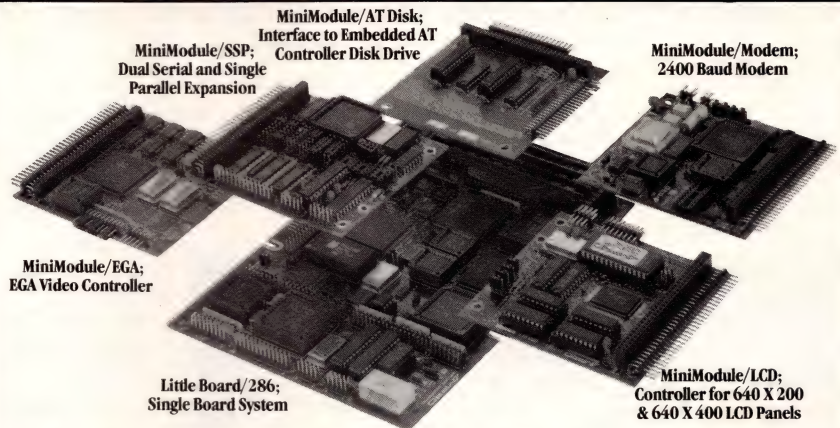
# Build your embedded PC or AT any way but big.



## Little Board plus Minimodules™

**Embedded applications.** Ampro's Little Board PC and AT compatible single board systems are ideal for embedded or dedicated applications. Specifically, applications which demand small size, high reliability, rugged design and low power consumption. Now, Ampro MiniModules allow you to build Little Board systems into a wider range of applications while meeting these same requirements.

**Little Board/PC or /286.** Take your pick. PC compatible or AT compatible. Both single board systems are equivalent to a mother-board and four expansion cards in a single 5.75" X 8" card. Both offer low power consumption, single 5V supply operation and 0 to 70°C operating range.

**MiniModule Expansion.** Extend your Little Board based embedded system using Ampro MiniModules. These compact 3.5" X 3.8" boards provide CGA or EGA video interfaces,

LCD or EL panel controllers, Arcnet LAN controller, 2400 baud modem, serial/parallel port expansion or an interface to hard disks with embedded AT controllers. Stack 'em vertically or side by side. Build a big system in small space.

**Complete information. Fast.** Call us at the number below. We'll immediately forward specifications and details on the Little Board family of single board systems and MiniModules. Then, you can build your embedded system. Any way but big.

All trademarks are the property of their respective owners

**408-734-2800**

**AMPRO**

SINGLE BOARD SYSTEMS


Ampro Computers, Inc., 1130 Mountain View/Alviso Road Sunnyvale, CA 94089. FAX (408) 734-2939. TLX 4940302

Distributors: Reps: USA - contact AMPRO for the name of your nearest rep. Australia - 61 3 720-3298; Austria - 43 222/3109110; Canada - (604) 438-0028; Denmark - 455 3 66 20 20; Finland - 358 0 585-322; France - 331 4842-2222; Germany, West - 49 6151 7305-35; Hong Kong/PRC - 5 8613118; Israel - 972 3 49-16-95; Italy - 39 6 811 9406; Japan - 81 3 257-2630; Netherlands - 31 10-411 8521; Norway - 46 8 28-72-86; Sweden - 46 8 28-72-86; Switzerland - 41 1 740-41-05; United Kingdom - 44 2 964 35511



# NEW PRODUCTS

## TEST & MEASUREMENT INSTRUMENTS

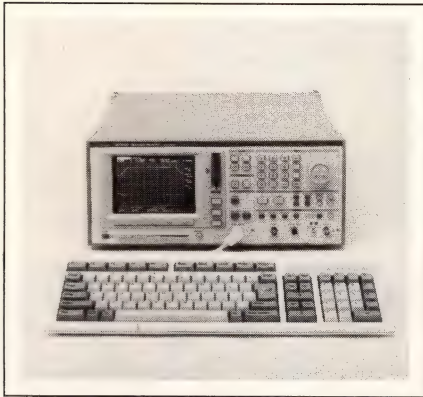

### 1-GHz Vector Network Analyzer

- Resolves  $10^{-3}$  Hz from 10 kHz to 1 GHz
  - Has a dynamic range of 120 dB
- The MS3606A vector network analyzer has a frequency resolution of  $10^{-3}$  Hz from 10 kHz to 1 GHz and a dynamic range of 120 dB. The in-

strument functions as a scalar analyzer when testing devices whose inputs and outputs are at different frequencies. The instrument's frequency synthesizer switches frequencies in 150  $\mu$ sec, allowing the unit to make measurements in 400  $\mu$ sec. The frequency standard has an aging rate of  $2 \times 10^{-8}$ /day. Output is adjustable in 0.01-dB steps from -80 to +15 dBm. At 10 kHz from a 1-GHz carrier, single-sideband phase noise is 95 dB below carrier level. You can equip the unit with memory cards that store software and allow the unit to act as an instrument controller. \$23,500. Delivery, 12 weeks ARO.

**Anritsu America Inc.**, 15 Thornton Rd, Oakland, NJ 07436. Phone (800) 255-7234; in NJ, (201) 337-1111. **Circle No. 377**




### Unix Instrument Drivers For PS/2 Computers

- Work with vendor's Micro Channel IEEE-488 interface
- Available for SCO Xenix and IBM AIX OSs

The NI-488M software drivers allow the vendor's MC-GPIB MCA (Micro Channel Architecture) bus IEEE-488 interface to control instruments from 80386-based IBM PS/2-family computers running under two versions of Unix. The sup-

## When it comes to heat sinks...

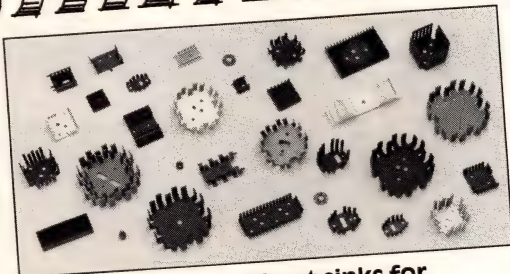

- ✓ Widest variety of heat sinks for semiconductors and ICs
- ✓ Unique staggered finger design increases heat dissipation
- ✓ Tight process control and quality materials provide superior heat transfer
- ✓ Just-in-time delivery from factory and local stocking distributors

## IERC fills the bill!

**International Electronic Research Corporation**  
a subsidiary of Dynamics Corporation of America  
135 W. Magnolia Blvd., Burbank, CA 91502  
(213) 849-2481 • (818) 842-7277 • FAX (818) 848-8872



CIRCLE NO. 95

### ARBITRARY FUNCTION GENERATOR

- Duplicate and edit real-life transients.

You can download real-life transients stored on disk in any ASCII file to the R4000, and then output the arbitrary waveform.


- Waveforms from extensive library.

Resident in the software are a number of standard waveforms, including sine, square, triangle, ramp, pulse, DC and white noise, which can be varied in amplitude or duration.

- Waveforms to 10MHz.

Outputs in sweep, burst or continuous modes, and provides a 16,000 point waveform memory, 12 bit D/A resolution, and choice of keyboard or mouse interface. Internal, external and gated trigger modes. \$2495.

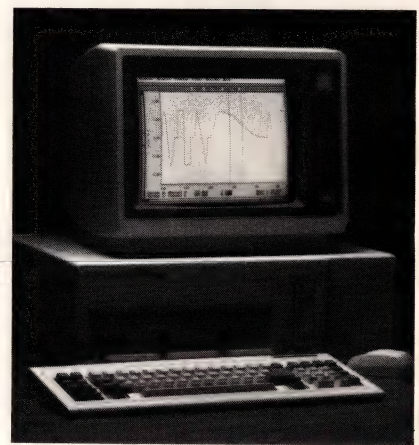**Rapid Systems**, 433 N. 34th St., Seattle, WA 98103. Phone (206) 547-8311. FAX (206) 548-0322.



**RAPID SYSTEMS**

CIRCLE NO. 96





ported operating systems are Santa Cruz Operations' SCO Xenix and IBM's AIX (Advanced Interactive Executive). The software packages include a high-speed driver, a C-language interface, and utilities for debugging application programs. The software allows porting of applications originally written to run under MS-DOS and OS/2 as well as those written for the Macintosh and for Sun workstations. NI-488M SCO Xenix, \$200; NI-488M IBM AIX, \$495; MC-GPIB, \$495.

**National Instruments**, 12109 Technology Blvd, Austin, TX 78727. Phone (800) 433-3488; in TX, (512)794-0100. FAX 512-250-9319.

Circle No. 378

tute of Standards Technology, formerly the National Bureau of Standards) attests to the instrument's accuracy. \$395, including a 3-year warranty.

**Tegam Inc**, 7230 N Ridge Rd, Madison, OH 44057. Phone (216) 428-7505. FAX 216-428-1068.

Circle No. 379

## Logic Analyzer For RISC Processors

- Supports 88000 to 50 MHz
- Replaces addresses with source-level-program mnemonics

The 88000  $\mu$ P-analysis package (MAP) enables the vendor's CLAS 4000 logic-analysis systems to debug systems based on Motorola's



## DOT MATRIX LCD's

- Wide viewing angle
- Wide operating temperature
- High reliability for a wide range of applications
- Large character (5.44 mm x 9.3 mm) available

**Super twisted (better contrast & viewing) option available on all models**

Char. x Line	Outside Dim. (w x h x d)
16 x 1	80 x 36 x 9.50 (mm)
16 x 2	80 x 36 x 9.50
16 x 2	160 x 52 x 12.00 (large char.)
20 x 1	116 x 37 x 9.50
20 x 2	116 x 37 x 9.50
20 x 4	98 x 60 x 12
24 x 1	118 x 36 x 12
24 x 2	118 x 36 x 12
40 x 1	182 x 33.5 x 12
40 x 2	187 x 40 x 11.00
40 x 4	195 x 70 x 11.00

Row x Column	Outside Dim. (w x h x d)
240 x 64	180 x 75 x 12.00
256 x 64	180 x 70 x 12.00
480 x 64	298 x 80 x 11.00
640 x 200	270 x 150 x 13.00
640 x 400	270 x 198 x 13.5

All models with Electro Luminescence Back Light option.



Write for "Liquid Crystal Displays" brochure.



## Thermocouple Calibrator And Thermometer

- Comes in a handheld unit
- J-, K-, and T-type compatible

The model 840 is a handheld, combined calibrator and digital-readout thermometer suitable for use with J-, K-, and T-type thermocouples. You can generate or measure thermocouple voltage levels with a full-range resolution of 0.1°F over a range of -340 to +2500°F. In both calibrate and measure modes, you can store 10 points in nonvolatile memory. A calibration certificate traceable to NIST (National Insti-


## SUPERTEK ELECTRONICS, INC.

543 W. Algonquin Road  
Arlington Heights, IL 60005  
Phone: (312) 981-5655  
FAX: (312) 981-9076  
TWX: 910-687-2847

CIRCLE NO. 97



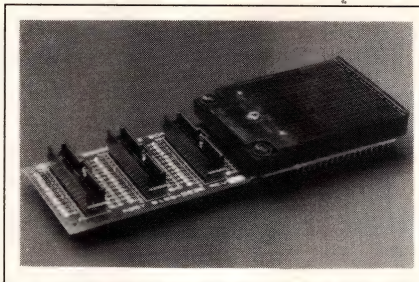88000 series RISC processors. The analyzer supports chips operating at 50 MHz—the fastest clock speed Motorola currently offers. The package includes a 1.75-in.-square, low-profile socket for the  $\mu$ P and a disassembler that lets you replace addresses with mnemonics from the source-level program. The disas-



sembly display shows all bus cycles with type information and mnemonics and lets you delete unexecuted instructions and data read/write cycles. The unit loads the  $\mu$ P signals minimally (1 M $\Omega$  in parallel with 10 pF), resolves event timing to 5-nsec, and captures 3-nsec glitches. \$2950; CLAS 4000, from \$19,950.

**Gould Inc.**, 19050 Pruneridge Ave, Cupertino, CA 95014. Phone (800) 538-9320. FAX 408-988-1647.

Circle No. 380

## Turn Good Ideas Into Good Articles


*With EDN's FREE Writer's Guide!*

Would you like to get paid for sharing your clever engineering ideas and methods with your professional colleagues? If so, then send for EDN's new FREE writer's guide and learn how.

You don't need the skills and experience of a professional writer. And you don't need to know publishing jargon. All you *do* need are a little perseverance, your engineering skills, and the ability to communicate your ideas clearly.

Our new writer's guide takes the mystery and intimidation out of writing for a publication. It shows you how to write for EDN using skills you already have. Plus, it takes you step-by-step through the editorial procedures necessary to turn your ideas into polished, professional articles.

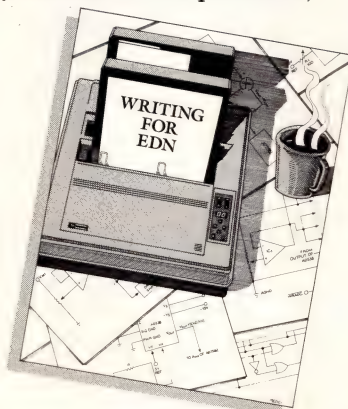Get your *FREE* copy of EDN's writer's guide by circling number 800 on the Information Retrieval Service Card or by calling (617) 964-3030.



### 60- And 100-MHz Bandwidth DSOs

- Acquire 250M samples/sec
- Reproduce transients containing 25-MHz information

The PM 3355 and PM 3375 DSOs (digital storage oscilloscopes) acquire 250M samples/sec. With repetitive signals, the PM 3355 has an analog bandwidth of 60 MHz; the corresponding figure for the PM 3375 is 100 MHz. When you use the scopes to capture single-shot phenomena, the vendor recommends that you take 10 samples/cycle of the highest frequency component of interest. Hence you can use the scopes to capture transients that contain 25-MHz information. Vertical resolution is 8 bits, and signal averaging improves the S/N ratio of repetitive signals. Both scopes have four acquisition memories each of which holds 4k samples. Both units trigger on 150-MHz signals and provide post triggering to 5000 divisions. LCD panels adjacent to the screen indicate control settings. PM 3355, \$4500; PM 3375, \$5390.

**John Fluke Mfg Co Inc**, Box C9090, Everett, WA 98206. Phone (800) 443-5853, ext 77. TLX 185102.

Circle No. 381

**Philips Test and Measurement**, Bldg HKF, 5600 MD, Eindhoven, The Netherlands. Phone local office.

Circle No. 382



# EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number  
for additional information from manufacturers.

**X.25      SDLC  
QLLC      HDLC  
ADCCP    PAD**

- C source code
- ROM-able
- Hardware independent
- No OS required




**GCOM, Inc.**  
41 E. University  
Champaign IL 61820  
(217) 352-4266

Specialists in Computer Communications  
Telex 910-240-1477 FAX 217-352-2215

CIRCLE NO 325

## Thermal-Reliability Analysis

**BETAsort-R**  
gives you

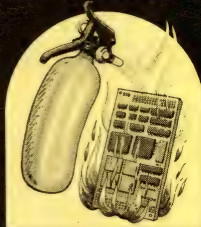

- \* Mean Time Between Failure of Boards
- \* Failure Rate of each component
- \* MIL-HDBK-217E Compatible
- \* Interface to P-Cad, PADS-PCB, Auto-CAD, and Racal etc.
- \* 3-D Thermal Modelings for SMT boards
- \* Menu-driven, 2,500 component library
- \* 2.5 min on IBM/AT per 100 components

**BETAsort-R      \$2,995**  
**Free Demo. Dynamic Soft Analysis, Inc.**  
Tel. 412-781-3016 Fax 412-781-3098

CIRCLE NO 326

## Tango-Schematic Series II.™ It simply works better.

We listened to your suggestions and built the best in PC-based schematic capture. More versatile than OrCAD.™ More features than Schema.™ Easier to use than DASH.™ Thanks to our streamlined interface and integrated approach, Tango-Schematic makes creating complex schematics simple. Compare for yourself.

**Tango™**

Tango-Schematic features SEDCO™ libraries, with over 8,000 parts guaranteed for accuracy; integrated component creation; true ANSI/IEEE support; forward- and back-annotation; PostScript and DXF output; free tech support; and much more. It's all there for just \$495—guaranteed.



### FREE EVALUATION PACKAGE

**800 433-7801** 619 554-1000 619 554-1019 Fax

ACCEL™ Technologies ■ 6825 Flanders Drive ■ San Diego, CA 92121 USA  
International prices may vary. Contact us for the distributor nearest you.

CIRCLE NO 327



## Schematic and PCB Software

Create and revise schematics and PCBs quickly and simply with **HiWIRE-Plus®** and your IBM PC. Use symbols from HiWIRE-Plus's extensive library, modify them, or create your own quickly and painlessly. Netlist, bill-of-materials, and design-checking utilities are included. **HiWIRE-Plus** is \$895 and comes with a thirty-day money-back guarantee.

### Wintek Corp.

1801 South St., Lafayette, IN 47904  
(800) 742-6809 or (317) 742-8428

CIRCLE NO 328



**DATA I/O PROGRAMMERS:  
GREAT, H/W FLEXIBLE.**



**SAILOR PROGRAMMERS:  
GREAT, S/W FLEXIBLE.**


Find out why. Please call for a free demo disk.  
Sailors support: ★ 7ns PALs ★ 12ns GALs  
★ 2-MEG EPROMs ★ PROMs ★ EEPROMs  
★ EP900 ★ EP1800 ★ 8751 and many more



Data I/O: trade mark of Data I/O Corp. ★ Sailor: trade mark of Advin Systems Inc.

CIRCLE NO 329

## New Color Touch Control Screen

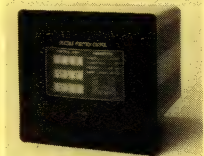

- Operator interface for computer-controlled machines.
- Local screen storage.
- Powerful firmware eases software development.



**John Fluke Mfg., Co., Inc.**, P.O. Box C9090 M/S 250C  
Everett, WA 98206 Toll Free 1-800-426-0361 © 1988, Fluke

CIRCLE NO 330

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## End-to-end CAD

Schematic Capture • PCB Layout • Autorouting



Design Computation offers DC/CAD IV-Level 1 with no copy protection for complete end-to-end PCB design:

- High Capacity Schematic Capture
- Multi-strategy Autoplacer
- Gridless "1-mil" Parts Placement and Autorouting
- Interactive Routing with Diagonal Hugger
- Gridless, Diagonal RipUp/Retry Autorouter
- Thorough Annotating Design Rule Checker
- Full 2-way GERBER support
- Full 2-way DXF support

Several high performance packages available. CALL TODAY!

**DESIGN  
COMPUTATION**


Route 33 Sherman Square, Farmingdale, NJ 07727  
(201) 938-6661 FAX: (201) 938-6662 Telex: 510 601 8352

CIRCLE NO 331

## PLD PROGRAMMER

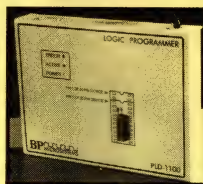**\$798**

- Lifetime **FREE** software updates
- Programs, reads, tests duplicates, & secures over 970 20- & 24-pin logic devices from 17 mfg's
- Automatically tests with vectors and secures after programming
- Approved by manufacturers
- Edits fuse maps and test vectors
- Just **\$798**, includes: software, cable, manual, **FREE** updates (via BBS), toll-free technical support, one-year warranty and an unconditional 30-day money-back guarantee



**The Engineer's Programmer™**


Call **1-800-225-2102**

**BP MICROSYSTEMS**

10681 Haddington, Suite #190 Houston, TX 77043  
713-461-9430 FAX 713-461-7413

CIRCLE NO 332

## Worstcase at its Best!

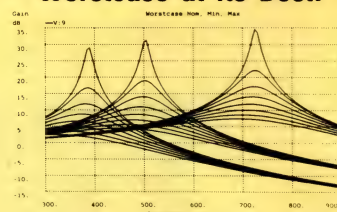


### Analog Circuit Simulation

**ECA-2** Electronic Circuit Analysis offers the best Monte Carlo and Worst-Case analyses with the capability to concurrently plot random samples or Min/Max/Nominal values.


- AC, DC, Transient
- Fourier, Temperature
- Sine, Pulse, PWL, SFFM, and Exponential generators
- 2 to 50 times faster than SPICE
- Interactive/batch modes
- Full nonlinear simulator
- Over 500 nodes
- Multiple plots

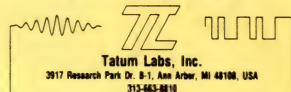ECA-2 2.50 IBM PC or Mac \$775  
Call 313-863-8810 for **FREE DEMO disk**



CIRCLE NO 333
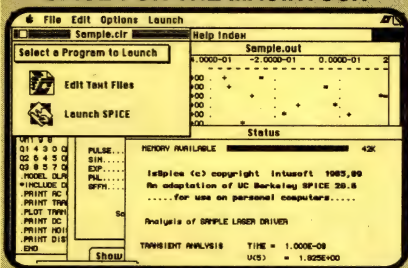
## Analog Circuit Simulation SPICE FOR THE MACINTOSH



**Intusoft introduces the NEW II IsSpice/MAC.** The only Spice program to run on all Macintoshes (Plus, SE, SE/30 and Mac II) in as little as 1 megabyte of RAM. The simulatable circuit size is only limited by the amount of RAM. Coprocessor (\$210) and Non-coprocessor (\$95) versions are available. Also available is **PreSpice/MAC** (\$175) which contains extensive model libraries, the IsSpice netlist editor and ICAPS, an easy to use menu system especially adapted for the MAC environment.

P.O. Box 6607  
San Pedro, CA  
90734-6607



(213) 833-0710  
30 Day Money  
Back Guarantee

Macintosh is a registered trademark of Apple Computer

CIRCLE NO 334

## C for the 8051 Compare:

**Benchmark Results** — Sample program: Eratosthenes sieve program from BYTE (1/83), expanded with I/O and interrupt handling.

	Archimedes ICC51 v2.20A	MCC51 v1.2	FRANKLIN C51 v2.1
Compilation time	12 sec ✓	18 sec	17 sec
Linkage time	29 sec	9 sec	6 sec ✓
Execution time	11.45 sec	9.00 sec	0.88 sec ✓
Total code size	5318 bytes	3798	1726 ✓
Sieve module size	736	1021	541 ✓

Call now for your free **DEMO disk**.



888 Saratoga Ave. #2 • San Jose, CA 95129  
(408) 296-8051 • FAX (408) 296-8061


CIRCLE NO 335

## Combine Your Product Mart Ads

In EDN's Magazine  
**and**  
News Editions for  
**higher impact and a  
lower rate.**

CIRCLE NO 336

## JE680 Universal Programmer

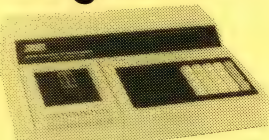

- Programs PROMs, EPROMs, EEPROMs, PALs, GALs, RALs, EPLs and PLDs
- Stand-alone or computer controlled modes w/MS-DOS menu-driven software
- JEDEC standard supported
- Parallel and RS232C interface ports
- Optional 40-pin MPU module available

Listing of programmable devices and 80-page catalog available upon request!

**JE680 Universal Programmer.....\$1799.95**



1355 Shoreway Road, Belmont CA 94002  
Phone (415) 592-8097  
FAX (415) 592-2503

CIRCLE NO 337

## \$249. TERMINAL




- Featuring:
- Standard RS-232 Serial Asynchronous ASCII Communications
  - 48 Character LCD Display (2 Lines of 24 Each)
  - 24 Key Membrane Keyboard with embossed graphics
  - Ten key numeric array plus 8 programmable function keys
  - Optional RS-422 multidrop protocol mode
  - Keyboard selectable SET-UP features — baud rates, parity, etc.
  - Size (5.625" W x 6.9" D x 1.75" H), Weight 1.25 lbs.
  - 5 x 7 Dot Matrix font with underline cursor
  - Displays 96 Character ASCII Set (upper and lower case)
  - Optional Bar Code Wand (shown)

**COMPUTERWISE, INC.**

302 N. Winchester • Olathe, KS 66062 • 800-255-3739 • FAX (913) 829-0810

CIRCLE NO 338

## STOP NOISE IN PGA, LCC PACKAGES

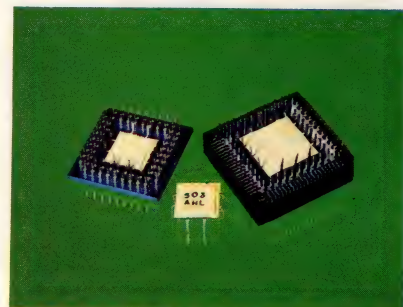


**MICRO/Q 3000** decoupling capacitors stop low-inductance, high-frequency noise for PGA, LCC packages on complex board layouts. Fit them neatly under PGA or LCC sockets, use no extra board space. Choose from many pinout configurations. **Rogers Corp.**, 2400 S. Roosevelt St., Tempe, AZ 85282. 602/967-0624.

CIRCLE NO 339

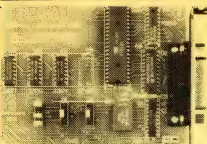To advertise in Product Mart, call Joanne Dorian, 212/463-6415





## LOW COST INTERFACE CARDS FOR PC/XT/AT

### RS-485/422 Card [PC485] \$95/125

- Serial Async. Communication up to 4,000ft; 2 or 4 wires; NS16450 UART;
- COM1-4; Max. Baud Rate 56KB; High speed version (256KB) - \$165.
- Dual drivers/receivers; handles 64 devices; Compatible with most comm. S/W.
- DB9 or phonejack. Sample programs included. Optional S/W (w/ source) - \$150

### IEEE-488 Card [PC488A] \$145

- Includes INSTALLABLE DOS DEVICE DRIVER and support for BASIC.
- Additional Support for ASSEMBLY, C, Pascal and FORTRAN - \$ 50.
- Selectable IRQ (1-6). DMA channel 1 or 2. Up to four boards per computer.
- Compatible with most IEEE-488 Software packages for IBM-PC (e.g. ASYS-TANT-GPIB, Lotus Measure). Compatible with NT's GPIB-PCIIA.

### IEEE-488 Card [PC488B] With Built-In Bus Analyzer \$345

- Software Support for BASIC, QuickBASIC and GWBASIC (PC488C only)
- Additional libraries for C, Pascal, FORTRAN. Assembly available - \$50 (all)
- Powerful menu-driven BUS ANALYZER runs in the background while 488 programs or commands are executed. Features Program Stepping, Break points, real time bus data capture (4K buffer), instant screen toggling.
- Complete Controller / Talker / Listener capability. Based on TTY - TMS-9914.
- NEC-7210 based card (compatible with National Instruments PCII) - \$445.

### Stepper Motor Card [PCL738] \$395

- Capable of independent and simultaneous control of up to 3 stepper motors.
- Programmable speed from 3.3 PPS to 3410 PPS. Built-in acceleration control.
- Step Position Read-back. Opto-isolated outputs. Crystal based timing.
- Pulse/Direction or CW/CCW pulse output. Includes 8 bit digital I/O port.

MC / VISA / AMEX


Call today for datasheets!



**B&C MICROSYSTEMS INC.**  
355 West Olive Ave., Sunnyvale, CA 94086 USA  
TEL: (408) 730-5511 FAX: (408) 730-5521

CIRCLE NO 340

## +125°C DC-DC CONVERTER

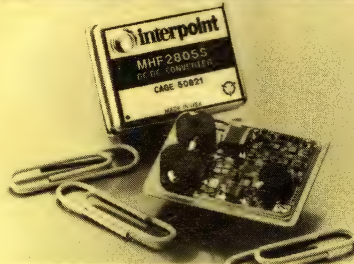

Now you can have space-efficient distributed power in HI-REL programs. Interpoint's new low profile (.315 inch), MHF dc-dc converters provide 12 watts in less than 1/2 cubic inch over -55 to +125°C temperature range. Full military environmental screening available. 600 kHz operation gives up to 84% efficiency in 5, 12, and 15 volt single or dual output models.


**interpoint**

Full MIL-STD-1772 Qualified

10301 Willows Rd.  
Redmond, WA 98052  
800-822-8782

CIRCLE NO 341

## T-1600 GANG/SET PROGRAMMER

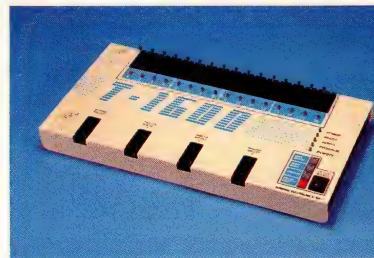


- PROGRAM 16 AT ONCE—SAME OR SET
- 24, 28 OR 32 PIN EPROM'S
- STAND ALONE AND MS-DOS DRIVEN
- INTELLIGENT DEVICE SELECTION
- SIMPLE OPERATION
- QUICK FLIP LCC AND SMT ADAPTERS



SUNRISE ELECTRONICS, INC.  
524 South Vermont Avenue, Glendora, California 91740  
(818) 914-1926

CIRCLE NO 342

## Analog PC Board Layout

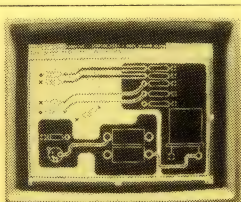

**AT LAST!**  
**A System**  
**specifically designed for laying out**  
**Analog boards. All the features you**  
**need for your most difficult boards,**  
**including digital designs. Only \$975**

- Groundplanes with dynamic airgap calculation
- Solid and hatched groundplanes
- Odd-shaped pads and copper-fill areas
- Curved, tapered and irregular traces
- Total control of trace length, width and angle
- Incremental component rotation
- Rounded and chamfered bending points
- Round and odd-shaped boards, and much more

**CADPOINT**

**714-494-1167**

3857 Birch St, Suite 584, Newport Beach, CA 92660-2660

CIRCLE NO 343

## WANTED LAS Bug #115042



**Gen. Circuitbug**

Bring him to justice with the versatility of the  
**Logic Analysis System**

4k to 64k memory depth  
16 level triggering with pass counter  
40 to 320 channels  
A complete Logic Analyzer on a Card  
Interactive software under Microsoft™ Windows  
Source code in C for automatic testing



701 River Street  
Troy, NY 12180  
(800) 367-5906  
(518) 274-0755  
FAX (518) 274-0764

CIRCLE NO 344



**Dynamic C**

**For Real-Time Embedded Systems**

**Z80/Z180/HD64180**



A new idea!

An integrated C

development environment with editor,  
compiler and source level debugger.

Memory-resident on your host PC.

Compiles, while downloading to the  
target, at 25,000 source lines per minute.  
Complete, low-priced system includes an  
IC180 in-circuit emulator and Dynamic  
C software. Ask for a Free Demo Disk.

1340 Covell Blvd. • Davis, CA 95616  
(916) 753-3722 • Fax: (916) 753-5141

CIRCLE NO 345

**8051**

## PC BASED EMULATORS



- Source Level Debug for PLM and C
- Source Level trace
- Debug with symbols, not HEX data
- Source Level disassembly with in-line assembler
- Interchangeable probe cards
- Up to 128K emulation memory
- 20 MHz real-time emulation
- Up to 4K trace buffer
- Performance analyzer
- TRUE 8051 Emulation including all I/O ports, idle, power down, DMA, and WatchDog timers at NO additional cost
- Breaks set symbolically
- Fully documented
- Serially linked to PC
- OEM supplier to 8051 IC manufacturers
- Unlimited FREE technical support
- From \$1495\*

**Metalink™...Originators of the  
PC Based 8051 Emulator**

We have more 8051 emulators than anyone  
in the world: 8031, 8051, 8032, 8052, 8344, 8044,  
80C152JA/JB/JC/JD, 83C152JA/JC, 80C452,  
80C51FA, 8051S, 8053S, 80512, 80532, 80513,  
80517, 80C521, 80C541, 80C321, 8053, 80C154,  
80C451, 80C552, 80C562, 80C652, 80C751,  
80C752, 80C537, CMOS, EPROMs, OTPs

Call or write for Free demo diskette

**1-800-METAICE®**



Metalink Corporation P.O. Box 1329, Chandler, AZ 85244-1329  
(602) 926-0787 FAX: (602) 926-1196 TELEX 498055 MTLINK  
\*Price in U.S. dollars

**NOW  
80C552 & 80C517  
SUPPORT**

CIRCLE NO 346

presenting  
**PADS**  
SUPERSTATION  
for TOTAL  
INTEGRATION

Obtain complete cradle-to-grave performance from your personal computer CAD system when performing electronic packaging design. From schematic capture to printed circuit design, to 100% completion autorouting capabilities, it's all here. Now you have one more reason you should be using PADS: Total Integration. Call our Sales Hotline today to receive a free Integrated Evaluation Package for the PADS-SUPERSTATION.

Call Your Local Authorized Dealer


In MA: (508) 486-8929  
Outside MA: (800) 255-7814

**CAD**  
Software, Inc.  
119 Russell St.  
Littleton, MA 01460

CIRCLE NO 347

## Telecom Design!

**CALL PROGRESS  
TONE DETECTORS**

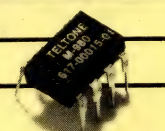

Tone detector ICs for all telecommunications products. 5V, 3.58 MHz time base, tristatable outputs.

- **M-980** band pass detector from 340 Hz to 620 Hz. Ideal for detecting non-precise call progress tones. 8 pin.
- **M-981** provides precise detection of 350, 400, 440 and 480 Hz. 22 pin.
- **M-982** provides precise detection of 350, 440, 480 and 620 Hz. 22 pin.

For more info call: **1-800-426-3926**  
(In Washington State: 206-827-9626)



10801-120th Avenue NE, Kirkland, WA 98033

CIRCLE NO 348

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## Surface Mount Chip Component Prototyping Kits—

Only  
\$49.95



CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1pF to .33µF. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 10Ω to 10MΩ. Sizes are 0805 and 1206. Each kit is ONLY \$49.95 and available for Immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, AMEX, COD, or Pre-paid orders. Company P.O.'s accepted with approved credit. Call for free detailed brochure.

**COMMUNICATIONS SPECIALISTS, INC.**  
426 West Taft Ave. • Orange, CA 92665-4296  
Local (714) 998-3021 • FAX (714) 974-3420

Entire USA 1-800-854-0547

CIRCLE NO 349

## RELIABILITY PREDICTION SOFTWARE


### ARE YOUR PRODUCTS RELIABLE?

The RelCalc 2 Software Package predicts the reliability of your system using the part stress procedure of MIL-HDBK-217E, and runs on the IBM PC and full compatibles. Say goodbye to tedious, time consuming, and error prone manual methods! RelCalc 2 is very easy to use, and features menu windows, library functions, global editing for what-if? trials, and clear report formats. Try our Demo Package for \$25.

**T-CUBED SYSTEMS**, 31220 La Baya Drive #110, Westlake Village, CA 91362. (818) 991-0057 • FAX: (818) 991-1281

CIRCLE NO 350

## 68HC05/68HC11 Emulators

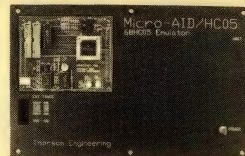


The Micro-AID in-circuit emulators provide complete development support for Motorola single chip microcomputers.

- In-Circuit Emulator – Real time in-circuit emulation for the 6805, 68HC05, and 68HC11 single chip microcomputers.
- Real-Time Trace – 2K x 32 memory captures up to 2048 cycles of qualified bus activity.
- Symbolic Debugger – Allows symbolic reference to parameters in emulator commands.
- PC Based Cross Assembler – Fast assembler automatically downloads object to emulator.
- EPROM Programmer – Programs on-chip EPROM.
- Low cost, from \$1200 to \$2395.

**THORSON ENGINEERING**

6225 76th St. S.E., Snohomish, WA 98290  
(206) 334-4214

CIRCLE NO 751

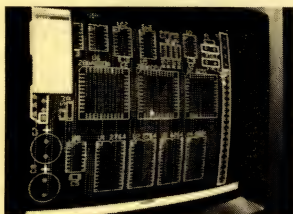

*Why Do  
Designers  
Choose  
Protel?*

*Protel  
gets the  
job done!*

**Professional Quality CAD Tools**  
Protel offers a full suite of PC-based high-performance PCB design tools with easy-to-use & consistent user interfaces, free tech & EMS support, BBS and 30-day money-back guarantee.

**Schematic** \$495  
Popular precision digital and analog schematic design.

**Autotrax** \$1295  
Complete PCB layout with automatic placement & routing for both through-hole and SMD designs. Supports standard printing, plotting formats and up to 8MB RAM.

**Traxstar** \$1495  
Powerful multi-layer rip-up and re-try autorouter. Handles over 700 ICs and a board of up to 20x32 inches.

**Traxview** \$695  
Full-featured interactive Gerber viewer and editor with automatic pannelization for multiple Gerber files.

Before you invest in a PCB design product tomorrow. Call toll free (800) 544-4186 for one of our free demo-disks today. In CA, HI, AK, or Canada, call: (408) 437-7771.

**Protel Technology Inc.**

50 Airport Parkway (408) 437-7771  
San Jose, CA 95110 fax (408) 437-4913

CIRCLE NO 752



### STEP MOTOR CONTROL 27K steps/sec! 16 Million steps!

New CY545. Rates up to 27K steps/sec, up to 16 million steps per single motion. Separately programmable start rate, accel/decel rate, and max rate. Pulse & direction output. External jog mode and limit switch detection. Serial or parallel interface, LED/LCD & Thumbwheel interface lines, and more. ASCII commands. Supports 64K external memory. CMOS 40-pin DIP. \$75 each (\$25/1000). Credit Cards OK.



**Cybernetic Micro Systems**

Box 3000, San Gregorio CA 94074

(415)726-3000 Tlx: 910-350-5842

CIRCLE NO 753

Now  
on Sun!

Facts about

**425,000**

**ICs and Semiconductors  
at Your Fingertips**

Cahners CAPS is the newest component search and selection tool for electronic design engineers:

- PC-driven, CD-ROM-based
- Includes unabridged manufacturers' datasheets
- Represents more than 400 manufacturers worldwide

Call toll-free: 1-800-245-6696

CAHNNERS

**CAPS**

Computer Aided  
Product Selection

275 Washington Street  
Newton, MA 02158-1630  
Telephone: 617-558-4960  
Facsimile: 617-969-6949  
Telex: 940573

CIRCLE NO 754

**COMMUNICATIONS**  
**LOW (508)485-1144**  
FAX 508-481-7222  
BBS 508-460-9203

### LOW BUDGET SPECIALS

19" COLOR SUPER VGA MONITORS  
LIKE NEW -- 6-MONTH WARRANTY \$800.00  
USED -- 3-MONTH WARRANTY \$600.00  
USED WITHOUT CASE \$300 TO \$500.00

19" COLOR SONY 1280X1024 \$1600.00  
THESE SONY TRINITRONS  
HAVE A FULL 6-MONTH PARTS  
AND LABOR WARRANTY.  
LIMITED QUANTITY.

16" Ikegami 64 kHz 1280X1024  
New \$899.00

16" Panasonic 64 kHz  
Used \$599.00

14" Ikegami TTL VGA chassis, New, 1-year warranty \$249.00

19" PHILIPS 1024X800 48 kHz GRAYSCALE . . \$350.00  
NEW, 1-YEAR WARRANTY. MAY BE ORDERED FOR VGA AT  
NO EXTRA CHARGE. IN VGA MODE, WILL RUN 800X600X256  
GRAYSCALE, OR 1024X768X16 GRAYSCALE ONLY.

CALL US ABOUT OUR LARGE VARIETY OF GRAPHIC CARDS!

194 Main Street Marlborough MA 01752

CIRCLE NO 755

**COMMUNICATIONS**  
**VISION 16 (508)485-1144**  
FAX 508-481-7222  
BBS 508-460-9203

### VISION 16 IMAGE CAPTURE

Vision 16 Cards:

**LOW-COST**

solution to your

imaging needs --

works with Crystal

3D, Lumena, Rio,

Picture Power.

Board and Colorchemie I software list for

\$1495.00 --


**Special OEM discounts for EDN**

readers: Please Call!!

We also have 19-inch Ikegami  
monitors, perfect for image capture, at a  
Special OEM Price!

194 Main Street Marlborough MA 01752

CIRCLE NO 756

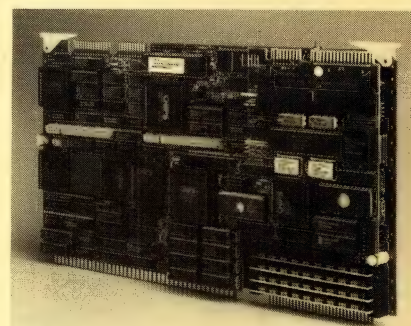

### MULTIBUS™ AT-COMPATIBLE SBC

Multibus I is now IBM PC/AT™ compatible with MAT286™ our newest single board solution. MAT286 includes all of the functions of a 10 MHz AT motherboard, plus 2 serial ports, a parallel port, two SBX expansion-module interfaces, up to 512K EPROM/EEPROM/VRAM, and up to 4M of parity-checked, dual-ported DRAM. A piggy-back card, MATxSYSIO, adds EGA, floppy, and SCSI interfaces. Embed all the guts of an AT, two SBX modules, and more, into two Multibus slots!

Phone (408) 253-0250 or write for more information.

**Single Board Solutions, Inc.**

20045 Stevens Creek Blvd, Cupertino, CA 95014

Multibus is a registered trademark of Intel Corp.


MAT286 and MATxSYSIO are trademarks of Single Board Solutions, Inc.

IBM and PC/AT are trademarks of International Business Machines Corp.

CIRCLE NO 757

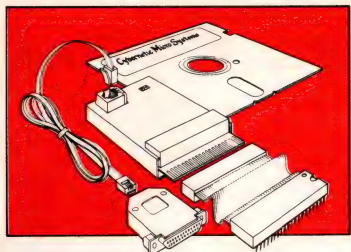To advertise in Product Mart, call Joanne Dorian, 212/463-6415





### 8051 Emulator - \$1250


**d<sup>2</sup>ICE** is a low cost, Full Speed, real time 8051 Emulator. Powerful user interface for Hi-level multi-window source code debugging. Uses IBM-PC COM1/2. No Slots! Portable, fits in shirt pocket. Assembler and test bed included.



**Cybernetic Micro Systems**  
Box 3000 • San Gregorio, CA 94074  
(415) 726-3000 • Telex: 910-350-5842

CIRCLE NO 758

### MODEM COMPONENTS

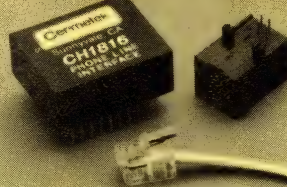

- Telephone Line Interface, DAA — DOC, FCC, International
- Error Correcting and Data Compression — MNP Level 5, V.42, X.25 LAP B
- Complete Modem Modules, pre-approved — 9600, 2400, 1200 BPS "AT" Compatible



Tel: 408-752-5000  
Fax: 408-752-5004


Cermetek Microelectronics  
1308 Borregas Ave. • Sunnyvale, CA 94089

CIRCLE NO 759

### DATA ACQUISITION CONTROLLER

Now for the first time the 7200 combines intelligent hardware and software with high resolution analog I/O. Everything you need is on one STD Bus card. Easy to use STD BASIC III software supports all on-card hardware. Ideal for data acquisition, positioning, and motion control. Program development software available for PC.

- 12-bit, 8 channel A/D
- 12-bit, 2 channel D/A
- Supports 2 MB on bus
- 32 TTL I/O lines
- 1 RS-232 serial port
- 1 RS-232/422 serial port
- Keypad port
- Battery-backed RAM
- Watchdog timer
- EEPROM programmer

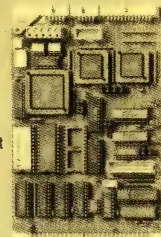

Call 303-430-1500 for more information.




**OCTAGON SYSTEMS CORPORATION**  
6510 W. 91st Avenue  
Westminster, CO 80030, Fax: 303-426-8126

CIRCLE NO 760
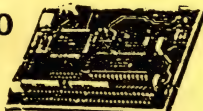
### INSTANT PRODUCT! \*\*\* just add software \*\*\*

**TDS9090**  
**FORTH**  
control  
computer



Powerful 4" x 3" single-board computer, based on the CMOS HD6303Y. High-level easy Forth language on board - **REAL-TIME DEBUG!** 30K RAM, 16K RAM/PROM, 2K EEPROM. Attach keyboard, lcd, I/O peripherals. Built-in interrupts, multi-tasking, watchdog timer, editor and assembler. 32 I/O lines, two RS-232 ports. 6 - 16 volts operating at 3ma. Optional **data-logging module**: 10-channel, 10-bit or 8-channel, 12-bit A/D, 128K RAM, D/A, date/time clock -- low-power mode **lasts one year on 9v battery!**. Includes lots of ready-made software solutions. Over 3000 are in use world-wide for machine control, data-logging, inspection, factory automation, robotics, remote monitoring, etc. Available on 30-day free trial.


\$219 (25 qty inc shipping)



**SAELIG Company**

1193 Moseley Rd, Victor, NY 14564  
(716) 425 3753 • fax (716) 425 7381

CIRCLE NO 761

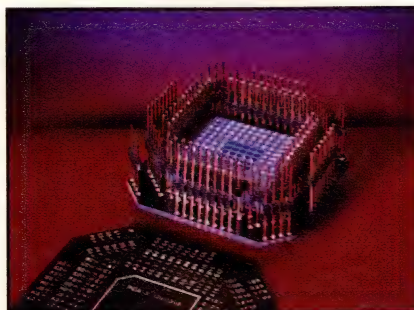

### Complete Line of Debug Tools


- Famous Bug Katcher™ makes it easy to attach test leads to ICs in LCC, PLCC, PGA, PQFP, and DIP packages.
- Eliminates need for noisy cables; reduces capacitance and inductance in your test set-up.
- You can also quickly isolate and reconnect sections of your socketed IC with our Bug Isolator™ (All packages.)
- Quick turnaround on custom engineering services, if needed. For a free catalog, contact:

Emulation Technology, Inc.  
2368-B Walsh Ave. Santa Clara, CA 95051  
Phone: 408-982-0660 FAX: 408-982-0664



CIRCLE NO 762
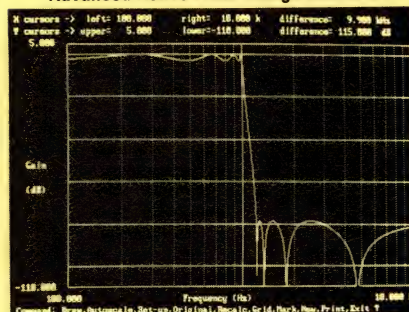
### New AFDPLUS Advanced Active Filter Design Software



- Fully Interactive
- On Screen Design & Evaluation
- On Screen Editing
- Menu Driven
- Automated Installation
- Schematic Display & Print
- Integrated AFDSIM

Introductory price \$850.00 (price effective through 01/31/90)  
Call for your **FREE DEMO DISK** (303)-499-7566 or to order AFDPLUS send check or purchase order to

**RLM Research**  
P.O. Box 3630  
Boulder CO 80307-3630



CIRCLE NO 763

### 8051/Z8

Debug in  
**C or Assembly**

MICRO/SLD V2.0


Source Language  
Debugger

- FULL HMOS and CMOS Chip Simulation.
- Power Enhanced Breakpoint Command.
- Macros for Quick Command Entry.
- EASY Circuit Simulation. • PC Only \$295.

**MCC** MICRO COMPUTER CONTROL  
Software Development Tools

P.O. Box 275 — Hopewell, NJ 08525 USA  
Tel (609) 466-1751 Fax (609) 466-4116  
Telex 9102404881 MICRO UQ

CIRCLE NO 764

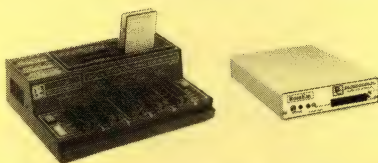

### RS232 EE/EPROM, MICRO & MEMORY CARD PROGRAMMER \$345-595

- Programs EE/EProms, Flash EProms, ZPROMs, Intel Micros, Memory Cards.
- Stand-Alone Mode for EE/EProms and Memory Card Duplication / Verify.
- All 24/28/32 pin EE/EProms to 4 Mbits (upgradable to 32 Megabits).
- Micros 8741(A, 2/A, 4, 8, 9, S1, C51, C51F, A/B, S2, S3, S5, C521, C541, 9761).
- Modular design; Accepts dedicated modules: Memory Card programming module (Seiko/Epson), 4 socket Gang Programming module, custom modules.
- Can be operated with any computer containing an RS-232 serial port.
- Optional built-in Eraser/Timer module (\$59). Top cover conductive foam pad.
- User friendly Menu-Driven Interface Program for IBM-PC and Macintosh.
- Full 1 year warranty. Customer support via voice line, fax or dedicated BBS.

### INTELLIGENT ROM EMULATOR \$395

- Emulates 2716 through 27512 EProms with a single unit. Access time 120ns.
- Connects to the standard parallel printer port via a standard printer cable.
- User friendly software. Command set includes: Load(data), Write(data), Display(memory), Type(of EProm), Edit(memory), Fill(memory), Calculator, Reset(target system), Activate(debugging feature), Monitor(selected feature).
- Debugging features include: Address Compare, Address Snapshot, Trigger.
- Fast data loading via parallel printer port (64k bytes in less than 10 sec).
- Cascadable up to 8 units. Includes interface cable with Trigger and Reset clips.
- CMOS (stand-alone) model with rechargeable NiCad battery backup: \$495



**B&C MICROSYSTEMS INC.**  
355 West Olive Ave, Sunnyvale, CA 94086 USA  
TEL: (408) 730-5511 FAX: (408) 730-5521

CIRCLE NO 765

### TRANSMISSION-LINE PROBLEMS?



### Interactive Transmission-Line Simulator

Designing digital systems? With today's fast edges, chances are good you've got transmission-line problems.

**LineSim** is a new tool just for transmission-line design.

- It features:
- a push-button schematic
  - two PCB-impedance calculators
  - models for major device families
  - an oscilloscope display
  - a totally interactive environment

**LineSim** shows you your signals when it makes the most sense: before you build boards. And it'll teach you more about how transmission lines work than a whole pile of dusty books.

30-day money-back guarantee. **\$595** Requires IBM PC with EGA.

**HyperLynx**


P.O. Box 3578 Redmond, WA 98073-3578 (206) 869-2320

CIRCLE NO 766

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## PLCC LoClip - PLCC Probe

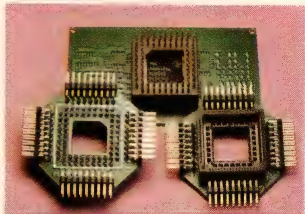

### NEW PRODUCT


The PLCC-LoClipXX line from Ironwood is a new product line allowing probing of surface mount PLCC's at a fraction of size of other clips. The U and L ver. have right angle leads (cable connect or probing). Device heights of 0.75", 0.57", and 0.45" for S, U, and L boards respectively enable probing of boards in backpanels. Interdevice spacing of 0.10" allowed. PLCC's from 24 to 84 pins supported. Kits of 10 with different sizes/carrying case available at substantial discount.

### IRONWOOD ELECTRONICS

P.O. BOX 21151, ST. PAUL, MN 55121  
(612) 431-7025

CIRCLE NO 767

## PROTOTYPING ADAPTORS

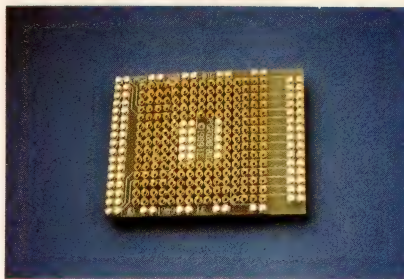

### BY THE HUNDREDS

Our line of prototyping adaptors for VLSI devices including PGA, PLCC, LCC, ZIP, DIP, and Plastic Quad Flatpak is the most extensive available in the industry. These devices allow easy prototyping of these difficult to handle devices. Pins and sockets used are gold plated and of the highest quality. Parts are available in solderdial or with 3 level wirewrap pins. All types of wirewrap panels are covered.

### IRONWOOD ELECTRONICS

P.O. BOX 21151, ST. PAUL, MN 55121  
(612) 431-7025

CIRCLE NO 768

## EMBEDDED DEVELOPMENT TOOLS

with Symbolic Debugging

In-Circuit Emulators	MPU	8 MHz	\$1995
HD64180	MPU	8 MHz	\$1995
Z180	ZTAT	8 MHz	\$2495
HD64180X	NPU	8 MHz	\$2495
HD64180S	CPU	8 MHz	\$1995
Z80			

Put Macrochip Research on your product development team. All of the products listed connect to the PC COM port and include PC based Macro Assembler, Symbolic Debugger, and Development Environment software. Macintosh development environment also supported. All units shipped with 12 month warranty and 30-day, "no risk", guarantee.

Developed and manufactured in the USA

Phone (214) 242-0450  
FAX (214) 245-1005

1301 N. Denton Drive  
Suite 204  
Carrollton, TX 75006

Call or write for detailed product information and prices.



CIRCLE NO 769



Software to release your creative genius

ELECTRONIC ENGINEERS CALL FOR YOUR FREE MAC & MSDOS CATALOG

- AC/DC circuit analysis
- Active & passive filter design & analysis
- Engineering graphics
- Signal processing
- Logic simulation
- Root locus analysis
- Microstrip design
- Thermal analysis
- Statistics/ More




Engineering Professional Software



To order call toll free 1-800-229-0283  
2023 Chicago Ave., Ste. B-13, Riverside, CA 92507

CIRCLE NO 770

## QUICK 'N STABLE

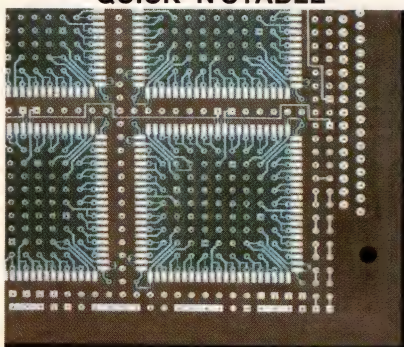

RO2800 (TM) PWB Laminates from Rogers. Low effective dielectric constant (2.8) improves electrical performances in high density, very high speed digital systems. Coefficient of thermal expansion, matched to copper improves plated thru-hole reliability and dimensional stability. **Rogers Corp.**, Rogers, CT 06263 203/774-9605

CIRCLE NO 771

## Communicate Weekly

to the electronics OEM through EDN's Magazine and News Editions Product Mart

CIRCLE NO 772

## TAKE THE FAST TRACK

80C286 AT CMOS SINGLE BOARD COMPUTER




The TEK224 integrates a PC/AT type computer on a single STD Bus card. It features an 80C286 at 16Mhz with zero-wait state, 2 Mbytes of system memory, two serial ports, one parallel port, and consumes less than 6 watts.

P.O. Box 455  
Ste-Thérèse (Québec)  
Canada J7E 4J8  
Tél: (514) 437-5682  
Fax: (514) 437-8053

**TEKNOR**  
MICROSYSTEMS INC.  
The right connection

CIRCLE NO 773

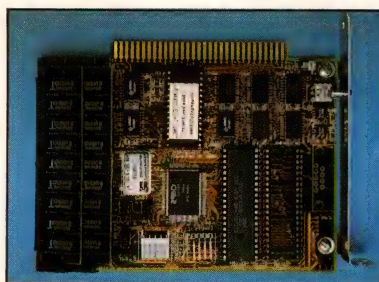

### TURBO XT CPU BOARD

- PC BUS, 4.2" x 5.4" (4 Layer)
- Compatible with MS-DOS 2.0 - 3.X
- Dual speed (4.77 MHz/10 MHz) CPU
- Up to 2 Meg DRAM on board (SIMMs)
- Includes EMS 4.0 Memory Manager
- Processor: V20 Coprocessor: 8087
- \$320 qty. 1; \$160 qty. 10

295 Airport Road  
Naples, FL 33942

1-800-634-0701



TEMPUSTECH, INC.

CIRCLE NO 774

## New EPROM Programmer



**A** \$495, Wintek's Universal EPROM Programmer is a low-cost and versatile tool for programming most industry-standard EPROMs

(2716-27256). Since it can operate with an IBM PC, as well as stand alone, the Programmer is ideal for use with PC-based microcomputer development software. Credit cards are welcome.

### Wintek Corporation

1801 South St., Lafayette, IN 47904  
(800) 742-6809 or (317) 742-8428

CIRCLE NO 775

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



# ...To get any of these functions, buy a KEPCO ATE Power Manager™




Your Kepco ATE Power Manager, like most *conventional* power supplies, is delivered with large output and feedback capacitors connected. This equips it to give you a rock steady voltage in the face of varying load currents.

The ATE, however, is no conventional power supply. The thing that makes it *unconventional* is the 50-terminal user port at the rear.


By simply (1) pulling out the mating connector, (2) rewiring it, and (3) putting it back, you can in a *matter of minutes* obtain access to a host of control functions. You can, for example, cut out the output and feedback capacitors and configure your ATE\* to give you a steady *current* against a varying *voltage*. Better yet, buy a blank connector (they're only \$18 apiece) and wire it up in the current stabilizer configuration. Then, you can make the transformation in moments.

What the Kepco user port does is give you the ability to connect any element in the ATE's control assembly with nearly any other. So the way you wire it determines the nature of the ATE. One configuration lets you control the voltage channel with a 0-10V analog d-c signal (or a digital signal via a Kepco SN or TLD digital interface); another lets you control the current channel with a 0-1V signal. Other configurations let you control voltage or current with a 2-terminal resistance, or a high impedance source; others turn your ATE into a self-powered, oversized op amp or a servo amplifier. And still others let you use the uncommitted amplifiers we've included in the ATE's control assembly, to sum, scale, invert, or integrate control signals. The possibilities are limited only by your imagination.

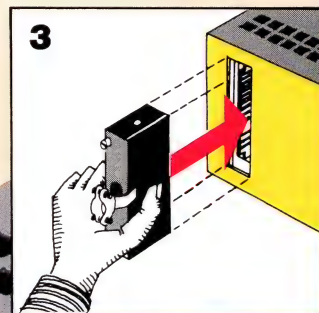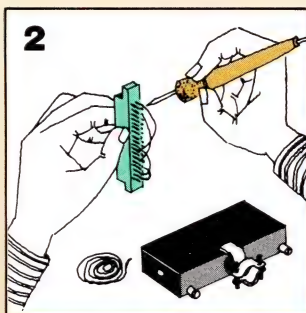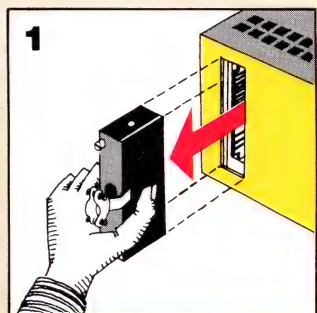\*On Size E models, you must also remove a link from the rear barrier strip.



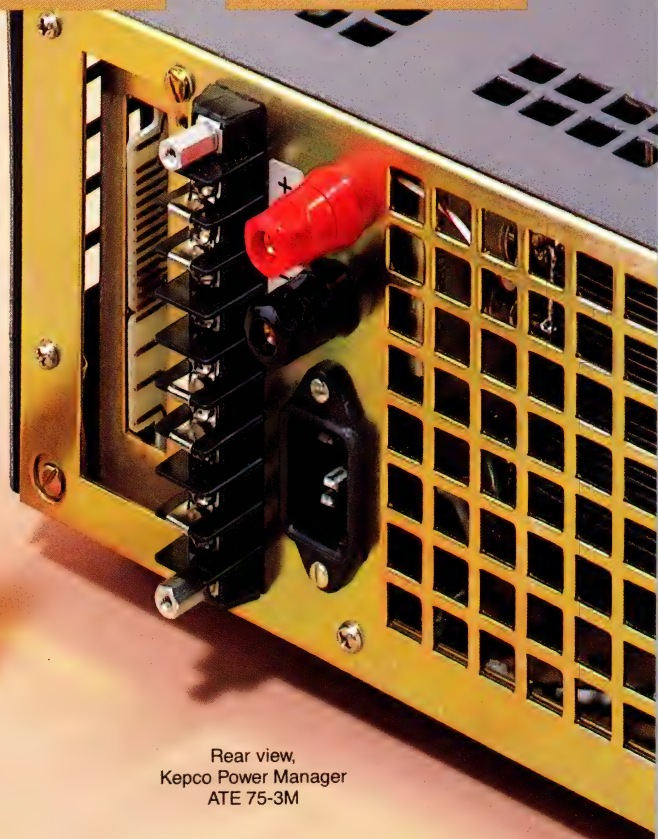50-terminal connector, supplied as PC-13, prewired for local control, slow mode, of 1/4-rack models, and as PC-14 for 1/2-, 3/4-, and full-rack models. Available unwired as PC-12.



Rear view,  
Kepco Power Manager  
ATE 75-3M



STATIC STABILIZATION TABLE

INFLUENCE QUANTITY	OUTPUT EFFECTS VOLTAGE MODE		OUTPUT EFFECTS CURRENT MODE		OFFSETS <sup>(4)</sup>	
	Typ.	Max.	Typ.	Max.	$\Delta E_{IQ}$	$\Delta I_{IQ}$
SOURCE VOLTAGE (min.-max.):	<0.0005% $E_o$ max.	0.001% $E_o$ max.	<0.002% $I_o$ max.	0.005% $I_o$ max.	<1 $\mu$ V	<1 nA
LOAD (no load-full load):	<0.001% $E_o$ max.	0.002% $E_o$ max.	<0.5 mA <sup>(1)</sup>	1 mA <sup>(1)</sup>	—	—
TIME (8-hour drift):	<0.005% $E_o$ max.	0.01% $E_o$ max.	<0.01% $I_o$ max.	0.02% $I_o$ max.	<20 $\mu$ V	<1 nA
TEMPERATURE, per °C:	<0.005% $E_o$ max.	0.01% $E_o$ max.	<0.01% $I_o$ max.	0.02% $I_o$ max.	<20 $\mu$ V	<2 nA
RIPPLE and NOISE <sup>(2)</sup> rms:	<0.1 mV	0.3 mV	<0.01% $I_o$ max.	0.03% $I_o$ max.	—	—
(Slow Mode) p-p: <sup>(3)</sup>	<1 mV	3 mV	<0.1% $I_o$ max.	0.3% $I_o$ max.	—	—
RIPPLE and NOISE <sup>(2)</sup> rms:	<1 mV	3 mV	<0.01% $I_o$ max.	0.03% $I_o$ max.	—	—
(Fast Mode) p-p: <sup>(3)</sup>	<10 mV	30 mV	<0.1% $I_o$ max.	0.3% $I_o$ max.	—	—

(1) For models with output current rating of 50A and higher, the load effect is 2 mA typical and 5 mA maximum. In slow mode, the leakage current through the output capacitor adds approximately 0-6 mA to the current mode load effect.  
(2) One terminal must be grounded for this measurement, or connected so that common mode current does not flow through the load or, in current mode, through the current-sensing resistor.  
(3) Peak-to-peak ripple is measured over a 20 Hz to 10 MHz bandwidth.  
(4) Uncommitted amplifier offsets.

GENERAL

Crowbar trigger time:

Slow mode — 50 $\mu$ sec.  
Fast mode — 500 $\mu$ sec delay, to avoid false triggering.

OVP action:

- 1) Short output with SCR.
- 2) Trip a-c circuit breaker.
- 3) Generate optically isolated flag signal.

Series operation:

To the 500V limit of the isolation voltage; master/slave operation is possible.

Parallel operation:

Master/slave operation, and redundant connections, are possible.

Isolation:

Output may be floated up to 500V off ground. Common mode current — 5 $\mu$ A rms, 50 $\mu$ A peak to peak, at 115V a-c.

Temperature:

Storage — -40°C to 85°C.  
Operating — 0°C to +55°C (derate to 90% of rated current at +65°C.)

Cooling:

Built-in fan (2 in full-rack models) exhausts air to rear.

D-C output terminal (Rear):

1/4-rack models — barrier strip.  
1/2- and 3/4-rack models — binding posts.  
Full-rack models — compression studs.

Meters:

1/4- and 1/2-rack models:  
Two 1½", 3%  
3/4- and full-rack models:  
Two 2½", 2%

Source voltage:

User selectable, 95-113, 105-125, 190-226, or 210-250V a-c, 50-65 Hz, single phase; do not use on 400Hz.

Source current:

See Table 1.

Output current:

Continuously adjustable or programmable, 0-100%.

Control voltage:

Local — 10-turn rheostat on front panel.  
Remote — 0 to 10V signal.

Control current:

Local — 10-turn rheostat on front panel.  
Remote — 0 to 1V signal.

Remote error sensing:

Provision made for 4-terminal connection to load; static drop of 0.5V/lead may be compensated, and an extra volt is provided for this purpose.

Program speed (programming time constant,  $\tau$ ):

Slow mode —  $\tau = R_1 \times C_{out}$  (see model tables).  
Fast mode — see Table 2.

Current recovery for a step load voltage:

Exponential with programming time constant,  $\tau$ .

Mode Indicators

Voltage — green LED, front panel.  
Current — amber LED, front panel.  
OVP — red LED, front panel.

Mode flags

TTL logic signals delivered to rear connector as optically isolated outputs.

OVP control:

Local — trimmer adjustable.  
Remote — 0-10V signal, or may be set to track output voltage.

Remote trigger:

Optically isolated "trigger-in" port allows overvoltage tripping by remotely generated pulse, so that OVPs of several power supplies can be interconnected or sequenced or simultaneous shutdown. Lower limit for OVP is 3V, adjustable to 110%  $E_o$ . Minimum threshold adjustment: 0.5V or 2% $E_o$ , whichever is greater.

Table 1 Source Current

(Measured, worst case, at 125V a-c source voltage)
Size A-1.4A max.
Size B-2.4A max.
Size C-6.0A max.
Size D-11.0A max.
Size E-20.0A max.

Table 2 Dynamic Specifications

Output Voltage Ratings	Bandwidth (-3dB) KHz	Programming Time Constant ( $\mu$ sec)
	Min.	Max.
6V	16.0	10.0
15V	10.6	15.0
25V	8.0	20.0
36V	6.4	25.0
55V	4.0	40.0
75V	3.5	45.0
100V	2.5	65.0
150V	1.7	95.0
325V	0.94	170.0


Voltage recovery: For step load change between 10% and 100%  $I_o$  maximum <50  $\mu$ sec typ., <100  $\mu$ sec max. to recover within 10mV






# KEPCO'S SERIES ATE™ VOLTAGE STABILIZERS DO MORE THAN...

...SUPPLY  
STABILIZED VOLTAGE

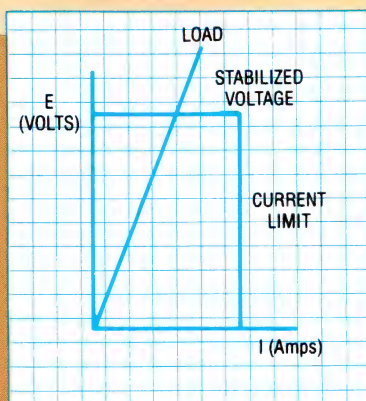


0.001% voltage stabilizer


AND CURRENT.

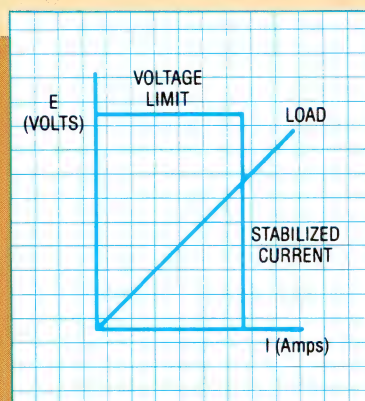

0.005% current stabilizer

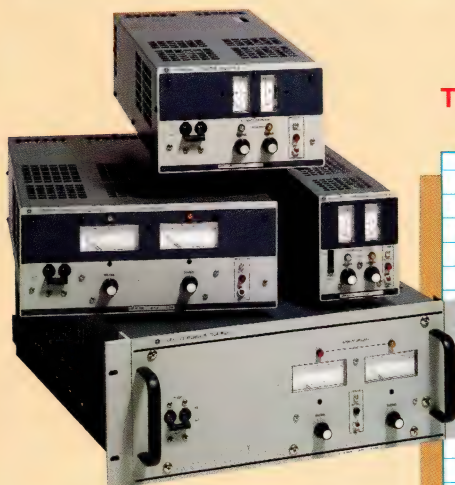


THEY'RE PROGRAMMABLE  
IN VOLTAGE MODE.

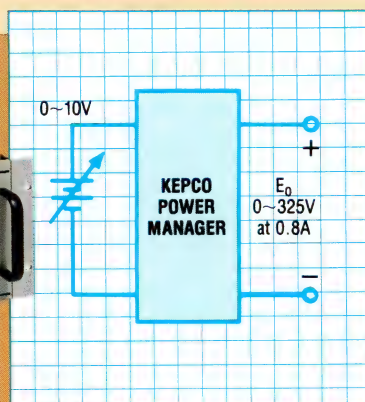

A voltage stabilizer controlled  
by a 0-10V d-c signal

THEY'RE PROGRAMMABLE  
IN CURRENT MODE.

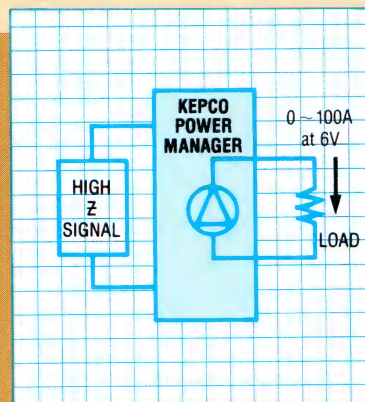


A current stabilizer controlled  
by a high impedance source




**KEPCO**  
THE POWER SUPPLIER™

THEY'LL ACCEPT  
FEEDBACK.

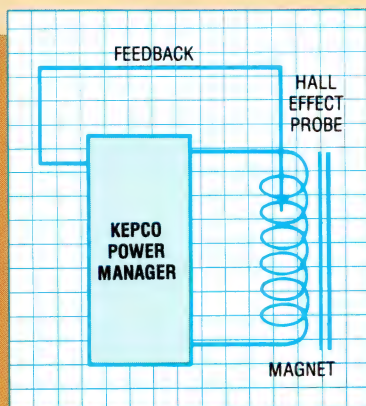


A magnetic field stabilizer  
controlled by a Hall-effect sensor

THEY'LL FUNCTION  
AS AN AMPLIFIER...

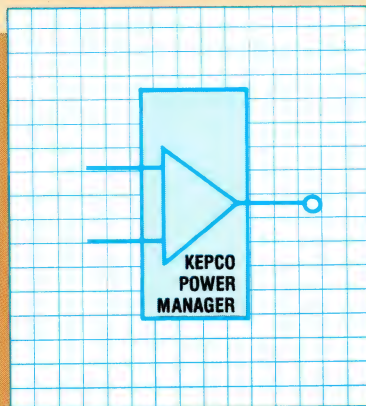

A self-powered oversized  
op-amp

OR CONTROL A MACHINE.

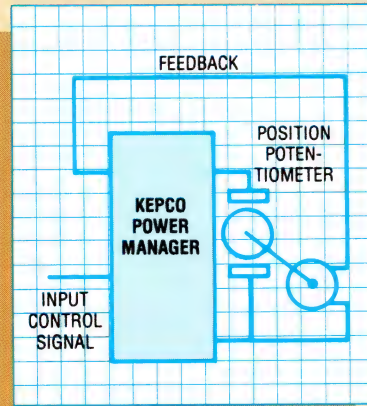

A servo amplifier to drive  
a positioning motor



ATE MODELS • QUARTER • HALF • THREE-QUARTER • FULL RACK

ACCESSORY FOR RACK MOUNTING: RA 37

<b>50 WATTS</b> 0-55°C No Derating QUARTER RACK SIZE A	MODEL	D-C OUTPUT RANGE		OUTPUT IMPEDANCE VOLTAGE MODE			OUTPUT IMPEDANCE CURRENT MODE		
		VOLTS	AMPS	SERIES RESISTANCE	SERIES INDUCTANCE SLOW	FAST	SHUNT (2) RESISTANCE	SHUNT CAPACITANCE SLOW	FAST
	ATE 6-5M	0-6	0-5	24 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	12 k $\Omega$	1,000 $\mu$ F	1 $\mu$ F
	ATE 15-3M	0-15	0-3	100 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	30 k $\Omega$	450 $\mu$ F	0.4 $\mu$ F
	ATE 25-2M	0-25	0-2	250 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	50 k $\Omega$	250 $\mu$ F	0.25 $\mu$ F
	ATE 36-1.5M	0-36	0-1.5	480 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	72 k $\Omega$	200 $\mu$ F	0.2 $\mu$ F
	ATE 55-1M	0-55	0-1	1.1 m $\Omega$	2 $\mu$ H	20 $\mu$ H	110 k $\Omega$	150 $\mu$ F	0.15 $\mu$ F
	ATE 75-0.7M	0-75	0-0.7	2.15 m $\Omega$	2 $\mu$ H	20 $\mu$ H	150 k $\Omega$	110 $\mu$ F	0.1 $\mu$ F
	ATE 100-0.5M	0-100	0-0.5	4 m $\Omega$	4 $\mu$ H	40 $\mu$ H	200 k $\Omega$	50 $\mu$ F	0.05 $\mu$ F
	ATE 150-0.3M	0-150	0-0.3	10 m $\Omega$	4 $\mu$ H	40 $\mu$ H	300 k $\Omega$	55 $\mu$ F	0.02 $\mu$ F

Size: 57/32" H x 45/32" W x 17 1/8" D (132.6mm H x 105.6mm W x 435.0mm D)<sup>(1)</sup> Net Weight: 14 lbs. (6.4 kg.)

<b>100 WATTS</b> 0-55°C No Derating QUARTER RACK SIZE B	MODEL	D-C OUTPUT RANGE		OUTPUT IMPEDANCE VOLTAGE MODE			OUTPUT IMPEDANCE CURRENT MODE		
		VOLTS	AMPS	SERIES RESISTANCE	SERIES INDUCTANCE SLOW	FAST	SHUNT (2) RESISTANCE	SHUNT CAPACITANCE SLOW	FAST
	ATE 6-10M	0-6	0-10	12 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	12 k $\Omega$	1,800 $\mu$ F	2 $\mu$ F
	ATE 15-6M	0-15	0-6	50 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	30 k $\Omega$	1000 $\mu$ F	0.8 $\mu$ F
	ATE 25-4M	0-25	0-4	125 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	50 k $\Omega$	500 $\mu$ F	0.5 $\mu$ F
	ATE 36-3M	0-36	0-3	240 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	72 k $\Omega$	350 $\mu$ F	0.4 $\mu$ F
	ATE 55-2M	0-55	0-2	0.55 m $\Omega$	2 $\mu$ H	20 $\mu$ H	110 k $\Omega$	200 $\mu$ F	0.3 $\mu$ F
	ATE 75-1.5M	0-75	0-1.5	1 m $\Omega$	2 $\mu$ H	20 $\mu$ H	150 k $\Omega$	110 $\mu$ F	0.2 $\mu$ F
	ATE 100-1M	0-100	0-1	2 m $\Omega$	4 $\mu$ H	40 $\mu$ H	200 k $\Omega$	80 $\mu$ F	0.1 $\mu$ F
	ATE 150-0.7M	0-150	0-0.7	4 m $\Omega$	4 $\mu$ H	40 $\mu$ H	300 k $\Omega$	55 $\mu$ F	0.04 $\mu$ F

Size: 57/32" H x 45/32" W x 17 1/8" D (132.6mm H x 105.6mm W x 435.0mm D)<sup>(1)</sup> Net Weight: 17 lbs. (7.7 kg.)

ACCESSORY FOR RACK MOUNTING: RA 37

<b>250 WATTS</b> 0-55°C No Derating HALF RACK SIZE C	MODEL	D-C OUTPUT RANGE		OUTPUT IMPEDANCE VOLTAGE MODE			OUTPUT IMPEDANCE CURRENT MODE		
		VOLTS	AMPS	SERIES RESISTANCE	SERIES INDUCTANCE SLOW	FAST	SHUNT (2) RESISTANCE	SHUNT CAPACITANCE SLOW	FAST
	ATE 6-25M	0-6	0-25	4.8 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	12 k $\Omega$	11,000 $\mu$ F	5 $\mu$ F
	ATE 15-15M	0-15	0-15	20 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	30 k $\Omega$	5,800 $\mu$ F	2 $\mu$ F
	ATE 25-10M	0-25	0-10	50 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	50 k $\Omega$	2,900 $\mu$ F	1.25 $\mu$ F
	ATE 36-8M	0-36	0-8	90 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	72 k $\Omega$	2,400 $\mu$ F	1 $\mu$ F
	ATE 55-5M	0-55	0-5	0.22 m $\Omega$	2 $\mu$ H	20 $\mu$ H	110 k $\Omega$	1,400 $\mu$ F	0.75 $\mu$ F
	ATE 75-3M	0-75	0-3	0.5 m $\Omega$	2 $\mu$ H	20 $\mu$ H	150 k $\Omega$	850 $\mu$ F	0.5 $\mu$ F
	ATE 100-2.5M	0-100	0-2.5	0.8 m $\Omega$	4 $\mu$ H	40 $\mu$ H	200 k $\Omega$	375 $\mu$ F	0.25 $\mu$ F
	ATE 150-1.5M	0-150	0-1.5	2 m $\Omega$	4 $\mu$ H	40 $\mu$ H	300 k $\Omega$	275 $\mu$ F	0.1 $\mu$ F
	ATE 325-0.8M	0-325	0-0.8	8.1 m $\Omega$	100 $\mu$ H	1 mH	650 k $\Omega$	180 $\mu$ F	0.01 $\mu$ F

Size: 57/32" H x 8 1/32" W x 17 9/64" D (132.6mm H x 211.9mm W x 435.4mm D)<sup>(1)</sup> Net Weight: 35 lbs. (15.9 kg.)

ACCESSORY FOR RACK MOUNTING: RA 37

<b>500 WATTS</b> 0-55°C No Derating THREE-QUARTER RACK SIZE D	MODEL	D-C OUTPUT RANGE		OUTPUT IMPEDANCE VOLTAGE MODE			OUTPUT IMPEDANCE CURRENT MODE		
		VOLTS	AMPS	SERIES RESISTANCE	SERIES INDUCTANCE SLOW	FAST	SHUNT (2) RESISTANCE	SHUNT CAPACITANCE SLOW	FAST
	ATE 6-50M	0-6	0-50	2.4 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	12 k $\Omega$	12,000 $\mu$ F	10 $\mu$ F
	ATE 15-25M	0-15	0-25	12 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	30 k $\Omega$	8,000 $\mu$ F	4 $\mu$ F
	ATE 25-20M	0-25	0-20	25 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	50 k $\Omega$	5,800 $\mu$ F	2.5 $\mu$ F
	ATE 36-15M	0-36	0-15	48 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	72 k $\Omega$	4,900 $\mu$ F	2 $\mu$ F
	ATE 55-10M	0-55	0-10	0.11 m $\Omega$	2 $\mu$ H	20 $\mu$ H	110 k $\Omega$	2,900 $\mu$ F	1.5 $\mu$ F
	ATE 75-8M	0-75	0-8	0.19 m $\Omega$	2 $\mu$ H	20 $\mu$ H	150 k $\Omega$	1,200 $\mu$ F	1 $\mu$ F
	ATE 100-5M	0-100	0-5	0.4 m $\Omega$	4 $\mu$ H	40 $\mu$ H	200 k $\Omega$	600 $\mu$ F	0.5 $\mu$ F
	ATE 150-3.5M	0-150	0-3.5	0.86 m $\Omega$	4 $\mu$ H	40 $\mu$ H	300 k $\Omega$	440 $\mu$ F	0.2 $\mu$ F

Size: 57/32" H x 12 17/32" W x 17 9/64" D (132.6mm H x 318.3mm W x 435.4mm D)<sup>(1)</sup> Net Weight: 43 lbs. (19.5 kg.)

The full rack model is supplied with brackets for direct mounting in a standard 19-inch rack.

<b>1000 WATTS</b> 0-55°C No Derating FULL RACK SIZE E	MODEL	D-C OUTPUT RANGE		OUTPUT IMPEDANCE VOLTAGE MODE			OUTPUT IMPEDANCE CURRENT MODE		
		VOLTS	AMPS	SERIES RESISTANCE	SERIES INDUCTANCE SLOW	FAST	SHUNT (2) RESISTANCE	SHUNT CAPACITANCE SLOW	FAST
	ATE 6-100M	0-6	0-100	1.2 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	12 k $\Omega$	22,000 $\mu$ F	15 $\mu$ F
	ATE 15-50M	0-15	0-50	6 $\mu\Omega$	0.5 $\mu$ H	5 $\mu$ H	30 k $\Omega$	12,000 $\mu$ F	6 $\mu$ F
	ATE 25-40M	0-25	0-40	12.5 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	50 k $\Omega$	11,000 $\mu$ F	4 $\mu$ F
	ATE 36-30M	0-36	0-30	24 $\mu\Omega$	1 $\mu$ H	10 $\mu$ H	72 k $\Omega$	9,500 $\mu$ F	3 $\mu$ F
	ATE 55-20M	0-55	0-20	55 $\mu\Omega$	2 $\mu$ H	20 $\mu$ H	110 k $\Omega$	5,200 $\mu$ F	2.25 $\mu$ F
	ATE 75-15M	0-75	0-15	0.1 m $\Omega$	2 $\mu$ H	20 $\mu$ H	150 k $\Omega$	3,400 $\mu$ F	1.5 $\mu$ F
	ATE 100-10M	0-100	0-10	0.2 m $\Omega$	4 $\mu$ H	40 $\mu$ H	200 k $\Omega$	1,200 $\mu$ F	0.75 $\mu$ F
	ATE 150-7M	0-150	0-7	0.42 m $\Omega$	4 $\mu$ H	40 $\mu$ H	300 k $\Omega$	1,050 $\mu$ F	0.3 $\mu$ F

Size: 63 1/32" H x 16 1/2" W x 20 1/64" D (177.0mm H x 419.1mm W x 508.4mm D)<sup>(1)</sup> Net Weight: 87 lbs. (39.5 kg.)

<sup>(1)</sup>Add 21/2" (63.5mm) for connector protrusion. <sup>(2)</sup>Based on 0.5 mA load effect in FAST mode.  
<sup>(3)</sup>For determining dynamic impedance in voltage mode. <sup>(4)</sup>For determining dynamic impedance in current mode.




**Kepeco ATE Power Managers** are unipolar linear programmable power supplies that give you full external control over both voltage and current, with automatic crossover. They have panel-mounted meters for monitoring both channels, and front panel LEDs (and optically isolated flags accessible through the user port) to tell you which channel is in charge. Local control is by panel-mounted 10-turn rheostats.




ATE POWER SUPPLIES  
50 Watts to 1000 Watts

### ATE CAN SUM INPUT CONTROL SIGNALS

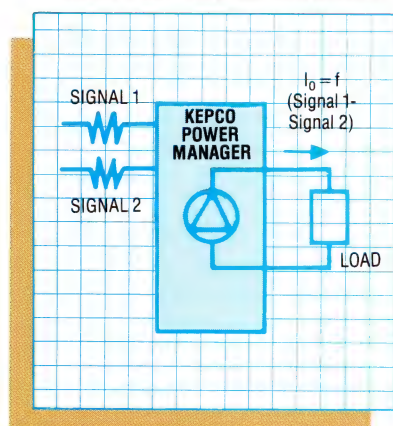


A current stabilizer controlled  
by the difference between  
two signals

### ...BE DRIVEN BY AN ANALOG FUNCTION

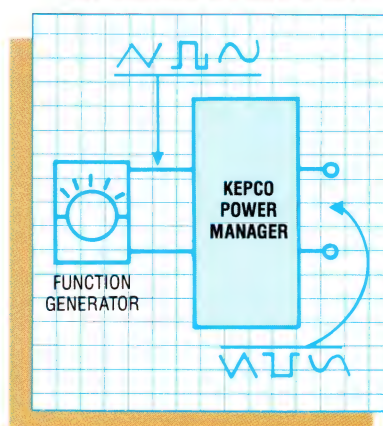

A voltage stabilizer controlled  
by a signal generator
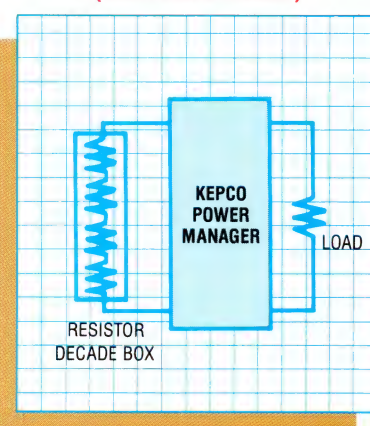
### OR INTERFACE TO THE DIGITAL WORLD (See back cover).



A voltage stabilizer controlled  
by a passive resistance  
decade box

"Power Manager," "ATE Power Manager,"  
"BOP Power Manager" and "Kepeco Power Manager"  
are Trade Marks of Kepeco, Inc.



Data subject to change without notice.  
© 1989 KEPCO, INC. Litho in U.S.A.



## Kepeco's Series ATE power supplies are "MATE-verified" for use in Modular Automatic Test Equipment that is addressed in the (CIIL) Control Interface Intermediate Language.

Kepeco's TLD 488-16 interactive digital interface is an IEEE-488-driven talker-listener that has been verified as a TMA (Test Module Adapter) for Kepeco's ATE and BOP<sup>(1)</sup> power supplies.



On October 1, 1987 Kepeco's TLD officially achieved "MATE-verified" status. The certificate shown was issued by the MATE program office, Kelly AFB, Texas.

The TLD 488-16 responds to commands in CIIL (Control Interface Intermediate Language) over the IEEE-488 bus from your computer or digital controller, and passes them along to the Power Managers under its control. It can control up to 16 Kepeco ATE and/or BOP Power Managers at once, and if one of them cannot obey a command, it sends back a flag which the TLD 488-16 translates into CIIL and passes along to the controller as an "error message." Among the error messages it can send are "crowbarred," "overload," "voltage comparison error," and "current comparison error."

You can give your commands to the TLD 488-16 directly in Volts and Amps, because it knows the voltage and current ranges of every Power Manager under its control and can calculate what percentage of full scale a given voltage or current setting is.

(1) BOP are Kepeco Bipolar Power Supplies. Please see brochure 146-1636.

## Kepeco Series ATE power supplies may be listener-addressed using a selection of 1-, 4- and 8-channel digital interfaces.

SN 488 works with the IEEE-488 bus, and SN 500 works with buses using bit-parallel data transfer, but they're otherwise identical. They're both available with one channel or with two isolated channels, and if you buy a single channel model, you can buy a field-installable second channel any time you need it.

SNR 488-4 and SNR 488-8 are card cages into which you can plug four to eight dual channel programming cards.

Output of all SN cards is 0 to  $\pm 1V$  or 0 to  $\pm 10V$  selectable, and all offer models that accept data in 12-bit hex or 3 digit BCD.

### TYPE SN STAND ALONE INTERFACE



MODEL	SINGLE AND DUAL CHANNEL PROGRAMMERS, 1/4-RACK SIZE							
	SN488-				SN500-			
	121	122	031	032	121	122	031	032
NUMBER OF CHANNELS	1	2	1	2	1	2	1	2
INPUT DATA CODING FORMAT	Hex		Decimal		Hex		Decimal	
RESOLUTION	12 Bit		3 Digit		12 Bit		3 Digit	

**TYPE SNR 488-4**  
(Addresses up to 4 ATE power supplies)


**TYPE SNR 488-8**  
(Addresses up to 8 ATE power supplies)

#### SNR Housings

MODEL	HOLDS
SNR 488-4	4 Cards
SNR 488-8	8 Cards

#### Interface cards

MODEL	DATA FORMAT	RESOLUTION
SN 488-B	Hex	12-bit binary
SN 488-D	Decimal	3-digit BCD

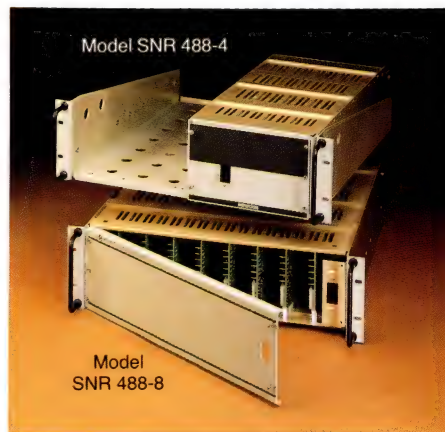



# CAREER OPPORTUNITIES

## 1990 Recruitment Editorial Calendar

Issue	Issue Date	Ad Deadline	Editorial Emphasis
Magazine Edition	Mar. 1	Feb. 8	Computer-Aided Engineering/ASICs, Computers & Peripherals, Digital ICs/Microprocessors, Semicustom ICs
News Edition	Mar. 8	Feb. 15	Analog/ICs, Automotive Electronics, Special Supplement: RISC/Microprocessors
Magazine Edition	Mar. 15	Feb. 22	Analog ICs, Components, Engineering Software, Special Design Project #1
News Edition	Mar. 22	Mar. 2	Optoelectronics, Peripherals, Regional Profile: New York, Pennsylvania & Connecticut
Magazine Edition	Mar. 29	Mar. 8	Software Special Issue—Interface ICs, Software/Programming/Microprocessors/ASICs, April Fools Section, Special Design Project #2
News Edition	Apr. 5	Mar. 16	IC/Logic ICs, Distribution, Special Supplement: Distribution
Magazine Edition	Apr. 12	Mar. 22	Communications Special Issue—Communication ICs, Communication Systems, Microprocessors, Special Design Project #3
News Edition	Apr. 19	Mar. 30	ICs/Graphics Controllers/Microprocessors, Industrial Automation, Regional Profile: So. California
Magazine Edition	Apr. 26	Apr. 5	Computer Boards/Microprocessors, Power Sources, Sensors/Transducers, Special Design Project #4, Electro Show Issue
News Edition	May 3	Apr. 12	CAE/Board Layout, Education, Special Supplement: ASICs, Electro Show Issue
Magazine Edition	May 10	Apr. 19	Analogy Technology Special Issue—Analog ICs, Analog Instruments, Digital ICs/Microprocessors/ASICs, Special Design Project #5
News Edition	May 17	Apr. 27	ICs/Memory ICs, Test & Measurement, Regional Profile: Massachusetts & New Hampshire
Magazine Edition	May 24	May 3	Microprocessors, Computers & Peripherals, Semicustom ICs/ASICs, Components, Sensors & Transducers
Magazine Edition	June 7	May 17	Software, Design Tools, Microprocessor I/O Chips, $\mu$ P Support Chip Directory
News Edition	June 14	May 24	Peripherals/Input Devices, Software, Special Supplement: EDA
Magazine Edition	June 21	May 31	Computer-Aided Engineering, Computers & Peripherals, Power Semiconductors, Semicustom ICs/ASICs
News Edition	June 28	June 8	ICs/RISC/Microprocessors, Image Processing, Regional Profile: Oregon & Washington
Magazine Edition	July 5	June 14	Product Showcase—Volume I: Hardware & Interconnect, Power Sources, ICs & Semiconductors, Software
News Edition	July 12	June 21	Analog/Communication ICs, ASICs, Special Supplement: Automotive Electronics, Regional Profile: Washington, DC.
Magazine Edition	July 19	June 28	Product Showcase—Volume II: CAE/ASICs, Computers & Peripherals, Components, Test & Measurement
Magazine Edition	Aug. 2	July 12	Digital ICs/Microprocessors, Computer-Aided Engineering, Computers & Peripherals, Test & Measurement, Technical Article Database
News Edition	Aug. 9	July 20	CAE/Software, Aerospace, Special Supplement: Defense
Magazine Edition	Aug. 20	July 30	Military Special Issue, Vision/Image Systems, ICs & Semiconductors, Memory Technology, Software
News Edition	Aug. 23	Aug. 3	Electromechanical, Opportunities in Non-EOEM, Regional Profile: New Mexico, Arizona
Magazine Edition	Sept. 3	Aug. 13	ASICs Special Issue—Semicustom ICs, Computer-Aided Engineering, Digital Components, ICs & Semiconductors
News Edition	Sept. 6	Aug. 17	CAE/Software, CASE/CAE, Special Supplement: DSP

Call today for information:

East Coast: Janet O. Penn (201) 228-8610

Nancy Olbers (603) 436-7565

National: Robert Renard (201) 228-8602



## Something Great Is Happening ...

At GE Medical Systems there is a unique spirit! It is the feeling that comes when you are a true global leader. It is the feeling that comes when you are innovator in state-of-the-art medical diagnostic systems.

Our people are part of that spirit. Smart. Proud. Think'ers and Do'ers working with an elite group in the evolution of CT and PET imaging systems. Join our world class team functioning as **SENIOR LEAD CONTRIBUTOR** in a sophisticated scientific environment as:

### MANAGER, POWER AND ANALOG ELECTRONICS

Lead the electrical design of motion control, data acquisition and high-voltage subsystems from concept through manufacturing.

### UNIX SOFTWARE PROJECT LEADER:

Sun, Unix languages, computer-aided development tools.

### REAL-TIME SOFTWARE ARCHITECT:

C, Unix, Sun, process control, communications.

### LOW LEVEL ANALOG DATA

### ACQUISITION:

Custom sub pico-amp, 20 bit data acquisition systems, low noise circuit design, hi-speed, multi-channel data acquisition.

### DIGITAL SIGNAL PROCESSING:

Algorithm to circuitry translation, DSP, ASIC, hi-speed signal distribution, Mentor circuit simulation, use of design tools for gate array and Xilinx design/simulation.

### MECHANICAL DESIGN ENGINEER:

Develop mechanical structure and packaging design using Apollo CAD tools.

### ELECTRONICS CAE SYSTEM ENGINEER:

Implement Mentor CAE systems, digital design, ASIC and circuit simulations, new product design.

### SOFTWARE SYSTEM DESIGNER & ARCHITECT:

Lead complex software architecture and development, algorithm implementation, real-time data acquisition, digital signal processing, cost/reliability analysis.

### EXPERT SYSTEMS SOFTWARE ENGINEER:

C, Unix, image processing, networking and interprocess communications, hardware architecture familiarity.

All positions require BS/MS/PhD (EE, CS, Physics or Applied Math) and experience with advanced design tools, image processing, signal processing and real-time data acquisition.

### A GREAT OPPORTUNITY TO JOIN A GREAT TEAM!

GE's highly competitive salary and benefits package befits an industry leader. Please send your resume in strictest confidence indicating position of interest to: MC, GE Medical Systems, P.O. Box 414, W407, Milwaukee, WI 53201. Replies will be made to candidates of interest only.



**GE Medical Systems**

Equal Opportunity Employer



A contest of skill or ability calling for individuals with an indomitable spirit and unwavering self-confidence.

The competition is fierce. Motorola Inc. — recipient of the 1988 Malcolm Baldrige National Quality Award — meets the challenge with a style that's all our own. Which is why our Semiconductor Products Sector has a winning spirit and a worldwide reputation for innovation. If you share our spirit, consider the opportunities available for:



**VLSI CMOS Circuit Designers** — Requires BSEE/MSEE and 2+ years experience; background in microprocessor and SRAM peripherals, knowledge of IC test a plus.

**Drafter Mask, Layout/Designers** — Requires 2 year technical degree; 1-2 years IC layout design experience preferred.

**DSP Product Engineers** — Requires BSEE with 3+ years experience. Responsible for product improvement of SDP devices through yield improvement at wafer probe, assembly and test, device shrinks, plastic packaging improvements, and manufacturing efficiencies.

**Digital/Audio Applications Engineers** — Requires MSEE with 1+ years experience. Ability to program in C, and experience developing 16, 24 and 32-bit DSPS applications suitable for demonstration to customers.

**Diagnostics Software Design Engineers** — Background in C and Assembly language programming in a Unix environment is required. Knowledge of microprocessor and memory system design a plus. Bachelors or Masters degree in CS or EE essential.

**Compiler Software Engineers** — BS/MSCS with 3-5 years experience in compiler programming and development. Experience with parsers, code generators and optimizers desirable.

**Circuit Design & CAD Engineers** — Requires 2-5 years DRAM/SRAM design experience. Ability to innovate new circuits with CAE design and layout verification tools required. Recent experience with CMOS/BICMOS technology desired.

**Telecom IC & System Design Engineers** — 2-5 years experience with imbedded memory design, high level simulation, circuit and logic design, or systems level design required.

An international competitor in the semiconductor industry. Naturally, it's Motorola SPS. To explore all we have to offer, send resume to: Employment Dept. ATX-164, 505 Barton Springs Rd., One Texas Center, 4th Floor, Austin, TX 78704. (800) 531-5183, (512) 322-8814, Fax (512) 322-8811. An Equal Opportunity/Affirmative Action Employer.



**MOTOROLA**

**Semiconductor Products Sector**

## IT'S IN OUR NATURE.



# Take On The Ultimate Technological Challenge

***"The challenges and rewards don't get any bigger than this."***

—Manny Hernandez  
Senior Project Engineer

At TRW's Defense Communications Division, we're involved in the most important business around. National security is at stake. And that puts an incredible demand on our technological advancements. If you're up to the challenge of creating sophisticated electronic payloads, data links and related ground equipment for critical Department of Defense programs, explore the following opportunities:

## **Digital Development Laboratory**

This lab provides advanced technology for the design and development of spacecraft payloads. Areas of responsibility include wideband and high precision analog to digital converters, high speed logic (to gigabit rates), LSI, superchip and hybrid design, on board computers and digital signal processors, demodulators, bit synchronizers, and frequency synthesizers. Technology development in the areas of GaAs HBT, HEMT, and Silicon are underway with emphasis on next generation components and subsystems for state-of-the-art digital communications systems. The following openings require BS/MSEE, 4-10 years experience, strong analytical capability and hands-on hardware experience:

• **Senior Staff Engineers**—Will lead and participate in a wide range of digital design projects. Responsible for signal processor design, wideband multiplexing/formatting, computer architecture and special demodulators. Requires a BS/MSEE and 10+ years experience.

• **Frequency Synthesizer Design Engineers**—Will perform detailed design and manage the development of advanced frequency synthesizers incorporating custom components. Requires a BSEE and 4 years experience. Experience with phase noise analysis, stability and loop dynamics desired.

• **A/D Converter Design Engineers**—Design and development of custom A/D converters and their applications. Experience with architecture trades, detailed design and testing required. Requires BS/MSEE and a minimum of 4 years applicable experience. Both design and technical management positions are available.

• **Digital Processor Design Engineers**—Design and develop digital signal processors and computer systems for spacecraft and advanced technology applications. Work with VHSIC and ASIC technologies and advanced simulation and CAE tools. Requires an MSEE and four years experience. Detailed design, digital signal processing theory, or computer architecture background required.

## **Communications Laboratory**

This lab utilizes advanced technology to design and develop analog, microwave, and millimeter wave hardware for all TRW payloads. Hardware developed includes receivers, frequency converters, frequency sources, modulators, demodulators, low noise amplifiers, and transmitters. The lab conducts R&D in technology used to implement this hardware with current emphasis on GaAs and HEMT MMICs, HBT circuits, millimeter wave components, monolithic switch matrices, high rate modulators and demodulators, and solid state power amplifiers. These positions require a BS/MSEE, 2-12 years experience, strong theoretical/analytical background and hardware development experience.

• **Senior Staff Engineers**—Lead advanced technology projects, conduct subsystem studies, support proposals, manage flight hardware development both at TRW and at subcontracts. Requires BSEE/MSEE, 12 years experience, and a strong technology or subsystem design and analysis background. Ph.D. desirable.

• **Responsible Design Engineers**—Lead the design and development of state-of-the-art flight hardware, providing technical direction, managing design engineers and technical support personnel, and interfacing with subcontractors. Requires BSEE/MSEE, 8 years experience, and a strong background in unit design and development.

• **Microwave Design Engineers**—Design and develop advanced microwave circuits incorporating GaAs and HEMT MMIC, HBT, MIC, and discrete components for low noise and power amplifiers and analog applications covering UHF to microwave frequencies. Requires BSEE/MSEE and 2-8 years experience. Thorough knowledge of microwave and monolithic design techniques, CAD, and RF test desired.

• **Millimeter Wave Design Engineers**—Design and develop advanced millimeter wave components, including monolithic circuits, through 100GHz. Requires BSEE/MSEE and 2-8 years experience. Knowledge of millimeter wave design techniques, devices, and test desired.

TRW's comprehensive employee compensation package includes professional amenities that are among the best in our industry. Tomorrow is taking shape at a company called TRW. Please send your resume to: **B.R. Anderson, TRW ESG, Dept. EDN21, R10/1757, One Space Park, Redondo Beach, CA 90278. Telefax (213) 812-7874.**

**Equal Opportunity Employer  
U.S. Citizenship Required  
for most positions**

# **TRW**





IN ENGINEERING AND  
TACTICAL SYSTEMS,

# Quality of Technology Sets Us Apart.


Leonardo Da Vinci's exceptional foresight enabled him to make discoveries and achievements in the broad-based areas of art and engineering. Today, the Da Vinci spirit is thriving at Fortune-100 Raytheon, where vision is combined with diverse technical expertise to advance quality technology beyond current boundaries.

Raytheon's Missile Systems Laboratories has created many of today's most sophisticated air defense systems including HAWK, PATRIOT, and Sparrow. Due to continued expansion and new business, we seek engineering professionals with experience in the following disciplines:

- Infrared Systems Design & Development
- Digital CAD Systems
- Software Development
- Tactical Operations Analysis
- ATE Design
- MMIC Design
- Antenna & Radome Design
- Missile Guidance & Control
- Digital Design
- Test/Diagnostic Software
- Microwave Oscillator Source & Receiver Design
- Switching Power Supplies
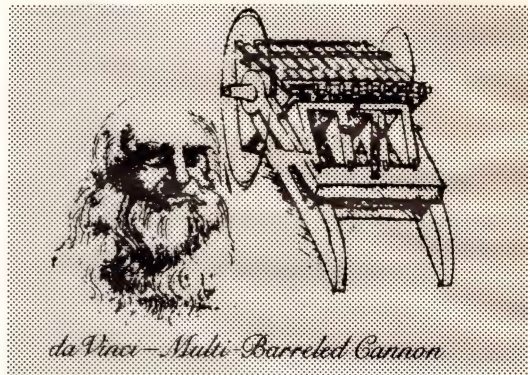
## Raytheon

*Where quality starts with fundamentals.*



Positions range from entry to senior-level and require a BS degree in EE, Physics, Math or Computer Science.

In addition to the unmatched educational, cultural and recreational resources prominent in the New England region, we offer competitive salaries, liberal relocation allowances and many company paid benefits including a 401(k) plan and tuition assistance.

Please send resume including salary requirements to:

**Raytheon Company, Missile Systems  
Laboratories, Employment Dept. N,  
50 Apple Hill Drive, Tewksbury,  
Massachusetts 01876. An Equal  
Opportunity Employer.**



It seems that every custom power supply project starts with inflexible performance specifications, impractical space limitations, and unrealistic completion schedules.


That is why Lorain custom power supplies start with Lorain Megahertz Power Modules. These compact, field proven modules contain a patented megahertz technology that provides exceptional power density, extremely high operating efficiency, quiet operation, and agency compliance. There are over 170 master and booster modules to accurately meet your system requirements.

To these, we add custom circuitry to match your input and output specifications; design-in visuals, forced load sharing, and other peripheral components; even allow for future expansion capabilities with additional plug-in booster modules.

If you are looking for a custom power solution that cuts turnaround time dramatically, practically eliminates debugging, and conserves space, call the Lorain Power Team. We are ready for your problem.

# The Flexible, Practical, Realistic solution to custom power
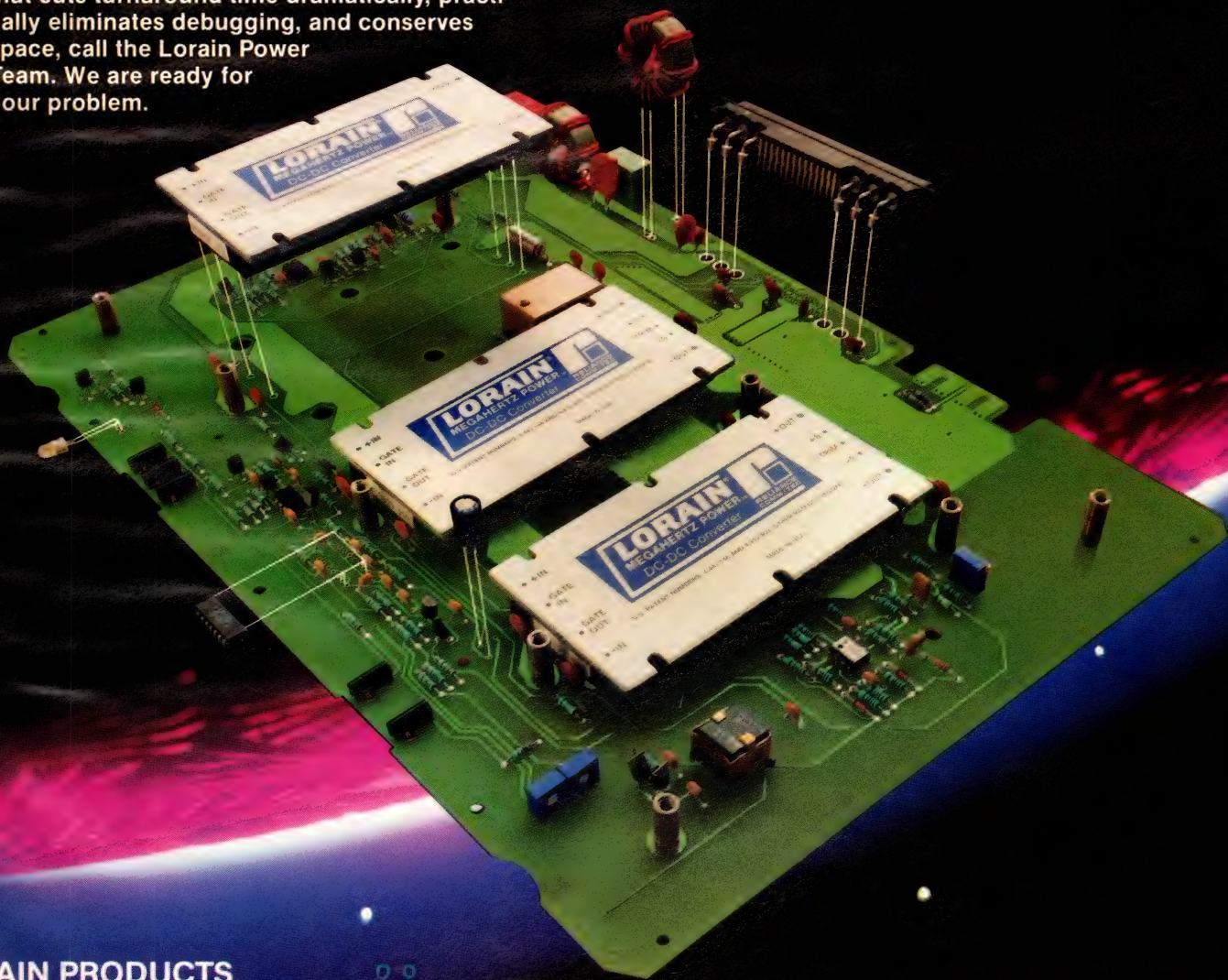
## Custom Lorain® Megahertz Power™ Supplies




### LORAIN PRODUCTS

1122 F Street, Lorain, OH 44052-2293, (216) 288-1122

RELIANCE COMM/TEC, CANADA  
St. Thomas, ONT., (519) 631-0780

**RELIANCE**  
**COMM/TEC**





# "Meets spec. But can we do it in budget?"

Your design is like a baby. First, it's conceived. Then you nurture it. And prepare it for the real world.

To your design, however, the real world is a manufacturing plant. And if your design can't be manufactured cost-effectively, it will never get past the infancy stage.

Fortunately, there's National Design. Where the nation's premier OEM specialists will help you create designs that combine the best of your creative skills with producibility.

At National Design, you'll see innovative systems and technologies from over 800 OEM exhibitors. Plus leading CAD/CAM/CAE exhibits to help you create more freely. And the full spectrum of OEM components and materials for every stage of your design's development.

There's also a complete Conference program sponsored by the ASME. With sessions and workshops that deal specifically with Design for Manufacturability.

These days, creating a design to be manufactured is an awesome responsibility. But you don't have to do it alone. Come to National Design. And discover how to prepare your design for the real world.



**National  
Design  
Engineering  
Show & Conference™**

February 26 - March 1, 1990  
McCormick Place North •  
Chicago, IL

**SPECIAL DISCOUNT OFFER!**

**Save \$15**

**Bring this ad to the show for  
discount admission of only \$10.**

For more information, call 203-964-8287 today.



**Cahners  
Exposition  
Group**

XL

A member of the Reed Exhibition Companies.

© Reed Publishing (USA) Inc., 1989

***We help designs make it  
in the real world.***



# EDN's INTERNATIONAL ADVERTISERS INDEX

Abbott Transistor Laboratories Inc . . . . .	64	Integrated Device Technology Inc . . . . .	28	Sony Component Products . . . . .	76-77
ACCEL Technologies Inc . . . . .	169	Interphase Corp . . . . .	131	Sophia Systems Inc . . . . .	67
Advanced Analog . . . . .	75	Interpoint . . . . .	172	Stag Microsystems Inc . . . . .	109
Advanced Micro Devices . . . . .	8-9	Intusoft . . . . .	170	STD Mfg Group . . . . .	70
Advin Systems Inc . . . . .	169	Ironwood Electronics Inc . . . . .	174	Stockholm International Fairs** . . . . .	122A-B
AEG Corp . . . . .	161	ITT ElectroMechanical Components Worldwide . . . . .	12-13	Sunrise Electronics Inc . . . . .	171
Aerospace Optics . . . . .	133	Jameco Electronics . . . . .	170	Supertek Electronics . . . . .	167
AMP . . . . .	98-99	John Fluke Manufacturing Co Inc . . . . .	169	Swiss Precision Instr . . . . .	171
Ampro Computers . . . . .	165	Keeco Inc . . . . .	175-176	Tatum Labs . . . . .	170
Analogic Corp . . . . .	145	Lanier Voice Prod . . . . .	38	T-Cubed Systems Inc . . . . .	170
Anritsu America . . . . .	147	LeCroy Corp . . . . .	146	TEAC Corp** . . . . .	14
Apex Microtechnology Corp . . . . .	2	Linear Technology Corp . . . . .	138	Teknor . . . . .	174
Applied Microsystems Corp . . . . .	37	Logical Devices . . . . .	38	Tektronix Inc . . . . .	60-63
Augat . . . . .	150	Lorain Products . . . . .	181	Teltone Corp . . . . .	171
B&C Microsystems . . . . .	171, 173	Macrochip Research . . . . .	174	Tempustek . . . . .	174
BanComm . . . . .	154	Maryland Bank . . . . .	69	Texas Instruments Inc . . . . .	42-45, 71-74
Bitwise Designs Inc . . . . .	171	Matrix Systems . . . . .	129	Themis Computer . . . . .	C2
BP Microsystems . . . . .	170	MetaLink Corp . . . . .	171	Thorson Engineering Co . . . . .	172
Bud Industries Inc* . . . . .	120	Microcomputer Control . . . . .	173	Toshiba America Inc . . . . .	116-117
BV Engineering . . . . .	171	Mini-Circuits Laboratories . . . . .	3, 4, 18-19, 141	Universal Data Systems . . . . .	C3
CAD Software Inc . . . . .	171	Molex Inc . . . . .	184	Vicor . . . . .	40-41
Cadpoint . . . . .	171	Octagon Systems . . . . .	173	VME Microsystems . . . . .	152
Cahners Exposition Group . . . . .	182	OKI Semiconductor . . . . .	20-21	VMETRO Inc . . . . .	160
Capital Equipment Corp . . . . .	157-159	Omnibyte Corp* . . . . .	123-124	VTC Inc . . . . .	59
Cermetek . . . . .	173	Optoelectronics Inc . . . . .	156	Wandel & Goltermann . . . . .	100-101
Communication Specialists . . . . .	172	Orbit Semiconductor . . . . .	53	Westcor . . . . .	35
Computerwise Inc . . . . .	170	OrCAD Systems Corp . . . . .	6	Western Digital . . . . .	26-27
Cybernetic Micro Systems . . . . .	172, 173	Pentek . . . . .	154	Wintek Corp . . . . .	169, 174
Cypress Semiconductor . . . . .	17	Phillips Components Inc** . . . . .	120-121	Yamaha LSI . . . . .	102
Dale Electronics Inc . . . . .	1	PLX Technology . . . . .	163	Zax Corp . . . . .	48
Data Translation Inc . . . . .	57	Power General . . . . .	162	Zilog Inc . . . . .	39
Datakey . . . . .	151, 153, 155	Protel . . . . .	172	Z-World . . . . .	171
Datel . . . . .	149	QSI Corp . . . . .	154		
Design Computation Inc . . . . .	170	Qualogy . . . . .	122		
DTK . . . . .	55	Racal-Redac . . . . .	48		
Dynamic Soft Analysis . . . . .	169	Radstone Technology . . . . .	91		
EDN Caravan . . . . .	136-137	Rainbow Tech Inc . . . . .	164		
Electronic Measurements Inc . . . . .	118-119	Rapid Systems . . . . .	166		
Emulation Technology Inc . . . . .	173	Raster Graphics . . . . .	134-135		
Epson America Inc . . . . .	113	Raytheon . . . . .	33		
Foxboro Co . . . . .	161	RLM Research . . . . .	173		
Franklin Software Inc . . . . .	170	Rockwell International . . . . .	80-81		
Fujitsu Component* . . . . .	148, 168	Rogers Corp . . . . .	170, 174		
Fujitsu Microelectronics Inc* . . . . .	10-11	Rohde & Schwarz** . . . . .	148		
F&W Communications . . . . .	172	Rohm Corp . . . . .	93, 95		
GCOM Inc . . . . .	169	Saelig Co . . . . .	172		
G&H Technology Inc . . . . .	154	SBE . . . . .	97		
Hantronix Inc . . . . .	149	Seagate Technology . . . . .	24		
Harris Semiconductor . . . . .	143	Siemens AG** . . . . .	10-11		
Heurikon Corp . . . . .	111	Siemens Corp, Special Products Div* . . . . .	121		
Hewlett-Packard Co . . . . .	22-23, 78-79	Signal Transformer Co Inc . . . . .	C4		
Hitachi America Ltd* . . . . .	14	Signetics Corp . . . . .	115		
House** . . . . .	168	Silicon Systems . . . . .	30		
HyperLynx . . . . .	173	Single Board Solutions . . . . .	172		
IERC . . . . .	166				
ILC Data Device Corp . . . . .	46				

## Recruitment Advertising 177-180

\*Advertiser in US edition

\*\*Advertiser in International edition

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.



Molex Is Making the Connection Between...


# HIGH CURRENT & HIGH DENSITY

From power supply power distribution, Molex makes the connection.


Molex, the industry leader, now offers the most complete line of pin and socket connectors available. From standard wire-to-wire and wire-to-board versions, to the new high-performance "Mini-Fit Jr."

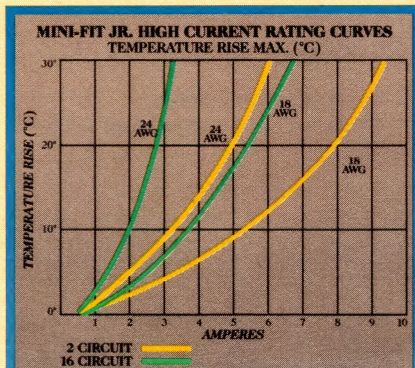**Mini-Fit Jr. meets today's demand for miniaturized design components.**

With current handling capability of up to 9 amps per circuit, and a connector mating force of only 1.54 pounds per circuit, the Mini-Fit Jr. offers the ideal solution to your high current and high density interconnection requirements.



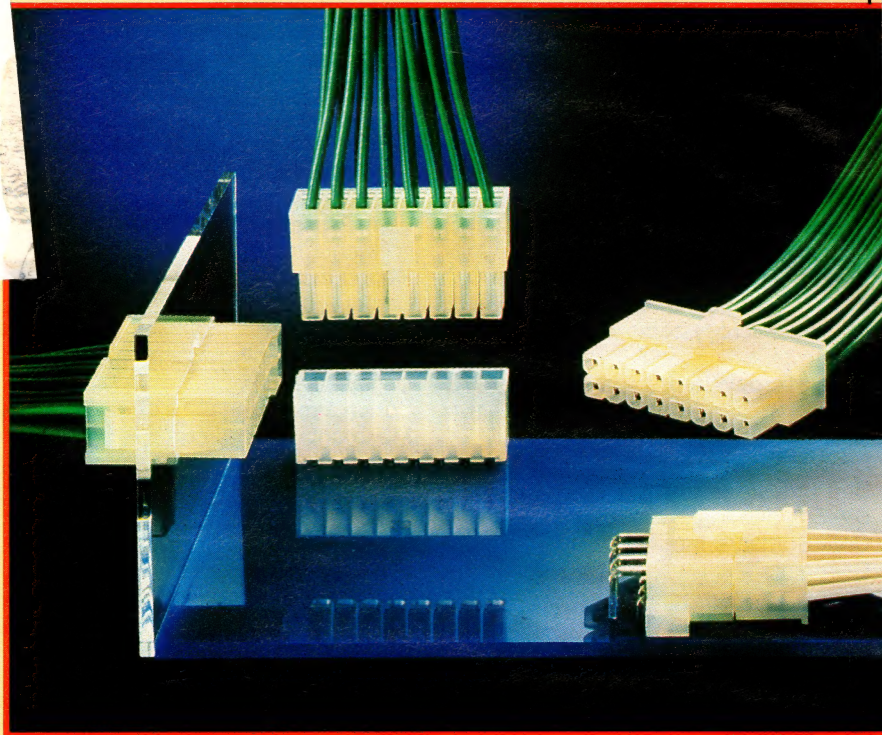Mini-Fit Jr. can handle high current (up to 9 amps) despite its small size.



**Molex is THE source for immediate delivery of pin and socket products.**

Molex has factory stock and distributor inventory around the world. Our pin and socket connectors meet full UL, CSA, VDE, and EAMCL standards. Features include silo protected terminals, positive lock, and pull tabs. They're available in brass or phos-bronze, with tin or selective gold plating for low cost and high performance.

Molex has the pin and socket connector you need, in the size and configuration you need, for every discrete wire application.

*Mini-Fit Jr. is our new generation power connector for your panel-to-wire, wire-to-wire, and board-to-wire applications.*

Service To The  
Customer...Worldwide







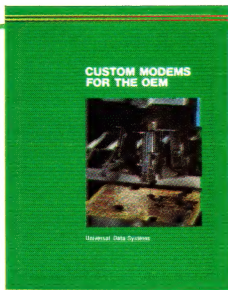
# Exotic Customs at UDS

The special requirements of data communications OEMs have resulted in some pretty exotic custom modem cards from Universal Data Systems.

Funny form factors are routine fare for our custom designers. Nooks, crannies and odd card configurations are no problem, given sufficient square inches of real estate. UDS engineers have even designed a circular 212A modem that fits in the back of a residential electric meter.



*For a generous sampling of UDS' custom design capabilities, ask for the new, free OEM modem brochure.*

Non-standard modem functions are another specialty of the house. For example, UDS engineers have already designed and delivered a hand-held RF modem operating at 4800 bps!

UDS has successfully handled more than 3,000 custom OEM modem design assignments — and we can handle yours. To begin an exotic custom, contact Universal Data Systems, 5000 Bradford Drive, Huntsville, AL 35805. Telephone 205/721-8000; Telex 752602 UDS HTV.



**Universal Data Systems**



**MOTOROLA INC.**  
Information Systems Group



# Dual Personality.

**Custom or standard, Signal's ingenious split bobbin designs offer flexibility - at a very rational price.**

You already know that Signal is the world leader in off-the-shelf transformers. What you may not know is that we're equally dedicated to our custom business.

But it's true. You can get any of the three transformers you see here as standard - or customized to your exact specs. From the versatile Split/Tran® to the low profile Flathead® to the half-sized 2-4-1.

Whichever you choose, you'll also get Signal's innovative design.


It's become an industry standard. Because, unlike ordinary transformers which require shielding to obtain high isolation, ours separate the primary and secondary windings using the split bobbin design we pioneered. Not only does this guarantee high isolation, it delivers healthy savings as well.

As for customization, we give you the full treatment. Flexible modifications or custom designs. Fast quotes and prototypes. Even annual contracts.

Signal also meets important international standards. Our off-the-shelf units are UL recognized. Many of them meet VDE and offer optional CSA certification. What's more, every custom transformer is designed to meet UL standards, too.

And we deliver PRONTO. Standard prototypes are shipped within 24 hours. Your order is shipped factory-direct - so there's no middleman...no hidden costs.

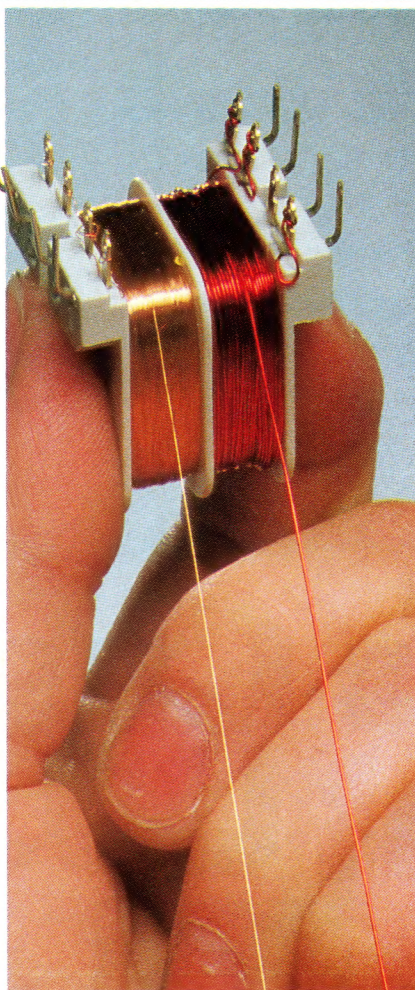Analyze the full line yourself. Call or write for our free catalog: Signal Transformer, 500 Bayview Avenue, Inwood, NY 11696.



## SPLIT/TRAN®



2500V RMS HIPOT. Non-concentric windings and low capacitive coupling. Available with 115V or dual 115/230V primaries. Split secondary windings can be series or parallel connected.

8 pin type DST. 6 pin type ST and


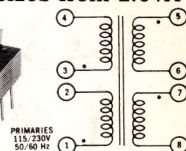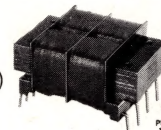
## FLATHEAD®


Ideal for low height, critical pc board power applications. 5 sizes from 2.5VA to 48VA. (Semi-toroidal windings.)



## 2-4-1

2500V RMS HIPOT. The signal for a 50% cut in transformer size and weight at a significantly lower cost.


Six sizes from 2.4VA-100VA.

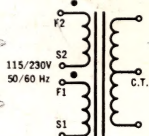

Dual primary. Single primary also available.

**BUY DIRECT**

**(516) 239-5111**

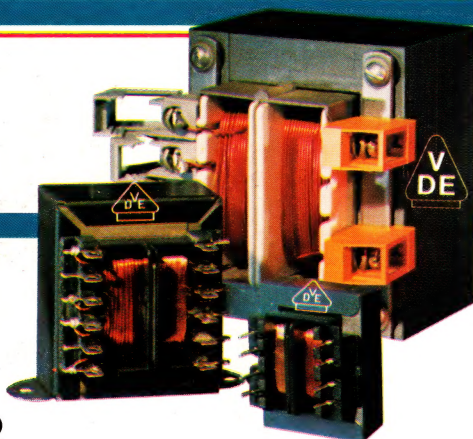

**Insilco**  
International Specialty Companies

# Signal Transformer.

# The American Original.